

Comparing shunt- and hall-based isolated current-sensing solutions in HEV/EV

Krunal Maniar



Introduction

The global market for electric vehicles (EVs) and hybrid electric vehicles (HEVs) is rapidly growing as these vehicles offer higher fuel-efficiency and lower emissions compared to gasoline or diesel vehicles and use power from renewable energy sources. To control energy flow and optimize efficiency in HEV/EV powertrain subsystems such as traction inverters, on-board chargers (OBCs), DC/DC converters, and battery management systems (BMS), precise and accurate current measurement is essential. These high-voltage subsystems must measure large currents at high voltages, typically >400 V. Thus, these current measurements require isolation as well as high performance in harsh automotive environments.

Different Isolated Current Measurement Methods

Each HEV/EV application has different cost, accuracy, signal bandwidth, latency, measurement range, isolation ratings, and package size requirements. There are several isolated current measurements methods. However, the primary methods used in HEV/EV subsystems are either shunt-based using isolated amplifiers (Figure 1) or isolated modulators (Figure 2) or hall-based using open-loop (Figure 3) or closed-loop (Figure 4) hall sensors.

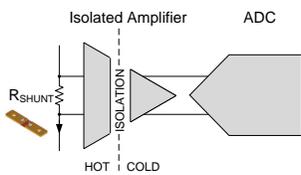


Figure 1.
Isolated Amplifier

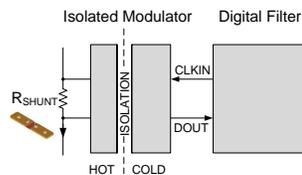


Figure 2.
Isolated Modulator

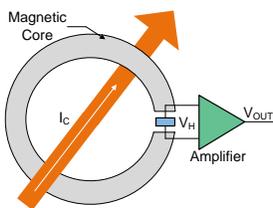


Figure 3.
Open-Loop Hall Sensor

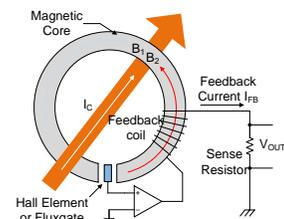


Figure 4.
Closed-Loop Hall Sensor

Comparison of Shunt- and Hall-Based Methods

Historically, designers preferred shunt-based solutions for low-current (<50 A), and hall-based solutions for high-current (>50 A) measurements. However, because of the increasing current measurement accuracy requirements, automotive suppliers are migrating from hall-based to shunt-based methods, especially in high-current environments. There is even a trend amongst automotive suppliers to move from isolated amplifier based solutions to isolated modulator based solutions to further improve measurement accuracy.

Texas Instruments offers best-in-class [isolated amplifiers](#) and [isolated modulators](#) that help achieve very accurate isolated current measurements over temperature when paired with high-precision shunts. [Table 1](#) shows the basic differences between shunt- and hall-based isolated current-sensing solutions in high-current automotive environments.

Table 1. Difference Between Shunt- and Hall-Based Isolated Current Sensing

CATEGORY	SHUNT-BASED	HALL-BASED
Solution size	Similar	Similar
offset	Very low	Medium
Offset drift over temperature	Low	Medium
Accuracy	<0.5% after calibration	<2% after calibration
Noise	Very low	High
Bandwidth	Similar	Similar
Latency	Similar	Similar
Nonlinearity	Very low	High
Long-term stability	Very high	Medium
Cost	Similar	Similar
Vibration impact	Very low	Low
Power dissipation	Low	Very low
Customization	Flexible	Limited

Analysis of Shunt- and Hall-Based Methods

- Hall-sensors are inherently isolated, which allows a single-module approach. On the other hand, shunt-based solutions require an isolated amplifier or modulator, and an isolated power-supply for the high common-mode voltage side.
- Shunt-based solutions have very low initial offset, have lower offset drift over temperature, and are less susceptible to external magnetic fields.

- Shunt-based solutions are linear over the entire voltage range compared to hall-based solutions that are nonlinear, especially at zero crossing and near the magnetic core saturation region.
- Shunt-based solutions achieve better DC accuracy over temperature compared to hall-based solutions with basic one-time calibration. The accuracy of shunt-based solutions is much better particularly at low currents because of limited sensitivity to external magnetic fields.
- The voltage drop across the inline shunt results in thermal dissipation and power loss. However, with improvements in shunt technology, the shunts have become lighter, the ohmic values have decreased, and the accuracy and drift performance have improved. The use of low-value ohmic shunts results in less thermal dissipation. Additionally, Texas Instruments' isolated amplifiers and modulators support very small input voltage ranges (± 50 mV and ± 250 mV) with a superior overall accuracy. These improvements in shunt technology and the availability of small input range isolated devices allow systems to have less thermal dissipation without compromising the overall measurement accuracy.
- Hall-based sensors generally have a limited operating temperature range (typically from -40°C to $+85^{\circ}\text{C}$), whereas shunt-based solutions can support higher operating temperature ranges (typically from -40°C to $+125^{\circ}\text{C}$).
- Both hall-based and shunt-based isolated amplifier solutions offer similar signal bandwidth, typically up to a few hundred kilohertz (kHz). However, isolated modulators provide a high-speed bit-stream output that allows the user to implement and customize digital filtering externally. This customization allows the user to develop high-signal bandwidth and low-latency solutions.

Isolated Shunt-Based Current Sensing in Traction Inverters

A traction inverter controls the electric motor and is a key component in the HEV/EV drivetrain. A traction inverter requires accurate current sensing at high common-mode voltages. Current measurements in traction inverters can therefore be realized using one of two shunt-based methods.

As shown in [Figure 5](#), the voltage drop across the shunt on the hot (high common-mode voltage) side is isolated from the cold side with an automotive grade, reinforced isolated amplifier such as the [AMC1301-Q1](#).

[Figure 6](#) shows the second shunt-based measurement method that uses an automotive-grade, reinforced isolated modulator such as the [AMC1305M25-Q1](#) to isolate the voltage drop across the shunt on the hot side from the cold side.

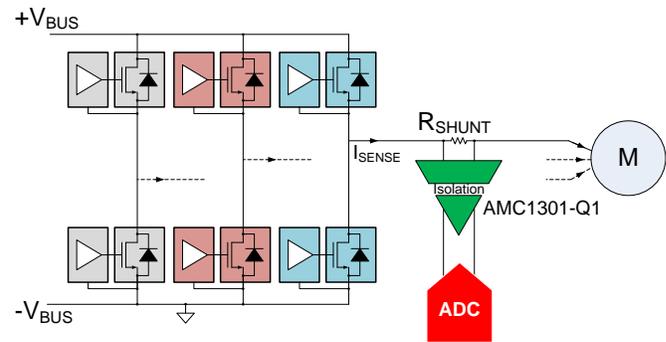


Figure 5. Isolated Current Measurement Using Isolated Amplifiers

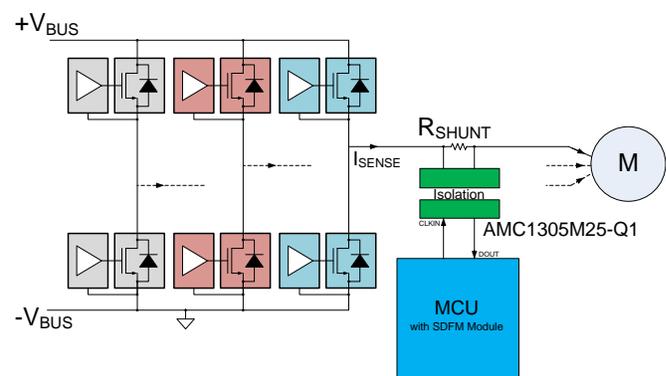


Figure 6. Isolated Current Measurement Using Isolated Modulators

For improved measurement accuracy, use an isolated modulator because this solution eliminates an additional analog-to-digital conversion stage and the associated subsequent errors. The high-speed bit-stream output from the isolated modulators is filtered by microcontrollers (MCUs) such as TI's [C2000 family](#) that have a built-in sigma-delta filter module (SDFM) or by an FPGA, allowing the user to fine-tune signal bandwidth and accuracy.

Automotive Isolated Device Recommendations

DEVICE	ISOLATION	DESCRIPTION
AMC1305-Q1	Reinforced	± 50 -mV, ± 250 -mV isolated modulator
AMC1301-Q1	Reinforced	± 250 -mV isolated amplifier
AMC1302-Q1	Reinforced	± 50 -mV isolated amplifier

Conclusion

Multiple measurement methods exist for isolated current sensing in HEV/EV subsystems including shunt-based and hall-based methods. With advancements in affordable high-precision shunts and high-performance isolated amplifiers and modulators, shunt-based solutions have become good alternatives to traditional hall-based solutions.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated