

Understanding Peak Source and Sink Current Parameters

Mateo Begue, High Power Drivers



Gate drivers are often confused as continuous current sources because of the I_{OH} and I_{OL} specifications in the datasheet. For example, designers looking at the UCC5320SC might read the parameters 4.3-A source and 4.4-A sink and mistakenly believe these devices are capable of providing these currents continuously. Gate drivers do not need to provide constant current because they only have to source/sink current when switching the gate of the MOSFET or IGBT. Refer to [Figure 1](#) for the turn-on waveforms.

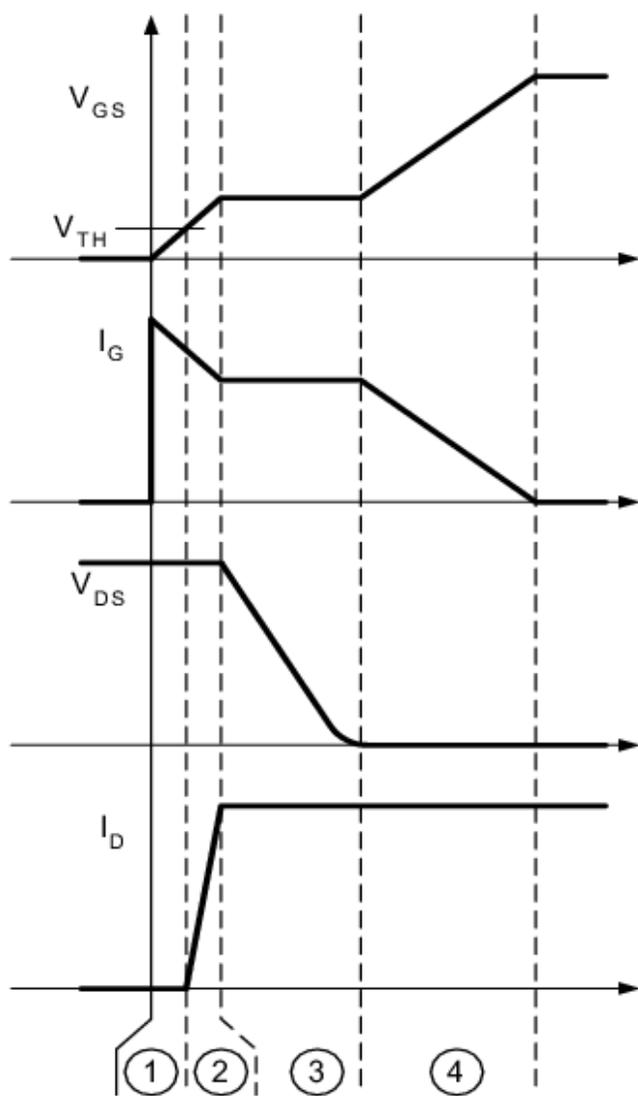


Figure 1. MOSFET Turn-On Time Intervals

In order to understand the I_{OH} and I_{OL} specifications, we need to look at the pull-up and pull-down structures inside the device. The output stage of a gate driver typically comes in some variation of [Figure 2](#). UCC5320SC is offered in a split output pinout that gives designers more control of the rise and fall times without adding extra components like schottky diodes.

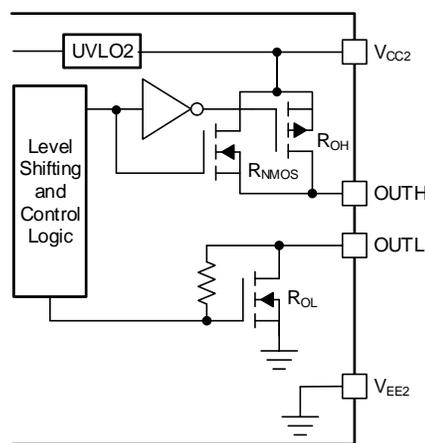


Figure 2. Gate Driver Output Stage

Under a no load condition, I_{OH} is determined by V_{CC2} and the parallel combination of R_{NMOS} and R_{OH} while I_{OL} is set by V_{CC2} and R_{OL} . R_{NMOS} helps the pull-up structure deliver the peak current with a brief boost in peak-sourcing current during the Miller plateau region shown as interval 3 in [Figure 1](#). This is done by turning on the N-channel MOSFET during a narrow instant when the output is changing states from low to high.

When driving MOSFETs and IGBTs high, the external gate resistor R_{ON} and the transistor's internal gate resistance R_{GFET_Int} , reduce the peak output current as shown in [Equation 1](#).

$$I_{OH} = \min \left(4.3 \text{ A}, \frac{V_{CC2}}{R_{NMOS} \parallel R_{OH} + R_{ON} + R_{GFET_Int}} \right) \quad (1)$$

Likewise, the peak sink current is limited by the external gate resistor R_{OFF} in series with R_{OL} and R_{GFET_Int} and is determined by [Equation 2](#)

$$I_{OL} = \min \left(4.4 \text{ A}, \frac{V_{CC2}}{R_{OL} + R_{OFF} + R_{GFET_Int}} \right) \quad (2)$$

This TI TechNote will use the isolated single-channel gate driver, UCC5320SC and a 100-nF capacitive load to demonstrate different techniques to determine the peak drive current. The first method calculates the expected peak currents based on Equation 1 and Equation 2. Use these equations to estimate the peak drive current when selecting a gate driver for your system.

In order to simulate driving a MOSFET or IGBT before installing it onto the PCB, select a load capacitor that is equivalent to the switch's input capacitance, C_{ISS} . Determine the input capacitance by looking up the required gate charge from the MOSFET or IGBT's datasheet at the drive voltage condition.

A second technique uses this C_{ISS} value and the dV/dt of the switching waveform to determine the source or sink current. Figure 3 measures the dV/dt using cursors set to a fixed 35-ns interval and swept across the rising edge in order to find the peak dV/dt . As a guideline, set the oscilloscope's cursors to a time interval, Δt of approximately 10% of the rise time to determine the current through the load capacitor.

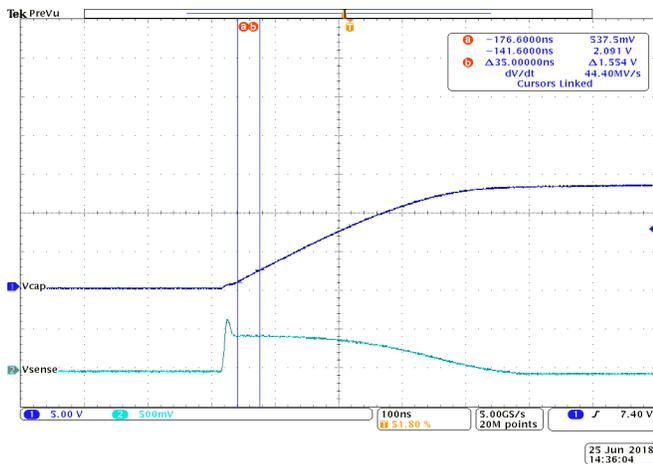


Figure 3. Measuring Peak dV/dt Across Load Capacitor

Use the measured peak dV/dt and load capacitor value along with Equation 3 to calculate the peak current.

$$I_C = C \frac{dV}{dt} \quad (3)$$

A third method inserts a 0.1- Ω sense resistor between the capacitor and ground to calculate I_{OH} or I_{OL} . Figure 4 shows the voltage waveform across the sense resistor, V_{SENSE} and its measurement coincides with the highest dV/dt value of the V_{cap} waveform.

The results of the three presented techniques are shown in Table 1. Even with the 0.1- Ω sense resistor in series with the capacitor, Equation 1 predicts 4.30-A sourcing current. Equation 3 uses the largest measured dV/dt value in the linear region of the gate drive waveform which gives an estimated 4.53-A. In this same linear region, the voltage across the sense resistor is measured in Figure 4 and Ohm's law is used to determine peak I_{OH} at 4.29-A.

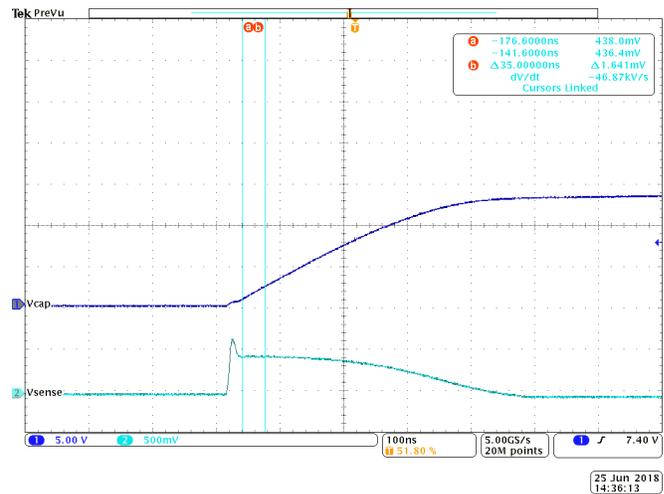


Figure 4. Voltage Across Series Sense Resistor

The first method is a good starting point when selecting a gate driver but it is not an actual measured value. The second method relies on the engineer to accurately measure the highest dV/dt by using a fixed Δt and sweeping it across the waveform. Lastly, the voltage measured across the 0.1- Ω sense resistor will give the engineer a value calculated from measurement of the peak drive current using Figure 4 and Ohm's law. The key to the third measurement technique is to select a small valued sense resistor to prevent any limitations in the peak output current. All presented methods are acceptable approximations of a gate driver's peak output current.

To reiterate, I_{OH} and I_{OL} are not continuous DC values. The peak current charges or discharges C_{ISS} in an instant and then reduces in value as the switch begins to turn on.

Table 1. Measurement Comparison

Theoretical vs. Measured	Method	Result
Theoretical	Equation 1: $I_{OH} = \min[4.30A, 4.44A]$	4.30A
Calculated from Measurement	Equation 3: $I_C = 102nF(44.4MV/s)$	4.53A
Calculated from Measurement	Ohm's Law: $I_{OH} = 438mV/102m\Omega$	4.29A

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated