

# CC1310 Skyworks PA Chinese AMR Reference Design Rev 2.x

Albin Zhang and Richard Wallace

## ABSTRACT

Automatic Meter Reading (AMR) is to collect the information of the amount of water, electric or gas consumed automatically that has been used from each household. When the AMR information has been received then the exact energy amount can be charged from the energy supplier company. Traditionally, this has been done by manual reading of meters but with wireless technology this can now be done automatically. Several countries now have laws requiring energy companies to charge for the exact amount of energy being consumed and not just a predicted energy bill. Each country has specific regulatory requirements for AMR.

This application report is targeting the Chinese AMR market (470 MHz to 510 MHz) with CC1310 [2]. To enhance the wireless operation range in China, TI provides the range extender reference design. The initial design was based upon a discrete PA solution [7]. To simplify the RF front design, TI worked with Skyworks Solutions to integrate the CC1310 wireless MCU with a compact, cost-effective front-end module (FEM). The CC1310 wireless MCU, together with SKY66115-11 [4] addresses customers' needs for easy-to-use, long-range, low-power and low-cost solutions serving applications across the Internet of Things (IoT). The reference design covered in this application report can support up to +20 dBm TX power with high power efficiency.

## Contents

1	Introduction .....	2
2	Design .....	2
3	Measurement Results .....	9
4	Summary .....	13
5	References .....	14

## List of Figures

1	CC1310EM-SKY66115-4051 Board.....	2
2	CC1310 Block Diagram .....	3
3	Schematic - CC1310EM-SKY66115-4051 Rev2_0_x .....	5
4	CC1310EM-SKY66115-4051 Layout.....	6
5	DIO Configuration in SmartRF Studio 7 .....	7
6	Tx Mode Configuration .....	8
7	Rx mode configuration .....	8
8	Conductive Spurious Emission on 510 MHz to 566 MHz .....	9
9	Matching of the Antenna With ANT1 and ANT2 Components .....	11
10	Return Loss With ANT1 and ANT2 Components .....	12
11	PCB Helical Antenna Efficiency .....	13

## List of Tables

1	SKY66115-11 Truth Table.....	7
2	Conducted Output Power and Harmonics, 3.3 V .....	10
3	TX Output Power, Current Consumption vs. Power Table, 3.3 V.....	10


## Trademarks

SmartRF is a trademark of Texas Instruments.

All other trademarks are the property of their respective owners.

## 1 Introduction

The Chinese AMR market has been allocated a frequency range of 470 MHz to 510 MHz. The maximum radiated output from the metering unit is not to exceed 17 dBm effective radiated power (ERP). The majority of meters are quite compact and require a compact antenna. The antenna efficiency is normally quite low due to the physical size so higher output power is desired to compensate for the antenna losses. The design covered in this application report is based on the CC1310 from the CC13xx family.

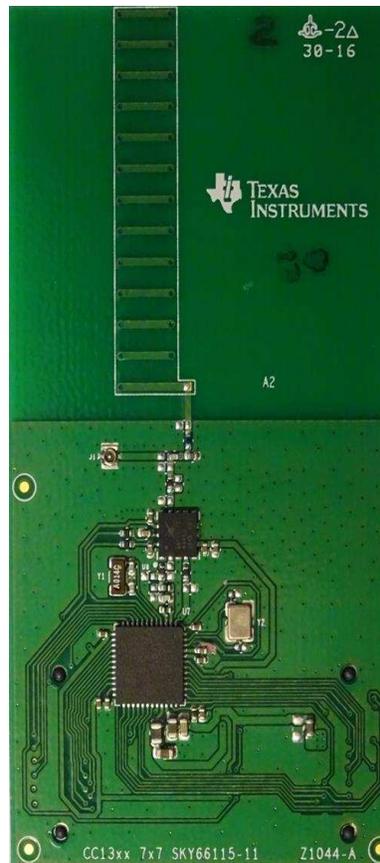

**Figure 1. CC1310EM-SKY66115-4051 Board**

## 2 Design

When designing an AMR system, the maximum range between the transmitter and receiver is one of the most important parameters that will dominate the system configuration and installation. In the AMR system, the range is critical so that all households' meters can be read otherwise this must be done manually or adding more concentrators, which is expensive. To achieve a long range the output power can be increased to the maximum limit specified by the regulations and the data rate reduced as much as possible for the application.

The AMR system must be able to work in a noisy RF environment since the number of meters in industrial complexes or high rise buildings can be positioned very close to each other so blocking and selectivity are critical requirements. More information on achieving optimum radio distance and blocking/selectivity is available in a device-specific application report [1].

## 2.1 CC1310

The CC1310 has been specifically designed for long range, city-wide low power networks. This is used in home automation, building automation and outdoor wide-area networks. The main advantages of CC1310 are high sensitivity (-124 dBm with a 0.625 kbps data rate), strong co-existence (up to 80 dB blocking), lowest power consumption (61  $\mu$ A / MHz ARM Cortex M3).

CC1310 can be basically split into four low-power sections as shown in [Figure 2](#):

- Main CPU with Cortex M3
- RF Core with radio controller. The RF core is a highly flexible and capable radio system that interfaces the analog RF and base-band circuitries, handles data to and from the system side, and assembles the information bits in a given packet structure.
- General Peripherals
- Sensor Controller

For more in-depth information on the CC1310, see the *CC1310 SimpleLink™ Ultra-Low-Power Sub-1 GHz Wireless MCU Data Sheet (SWRS181)*.

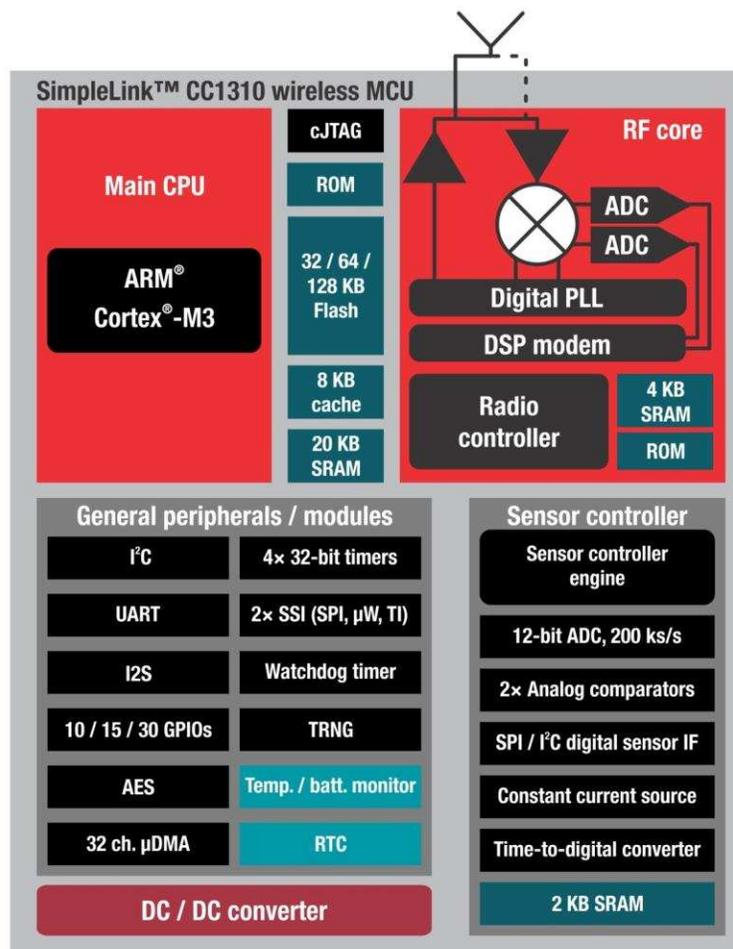


Figure 2. CC1310 Block Diagram

## 2.2 Schematic

The RF core of CC1310 is highly configurable and the radio front-end can be set to differential or single ended. With a differential output configuration, the maximum output is 14 dBm. With a single ended output, the maximum output is 11 dBm. Since many AMR customers have requested an output power up to 20dBm, the CC1310 transmitter was configured as a single ended port (RF\_P set to Tx) connected to an external FEM with an integrated amplifier, see [Figure 3](#). If an output power of 14 dBm is sufficient then the standard reference design for 420 MHz to 510 MHz can be used [\[8\]](#).

The schematic shown in [Figure 3](#) is a general schematic (Rev 2.0.x) to cover the ISM frequency bands from 400 MHz to 510 MHz; the BOM is specified for three different ISM frequency bands:

- 470 MHz – 510 MHz: BOM - CC1310EM-SKY66115-4051 Rev 2.0.1
- 420 MHz – 440 MHz: BOM - CC1310EM-SKY66115-4051 Rev 2.0.2
- 400 MHz – 420 MHz: BOM - CC1310EM-SKY66115-4051 Rev 2.0.3

The FEM used is from Skyworks (SKY66115-11). The SKY66115-11 consists of an amplifier and a switch contained in the package. It also includes a shutdown mode to minimize power consumption. The transmit path contains an amplifier optimized for saturated performance. SKY66115-11 is specifically matched for CC1310 which enables optimum transmit output power and efficiency for 50  $\Omega$  load impedance. The transmit path passes through a low-pass filter before being entering to one side of the SPDT switch. The receive path has a bypass function from the other side of the SPDT switch.

The reference design [\[3\]](#) shown in [Figure 3](#) is based upon 3.3 V supply voltage. Two RF output options are available. Mounting C72, the RF path is routed to the RF connector (J1) that allows an external antenna or conductive RF testing. Mounting C63, connects the compact PCB antenna. ANT1, ANT2 and ANT3 compose of the antenna matching circuit.

An optional low-pass filter (LPF) (C484, C485, C486 and L332 ) can be incorporated on the ANT port to provide additional rejection of PA output harmonic levels and/or limit unwanted signals from entering the receive path. For 470 MHz – 510 MHz band, there is no external LPF circuit needed. Since the FEM is specifically designed for the CC1310 470 MHz – 510 MHz band, there is no matching circuit needed on the TX inputs of the SKY66115-11. C487, C489 and L333 are only required for 433 MHz and 408 MHz.

CC1310 can support a several RF port options, which is described in the wiki page [\[9\]](#). For better Rx sensitivity, the reference design adopts a single-end, external-bias RF front-end design. L1 is used for the external bias circuit. C11, L11 and L12 compose a matching circuit to optimize the RX sensitivity.

The reference design [\[3\]](#) utilizes noise decoupling filtering on the power and control lines of the SKY66115-11.


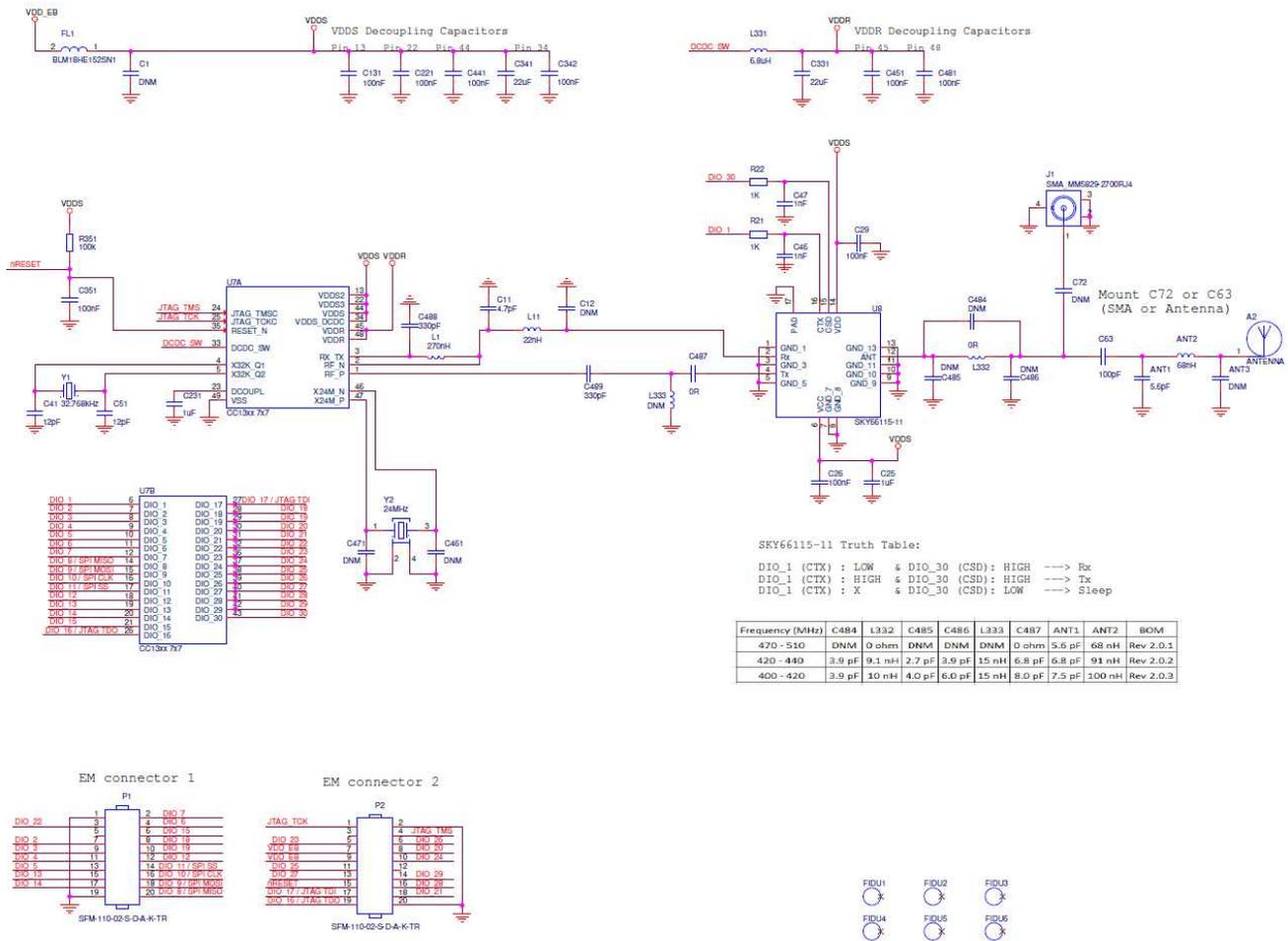


Figure 3. Schematic - CC1310EM-SKY66115-4051 Rev2\_0\_x

### 2.3 Layout

The design [3] is based upon a 0.8 mm thick, two-layer PCB. The top layer and bottom layer are shown in Figure 4. All components are positioned on the top layer apart from the evaluation module (EM) connectors. The CC1310EM-SKY66115-4051 is based upon the 7x7 QFN package. The RF front-end design can be re-used for 5x5 QFN and 4x4 QFN packages.

A PCB helical antenna is incorporated in the EM design. The antenna is routed on both the top and bottom layers. It is important to incorporate the matching components (ANT1, ANT2 and ANT3) as well if the antenna structure is to be copied to another design. Changing the PCB thickness will change the resonance of the antenna and this would require new antenna matching values for ANT1 and ANT2 (ANT3: DNM).

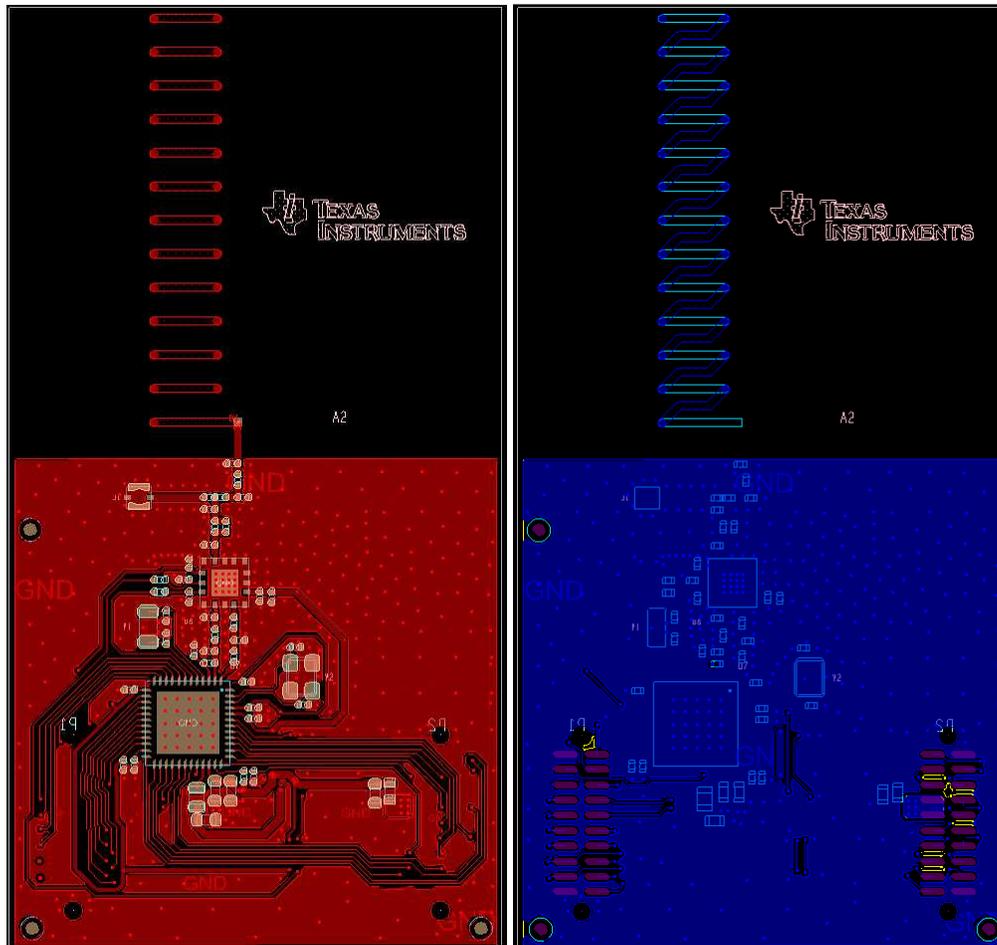

**Figure 4. CC1310EM-SKY66115-4051 Layout**

The top view is shown on the left side; the bottom view is shown on the right side.

## 2.4 SmartRF™ Studio

To evaluate the reference design it is recommended to use the EM on the SmartRF06EB with SmartRF Studio software. The supported functions are continuously being updated and the software can be downloaded [6].

With SmartRF studio 7 (version 2.4.3), new features have been added to support 433 MHz – 510 MHz reference designs.

- Default recommended setting on 430-510MHz band.
- DIOs configuration based on the truth table of the FEM.
- RF front-end mode configuration.


For more information on SmartRF Studio7, see <http://www.ti.com/tool/smartrfm-studio>. Figure 5, Figure 6 and Figure 7 illustrate how to configure the CC1310EM-SKY66115-4051 board.

### 2.4.1 DIO Configuration

Based on the truth table of the SKY66115-11 shown in Table 1, SmartRF Studio should have the DIO configured as shown in Figure 5.

**Table 1. SKY66115-11 Truth Table**

DIO\_1 (CTX) : LOW & DIO\_30 (CSD) : HIGH ----> Rx  
 DIO\_1 (CTX) : HIGH & DIO\_30 (CSD) : HIGH ----> Tx  
 DIO\_1 (CTX) : X & DIO\_30 (CSD) : LOW ----> Sleep

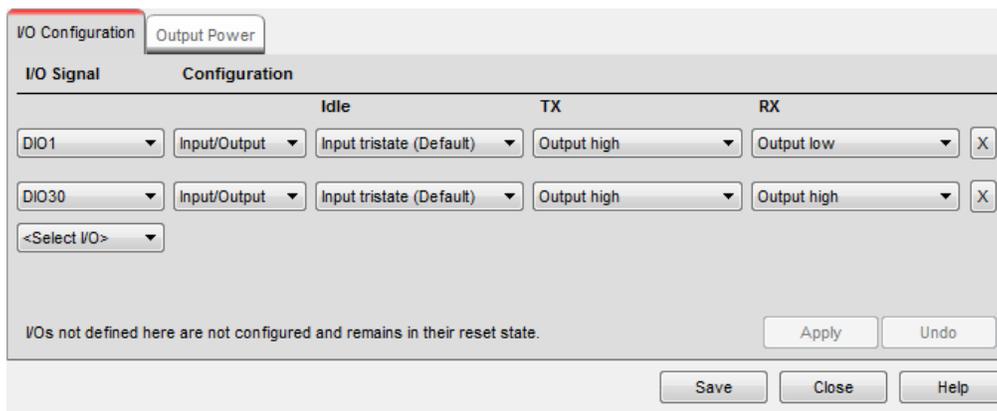

**Figure 5. DIO Configuration in SmartRF Studio 7**

### 2.4.2 RF Front-End Configuration

Figure 6 and Figure 7 show the configuration of Tx and Rx modes separately. This is configured in the CMD\_PROP\_RADIO\_DIV\_SE radio operation commands.

For the Tx path configuration shown in Figure 6, RF\_P is set to single-end option. The txpower parameters should also be configured based on Table 3.

For the Rx path shown in Figure 7, RF\_N is set to single-end option.

Radio Operation Commands		Value
▶	CMD_FS	
▶	CMD_PROP_TX	
▼	CMD_PROP_RADIO_DIV_SETUP	
	commandNo	0x3807
	status	0x0000
	pNextOp	0x00000000
	startTime	0x00000000
	startTrigger	0x00
	condition	0x01
	modulation	0x0321
	symbolRate	0x0080000F
	rxBw	0x24
	preamConf	0x04
	formatConf	0x00A0
	config	0x0009
	txPower	0x1CC7
	pRegOverride	0x00000000
	centerFreq	0x0364
	intFreq	0x8000
	loDivider	0x05

Bit Fields	Value
frontEndMode [0..2]	0x 1
biasMode [3..3]	0x 1
analogCfgMode [4..9]	0x 0
bNoFsPowerUp [10..10]	0x 0

Figure 6. Tx Mode Configuration

Radio Operation Commands		Value
▶	CMD_FS	
▶	CMD_PROP_TX	
▼	CMD_PROP_RADIO_DIV_SETUP	
	commandNo	0x3807
	status	0x0000
	pNextOp	0x00000000
	startTime	0x00000000
	startTrigger	0x00
	condition	0x01
	modulation	0x0321
	symbolRate	0x0080000F
	rxBw	0x24
	preamConf	0x04
	formatConf	0x00A0
	config	0x000A
	txPower	0x1CC7
	pRegOverride	0x00000000
	centerFreq	0x0364
	intFreq	0x8000
	loDivider	0x05

Bit Fields	Value
frontEndMode [0..2]	0x 2
biasMode [3..3]	0x 1
analogCfgMode [4..9]	0x 0
bNoFsPowerUp [10..10]	0x 0

Figure 7. Rx mode configuration

### 3 Measurement Results

All measurements results were performed on the CC1310EM-SKY66115-4051 at 470 MHz – 510 MHz (BOM Rev 2.0.1) mounted on the SmartRF06EB. The  $V_{USB}$  power source is nominally 3.3 V on the SmartRF06EB. Software control is based upon SmartRF Studio 2.4.3.

#### 3.1 Spurious Emission

This design is fully compliant with Chinese Sub-1G SRRC regulation.

The ERP requirements set by the regulation requirements is 17 dBm\_max. Note that the EIRP = ERP + 2.15 dB. Therefore, the peak EIRP should not exceed 19.15 dBm.

Tx: the emissions should not exceed -36 dBm for 30 MHz – 1GHz, and -30 dBm for 1 GHz – 12.75 GHz.

Rx: the emissions should not exceed -57 dBm for 30 MHz – 1GHz and -47 dBm for 1 GHz – 12.75 GHz.

The conductive spurious emissions are fully compliant and Figure 8 shows one measurement in the 510MHz-566MHz band. In the Chinese regulation, the specification is -54 dBm for radiated measurements. The conductive test results shows 2.4 dB margin on the spurs in Figure 8 with txpower register 0x18C6. Further margin will be gained when measuring this parameter in radiated mode due to antenna efficiency. The solution passes the SRRC regulation with good margin.

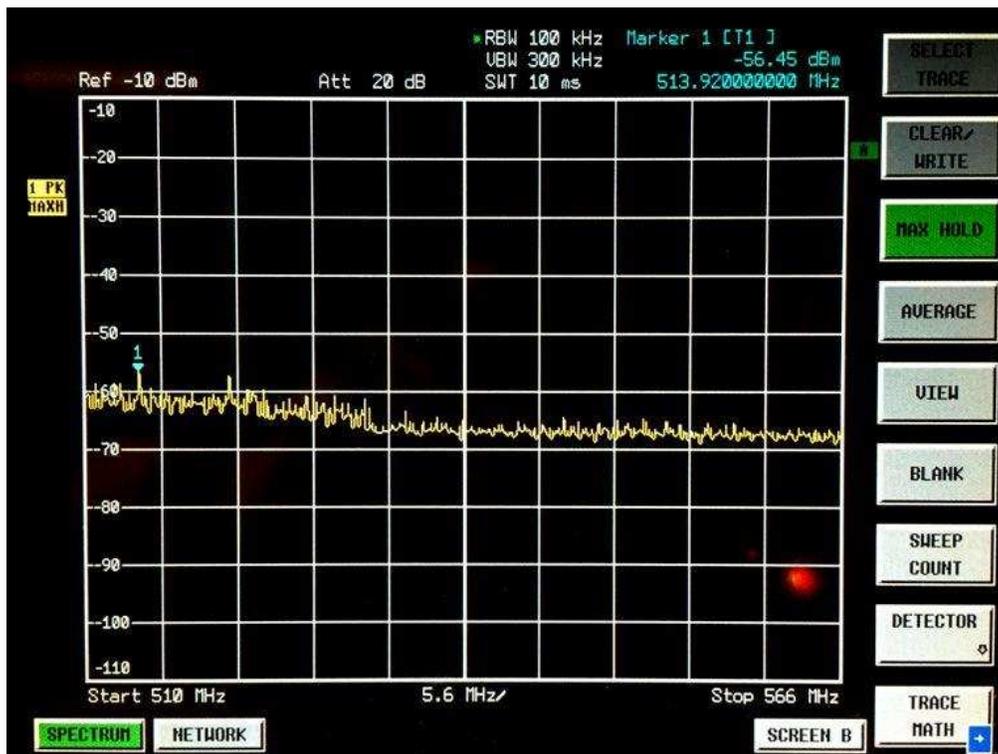


Figure 8. Conductive Spurious Emission on 510 MHz to 566 MHz

### 3.2 Tx Output Power and Harmonics

The output power was measured at 470 MHz, 490 MHz and 510 MHz. For each frequency, the harmonics were measured up to the 10th harmonic. The txpower register is set to 0x18C6.

**Table 2. Conducted Output Power and Harmonics, 3.3 V**

fc	2fc	3fc	4fc	5fc	6fc	7fc	8fc	9fc	10fc	
470	940	1410	1880	2350	2820	3290	3760	4230	4700	MHz
19.8	-40	-45	-49	-54	-55	-55	-55	-55	-55	dBm
490	980	1470	1960	2450	2940	3430	3920	4410	4900	MHz
20.1	-38	-47	-50	-55	-55	-55	-55	-55	-55	dBm
510	1020	1530	2040	2550	3060	3570	4080	4590	5100	MHz
19.7	-39	-46	-51	-54	-55	-55	-55	-55	-55	dBm

### 3.3 Tx Output Power Dynamic Range and Current Consumption

Output power and current consumption were measured across the power table at 470 MHz, 490 MHz and 510 MHz. The average results are shown in [Table 3](#).

In the CMD\_PROP\_RADIO\_DIV\_SETUP, the power can be configured in the txpower register, which is shown in [Figure 6](#).

**Table 3. TX Output Power, Current Consumption vs. Power Table, 3.3 V**

Power Table	0x08C0	0x0041	0x10C3	0x1043	0x14C4	0x18C5	0x18C6	0x1CC7	
Output power	14.9	18	18.9	19.3	19.5	19.7	19.9	19.9	dBm
Current consumption	56.5	68.1	72.6	75	76.6	77.8	78.7	79.4	mA
Solution efficiency	17.4	28.6	33	34.8	35.6	35.9	36.2	36.1	%

The SKY66115-11 maximum input power rating on the PIN\_TX is limited to 10dBm. CC1310 should limit the TX Power control IB bit of txpower register below 0x07. For optimized current consumption, the recommended value of the txpower is 0x18C6.

### 3.4 Rx Current Consumption

The static Rx current consumption was measured at 6.3 mA with 3.3 V power supply.

### 3.5 Sensitivity

The sensitivity was measured with 50 kbps datarate setting on CC1310EM-SKY66115-4051 at 470 MHz – 510 MHz (BOM Rev 2.0.1) to -107.5 dBm during normal temperature and 3.3 V power supply.

For the differential reference design with external biasing, the sensitivity is approximately -109.5 dBm for a data rate of 50 kbps. This reference design shown in [Figure 3](#) uses single ended configuration of Rx and Tx to avoid the need for another switch component and balun circuit. The sensitivity is reduced by 1 dB with single ended configuration compared to differential configuration. External biasing of the LNA is adopted for better Rx sensitivity. The SKY66115-11 switch has an insertion loss of approx. 0.6 dB. To keep the external BOM costs as low as possible, LQG inductors are used instead of wire-wound (WW) inductors which also causes an additional 0.4 dB of loss.

Therefore, the sensitivity delta of this reference design [\[3\]](#) with single-ended configuration, switch and LQG components compared to the standard reference design [\[8\]](#) with differential configuration is -2.0 dB.

The initial AMR 20 dBm China reference design based upon a discrete PA [\[7\]](#) had a sensitivity of approximately -106.5 dBm. This updated design with the Skyworks FEM has been improved by 1 dB to -107.5 dBm.

If the data rate is reduced from 50 kbps and Long Range Mode utilized, then the following sensitivity levels can be achieved on the on CC1310EM-SKY66115-4051 at 470 MHz – 510 MHz (BOM Rev 2.0.1) Ref Design:

- 5 kbps sensitivity: -117.5 dBm
- 2.5 kbps sensitivity: -119.5 dBm
- 1.25 kbps sensitivity: -120.5 dBm
- 0.625 kbps sensitivity: -121.5 dBm

### 3.6 Antenna Design

The PCB helical antenna shown in Figure 4 has been matched to 470 MHz – 510 MHz with ANT 1: 5.6 pF and ANT2: 68 nH. For more information, see Figure 9. The antenna is matched for the complete band of 470 MHz – 510 MHz. For more information, see Figure 10. The antenna was tested at 510 MHz in the anechoic chamber and the antenna efficiency is -4.1 dB (38.6 %). For the complete CTIA report summary, see Figure 11.

This antenna design, matching tuning and testing results are based on the CC1310EM-SKY66115-4051 board at 470 MHz – 510 MHz (BOM Rev 2.0.1) plugging on the SmartRF06EB board with the free space environment. In antenna design theory, some of the nearby materials will impact the antenna performances, for example, grounded conductor, plastic/rubber cases, and so forth. For a realistic product antenna design, it is necessary to consider the mechanical case impacts and do proper tuning.

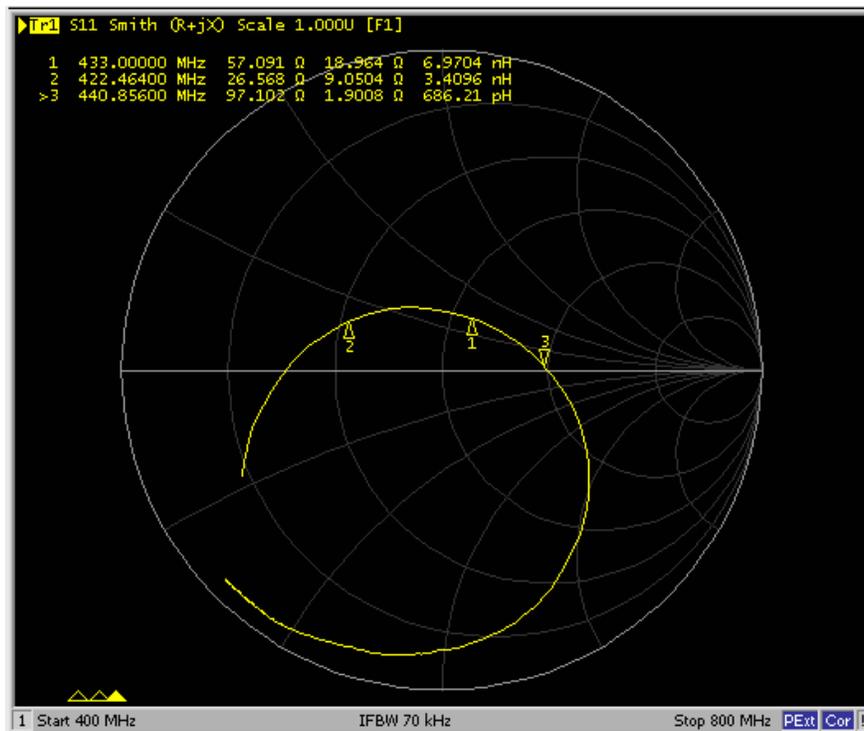


Figure 9. Matching of the Antenna With ANT1 and ANT2 Components

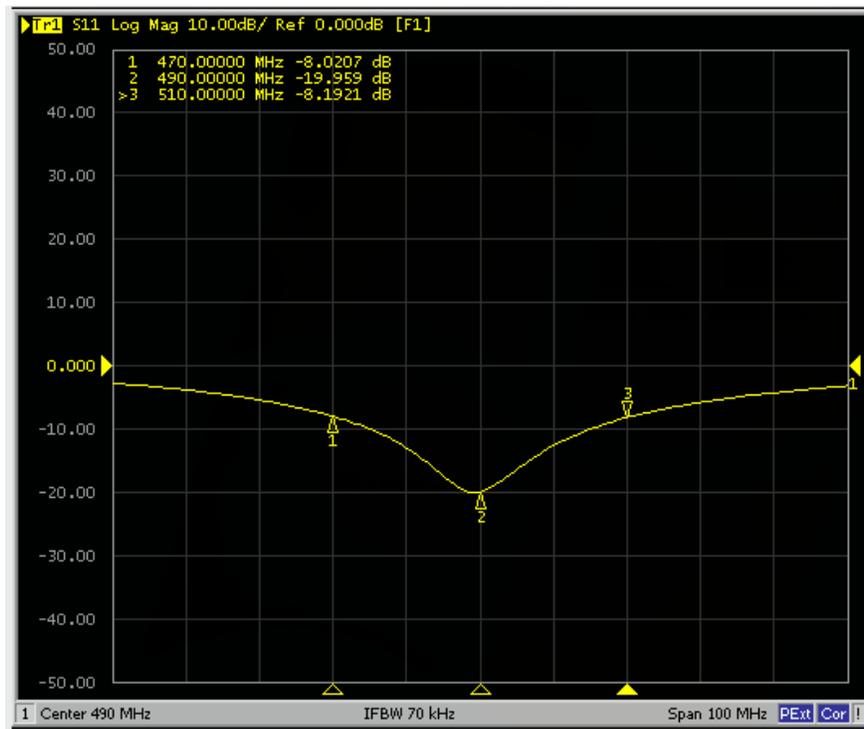


Figure 10. Return Loss With ANT1 and ANT2 Components

**OTA Evaluation Results:**

Total Radiated Power	-4,14 dBm
Peak EIRP	-1,04 dBm
Directivity	3,09 dBi
Efficiency	-4,14 dB
Efficiency	38,58 %
Peak Gain	-1,04 dBi
NHPRP 45°	-4,86 dBm
NHPRP 45° / TRP	-0,72 dB
NHPRP 45° / TRP	84,63 %
NHPRP 30°	-5,89 dBm
NHPRP 30° / TRP	-1,76 dB
NHPRP 30° / TRP	66,72 %
NHPRP 22.5°	-6,96 dBm
NHPRP 22.5° / TRP	-2,83 dB
NHPRP 22.5° / TRP	52,15 %
UHRP	-7,83 dBm
UHRP / TRP	-3,69 dB
UHRP / TRP	42,76 %
LHRP	-6,56 dBm
LHRP / TRP	-2,42 dB
LHRP / TRP	57,24 %
PGRP (0-120°)	-4,99 dBm
PGRP / TRP	-0,85 dB
PGRP / TRP	82,20 %
Front/Back Ratio	3,53
PhiBW	360,0 deg
PhiBW Up	360,0 deg
PhiBW Down	360,0 deg
ThetaBW	92,6 deg
ThetaBW Up	30,9 deg
ThetaBW Down	61,8 deg
Boresight Phi	285 deg
Boresight Theta	105 deg
Maximum Power	-1,04 dBm
Minimum Power	-25,38 dBm
Average Power	-5,16 dBm
Max/Min Ratio	24,34 dB
Max/Avg Ratio	4,12 dB
Min/Avg Ratio	-20,22 dB
Worst Single Value	-38,05 dBm
Worst Position	Azi = 15 deg; Elev = 165 deg; Pol = Ver
Best Single Value	-1,34 dBm
Best Position	Azi = 195 deg; Elev = 105 deg; Pol = Hor

**Figure 11. PCB Helical Antenna Efficiency**

#### 4 Summary

AMR products are normally very compact with a small antenna, physically positioned in locations near metal objects and normally hidden in a remote storage area of a building. This causes a reduction in the ERP. The output power can be increased to assure a maximum ERP suited for each application.

The CC1310EM-SKY66115-4051 reference design at 470 MHz – 510 MHz (BOM Rev 2.0.1) is a low cost, easy-to-use, high efficiency solution with 20 dBm output power for 3.3 V supply. Tx current consumption at 20 dBm is approx. 79 mA. The antenna is also integrated into the PCB which provides a compact, costless antenna solution.

The initial AMR 20 dBm China reference design for 470 MHz – 510 MHz was based upon a discrete PA Rev 1.x.x [7]. The updated design with the Skyworks FEM Rev 2.0.1 [3] has improved sensitivity, lower component count and greater margins to Tx spurious emissions.

## 5 References

1. *Achieving Optimum Radio Range* ([SWRA479](#))
2. *CC1310 SimpleLink™ Ultra-Low-Power Sub-1 GHz Wireless MCU Data Sheet* ([SWRS181](#))
3. *CC1310EM-SKY66115-4051 Reference Design (Rev: 2.0.x)* ([SWRC334](#))
4. [SKY66115 -11 Data Sheet](#)
5. *Antenna Quick Guide* ([SWRA351](#))
6. [SmartRF Studio Download](#)
7. *CC1310EM-7PA-4751 Reference Design for China* ([SWRC311](#))
8. *SimpleLink CC1310 4-Layer 5x5 Differential 779-930 MHz v1.0.0 Design Files* ([SWRC311](#))
9. [CC1310 Front-end Configurations Wiki page](#)

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated