

TI-RSLK

Texas Instruments Robotics System Learning Kit



TEXAS INSTRUMENTS



Module 5

Lecture: Battery and voltage regulation




Power and Energy

Sources of Power

- 120/220 VAC 50/60 Hz
 - Needs an AC to DC converter
 - Needs a voltage regulator
- DC power supply (+5V on USB, +12V used in automotive)
 - USB power used to power TI's Launchpad (5V)
- Battery
 - Need to drive robot autonomously
 - Provide power to TI's Launchpad, motors, sensors
 - Voltage, energy, size, weight
 - Needs a regulator for **constant voltage**
- Energy harvesting like solar or EM field pickup

Power = $V \cdot I$ (watts)

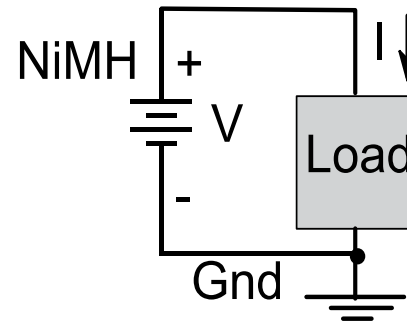Energy = $V \cdot I \cdot \text{time}$ (Joules)





Power Budget

Battery-powered embedded system


- Power Budget => Battery Life
Average Current < Energy Storage/ t_{life}
- Save Power :
Reduce voltage, Sleep modes, Clock, CPU,



TI's Launchpad MSP432 Low Power MCU

$$\text{Energy} = V * I * \text{time (J)}$$

$$\text{Storage} = I * \text{time (amp-hr)}$$

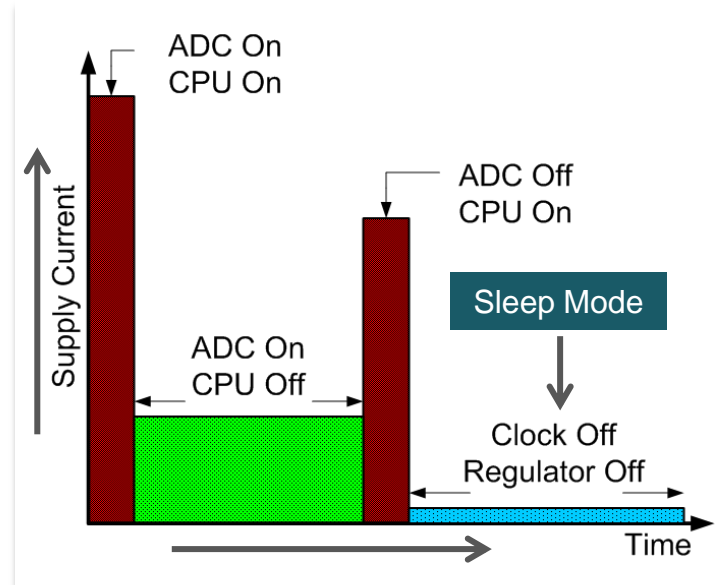

MSP432 : Supply current under different modes of operation



Batteries


Types of batteries

- Primary (not re-usable)
 - Heavy duty
 - Alkaline
 - Lead-acid
 - Lithium
- Secondary (rechargeable)
 - NiCad
 - NiMH
 - Li-ion
 - Supercap

7.2V requires
6 batteries

Energy = $V \cdot I \cdot \text{time}$
Storage = $I \cdot \text{time}$ (amp-hr)

Inside a Battery

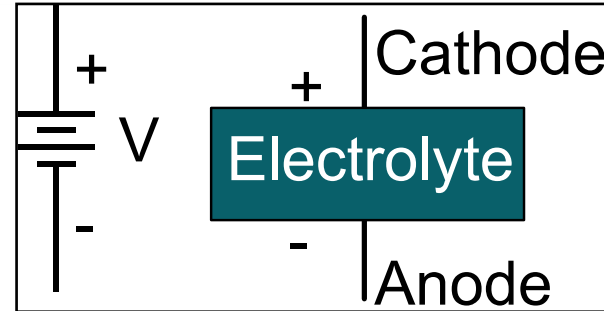



Batteries

AA Sized Batteries

$$\text{Energy} = V \cdot I \cdot \text{time}$$
$$\text{Storage} = I \cdot \text{time (amp-hr)}$$

Battery	Voltage (V)	Energy Storage (Ah)	Type
Alkaline	1.5	2	Primary
Lithium	1.5	3	Primary
NiCad	1.2	1.2	Secondary
NiMH	1.2	1.8	Secondary
Li-ion	3.6	1.9	Secondary

Most energy
for the same size
battery

Running at a $\frac{1}{2}$ amp, your robot will run for 3.6 hours


$$t_{\text{life}} = \text{Energy Storage} / I$$
$$= 1.8 / 0.5 = 3.6 \text{ hr (NiMH)}$$



Voltage regulation using a Linear Regulator

Properties

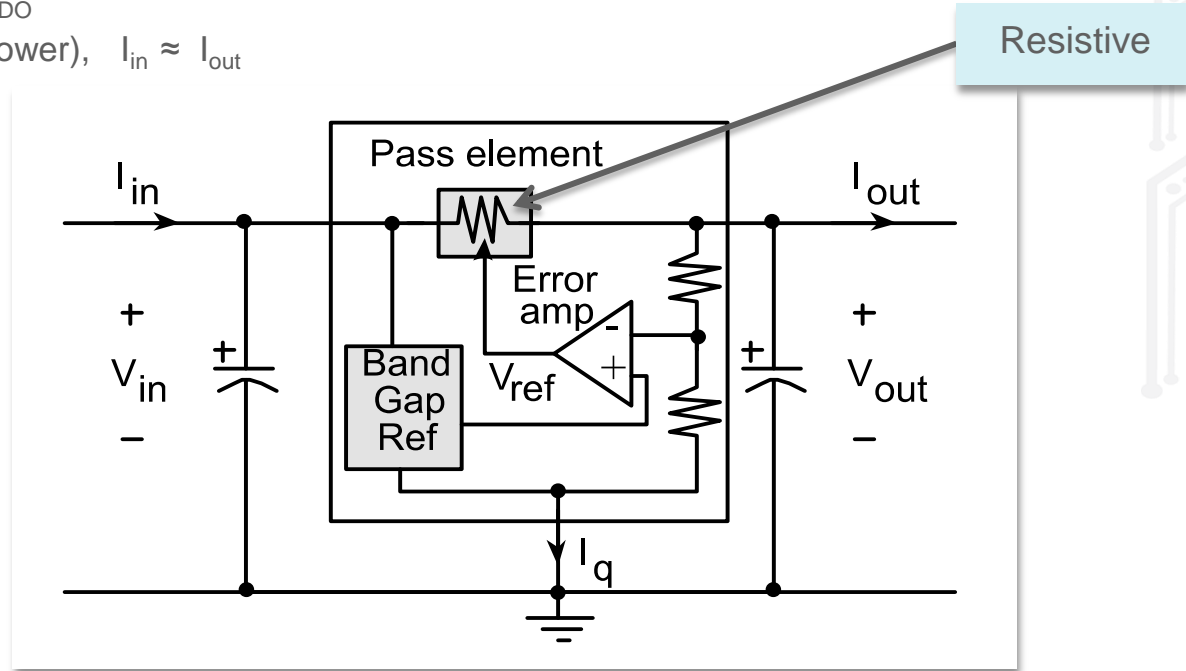- Generates a constant output voltage V_{out} for varying, input voltage V_{in} & load I_{out}
- Dropout voltage, $V_{in} > V_{out} + V_{DO}$
- Inefficient (dissipating more Power), $I_{in} \approx I_{out}$
- Low noise




Input Power – Output Power = $7.2\text{ V} * 100\text{ mA} - 5\text{ V} * 100\text{ mA} = 0.22\text{W}$ of Power Loss !!!

Voltage regulation using a Linear Regulator

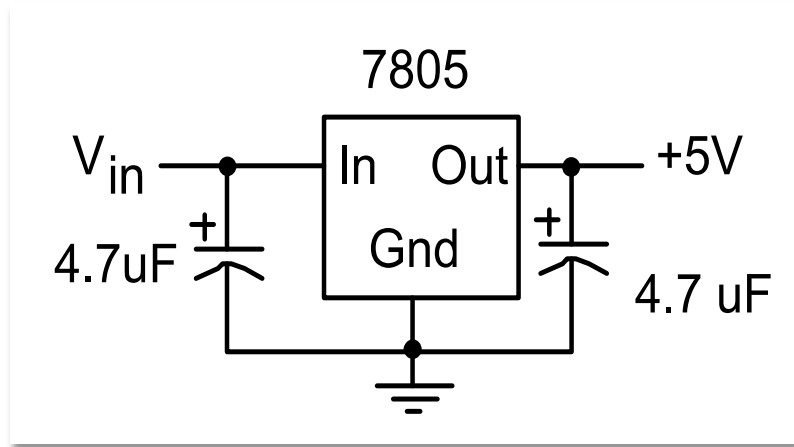Example +5V regulator

Specifications:

- $V_{in} > 7V$ ($V_{DO} = 2V$)
- $I_{out} < 1$ amp



Build this circuit if you do not have the TI-RSLK MAX chassis board from Pololu

WEBENCH® is a free design tool from Texas Instruments you can use to design power supply circuits (link to [WEBENCH Power Designer](#))



Voltage Regulation using Switching regulators

Properties

- Buck: Step-down ($V_{in} > V_{out}$)
- Boost: Step-up ($V_{in} < V_{out}$)
- Buck-boost: either/both
- Noisy due to switching




Power In \approx Power Out

$$V_{in} * I_{in} \approx V_{out} * I_{out}$$

$$\text{Efficiency} = (V_{out} * I_{out}) / (V_{in} * I_{in})$$


Or P_{out} / P_{in}

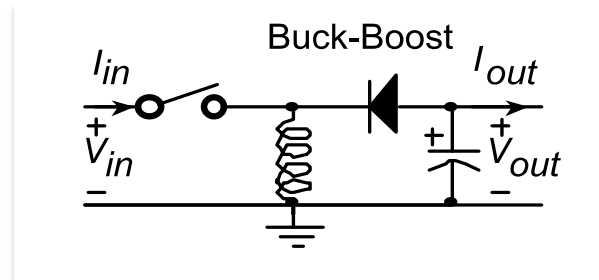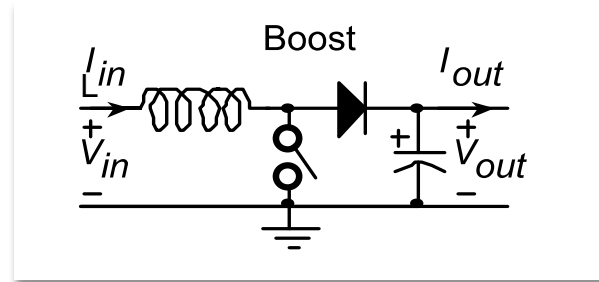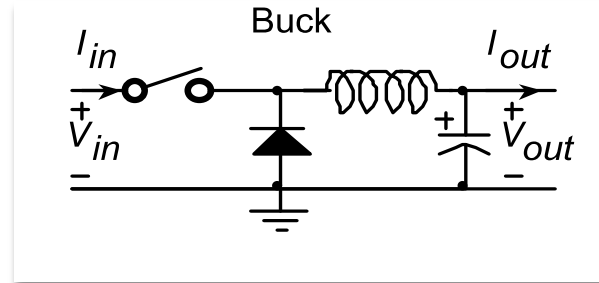To learn more about regulators go to ti.com/PMLK






Switching Regulator Circuit : An Example

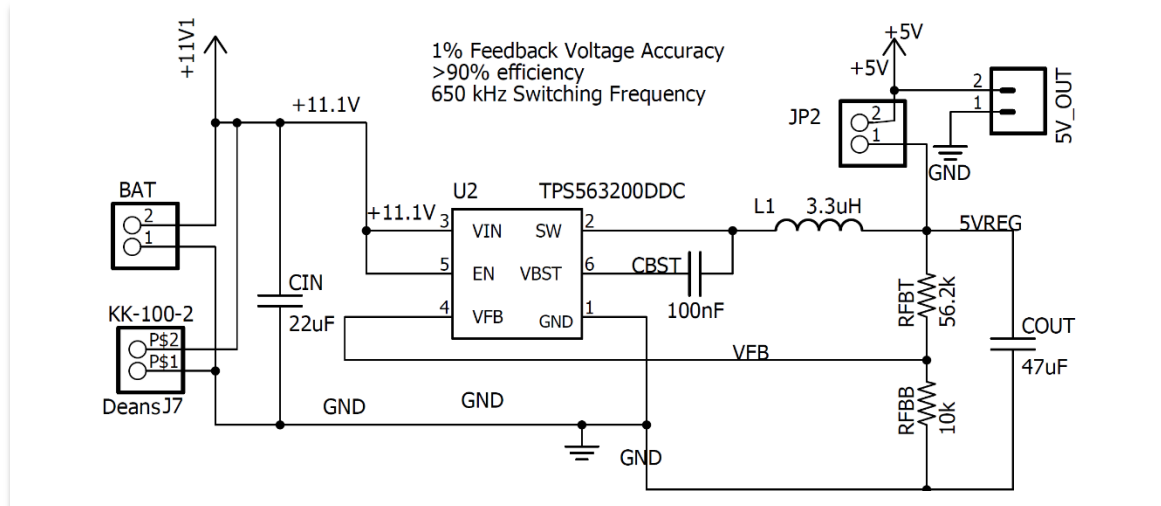

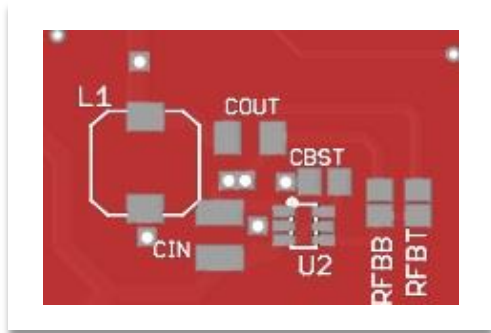Warning :
Pay careful attention
not to connect the
wire from output of
the regulator to
ground!!



Switching Regulator schematic & PCB using TI TPS563200 17-V Input, 2- A Synchronous Step-Down Voltage Regulator

The TI-RSLK Chassis board uses a similar regulator




Switching Regulator Circuit : An Example

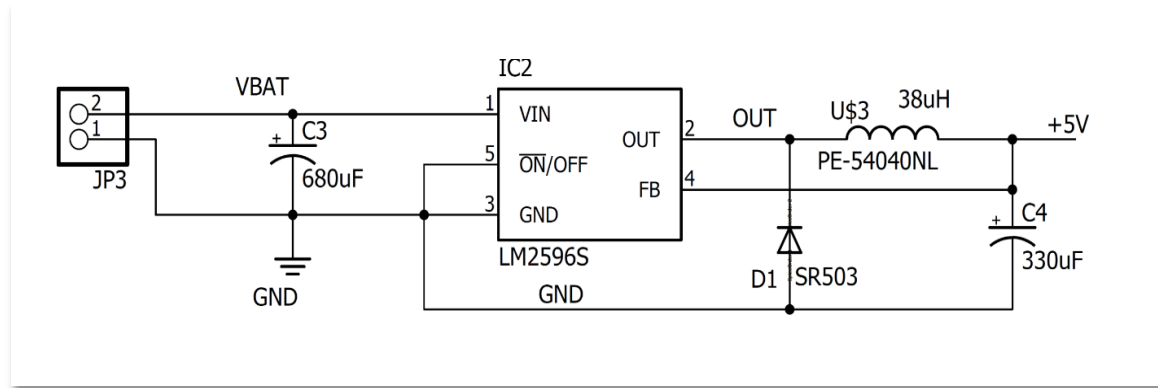- 3.3V, 5V, 12V, and Adjustable Output Versions
- Step-down (buck) switching regulator
- Available in TO-220 and TO-263 Packages
- Ensured 3A Output Load Current version.
- Requires Only 4 External Components
- 150 kHz Fixed Frequency Internal Oscillator
- High Efficiency
- Thermal Shutdown and Current Limit Protection



TO-220-5 package

These features provide circuit protection!




Build this circuit (or 7805) if you do not have the TI-RSLK chassis board

For more information on the power supply design go to <http://www.ti.com/tool/lm2596s-adjvsm>



Switching regulator circuit board using TI's LM2596

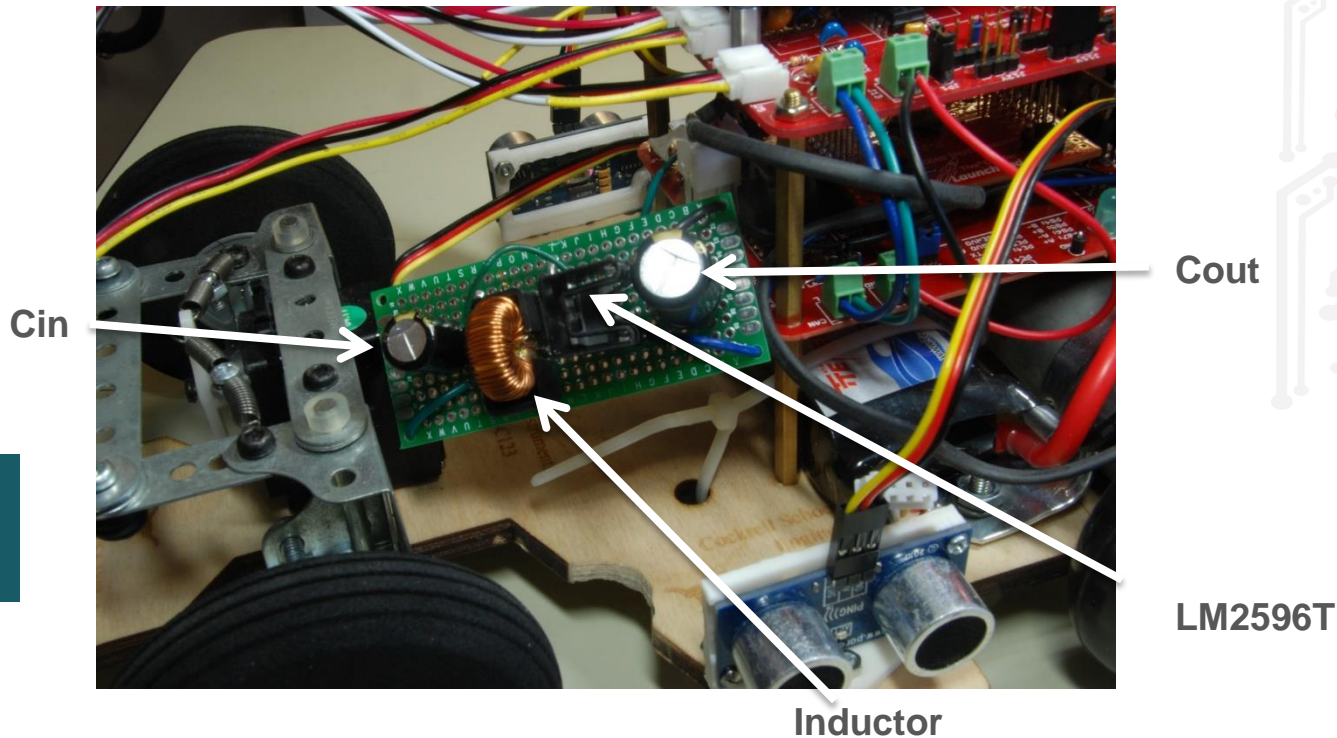- LM2596T-5.0
- All through-hole parts
- Student-proof



Build this circuit if you do not have the TI-RSLK chassis board



Batteries and Voltage Regulation

Summary

- Power Sources - Battery
 - Primary versus secondary
 - Power budget and Energy Storage
- Voltage Regulation - Linear Regulator
 - Low noise
 - Wasted power = $(V_{in} - V_{out}) * I_{out}$
 - Dropout voltage, $V_{in} > V_{out} + V_{do}$
- Voltage Regulation - Switching Regulator
 - Large voltage drop
 - Voltage increase
 - Higher Efficiency

Power = $V * I$
Energy = $V * I * \text{time}$
Energy Storage = $I * \text{time}$
Power Budget:
Average Current $< \text{Energy Storage} / t_{life}$






Module 5

Lecture: TI-RSLK chassis board



TI-RSLK Chassis Board features

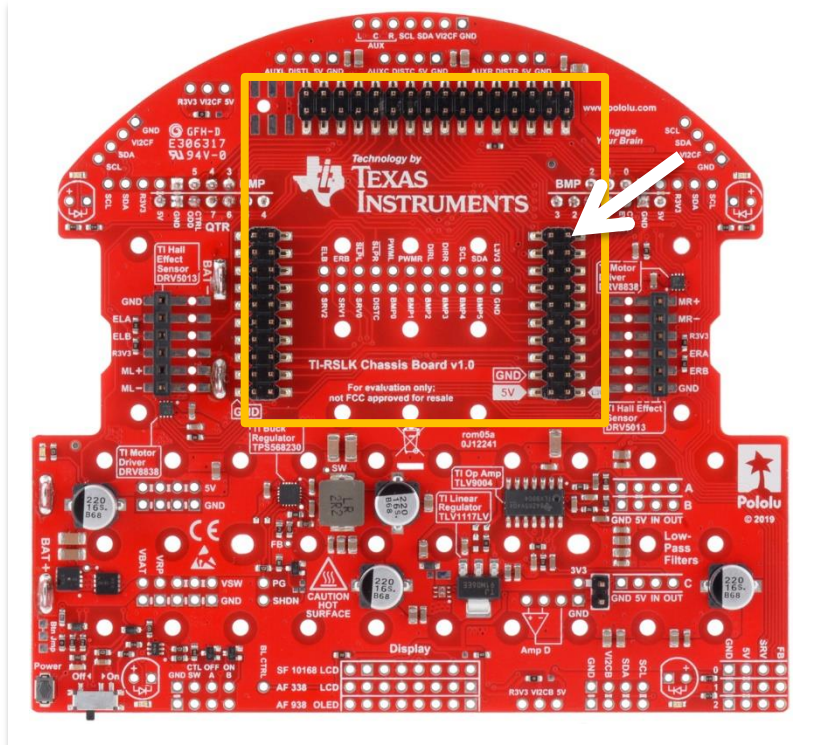- **Male-pinned connectors for the TI LaunchPad**
- Battery input section with on/off switch and latching button
- TI 5V Switching Regulator TPS568230
- TI 3.3V Linear Regulator TLV1117
- TI Op Amp TLV9004
- TI Motor Drivers DRV8838
- TI Hall Effect Sensors on the Motors themselves, DRV5013




TI-RSLK chassis board



TI-RSLK Chassis Board features

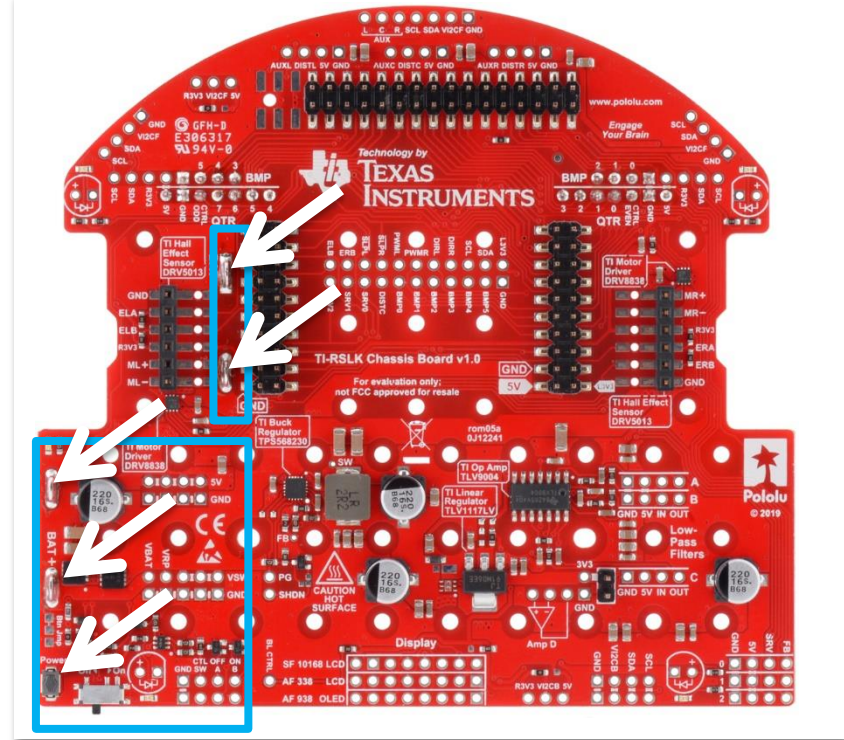- Male-pinned connectors for the TI LaunchPad
- **Battery input section with on/off switch and latching button**
- TI 5V Switching Regulator TPS568230
- TI 3.3V Linear Regulator TLV1117
- TI Op Amp TLV9004
- TI Motor Drivers DRV8838
- TI Hall Effect Sensors on the Motors themselves, DRV5013




TI-RSLK chassis board



TI-RSLK Chassis Board features

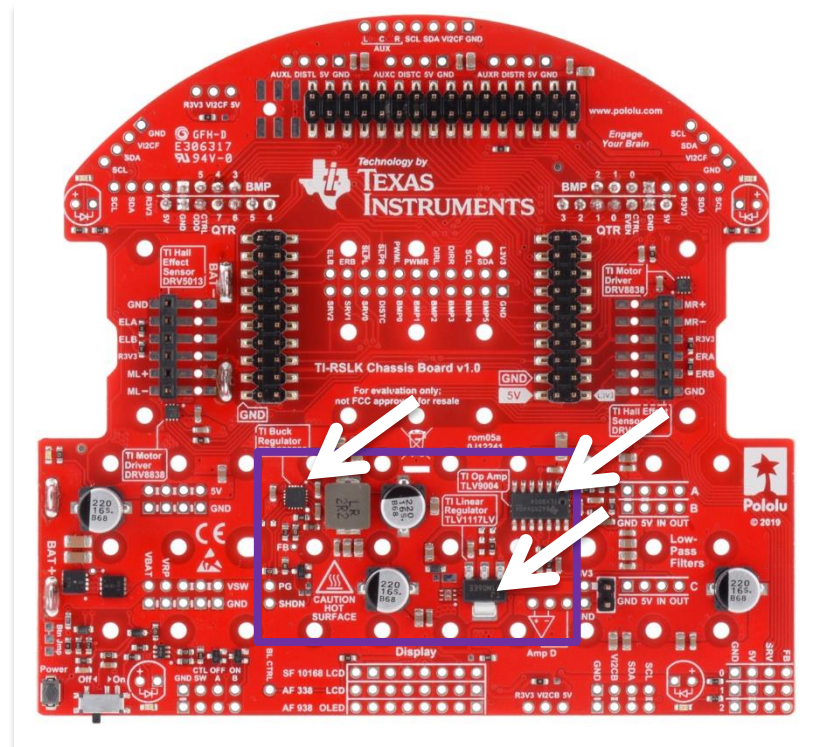- Male-pinned connectors for the TI LaunchPad
- Battery input section with on/off switch and latching button
- **TI 5V Switching Regulator TPS568230**
- **TI 3.3V Linear Regulator TLV1117**
- **TI Op Amp TLV9004**
- TI Motor Drivers DRV8838 and the TI Hall Effect Sensors on the Motors themselves, DRV5013




TI-RSLK chassis board



TI-RSLK Chassis Board features

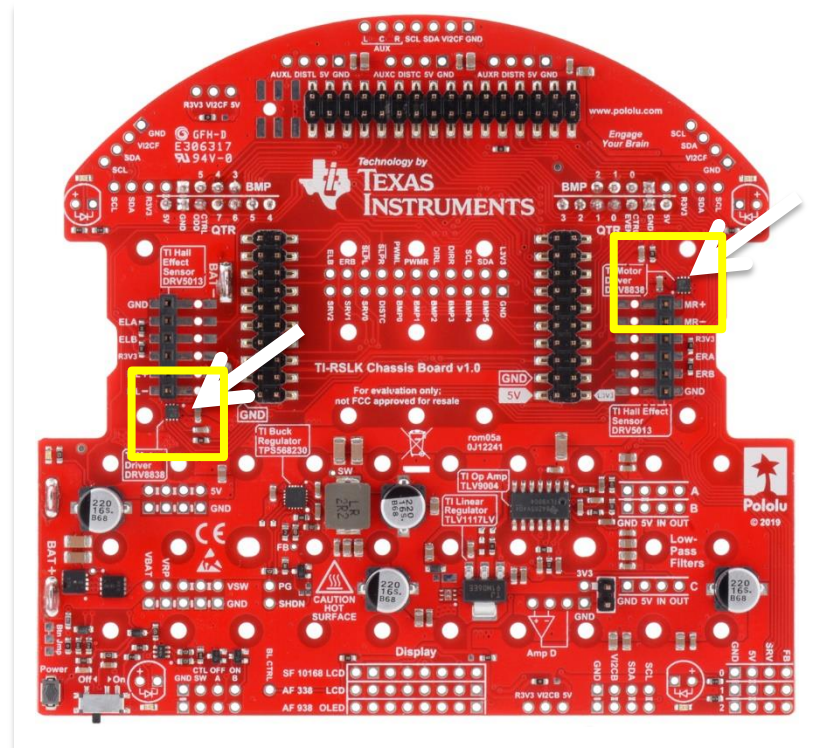- Male-pinned connectors for the TI LaunchPad
- Battery input section with on/off switch and latching button
- TI 5V Switching Regulator TPS568230
- TI 3.3V Linear Regulator TLV1117
- TI Op Amp TLV9004
- **TI Motor Drivers DRV8838**
- TI Hall Effect Sensors on the Motors themselves, DRV5013




TI-RSLK chassis board



TI-RSLK Chassis Board features

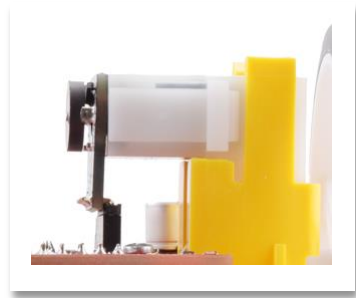- Male-pinned connectors for the TI LaunchPad
- Battery input section with on/off switch and latching button
- TI 5V Switching Regulator TPS568230
- TI 3.3V Linear Regulator TLV1117
- TI Op Amp TLV9004
- TI Motor Drivers DRV8838
- **TI Hall Effect Sensors on the Motors themselves, DRV5013**



Gearmotor and Encoder Assembly for Romi/TI-RSLK MAX robot kit




TI-RSLK Chassis Board features – Power and Gnd

+3.3V

+5V

+7.2V

Gnd

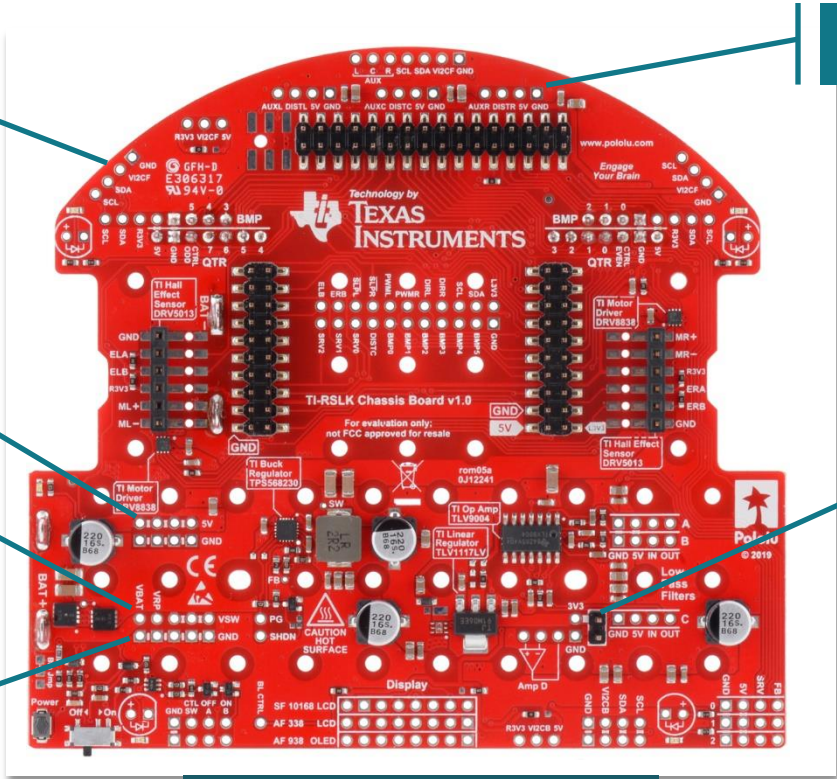


Power to sensor

Important safety feature

TI-RSLK chassis board




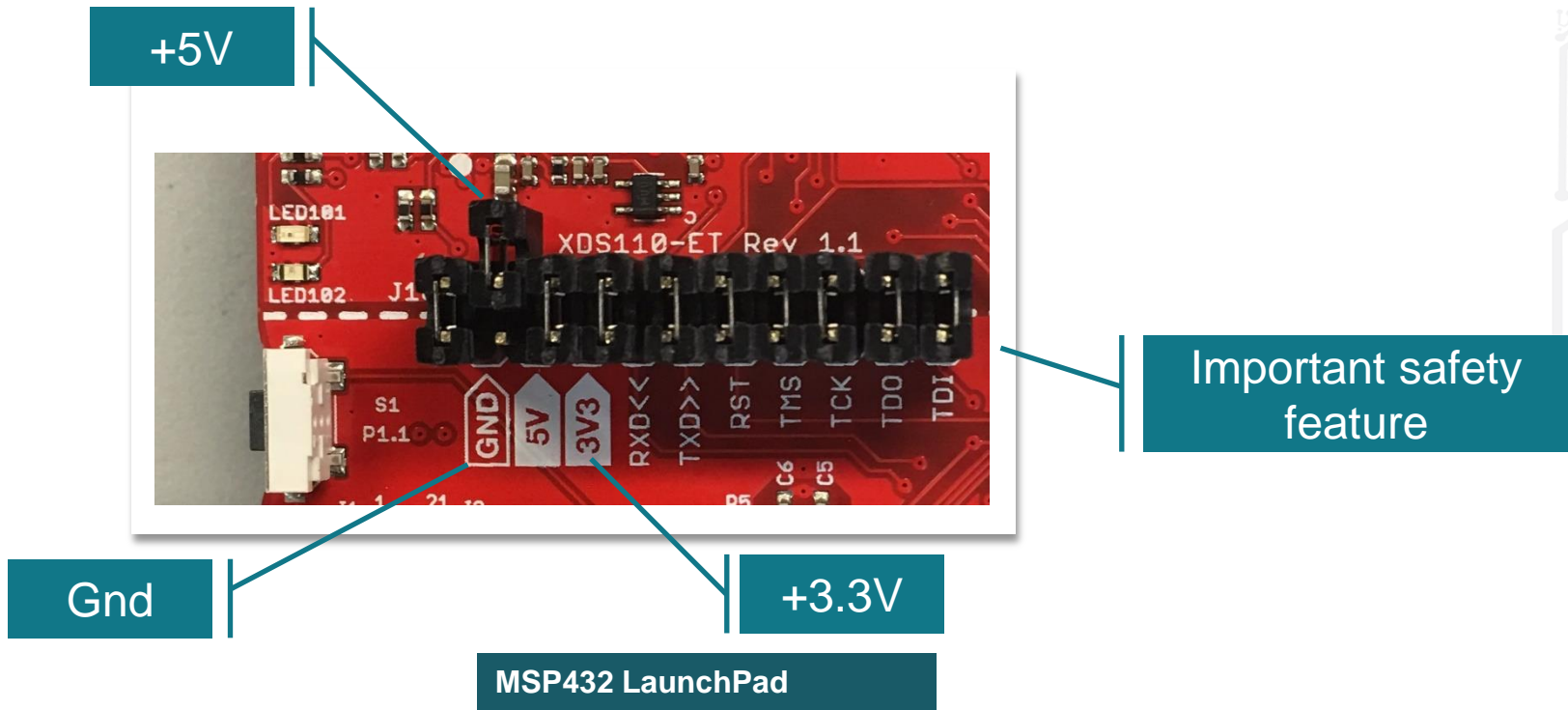TI-RSLK Chassis Board features – Power and Gnd





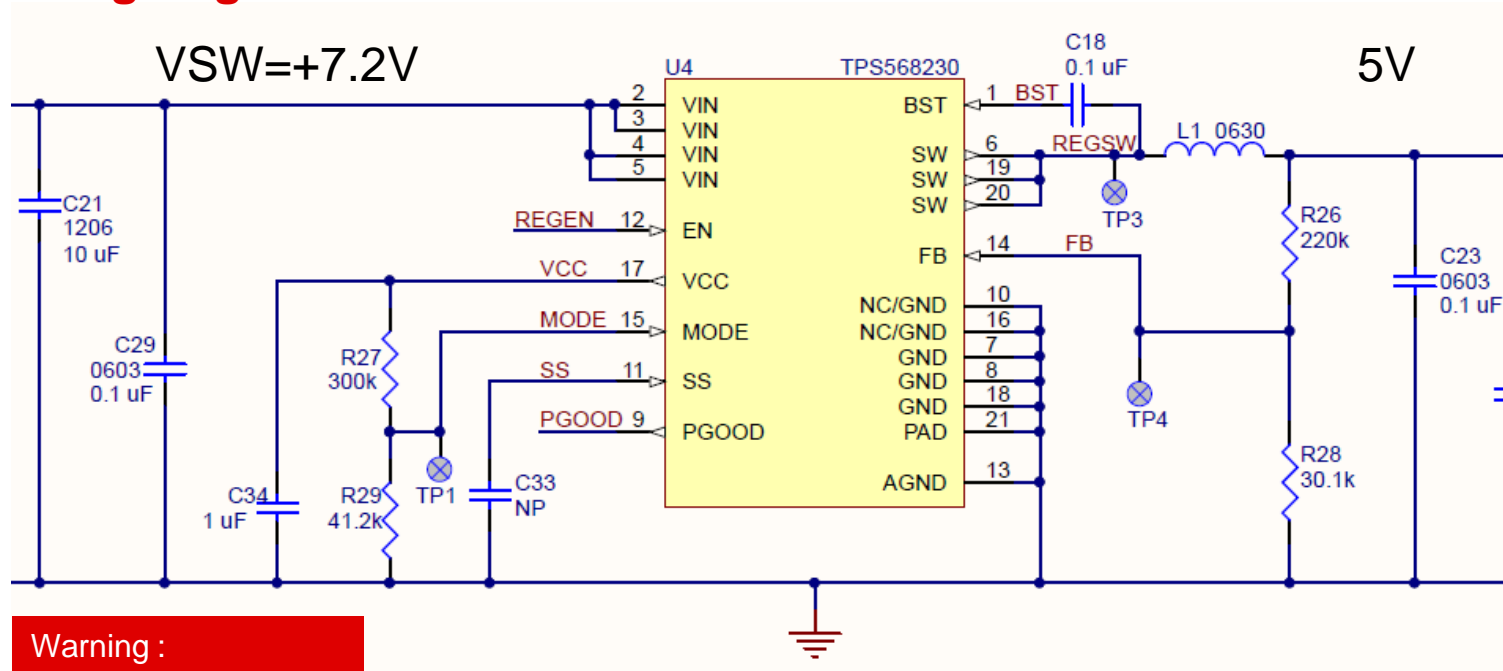Switching Regulator Circuit : TI-RSLK MAX chassis board




Warning :
Pay careful attention
not to connect the
wire from output of
the regulator to
ground.!!

TI-RSLK chassis board uses a TI
TPS568230 4.5 to 18-V input, 5V 8-A
output, synchronous step-down
voltage regulator



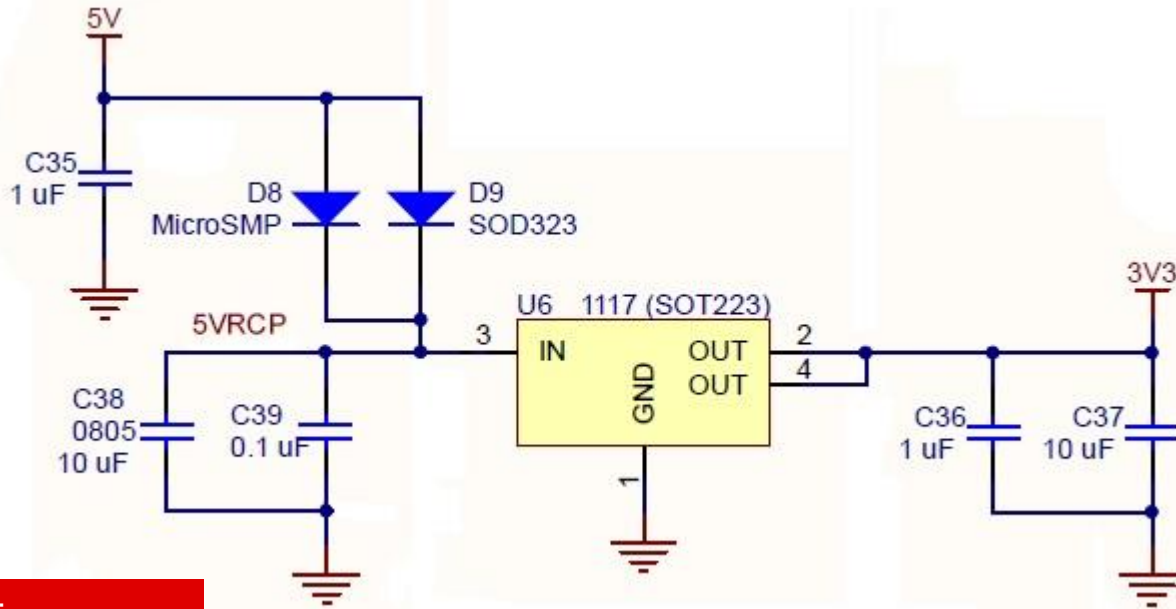Linear regulator circuit: TI-RSLK MAX chassis board




Warning :
Pay careful attention
not to connect the
wire from output of
the regulator to
ground.!!

TI-RSLK chassis board uses a TI
TLV1117 4.7 to 15-V input, 3.3V 800 mA
output, linear regulator



TI-RSLK MAX overview

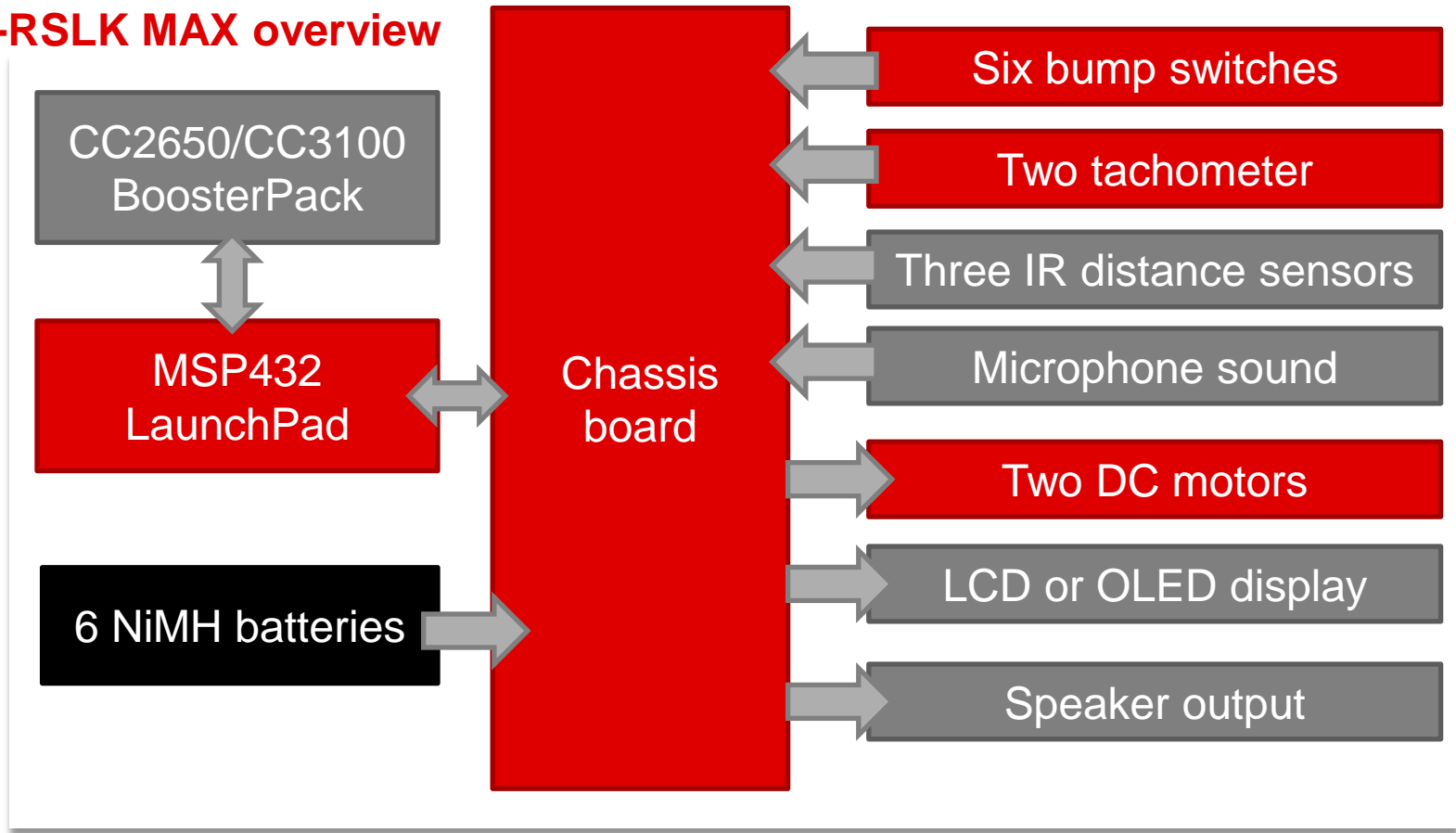

TI-RSLK MAX kit

Not in kit


Optional purchase



TI-RSLK Chassis Board

Summary

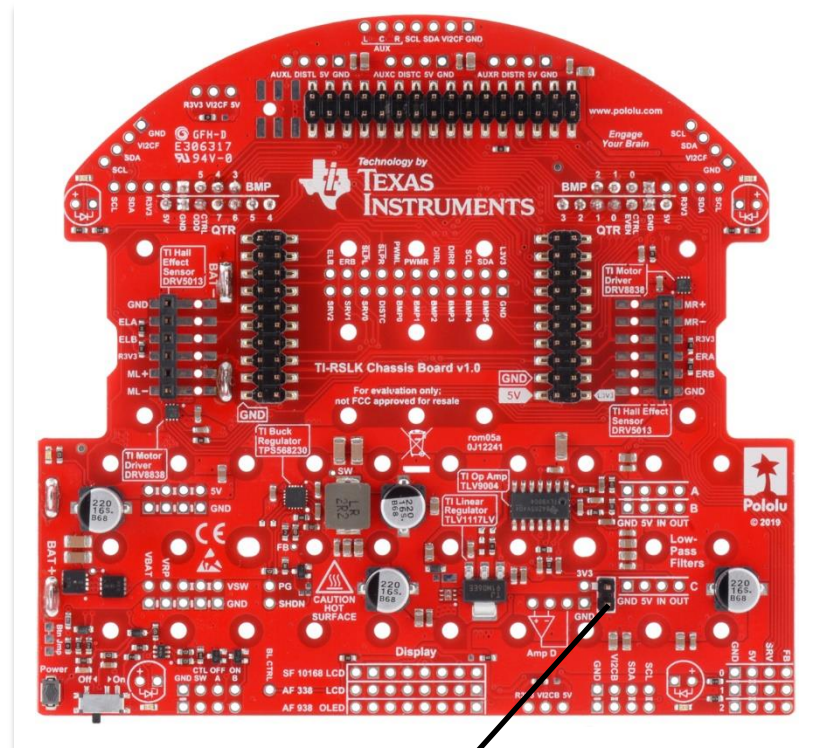- Power
 - Battery
 - +5V and +3.3V regulators
- Interfaces
 - 2 DC motor drivers
 - 2 tachometer interfaces
 - 3 analog log pass filters
 - Extra analog op amp
 - I2C connectors
 - LCD/LED connectors
- Systems approach to robotics
 - Power and interface board
 - MSP432 LaunchPad and software
 - BoosterPacks for wireless communication



Important safety feature

ti.com/rslk



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated