

High-Efficiency Power Solution Using DC/DC Converter for the DM365

*Ambreesh Tripathi**PMP - DC/DC Low Power Converters*

ABSTRACT

This reference design is intended for users designing with TMS320DM365 Processor. This design is ideal for achieving the requirement of a input voltage of 5V, and uses single-output high-efficiency DCDC Converters with integrated FETs for a highly flexible and small configuration.

Contents

1	Introduction	2
2	Power Requirements	2
3	Features	3
4	List of Material	5
5	Test Result	6

List of Figures

1	PMP5047 Reference Design Schematic	4
2	Shows Sequencing in Start up Waveform.....	6
3	Efficiency vs Output Current (TPS62290)	6
4	Efficiency vs Output Current (TPS62260)	6
5	Efficiency vs Output Current (TPS62231)	7

List of Tables

1	TMS320DM365 Power Specs	2
2	PMP5047 List of Materials	5

1 Introduction

In multi-voltage architectures, coordinated management of power supplies is necessary to avoid potential problems and ensure reliable performance. Power supply designers must consider the timing and voltage differences between core and I/O voltage supplies during power up and power down operations.

Sequencing refers to the order, timing and differential in which the two voltage rails are powered up and down. A system designed without proper sequencing may be at risk for two types of failures. The first of these represents a threat to the long term reliability of the dual voltage device, while the second is more immediate, with the possibility of damaging interface circuits in the processor or system devices such as memory, logic or data converter ICs.

Another potential problem with improper supply sequencing is bus contention. Bus contention is a condition when the processor and another device both attempt to control a bi-directional bus during power up. Bus contention may also affect I/O reliability. Power supply designers should check the requirements regarding bus contention for individual devices.

2 Power Requirements

The power specifications and sequencing requirements for TMS320DM365 Processor is shown in the table below.

Table 1. TMS320DM365 Power Specs

	PIN NAME(s)	VOLTAGE (V)	I _{max} (mA)	TOLERANCE	SEQUENCING ORDER
Core	CVDD, VDD12_PRTCSS, VDDA12_DAC, VPP	1.2*	650	±5%	1
I/O	VDDS18, VDD18_PRTCSS, VDDMXI, VDD18_SLDO, VDD18_DDR, VDDA18_PLL, VDDA18_USB, VDDA18_VC, VDDA18_ADC, VDDA18_DAC	1.8	95	±5%	2
I/O	VDDS33, VDDA33_USB, VDDA33_VC	3.3	51	±5%	3
I/O	VDD_AEMIF1_18_3 3, VDD_AEMIF2_18_3 3, VDD_ISIF18_33	1.8 / 3.3	65	±5%	Ramp with appropriate voltage
Note: <ul style="list-style-type: none"> • If running DM365 @ 300MHz, then CVDD, VDD12_PRTCSS, VDDA12_DAC and VPP = 1.35V and I_{max} = 800mA. • If using PRTCSS, power-up sequencing changes to: <ol style="list-style-type: none"> 1. Power on PRTCSS core (1.2-V) while RESET is low 2. Power on PRTCSS I/O (1.8-V) 3. Power on Main core (1.2-V) 4. Power on Main I/O (1.8-V) 5. Power on Main/Analog I/O (3.3-V) 					

3 Features

The design uses the following high-efficiency DCDC Converters with integrated FETs

Devices:	TPS62260(3.3V), TPS62290(1.2V), TPS62231(1.8V)
Power supply specs:	
Vin	5 V ± 10%
Vout1	1.2 V ± 5% at 800 mA
Vout2	1.8 V ± 5% at 200 mA
Vout3	3.3 V ± 5% at 200 mA
Sequencing	1) Vout1 2) Vout2 3) Vout3

TPS62260

- High Efficiency Step Down Converter
- Output Current up to 600mA
- Power Save Mode at Light Load Currents
- Allows < 1 mm Solution Height

TPS62290

- High Efficiency Step Down Converter
- Up to 1-A Output Current
- Power Save Mode at Light Load Currents
- Output Voltage Accuracy in PWM mode ±1.5%

TPS62231

- 3 MHz switch frequency
- Up to 94% efficiency
- Output Peak Current up to 500 mA
- Small External Output Filter Components (1.0μH/ 4.7μF)
- Small 1 × 1.5 × 0.6mm³ SON Package
- Fixed 1.8 V eliminates need for external voltage-setting resistors

More information on the Devices can be found from the data sheets.

TPS62260 – [SLVS763B](#)

TPS62290 – [SLVS764C](#)

TPS62231 – [SLVS941](#)

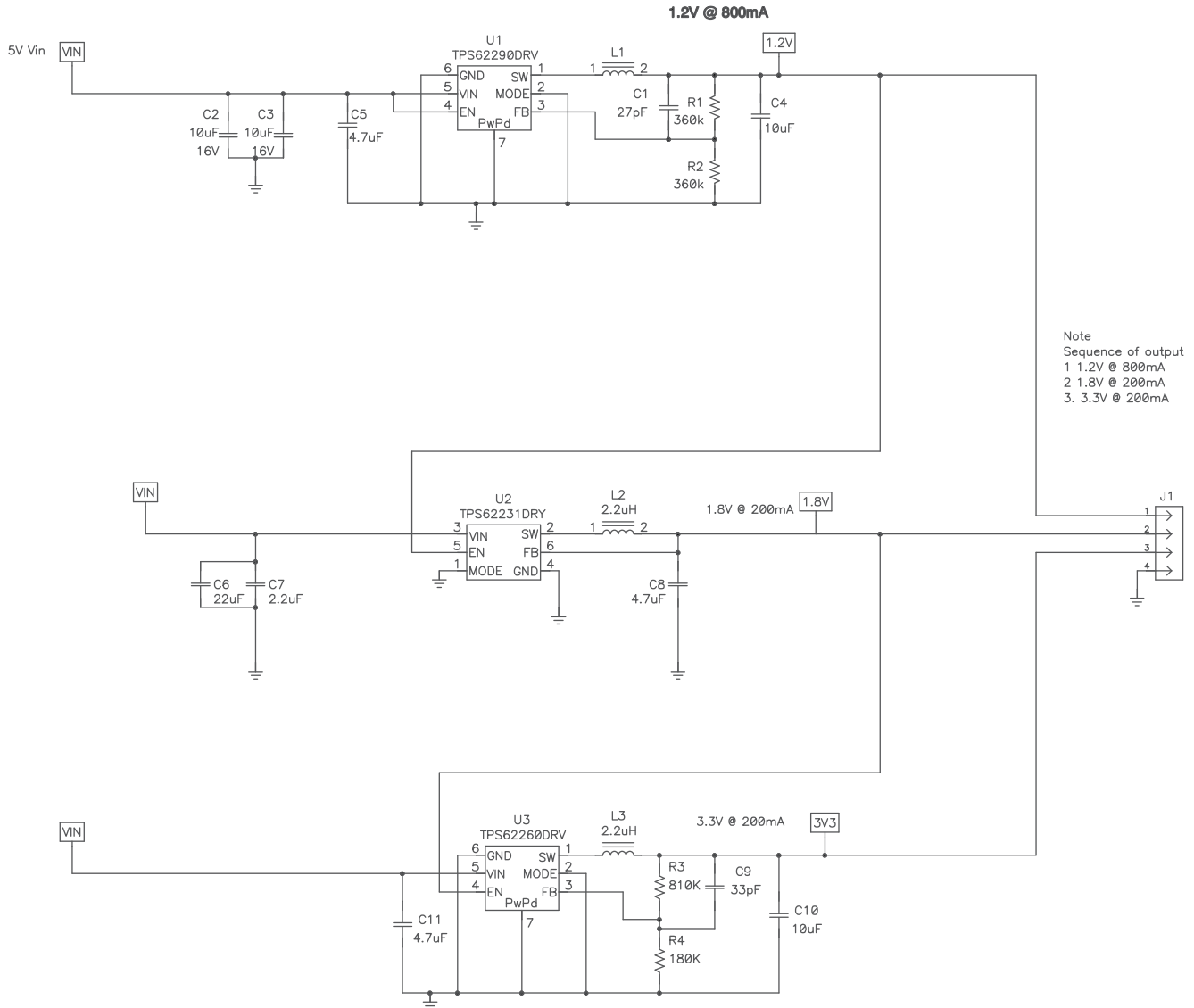


Figure 1. PMP5047 Reference Design Schematic

Proper sequencing is insured in the design with the use of enable pins. The Core 1.2V at 1000mA (TPS62290) comes first, which in turn enable the TPS62231 and output of TPS62231 enables TPS62260 device thus, following the required sequence.

4 List of Material

Table 2. PMP5047 List of Materials

Count	RefDes	Value	Description	Size	Part Number	MFR	Area
1	C1	27 pF	Capacitor, Ceramic, 0.01 μ F, 10-V, X7R, 15%	0603	Std	TDK	5650
2	C2	10 μ F	Capacitor, Ceramic, 16V, X7R, 20%	1206	C3216X7R1C106MT	TDK	15390
	C3	10 μ F	Capacitor, Ceramic, 16V, X7R, 20%	1206	C3216X7R1C106MT	TDK	15390
1	C4	10 μ F	Capacitor, Ceramic, 6.3V, X5R, 10%	0603	C0603CH0J106k	TDK	5650
1	C5	4.7 μ F	Capacitor, Ceramic, 10V, X5R, 10%	0603	C0603CH1A475K	TDK	5650
1	C6	22 μ F	Capacitor, Ceramic, 10V, X5R, 20%	1210	Std	Std	83,600
1	C7	2.2 μ F	Capacitor, Ceramic, 6.3V, X5R, 20%	0402	JDK105BJ225MV	Taiyo Yuden	2800
1	C8	4.7 μ F	Capacitor, Ceramic, 6.3V, X5R, 20%	0402	JDK105BJ475MV	Taiyo Yuden	2800
1	C9	33 pF	Capacitor, Ceramic, 16V, X7R, 15%	0402	Std	TDK	2800
1	C10	10 μ F	Capacitor, Ceramic, 6.3V, X5R, 15%	0603	Std	TDK	5650
1	C11	4.7 μ F	Capacitor, Ceramic, 6.3V, X5R, 15%	0603	Std	TDK	5650
1	J1	PEC36SAAN	Header, Male 4-pin, 100mil spacing, (36-pin strip)	0.100 inch x 4	PEC36SAAN	Sullins	50000
1	L1	2.2 μ H	Inductor, SMT, 2.1A, 0.110 Ω	0.118 x 0.118 inch	LPS3015-222ML	Coilcraft	26,560
1	L2	2.2 μ H	Inductor, SMT, 0.7A, 230-m Ω	0805	MIPSS220120D2R2	FDK	10160
1	L3	2.2 μ H	Inductor, 1A, 200-m Ω	0.080 x 0.080 inch	EPL2010-222ML	Coilcraft	108,300
2	R1	360k	Resistor, Chip, 1/16W, 1%	0603	Std	Std	5650
	R2	360k	Resistor, Chip, 1/16W, 1%	0603	Std	Std	5650
1	R3	810K	Resistor, Chip, 1/16W, 1%	0402	Std	Std	2800
1	R4	180K	Resistor, Chip, 1/16W, 1%	0402	Std	Std	2800
1	U1	TPS62290DRV	IC, 1A xx V Step Down Converter	SON-6	TPS6229xDRV	TI	16416
1	U2	TPS62231DRY	IC, 3MHz Ultra Small Step Down Converter, x.x V	QFN	TPS62232DRY	TI	6020
1	U3	TPS62260DRV	IC, 2.25MHz 600mA Step-Down Converter	SON-6[DRV]	TPS62260DRV	TI	20736

- Notes: 1. These assemblies are ESD sensitive, ESD precautions shall be observed.
2. These assemblies must be clean and free from flux and all contaminants. Use of no clean flux is not acceptable.
3. These assemblies must comply with workmanship standards IPC-A-610 Class 2.
4. Ref designators marked with an asterisk (***) cannot be substituted. All other components can be substituted with equivalent MFG's components.

5 Test Result

The startup waveform, shown in Figure 2, demonstrates that the required sequencing order is followed.

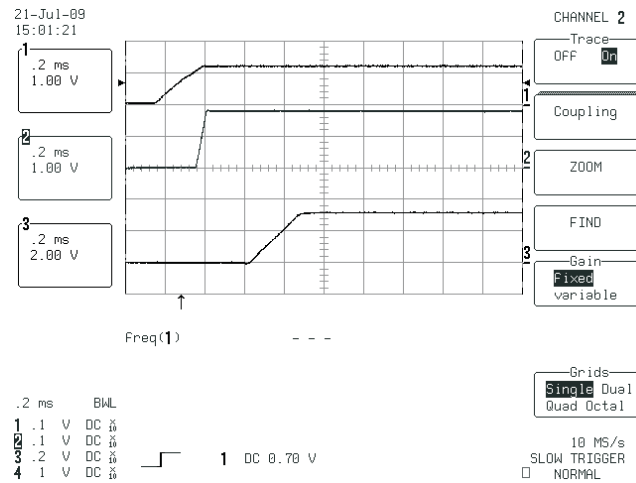


Figure 2. Shows Sequencing in Start up Waveform

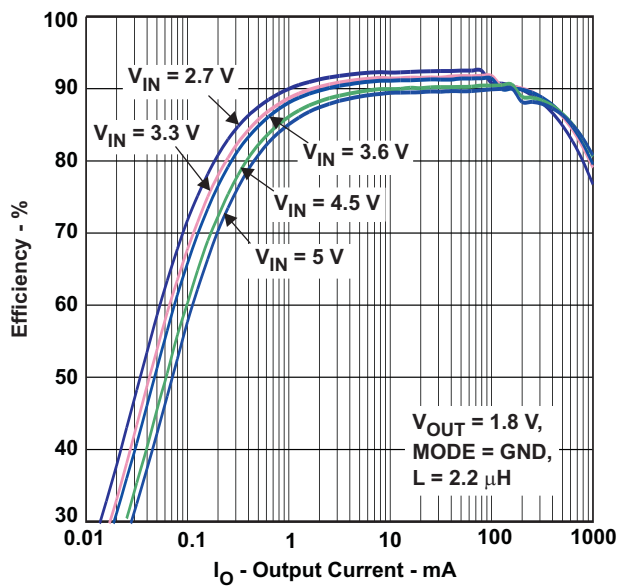


Figure 3. Efficiency vs Output Current (TPS62290)

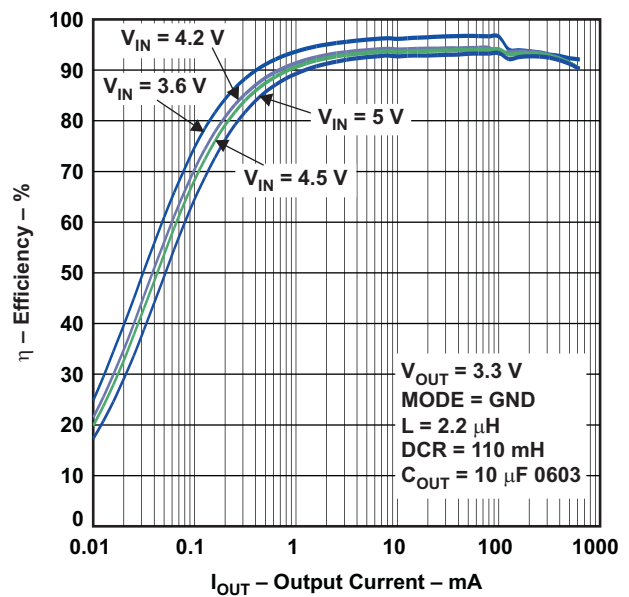


Figure 4. Efficiency vs Output Current (TPS62260)

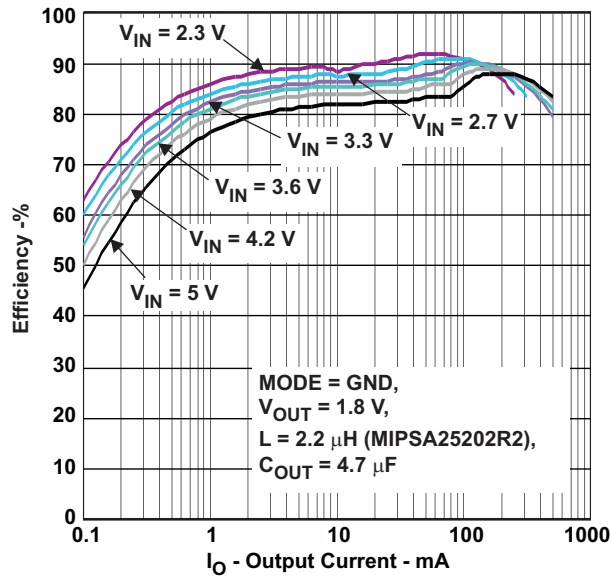


Figure 5. Efficiency vs Output Current (TPS62231)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated