

Test Report: PMP30555


3.5-W Isolated Push-Pull Reference Design for Auxiliary Power Supply



Description

This reference design is an isolated open-loop push-pull with “cascode” FETs that finds its typical application in isolated gate drive supply. The cascode connection extends the input voltage range of SN6505B from 5 V to 24 V, and two outputs supply 15 V at 120 mA and 5 V at 350 mA. Its 2-mm transformer makes the solution ultra-thin.

 [The PMP30555 Rev_B Reference Design has been built on PMP30555 Rev_A PCB.](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage	24 V \pm 10% (DC)
Output #1, Voltage	15 V \pm 10% (DC) at 24 Vin
Output #1, Current	120 mA
Output #2, Voltage	5 V \pm 10% (DC) at 24 Vin
Output #2, Current	350 mA

1.2 Required Equipment

- 0...30 V, (min. 300 mA), constant voltage source (VS1)
- 0...20 V, (0...150 mA), constant current electronic load
- 0...10 V, (0...500 mA), constant current electronic load
- Oscilloscope (min. 100 MHz bandwidth)


1.3 Considerations

- a) Connect the source VS1 to pin 1 & 2 of J1.
- b) Connect the loads to J2 (pin 1 & 2) with common ground to pin 3, set to CC mode.
- c) Connect oscilloscope probes to Q2-Drain and Q2-Source versus primary ground.
- d) Connect oscilloscope probes to C1, C4 and anode terminal of D4.

2 Testing and Results

 2.1 Efficiency Graphs:

The efficiency graphs, versus output currents, are shown below. The voltage of power source has been set to 21.6 V, 24 V and 26.4 V (24 V \pm 10 %).



2.2 Efficiency Data:

The efficiency graph reports the data from the tables shown below:

Vin(V)	Iin(mA)	Pin (W)	V15 (V)	I15 (mA)	V5 (V)	I5 (mA)	Pout (W)	Efficiency (%)
21.63	13.2	0.286	14.87	0	4.985	0	0	0%
21.64	20.4	0.441	14.81	6.2	4.950	13.5	0.159	35.94%
21.62	30.1	0.651	14.76	12.3	4.907	37.6	0.366	56.25%
21.61	45.9	0.992	14.70	23.8	4.872	72.3	0.702	70.78%
21.59	97.1	2.096	14.55	63.5	4.794	173.8	1.757	83.82%
21.62	177.8	3.844	14.35	119.4	4.683	350.5	3.355	87.27%


Vin(V)	Iin(mA)	Pin (W)	V15 (V)	I15 (mA)	V5 (V)	I5 (mA)	Pout (W)	Efficiency (%)
24.02	14.1	0.339	16.54	0	5.566	0	0	0%
24.04	21.6	0.519	16.48	6.6	5.527	13.5	0.183	35.32%
24.03	30.6	0.735	16.44	11.6	5.493	37.7	0.398	54.10%
24.03	46.9	1.127	16.38	23.8	5.458	72.3	0.784	69.61%
24.01	97.0	2.329	16.22	61.8	5.374	173.9	1.937	83.17%
24.02	180.1	4.326	16.01	121.1	5.261	350.5	3.783	87.44%

Vin(V)	Iin(mA)	Pin (W)	V15 (V)	I15 (mA)	V5 (V)	I5 (mA)	Pout (W)	Efficiency (%)
26.42	14.9	0.394	18.21	0	6.153	0	0	0%
26.43	22.6	0.597	18.15	6.6	6.111	13.5	0.202	33.87%
26.43	32.2	0.851	18.11	12.8	6.076	37.7	0.461	54.15%
26.42	47.9	1.266	18.05	23.8	6.040	72.3	0.866	68.45%
26.40	98.2	2.592	17.89	62.3	5.955	173.9	2.150	82.94%
26.40	181.7	4.797	17.66	122.1	5.838	350.5	4.203	87.61%


2.3 Output Voltage Regulation

The output voltage regulation graphs, for each output, are shown below. Both outputs have been loaded with the same percent, at the same time, of their nominal currents.

15 V output voltage:



 



5 V output voltage:

 

   2.4 Cross Regulation

While one output of the converter was loaded at constant fixed current (0, 50 % and 100 % of nominal load), in the other one the load current has been varied from 0 to 100 % and the cross-regulation performance has been measured. The input voltage of the converter was 24 V.



 

2.5 Dimensions

The board dimensions are 51.56 mm x 17.27 mm, height = 2 mm (without terminal blocks).


3 Waveforms

3.1 Switching

The switching waveforms have been measured by supplying the converter at 24 V in full load condition (120 mA and 350 mA), with waveforms referred to primary ground.

C1: Drain voltage of Q2 (20 V/div, 500 nsec/div, no BWL)

 C4: Source voltage of Q2 (2 V/div, no BWL)




3.2 Output Voltage Ripples and D4 Anode Voltage

The output voltage ripples, and the switch-node of output diode D4 have been measured by supplying the converter at 24 V, in full-load condition.

C1: 15V output voltage (100 mV/div, 500 nsec/div, AC coupling, 20 MHz BWL)

C3: 5V output voltage (50 mV/div, AC coupling, 20 MHz BWL)

 C4: D4-Anode voltage (20 V/div, 200 MHz BWL)



3.3 Startup

The behavior of the converter, showing V_{in} and output voltages, is shown below.


In these graphs, V_{in} has been applied by connecting the source to the power supply, when it was already on.

Conditions: $V_{in} = 24 V$, both outputs fully loaded.


C1: 15V output voltage (5 V/div, 2msec/div, 20 MHz BWL)

C3: 5V output voltage (2 V/div, 20 MHz BWL)


C4: Input voltage (10 V/div, 20 MHz BWL)

 

 Same conditions like previous graph, but with smaller time scale (100 usec/div).



 Conditions: $V_{in} = 24\text{ V}$, both outputs at zero load.
 C1: 15V output voltage (5 V/div, 2msec/div, 20 MHz BWL)
 C3: 5V output voltage (2 V/div, 20 MHz BWL)
 C4: Input voltage (10 V/div, 20 MHz BWL)



3.4 Shut Down


The behavior of the converter, during shut down, has been measured and shown below.

Conditions: $V_{in} = 24\text{ V}$, both outputs fully loaded.

C1: 15V output voltage (5 V/div, 500 usec/div, 20 MHz BWL)

C3: 5V output voltage (2 V/div, 20 MHz BWL)

C4: Input voltage (10 V/div, 20 MHz BWL)

 

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated