

**Test Data
For PMP10645
04/22/2015**



Contents

- 1) Overview
- 2) Power Specification
- 3) Block Diagram
- 4) Connector Description
- 5) Test result

1. Overview

The PMP10645 reference design is designed for SM74101 mosfet driver with a Fly-Buck power supply to drive half bridge. The SM74101 is a tiny 7A mosfet driver which can support 3A source current and 7A sink current. It has a tiny WSON-6 package and an 8-Lead exposed-pad MSOP package. It also provides both inverting and non-inverting inputs to satisfy requirements for inverting and non-inverting gate drive with a single device type. The isolated output Fly-Buck power supply has four outputs to supply the gate driver bias in motor drive or inverter applications. It features the LM5017, 7.5-100V wide V_{in} , 600mA, Constant On-Time (COT), synchronous buck regulator configured in the Fly-Buck topology. The Fly-Buck converter is a simple, cost effective and compact isolated power solution. The reference board generates two pairs of +8 V and -4.5V outputs each with 100mA current capability. The user can use jumpers to set Unipolar or Bipolar PWM gate driver. The user can also set higher gate voltage by changing the Fly-buck feedback resistor when set the Unipolar PWM gate driver.

2. Power Specification

For gate driver:

Input: 5V PWM signal

Output: Unipolar or Bipolar PWM gate driver

For Fly-Buck:

V_{in} range: 19V – 30V

Nominal V_{in} = 24V

Quad Isolated Outputs: 2 x (+8V@100mA, -4.5V@100mA)

F_{sw} = 350kHz

3. Block Diagram


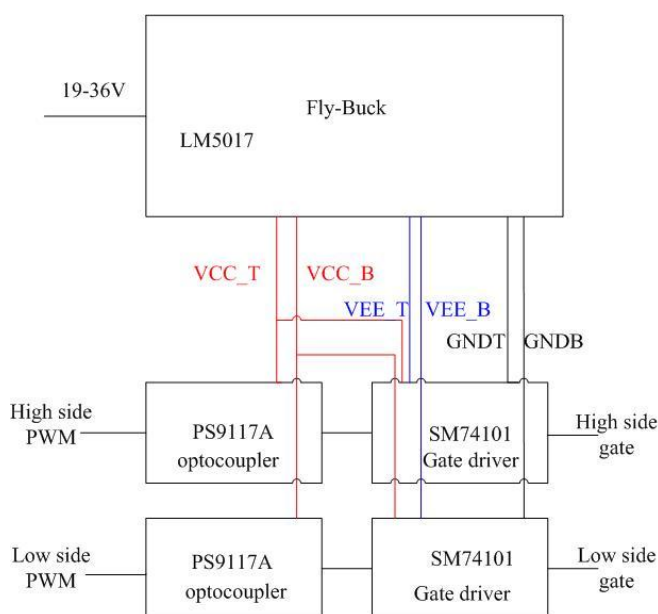



Figure 1

The Fly-Buck can provide the isolated power supply for the gate driver. We also use the optocoupler and the small delay time tiny gate driver to isolate and drive the pwm signal. Because the optocoupler is inverting logical. So we can set the gate driver inverting logical too to get the right logic.

4. Board Photo

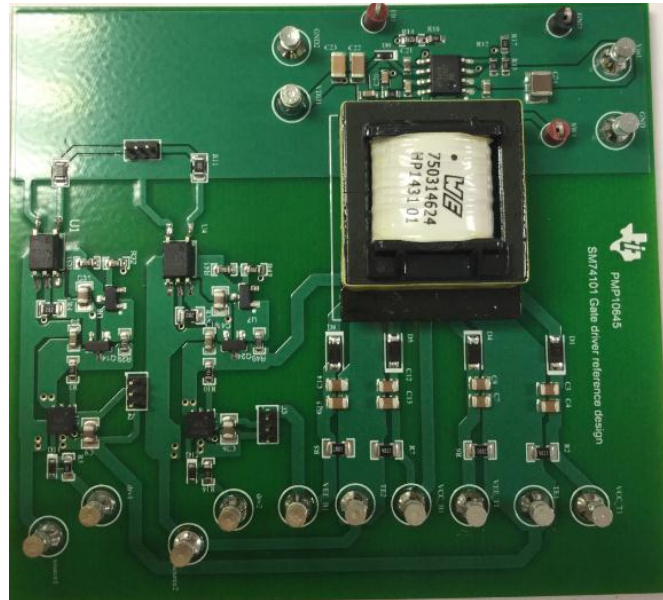

(a) Top

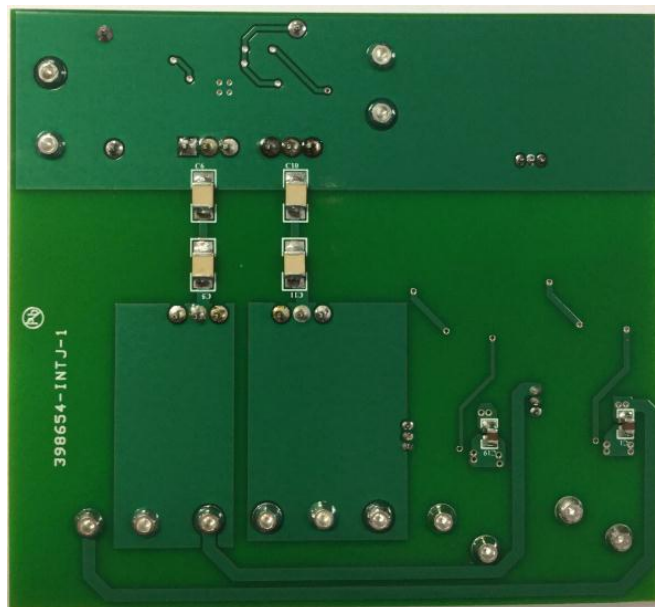

(b) Bottom

Figure 2

Size: 78x71mm²

4. Connector Description

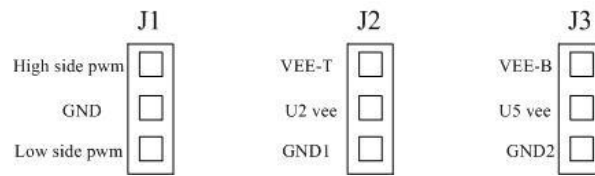


Figure 3

J1 –is high side and low side pwm signal can provide by the MCU (Micro Controller Unit).

J2 –is optional for the Unipolar or Bipolar PWM high side gate driver.

J3 –is optional for the Unipolar or Bipolar PWM low side gate driver.



Figure 4

If connect the jumper as figure 4(a), user can get the Bipolar PWM gate signal. If connect the jumper as figure 4(b), user can get the Unipolar PWM gate signal.

5. Test result

1) Delay time test: Give a signal at the input of the optocoupler, then test the delay time between the optocoupler and the output signal of SM74101.

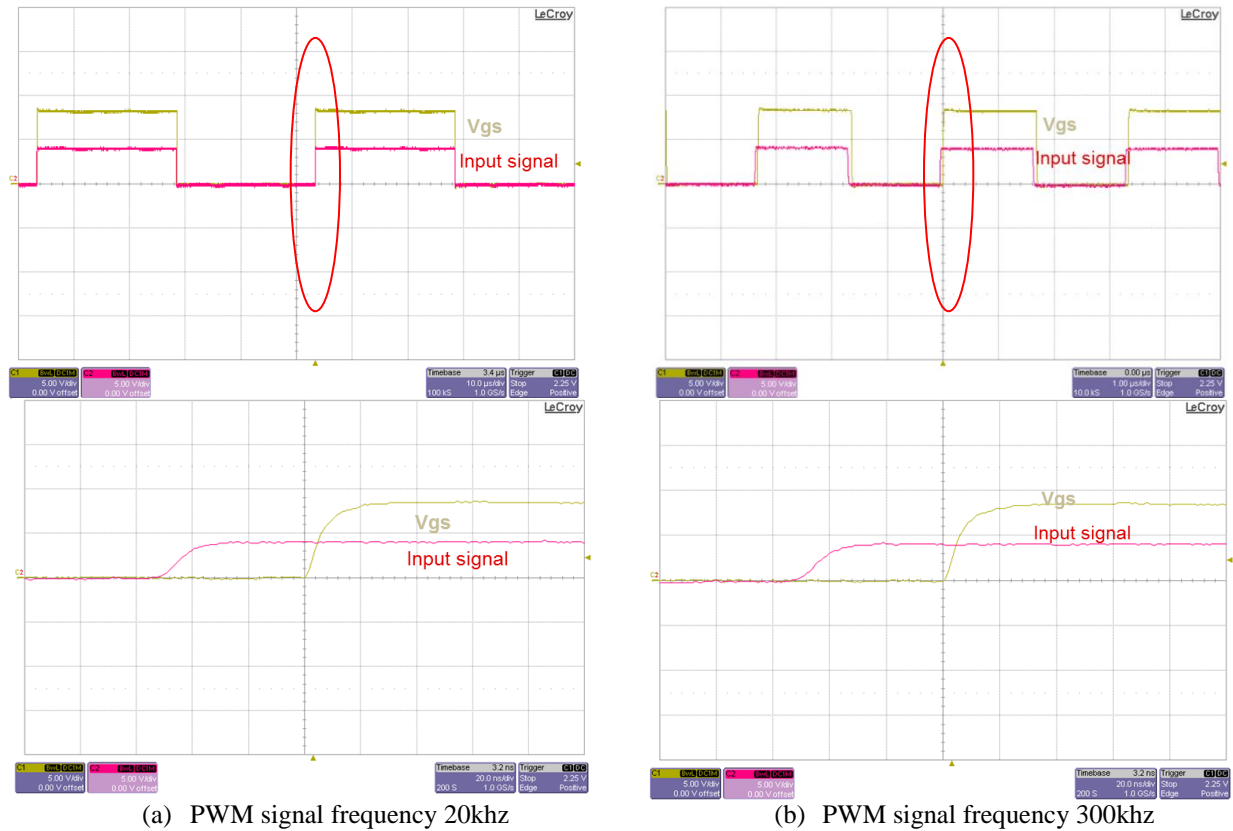


Figure 5

Test Result: The total delay time of the optocoupler and the gate driver is only 30ns when the pwm signal frequency is 20khz or 300khz.

2) Source and sink current test: Give a 20khz PWM signal at the input of the optocoupler, use 1ohm drive resistor and 100nF capacitive load. Check the voltage drop on 1 ohm resistor.

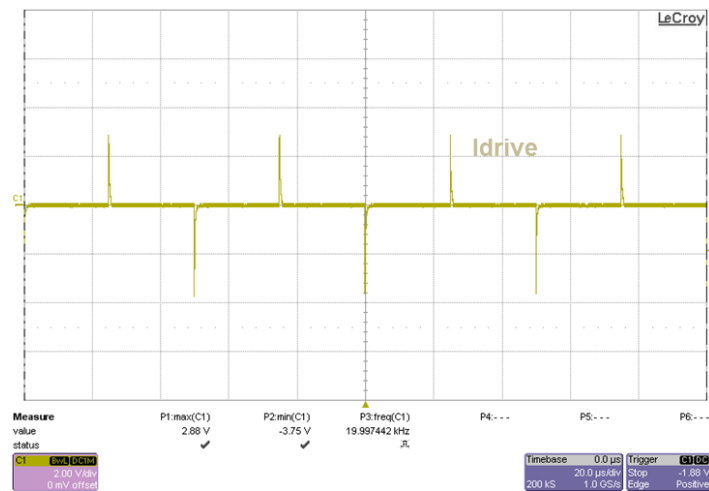


Figure 6

Test Result: SM74101 can provide 3A source current according to figure 6, the sink current can be higher when use a smaller drive resistor.

3) Rise and fall time test: Give a 300khz PWM signal at the input of the optocoupler, use 1ohm drive resistor and 2.2nF capacitor load. Check the output signal waveform rise and fall time.

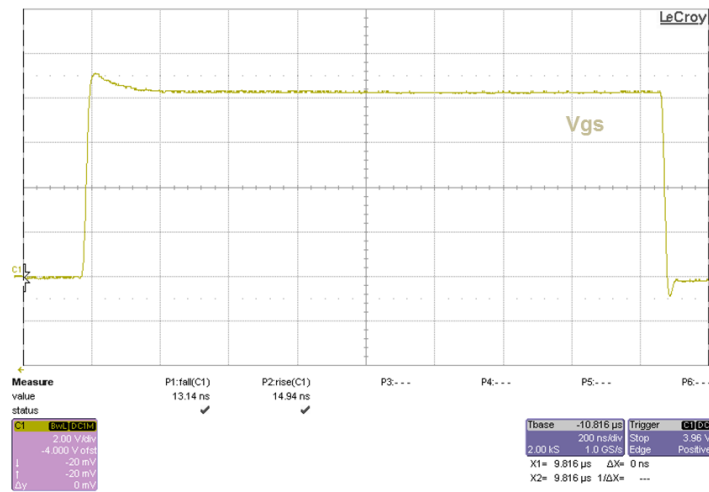


Figure 7 VCC=8V

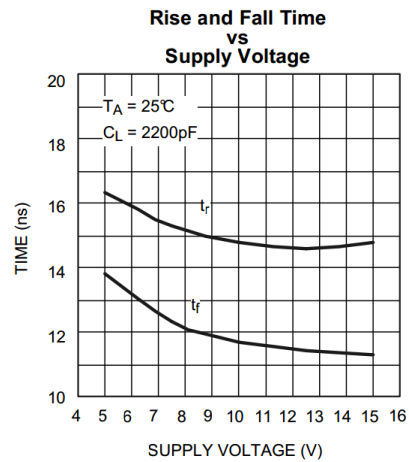


Figure 8 rise and fall time vs supply voltage (from SM74101 datasheet)

Test Result: The rise time is only 15ns, and the fall time only 13ns, almost the same as the datasheet data.

4) Bipolar PWM test: connect the J2 & J3 as the figure 4(a).

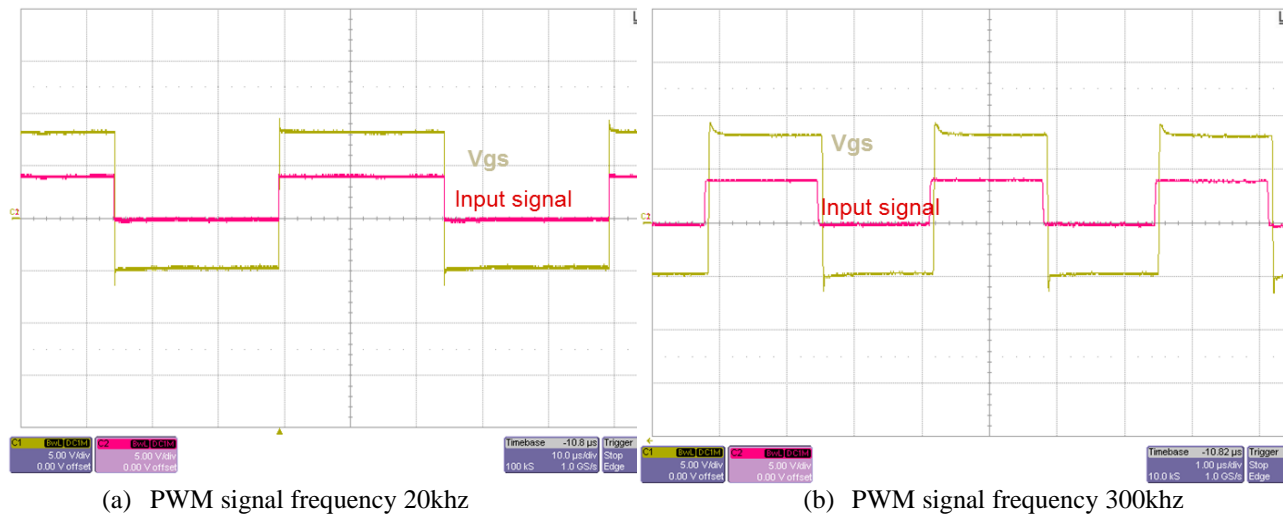


Figure 9

Test Result: The board works well when the user set the Bipolar PWM gate signal out.

For Fly-buck:

Ti has many Fly-Buck reference designs, so this test report focuses on the gate driver SM74101. But the LM5017 Fly-Buck design is also a simple, cost effective and compact isolated power solution and it has very good cross regulation and line/load response.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated