
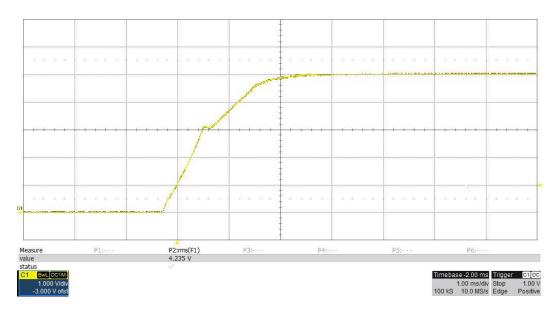

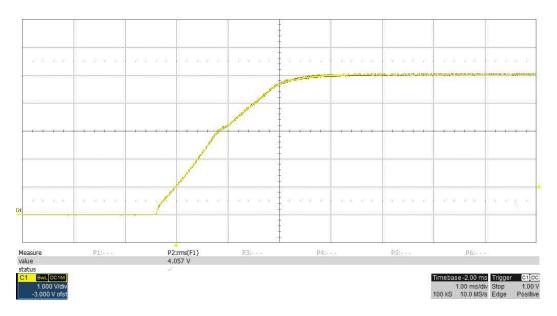
### 1 Startup

Output voltage startup waveform, 0A load 1V/ div, 1mS/ div




Output voltage startup waveform, 3A load 1V/ div, 1mS/ div




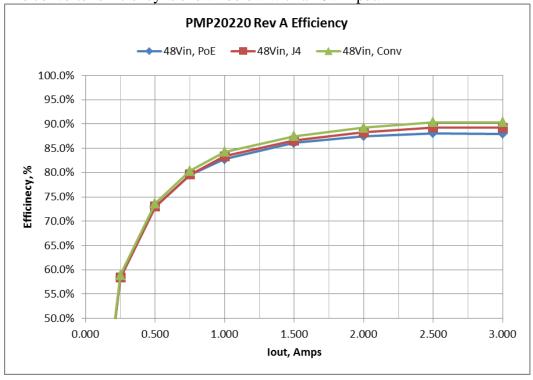
## 2 Efficiency


The converter efficiency is shown below with a 48V input.



## 3 Output Ripple Voltage

Output ripple voltage across C18 10mV/div, 2uS/div


Measured 12.3mVpp

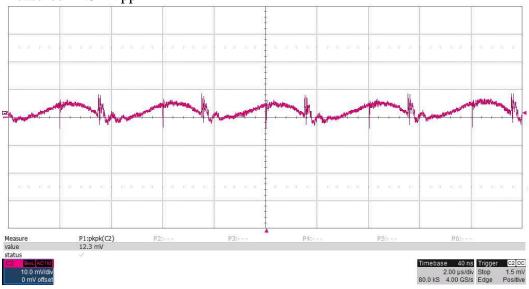



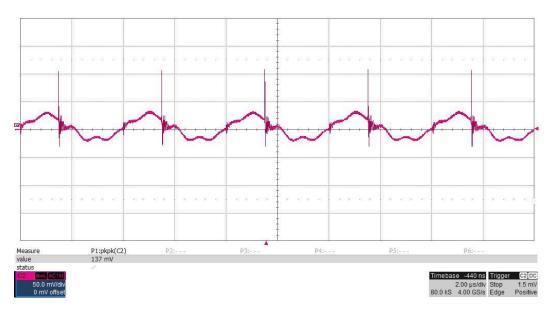
## 4 Input Ripple Voltage

Input ripple voltage across C12 50mV/div, 2uS/div Measured 137mVpp


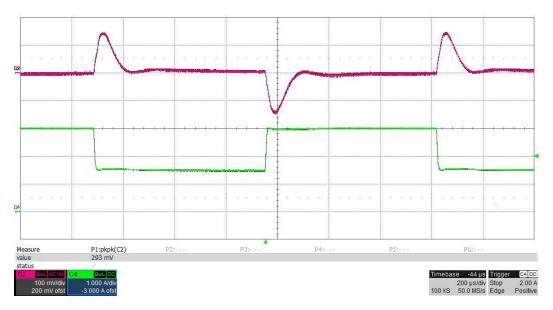
#### 5 Load Transients

Output voltage response (ac coupled)
1.5A to 3Aload step, 250mA/usec slew rate
100mV/div, 1A/ div, 200uS/ div
Measured 293mVpp




#### 6 Switch Node Waveforms

Drain voltage of Q1, 57V input and 3A load.

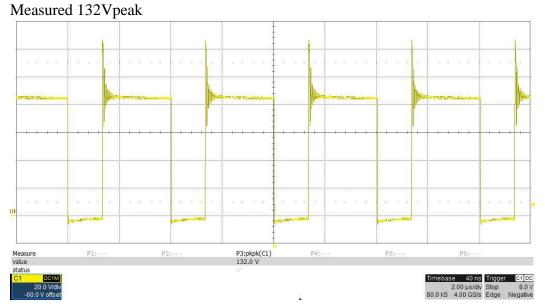
## PMP20220 Test Results



 $20V/\ div,\ 2.00uS/\ div,\ 750MHz\ bandwidth$ 



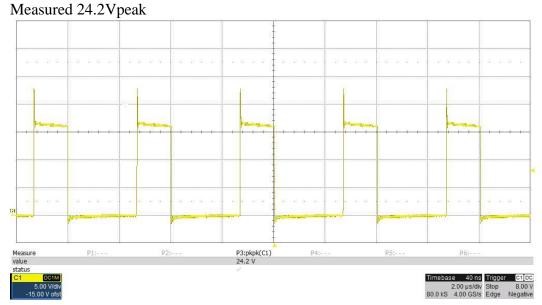Drain voltage of Q1, 57V input and 3A load. 5V/div, 2.00uS/div, 750MHz bandwidth






# 7 Control Loop Gain / Stability

The converter's loop response with a 48V input and 5V/3A output is shown below.

Band Width = 6.422KHz


Phase Margin = 55.81 degrees

Gain Margin=10dB

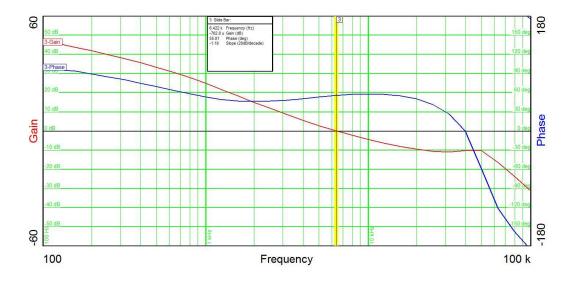
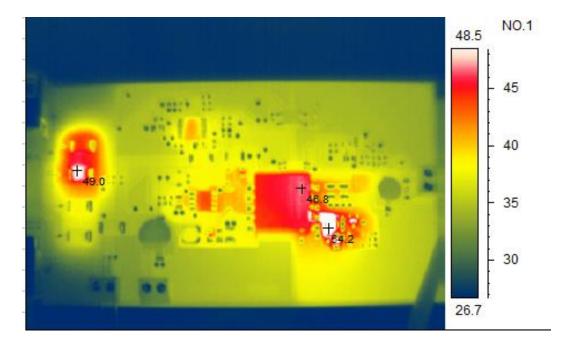
### 8 Thermal Image

The thermal image below shows operation at 48V input and 5V/3A output with no airflow






### 9 Photo

Top:



#### Bottom:

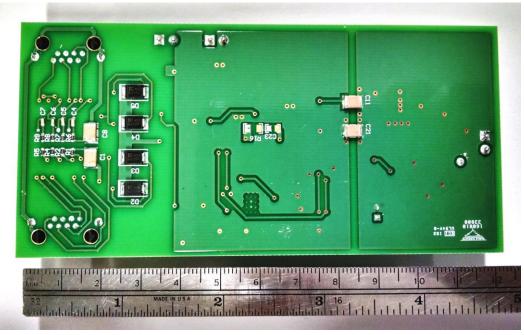

#### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated