

DAC Post-Filter Design Based on DRV6xx Family

Ryan (Fan) Wang

HPA-AIP-Home Audio Amplifiers

ABSTRACT

This application report describes DAC post-filter design based on the Texas Instruments DirectPath™ line driver products. Theories, detailed design steps, and application circuits are discussed for Blu-ray™ DVD players, as an example. These theories, detail design steps, and application circuits are applicable to any other applications with the use of DACs.

Contents

1	Introduction	1
2	DAC Post-Filter Design Principles	2
	2.1 Butterworth Filter Basics	2
	2.2 Butterworth Filter Design Based on MFB	2
3	Design Steps and Example	3
4	Interfacing to Differential Output DAC	5
5	Reference Circuit for 2-Vrms Output Application	6
	5.1 Interfacing DRV6xx to PCM1754	6
	5.2 Interfacing DRV6xx to PCM1789	7
6	Conclusion	7
7	References	7

List of Figures

1	Single-Ended Input MFB Topology	2
2	Circuit for Interfacing to Differential Output DAC	5
3	Simplified Circuit for Interface to Differential Output DAC	6
4	Interfacing DRV6xx to PCM1754	6
5	Interfacing DRV6xx to PCM1789	7

List of Tables

1	Coefficients for Butterworth Filter	2
2	Parameters for PCM1754 2Vrms Output Circuit	6
3	Parameters for PCM1789 2Vrms Output Circuit	7

1 Introduction

The DRV6xx family of devices is 2-to-3 Vrms, pop-free, stereo line drivers, which are designed to allow simplified system architecture and reduce total component count and cost. Designed using the Texas Instruments patented DirectPath™ technology, the device integrates a charge pump to generate a negative supply rail that provides a clean, pop-free, ground-biased output capable of driving up to 2 Vrms with only a single 3.3-V supply voltage.

The DRV6xx family has built-in shutdown control (Enable pin) for pop-free, on/off control. Some family members such as the DRV603 have an external undervoltage protection (UVP) pin that can be used to detect system power loss and mute the outputs automatically. This function can fully eliminate pop noise generated by a prestige circuit (such as a DAC) during power loss.

DirectPath is a trademark of Texas Instruments.
Blu-ray is a trademark of Blu-ray Disc Association.

These advantages make the DRV6xx family excellent choices for digital-to-analog converter (DAC), 2-Vrms-output, post-filter applications, especially in television, set top box, and Blu-ray DVD audio line-out applications. This application report describes a step-by-step guide for DAC post-filter design based on the DRV6xx family.

2 DAC Post-Filter Design Principles

2.1 Butterworth Filter Basics

The Butterworth filter architecture provides maximum pass-band flatness and is often used as a post-filter for DAC outputs, providing flat gain in the 20-Hz to 20-kHz audio frequency range. A second-order filter also helps suppress out-of-band noise with an attenuation of 40 dB/decade.

The general transfer function of second-order, low-pass filter is:

$$H(f) = \frac{H_0}{1 + a_1 \frac{f}{f_c} \times j + b_1 \left(\frac{f}{f_c} \times j \right)^2} \quad (1)$$

The quality factor Q of the low-pass filter (Equation 1) is defined as:

$$Q = \frac{\sqrt{b_1}}{a_1} \quad (2)$$

For a Butterworth filter, the filter coefficients are as shown in Table 1.

Table 1. Coefficients for Butterworth Filter

Butterworth Second-Order, Low-Pass Filter Coefficients			
Parameter	a1	b1	Q
Value	1.414	1	0.707

2.2 Butterworth Filter Design Based on MFB

A Butterworth low-pass filter can be created by a multiple feedback (MFB) topology circuit with appropriate parameters; a single-ended input MFB circuit is shown in Figure 1:

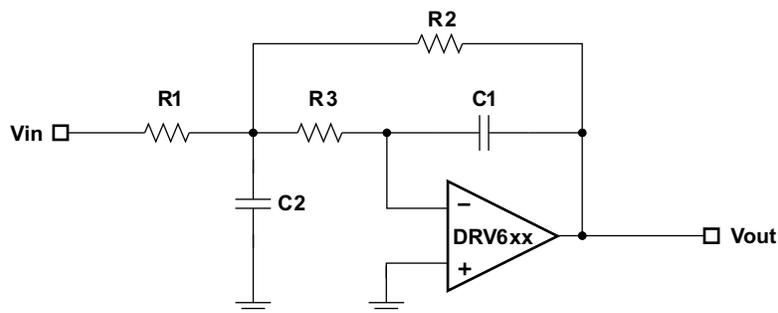


Figure 1. Single-Ended Input MFB Topology

The transfer function of the circuit in Figure 1 is:

$$H(f) = \frac{-\frac{R_2}{R_1}}{1 + 2\pi f_c C_1 \left(R_2 + R_3 + \frac{R_2 R_3}{R_1} \right) \frac{f}{f_c} \times j + (2\pi f_c)^2 C_1 C_2 R_2 R_3 \left(\frac{f}{f_c} \times j \right)^2} \quad (3)$$

Coefficient comparison with Equation 1 obtains the following relations:

$$H_0 = -\frac{R_2}{R_1}$$

$$a_1 = 2\pi f_c C_1 \left(R_2 + R_3 + \frac{R_2 R_3}{R_1} \right) = 1.414$$

$$b_1 = (2\pi f_c)^2 C_1 C_2 R_2 R_3 = 1$$
(4)

Given C1, C2, and H0, and solving for the resistors R1, R2, and R3:

$$R_2 = \frac{a_1 C_2 \pm \sqrt{a_1^2 C_2^2 - 4b_1 C_1 C_2 (1-H_0)}}{4\pi f_c C_1 C_2}$$

$$= \frac{1.414 \times C_2 \pm \sqrt{(1.414 \times C_2)^2 - 4 \times C_1 C_2 (1-H_0)}}{4\pi f_c C_1 C_2}$$

$$R_3 = \frac{b_1}{4\pi^2 f_c^2 C_1 C_2 R_2} = \frac{1}{4\pi^2 f_c^2 C_1 C_2 R_2}$$

$$R_1 = -\frac{R_2}{H_0}$$
(5)

In order to obtain real values for R2, C2 one must satisfy the following condition:

$$C_2 \geq C_1 \frac{4b_1(1-H_0)}{a_1^2}$$
(6)

3 Design Steps and Example

Step 1. Decide pass-band dc gain:

Pass-band dc gain provides scalable output for the DAC output. Taking PCM1754 for an example, the maximum single-ended analog output is 1.414 Vrms. If a 2-Vrms output from the DRV6xx post-filter is desired, the pass-band gain must be set to 1.414 V/V, or 3 dB. Thus:

$$H_0 = -\frac{R_2}{R_1} = -1.414$$
(7)

Step 2. Choose a suitable value for C1:

The recommended value for C1 for DRV6xx is from 15 pF to 220 pF. Select 100 pF for C1; C2 can be selected according to Equation 6:

$$C_2 \geq C_1 \frac{4b_1(1-A_0)}{a_1^2} = 483 \text{ pF}$$
(8)

Choose standard value 560 pF for C2.

Step 3. Choose cutoff frequency according to desired application:

The Blu-ray™ DVD players require the audio frequency response to be within ±0.1 dB between 20 Hz and 20 kHz. Thus, the cutoff frequency (–3-dB point) is set at 54 kHz, according to Equation 1, resulting in an attenuation of only 0.08 dB at 20 kHz.

$$f_c = 54 \text{ kHz}$$
(9)

Step 4. Calculating resistance value:

Using the selected values of C1, C2, Fc, and dc gain Ho, resistors R1, R2, and R3 can be calculated according to Equation 5. The equations have two possible solutions, providing two groups of results. In this example:

$$\text{Solution 1} = \begin{pmatrix} R_1 = 9.27 \text{ k}\Omega \\ R_2 = 13.108 \text{ k}\Omega \\ R_3 = 11.834 \text{ k}\Omega \end{pmatrix} \text{ and } \text{Solution 2} = \begin{pmatrix} R_1 = 20.203 \text{ k}\Omega \\ R_2 = 28.567 \text{ k}\Omega \\ R_3 = 5.43 \text{ k}\Omega \end{pmatrix} \quad (10)$$

Input resistor R1 must be larger than 10 kΩ for a good, low-frequency response, Solution 2 satisfies this condition. Choose standard values for Solution 2:


$$\text{Solution} = \begin{pmatrix} R_1 = 20 \text{ k}\Omega \\ R_2 = 28 \text{ k}\Omega \\ R_3 = 5.49 \text{ k}\Omega \end{pmatrix} \quad (11)$$


Step 5. Final result and gain and phase response curve:

The final result for the given design specification is:

$$\text{Final Results} = \begin{pmatrix} C_1 = 100 \text{ pF} \\ C_2 = 560 \text{ pF} \\ R_1 = 20 \text{ k}\Omega \\ R_2 = 28 \text{ k}\Omega \\ R_3 = 5.49 \text{ k}\Omega \end{pmatrix} \quad (12)$$

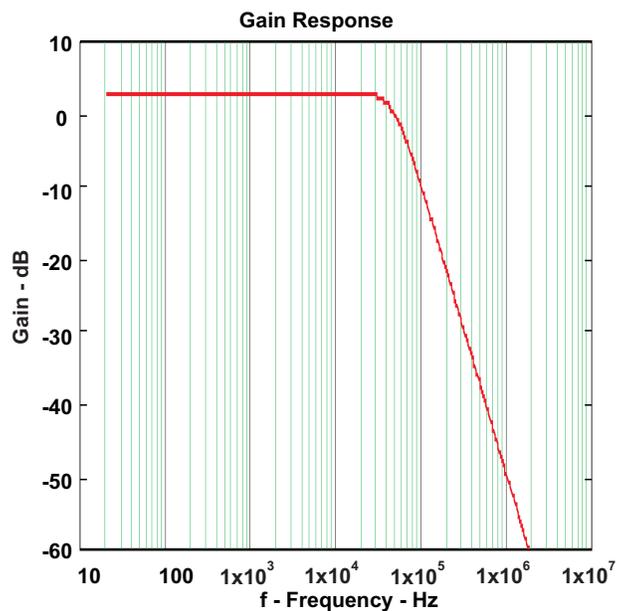The gain and phase response curves follow.



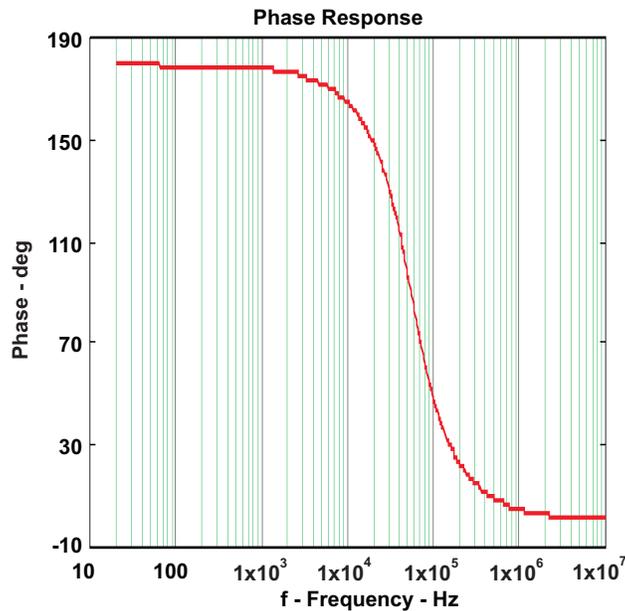

4 Interfacing to Differential Output DAC

Figure 2 shows a circuit diagram for interfacing DRV6xx to a differential output DAC. Note that symmetry is required for better performance and ease of design. The external component values are exactly the same as that derived from the single-ended input circuit previously discussed.

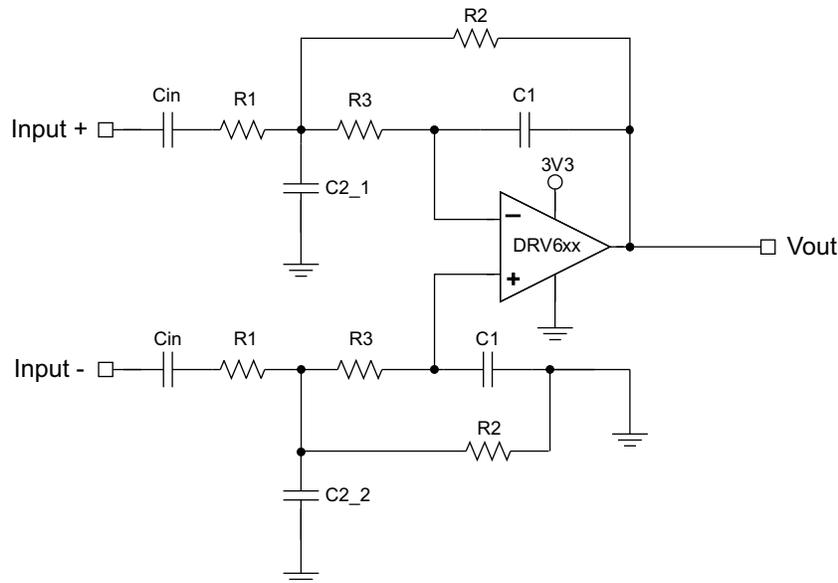
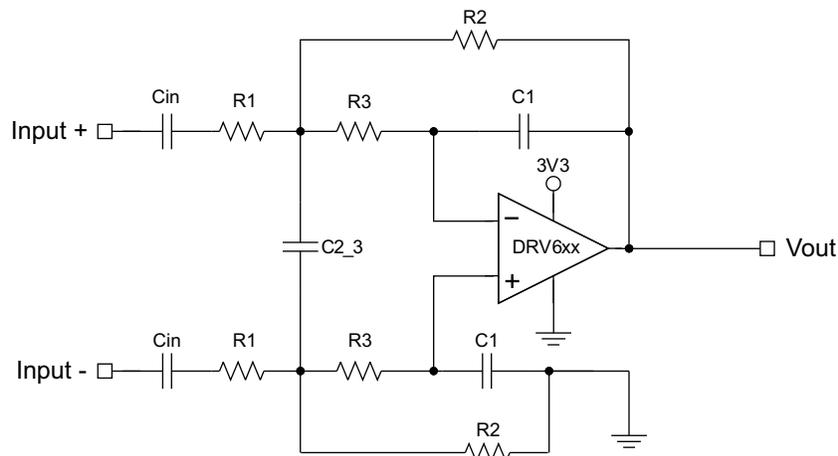


Figure 2. Circuit for Interfacing to Differential Output DAC

C_{2_1} and C_{2_2} can be combined into a single capacitor across the differential input node as shown in Figure 3. The capacitance of C_{2_3} is the same as the value of C_{2_1} and C_{2_2} in series (half of C_{2_1}).

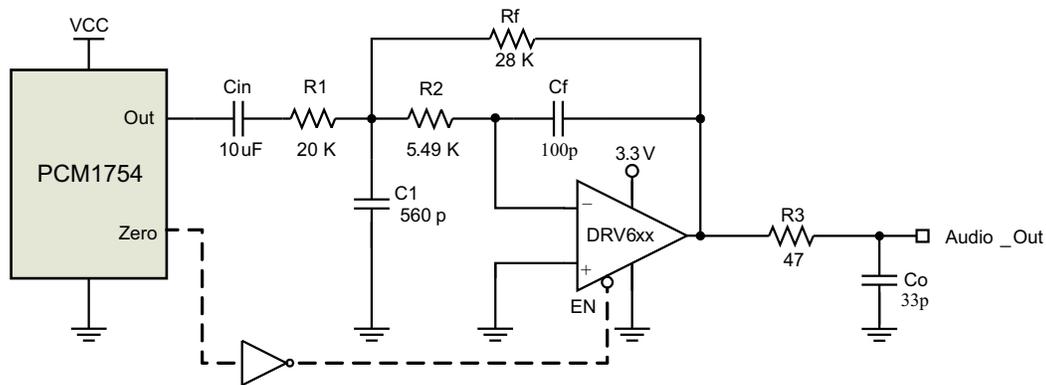

Figure 3. Simplified Circuit for Interface to Differential Output DAC

5 Reference Circuit for 2-Vrms Output Application

The Texas Instruments PCM1754 and PCM1789 are widely used as line-out DACs in many audio applications. The PCM1754 is a single-ended output device and the PCM1789 output is a differential output device. This section provides the reference circuits and parameters for using the DRV6xx as a post-filter to achieve 2-Vrms output.

5.1 Interfacing DRV6xx to PCM1754

Figure 4 shows DRV6xx interfacing with the PCM1754. The parameters are listed in Table 2.


Figure 4. Interfacing DRV6xx to PCM1754
Table 2. Parameters for PCM1754 2Vrms Output Circuit

Gain, db	Gain, V/V	Output	High Pass	Low Pass	C _{in}	C ₁	C _f	R ₁	R ₂	R _f	R ₃	C _o
+3 dB	1.414 V/V	2 Vrms	<10 Hz	54 kHz	10 μF	560 pF	100 pF	20 kΩ	5.49 kΩ	28 kΩ	47 Ω	33 pF

5.2 Interfacing DRV6xx to PCM1789

Figure 5 shows DRV6xx interfacing with the PCM1789. The parameters are listed in Table 3.

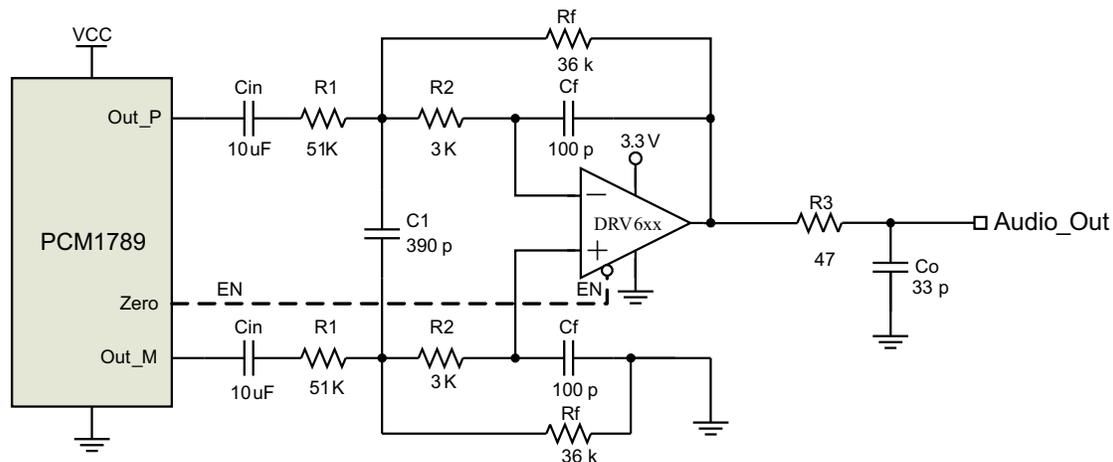


Figure 5. Interfacing DRV6xx to PCM1789

Table 3. Parameters for PCM1789 2Vrms Output Circuit

Gain, dB	Gain, V/V	Output	High Pass	Low Pass	Cin	C1	Cf	R1	R2	Rf	R3	Co
-3 dB	0.707 V/V	2 Vrms	<10 Hz	54 kHz	10 μ F	390 pF	100 pF	51 k Ω	3 k Ω	36 k Ω	47 Ω	33 pF

6 Conclusion

This application report provides a detailed guide for Butterworth second-order, low-pass filter design based on DRV6xx devices. Examples of interfacing DRV6xx devices with Texas Instruments audio DACs are also provided.

7 References

1. *Op Amps For Everyone* design reference ([SLOD006](#))
2. *Active Low-Pass Filter Design* application report ([SLOA049](#))
3. *DRV603, DirectPath™, 3-Vrms Line Driver With Adjustable Gain* data sheet ([SLOS617](#))
4. *DRV603EVM* user's guide ([SLOU252](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated