

Estimating the Power Dissipation in an LCD Level Shifter

Sokhna Diaara Diop

ABSTRACT

The power dissipation in a LCD gate-driving circuit is shared between the level shifter output stages and the parasitic components in the display. The dynamic characteristics of the level shifter output stage and the parasitic component values are frequently unavailable. Thus it is often difficult to estimate the power dissipation. This application note presents a method to evaluate the power dissipation in a typical level shifter application.

Contents

| | | |
|-----|--|---|
| 1 | Typical Level Shifter Application Description..... | 1 |
| 2 | Power Dissipation Estimation | 2 |
| 2.1 | Output Voltage and Current Measurements | 3 |
| 2.2 | Post-processing with Spreadsheet | 3 |
| 3 | Application example - TPS65192..... | 5 |
| 3.1 | Effect of Parasitic Inductance | 6 |

1 Typical Level Shifter Application Description

Figure 1 shows one channel of a level shifter with gate voltage shaping. On the rising edge of IN, Q1 turns on, Q2 and Q3 turn off, and OUT is driven to $V_{(VGH)}$. On the falling edge of FLK, Q1 turns off, Q3 is turned on, and the panel now discharges through Q3 and R_E . On the falling edge of IN, Q2 turns on and Q3 turns off, and OUT is driven to $V_{(VGL)}$. This sequence is repeated in turn for each channel.

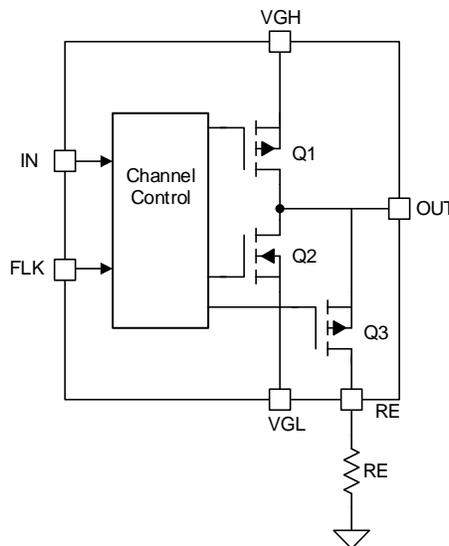


Figure 1. Level Shifter Channel With Gate Voltage Shaping

Level shifters that do not support gate voltage shaping (see [Figure 2](#)) are controlled only by the logic level applied to their IN pin. On the rising edge of IN, Q1 turns on, Q2 turns off, and OUT is driven to $V_{(VGH)}$. On the falling edge of IN, Q2 turns on, Q1 turns off, and OUT is driven to $V_{(VGL)}$.

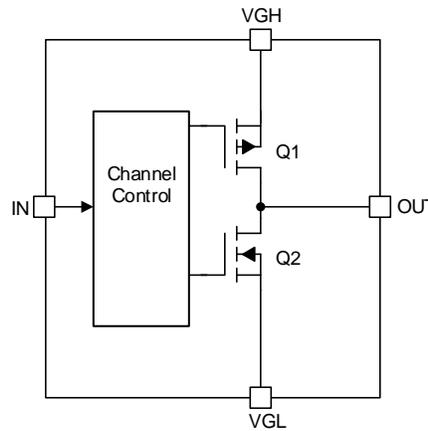


Figure 2. Level Shifter Channel Without Gate Voltage Shaping

2 Power Dissipation Estimation

In a typical level shifter application, the power dissipation is shared between the output stage of the level shifter and the parasitic components, as shown in [Figure 3](#). To calculate the power dissipated in the level shifter, the dynamic characteristic of the output stage and the exact values of the parasitic components must be known. This information is frequently unavailable or not reliable.

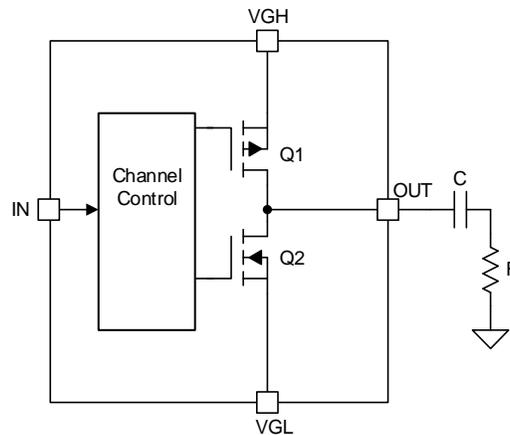


Figure 3. Level Shifter Channel With Load

[Section 2.1](#) and [Section 2.2](#) show a method to calculate the dissipated power in the level shifter without prior knowledge of any particular characteristics of the output stage or the parasitic components. This method works as follows: the voltage and current waveforms are captured with an oscilloscope and then are calculated using a spreadsheet. This is necessary because it is not possible to calculate the power dissipation of the level shifter in real time with an oscilloscope.

An example of the spreadsheet is available on [SLVC653](#).

2.1 Output Voltage and Current Measurements

When capturing the output voltage and current measurements with an oscilloscope, make sure to:


- Capture a whole number of periods (one, two, and so forth). The spreadsheet provided is usable when the capture length covers an exact period.
- Have enough samples. The measurement resolution must be high enough to make sure of an accurate result. The more samples the measurement contains, the more precise the estimated power is.

Two options are available for measuring the current waveform: use a current probe or measure the voltage drop across a sense resistor (see [Figure 4](#) and [Figure 5](#)). Measuring the voltage drop is the most convenient way to get the current measurement if a sense resistor is added to the circuit.

A current probe requires the addition of a wire between the output and the load and this adds some parasitic inductance to the circuit.

In [Section 3](#), the current is measured using both methods to show how each impact the result.

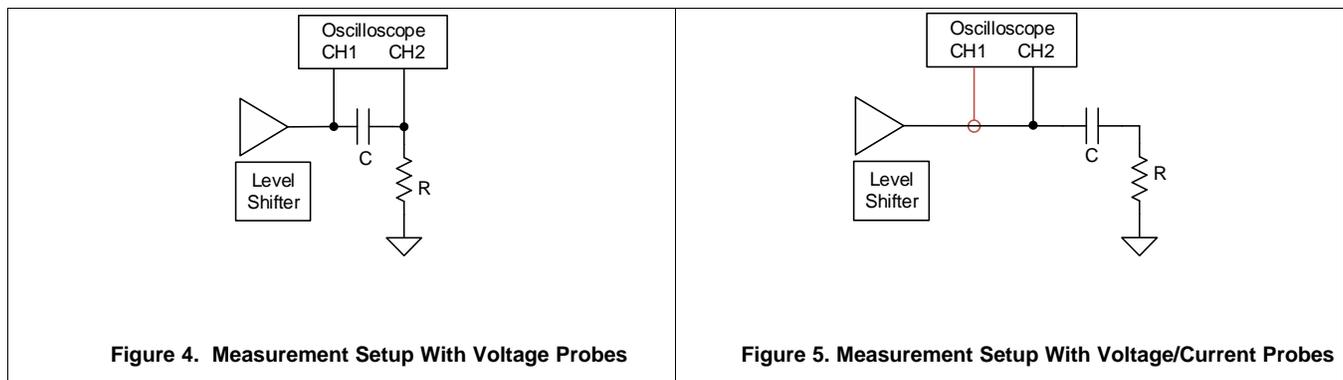The last step in the measurement process is to export the data into a CSV file for the post-processing operation.



2.2 Post-processing with Spreadsheet

The *Power Dissipation Estimation* spreadsheet, [SLVC653](#), is a tool that can calculate the power dissipation in the level shifter and display the graph of the power dissipated over the time. For that, fill in the extracted data (sampling time, $V_{(OUT)}$ and $I_{(OUT)}$) in the dedicated case and also:

- The number of samples
- The values of $V_{(VGH)}$ and $V_{(VGL)}$
- The value of the sense resistor if one was used to measure the output current, otherwise keep this value to the default $R = 1 \Omega$

When this step is completed successfully the power dissipated is finally calculated. For each sample, the voltage and the current are evaluated first. If the output current is measured as a voltage drop across a sense resistor, the current will correspond then to this voltage divided by the resistor value.

The voltage depends on the sign of the output current:

- If the output current is positive the voltage is equal to $V_{(VGH)} - V_{(OUT)}$
- And if it is negative the voltage equals $V_{(VGL)} - V_{(OUT)}$.

But the use of this algorithm increases the inaccuracy of the calculation. Therefore determine the voltage as follows (see [Figure 6](#)):

- In area 1, the voltage is equal to $V_{(VGH)} - V_{(OUT)}$
- And in area 2, it is equal to $V_{(VGL)} - V_{(OUT)}$

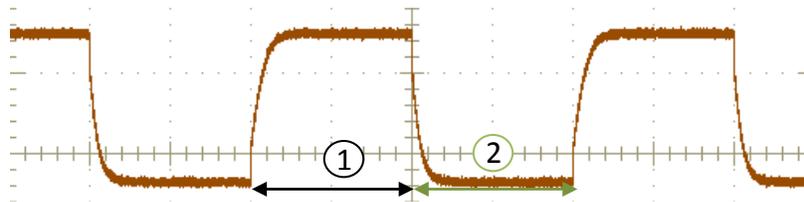


Figure 6. Output Voltage Calculation

After that, the power is calculated for each sample and then the power dissipated will correspond to the average over all samples (see [Equation 1](#)).

$$P_D = \frac{1}{n} \sum_{k=1}^n v_k i_k$$

where

- P_D is the power
- v_k is the voltage for the sample number k
- i_k is the current for the sample number k
- n is the number of samples

(1)

2.2.1 Gate Voltage Shaping

When the level shifter channel supports gate voltage shaping, the calculation of the dissipated power is adapted to take this into account. The waveform of the voltage of the pin RE $V_{(RE)}$ is captured with an oscilloscope in addition to the output voltage and current waveforms. The recommendations in [Section 2.1](#) hold for this operation.

In the spreadsheet, an additional column to fill in is reserved for $V_{(RE)}$. The calculation of the current does not change and for the voltage we can distinguish three cases (see [Figure 7](#)):

- In area 1, the voltage is equal to $V_{(VGH)} - V_{(OUT)}$
- In area 2, it equals $V_{(RE)} - V_{(OUT)}$
- And in area 3, it is equal to $V_{(VGL)} - V_{(OUT)}$

The following steps are the same as in the case without gate voltage shaping.


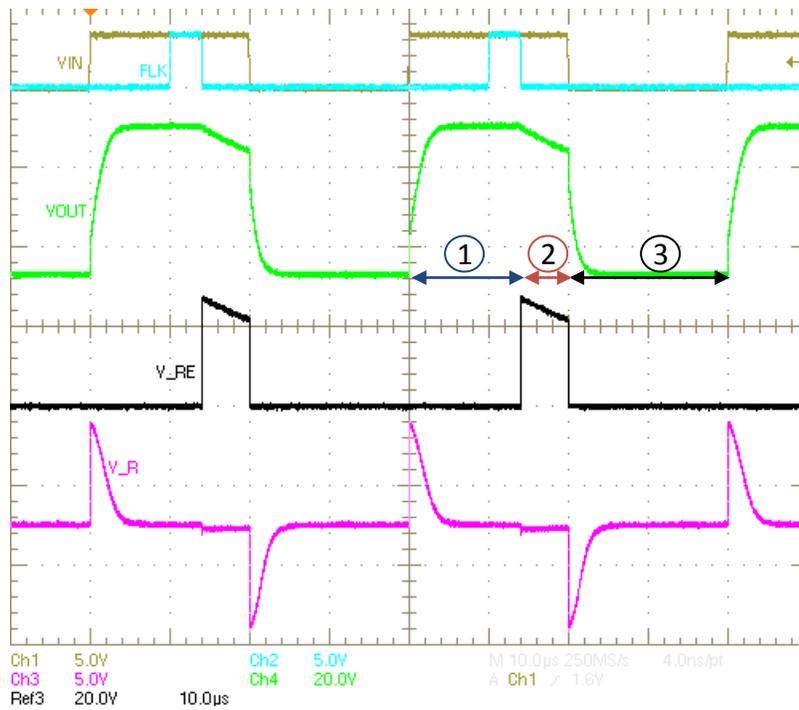


Figure 7. Output Voltage Calculation

3 Application example - TPS65192

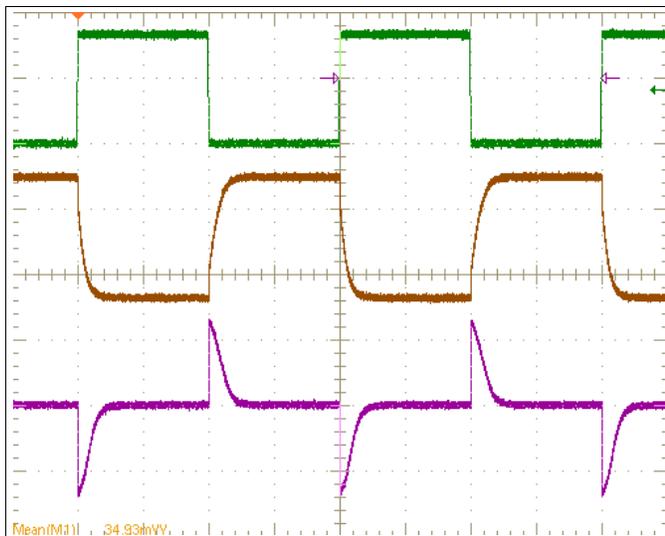The process described in the [Section 2.2.1](#) was used to calculate the dissipated power in the TPS65192 level shifter channel without flicker signal ([Figure 3](#)). The output current is measured as a voltage drop across the output resistor. The captured waveforms are shown in [Figure 8](#) and the result in [Figure 9](#).



$V_{(IN)}$ in green $V_{(OUT)}$ in brown $V_R = R I_{(OUT)}$ in purple

Figure 8. Voltage and Current Waveforms

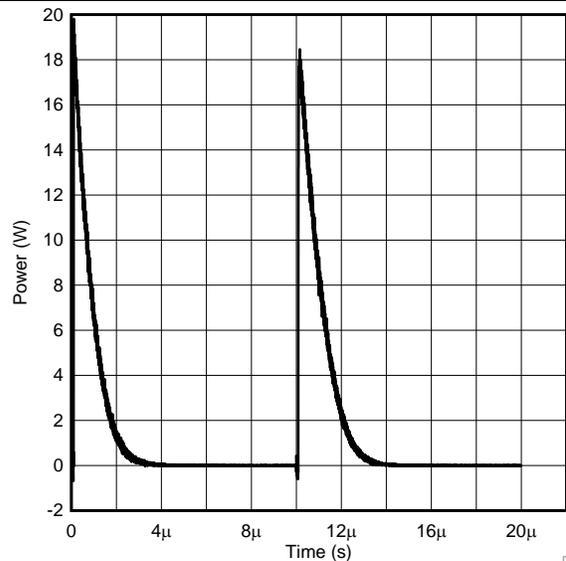


Figure 9. Power Dissipated in Level Shifter

This process was also used to calculate the level shifter power dissipation with different output loads and frequencies in order to make sure that the obtained results are consistent. The different test conditions and the corresponding results are available in [Table 1](#). The total power is calculated with [Equation 2](#).

$$P = fCV^2$$

where

- f is the level shifter's switching frequency
 - C is the capacitive load
 - V is the voltage swing across the capacitor
- (2)

Table 1. Test Conditions and Results

| Case | Total Power (W) | P _D (W) | Repartition of the power between | | |
|------|----------------------------------|--------------------|----------------------------------|------|-----|
| | | | Level Shifter | Load | |
| 1 | f = 50 kHz; R = 10 Ω; C = 33 nF | 2.26 | 1.7 | 75% | 25% |
| 2 | f = 25 kHz; R = 10 Ω; C = 33 nF | 1.13 | 0.83 | 73% | 27% |
| 3 | f = 25 kHz; R = 47 Ω; C = 33 nF | 1.13 | 0.3 | 23% | 77% |
| 4 | f = 25 kHz; R = 10 Ω; C = 100 nF | 3.4 | 2.4 | 70% | 30% |

These results validate the method used to evaluate the power dissipation in the level shifters. By comparing case 1 and case 2, the results show that the total power has doubled and the level shifter dissipates twice as much power.

The results of cases 2 and 3 indicate that the power dissipated in the level shifter decreases when the load resistor is increased and the capacitance is the same and the power dissipated in the load increases with the resistor as is predicted.


Finally, by comparing cases 2 and 4, the results show that the ratio between the power dissipated in the level shifter and the load is the same when the output resistance is not changed. The output capacitance has effect only on the total power.

3.1 Effect of Parasitic Inductance

To see the impact of the current measurement method in the results, the power dissipation is calculated with the same setup as in case 2 (refer to [Table 1](#)), but a current probe is used to measure the output current directly. For that, the shortest possible wire is added between the output and the load. This introduces a parasitic inductance which results in the addition of a spike in the output voltage waveform during transition edges (see [Figure 10](#)). The inductor current-voltage relationship ([Equation 3](#)) explains this behavior: a variation of the inductor current over time creates a voltage drop across its terminals.

$$V_L = L \frac{di}{dt}$$
(3)

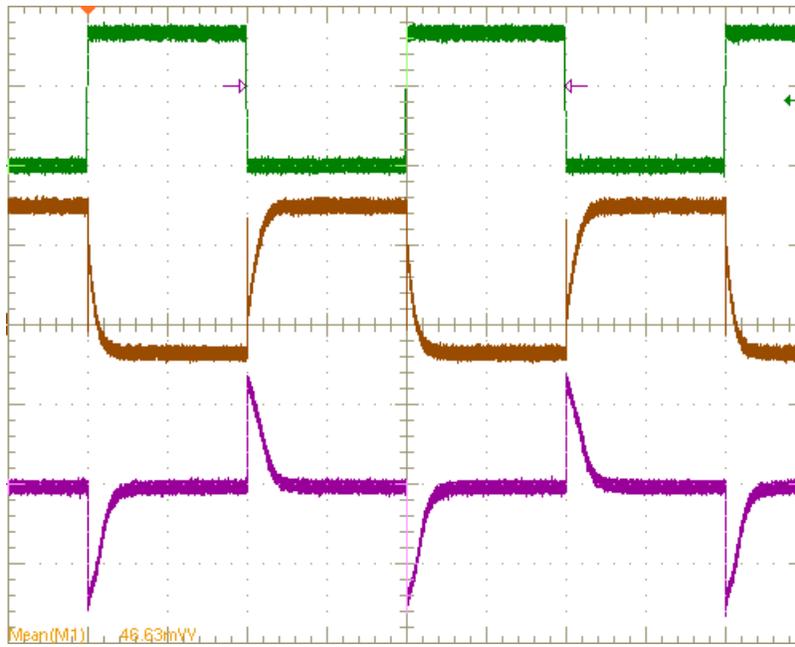The power dissipated in the level shifter is then equal to 0.831 W, which is 1 mW more than before. This indicates that the parasitic inductance does not have an important effect in the result and can thus be neglected.



$V_{(IN)}$ in green $V_{(OUT)}$ in brown $I_{(OUT)}$ in purple

Figure 10. Voltage and Current Waveforms

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

| | |
|------------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Applications Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Automotive and Transportation | www.ti.com/automotive |
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Video and Imaging | www.ti.com/video |

TI E2E Community

e2e.ti.com