

# AN-1863 LMH2180 Evaluation Board in DSBGA

#### 1 General Description

This evaluation board is designed to aid in the characterization of Texas Instruments LMH2180 75 MHz dual clock buffer in DSBGA package. This board simplifies the connection and ease of use of any oscillating input device. Use this evaluation board as a guide for high frequency layout and as a tool to aid in device testing and characterization.

#### 2 Basic Operation

The LMH2180 is a device that contains two 75 MHz clock buffer amplifiers. These amplifiers are specially designed to minimize the effects of spurious signals from the digital chip to other analog or mixed-signal chip. The LMH2180 also minimizes the influence of varying load resistance and capacitance to the oscillator and increases the drive capability. The buffers have a 106 V/µs internal slew rate at a supply current of only 1.3 mA for one channel enabled and 2.3 mA for two enabled channels. Each amplifier in the LMH2180 is capable of driving loads up to 20 pF. The input of each buffer is internally biased at 1 V. This allows AC coupling on the input. Each buffer offers an enable pin that can be used to disable the corresponding channel and to optimize consumption.

#### 3 Channel Activation

Either channel can be independently enabled or shut down. The enable logic can be provided to the evaluation board by shunting a jumper on JR1 and JR2. For the required control logic, see Table 1.

 Channel On
 Enable1
 Enable2

 IN1 to OUT1
 High
 Don't Care

 IN2 to OUT2
 Don't Care
 High

Table 1. States of LMH2180

## 4 Layout Considerations

Careful consideration for circuitry design and PCB layout eliminates problems and optimizes the performance of the LMH2180. It is best to have the same ground plane on the PCB for all decoupling and other ground connections.

To ensure a clean supply voltage, it is best to place decoupling capacitors close to the LMH2180, between  $V_{DD}$  and  $V_{SS}$ . On the evaluation board, capacitor C1 is placed on the bottom side.

Another important issue is the value of the components, which also determines the sensitivity to disturbances. Resistor values have to be low enough to prevent noise coupling and large enough to avoid a significant increase in power consumption while loading inputs or outputs to heavily.

All trademarks are the property of their respective owners.



Layout Considerations www.ti.com

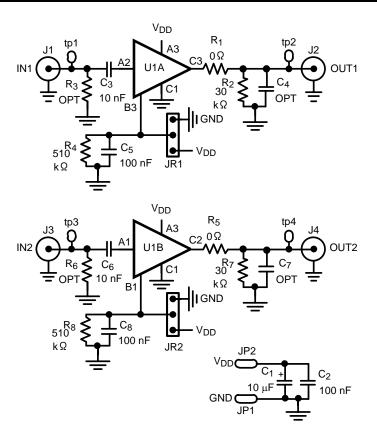


Figure 1. Schematic of the Evaluation Board

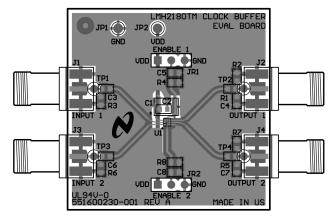


Figure 2. Layout of the Evaluation Board



www.ti.com Measurement Procedure

The Bill of Material (BOM) of the evaluation board is given in Table 2.

Tab			

Designator	Description	Comment	
R1, R5	0603 Resistor	0Ω	
R2, R7	0603 Resistor	30 kΩ	
R3, R6	0603 Resistor	Optional	
R4, R8	0603 Resistor	510 kΩ	
C1	Case B, Tantalum Capacitor	10 μF 16V	
C2, C5, C8	0603 Capacitor	100 nF	
C3, C6	0603 Capacitor	10 nF	
C4, C7	0603 Capacitor	Optional	
JR1, JR2	Jumper	Header 1x3	
J1, J2, J3, J4	Connector	SMA	
JP1	Power Connector	pin 1.5 mm, Black	
JP2	Power Connector	pin 1.5 mm, Red	
U1	DSBGA	LMH2180	

#### 5 Measurement Procedure

The performance of the LMH2180 can be measured with the setup given in Figure 3.

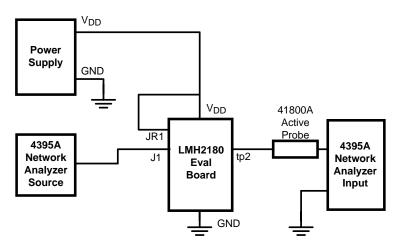


Figure 3. Measurement Setup

A supply voltage between 2.5 V to 5.0 V can be set by an external power supply connected to the JP2 (Red)  $V_{DD}$  pin and JP1 (Black) GND pin. In order to test its functionality, the buffer is tested by looking at the frequency response. Make sure to enable the buffer that has to be evaluated. The frequency response is tested by using a network analyzer (4395A). For small signal bandwidth evaluation, the source input should be set at -16 dBm. Be aware to measure the output of the buffer with the probe directly connected to TP2 or TP4 to measure the highest available bandwidth.



Measurement Results www.ti.com

## 6 Measurement Results

Figure 4 shows the frequency response of the LMH2180 at 2.7 V and 5.0 V power supply and a source input of  $V_{IN}$  = 0.1 $V_{PP}$  (-16 dBm @ 50  $\Omega$ ).

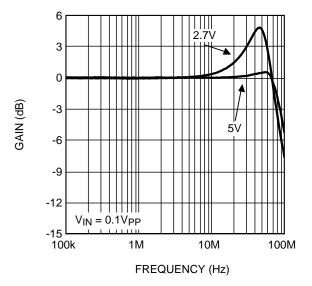


Figure 4. Frequency Response

#### IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have not been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

#### **Products Applications**

power.ti.com

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers microcontroller.ti.com Video and Imaging www.ti.com/video

**RFID** www.ti-rfid.com

Power Mgmt

**OMAP Applications Processors** www.ti.com/omap **TI E2E Community** e2e.ti.com

Wireless Connectivity www.ti.com/wirelessconnectivity