

## ***AN-1144 Maximizing Start-Up Loads with the LM3352 Regulated Buck/Boost Switched Capacitor Converter***

---

### **ABSTRACT**

This application report discusses maximizing start-up loads with the LM3352 regulated buck/boost switched capacitor converter.

---





The LM3352 is a regulated switched capacitor voltage converter. It achieves Buck/Boost operation by using a variety of different switching schemes to produce seven different gains between a minimum of  $\frac{1}{2}$  and a maximum of 2. At any given time the input and output comparators determine the required gain to give a regulated output voltage. The switching scheme used does however pose some minor restrictions regarding start-up of the IC with the output loaded. For the majority of applications a power-on reset circuit will be used. In these cases the restrictions are of no concern regardless of the type of load presented to the LM3352. For applications not using a power-on reset circuit, the restrictions are described.

As the part starts up, it cycles through the necessary gain regions (gains) until regulation is reached. Each gain region has an associated output impedance which may be greater than or less than its neighboring gain region. The greater the output impedance, the less current the part is able to supply without losing regulation. Therefore the weakest gain region (the gain with the highest output impedance) sets the maximum start up current for the part. For the LM3352, the weakest region is from  $V_{IN} = V_{OUT}$  to  $V_{IN} = V_{OUT} + 200\text{mV}$ . For some output voltage options, the part will never cycle through this region and therefore maximum start up current will be equal to the maximum rated load current.

The datasheet shows a maximum start up current of 45 mA. This number is a worst case number encompassing all voltage options across all input voltages as well as the worst case condition of  $T_A = 85^\circ\text{C}$ . As mentioned above, the weakest region is setting this limit. If the input range is more limited than the datasheet limits, the circuit may start up with loads greater than 45 mA. This effect can also change with different load types. For example, some CMOS loads will not draw significant current until a certain operational threshold voltage is reached. If this threshold voltage occurs after the LM3352 has cycled through the gain region of 1 there will be no start-up restrictions. However, systems with resistive loads will draw current as soon as voltage is applied. A description of the limitations for a resistive load follows.

Because the maximum load current during start-up is input voltage dependent (see graph titled Start-up Regions), lower input voltages will need to use the gain of 1 during start-up and therefore will have decreased current capabilities. Due to the added effect of the  $R_{OUT}$ , input voltages slightly higher than the output will be affected as well (see graphs titled Maximum Start-up Load Current vs. Input Voltage). These graphs are taken using a resistive load on the output.

With higher input voltages that do not need to use or go through the weakest gain region during start-up, the maximum load during start-up is dramatically increased. As the graphs show, much higher loads than 45 mA can be tolerated during start-up with high input voltage conditions. The graphs are also at the worst case condition of  $T_A = 85^\circ\text{C}$ . This should clarify the start-up issues involved with the LM3352 and allow more possibilities of use for those who are unable to use the part with the low stated maximum of 45 mA in the datasheet. If larger start-up currents are expected for an application that has a minimum input voltage lower than the minimum input required, a power-on reset circuit such as the LP3470 is still recommended.

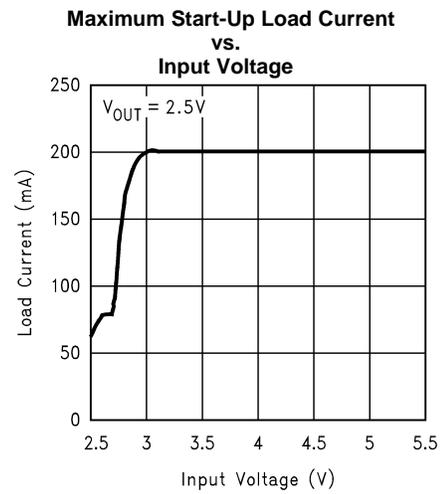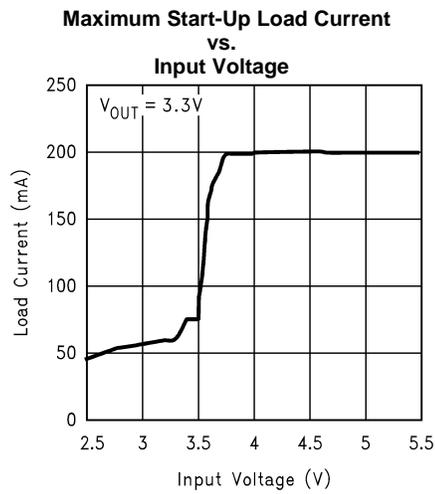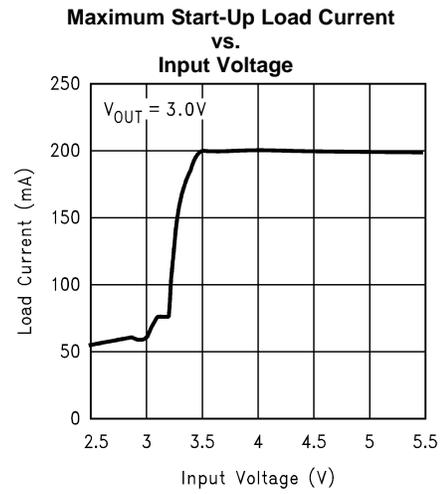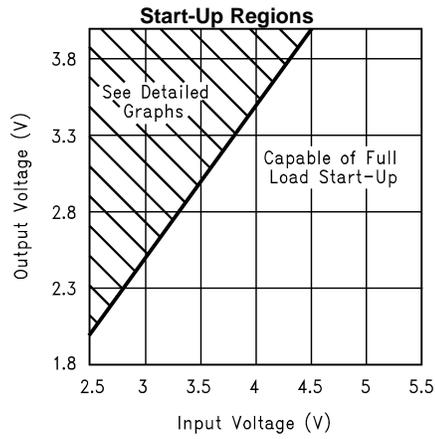

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)