

AN-2147 LM34923 Evaluation Board

1 Introduction

The LM34923 EVAL evaluation board provides the design engineer with a fully functional buck regulator, employing the constant on-time (COT) operating principle. This evaluation board provides a 5V output over an input range of 6V to 75V. The circuit delivers load currents to 500 mA, with current limit set at a nominal 1 Amp.

The board's specification are:

- Input Voltage: 6V to 75V
- Output Voltage: 5V
- Maximum load current: 500 mA
- Minimum load current: 0A
- Current Limit: 1 Amp (nominal)
- Measured Efficiency: 94.75% ($V_{IN} = 6V$, $I_{OUT} = 100\text{ mA}$)
- Nominal Switching Frequency: 200 kHz
- Size: 2.6 in. x 1.6 in.

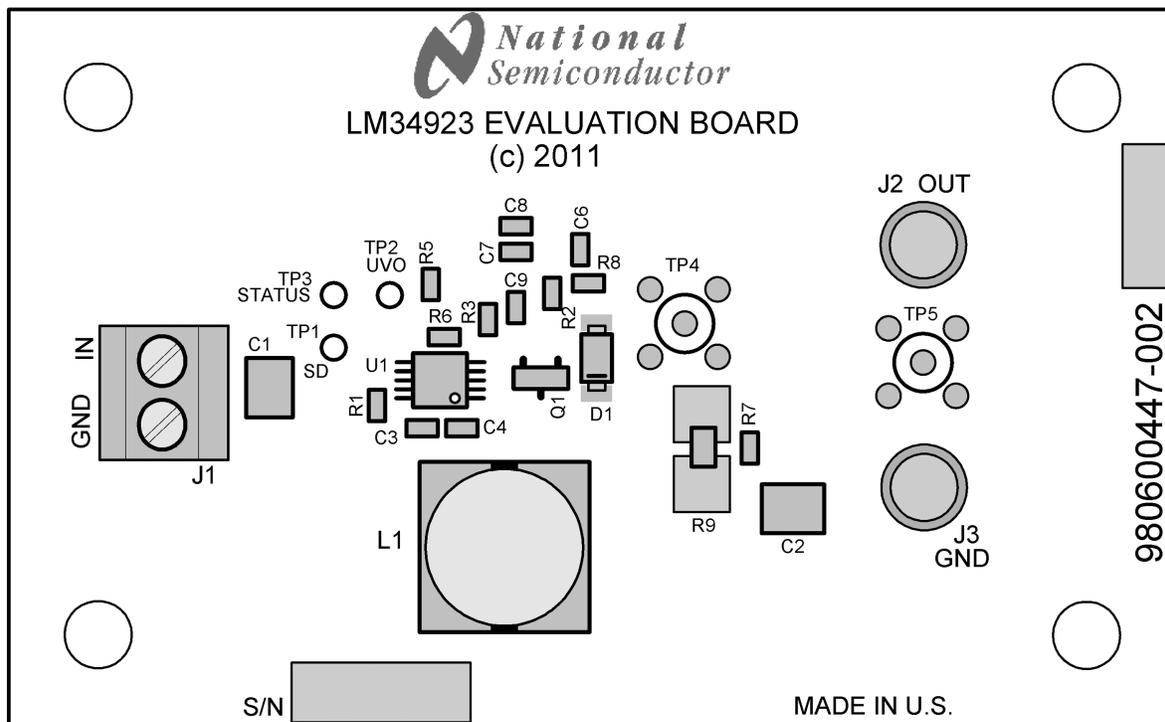


Figure 1. Evaluation Board - Top Side

2 Theory of Operation

Figure 6 shows the evaluation board schematic. When the circuit is in regulation, the buck switch is on each cycle for a time determined by R1 and VIN according to Equation 1:

$$t_{on} = \frac{1.25 \times 10^{-10} \times (R1 + 500\Omega)}{V_{IN} - 0.5V} + 30 \text{ ns} \quad (1)$$

The on-time of this evaluation board ranges from $\approx 4.38 \mu\text{s}$ at $V_{IN} = 6\text{V}$, to $\approx 351 \text{ ns}$ at $V_{IN} = 75\text{V}$. The on-time varies inversely with V_{IN} to maintain a nearly constant switching frequency. At the end of each on-time the minimum Off-Timer ensures the buck switch is off for at least 260 ns. In normal operation, the off-time is much longer. During the off-time, the load current is supplied by the output capacitor (C2). When the output voltage falls sufficiently that the voltage at FB is below 2.5V, the regulation comparator initiates a new on-time period. For stable, fixed frequency operation, a minimum of 25 mV of ripple is required at FB to switch the regulation comparator. For a more detailed block diagram, and a complete description of the various functional blocks, see the *LM34923 80-V 600-mA Constant On-Time Buck Switching Regulator Data Sheet* ([SNVS695](#)).

3 Board Layout and Probing

The pictorial in Figure 1 shows the placement of the circuit components. The following should be kept in mind when the board is powered:

- When operating at high input voltage and high load current, forced air flow may be necessary.
- The LM34923 may be hot to the touch when operating at high input voltage and high load current.
- Use CAUTION when probing the circuit at high input voltages to prevent injury, as well as possible damage to the circuit.
- At maximum load current, the wire size and length used to connect the load becomes important. Ensure there is not a significant drop in the wires between this evaluation board and the load.

4 Board Connection/Start-up

The input connections are made to the J1 connector. The load is connected to the J2 (OUT) and J3 (GND) terminals. Ensure the wires are adequately sized for the intended load current. Before start-up a voltmeter should be connected to the input terminals, and to the output terminals. The load current should be monitored with an ammeter or a current probe. It is recommended that the input voltage be increased gradually to 6V, at which time the output voltage should be 5V. If the output voltage is correct with 6V at V_{IN} , then increase the input voltage as desired and proceed with evaluating the circuit. DO NOT EXCEED 75V AT V_{IN} .

5 Output Ripple Control

The LM34923 requires a minimum of 25 mVp-p ripple at the FB pin, in phase with the switching waveform at the SW pin, for proper operation. The required ripple can be supplied from ripple at V_{OUT} , through the feedback resistors as described in Section 5.1. Section 5.2 and Section 5.3 provide lower output ripple with one or two additional components.

5.1 Option A) Lowest Cost Configuration

In this configuration R7 is installed in series with the output capacitance (C2). Since $\geq 25 \text{ mVp-p}$ are required at the FB pin, R7 must be chosen to generate $\geq 50 \text{ mVp-p}$ at V_{OUT} , knowing that the minimum ripple current in this circuit is $\approx 51 \text{ mA p-p}$ at minimum V_{IN} . Using 1Ω for R7, the ripple at V_{OUT} ranges from $\approx 51 \text{ mVp-p}$ to $\approx 280 \text{ mVp-p}$ over the input voltage range. If the application can accept this ripple level, this is the most economical solution. The circuit is shown in Figure 2, see Figure 8. R8, C6, C7, and C8 are not used in this configuration.

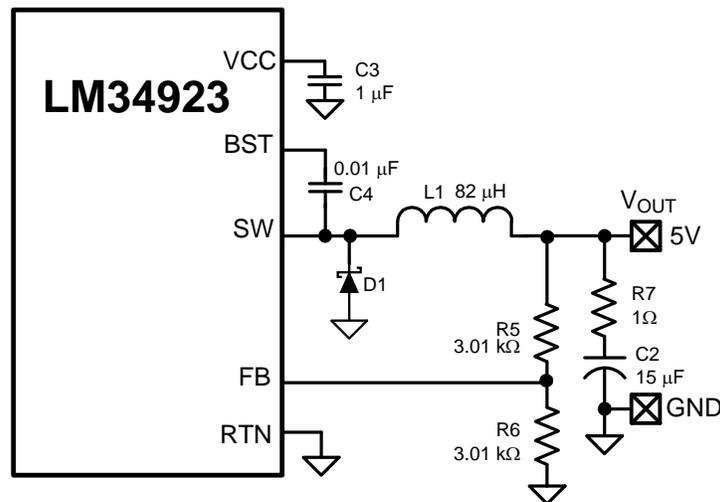


Figure 2. Lowest Cost Configuration

5.2 Option B) Reduced Ripple Configuration

This configuration generates less ripple at V_{OUT} than Section 5.1 by the addition of one capacitor (C8) across R5, as shown in Figure 3.

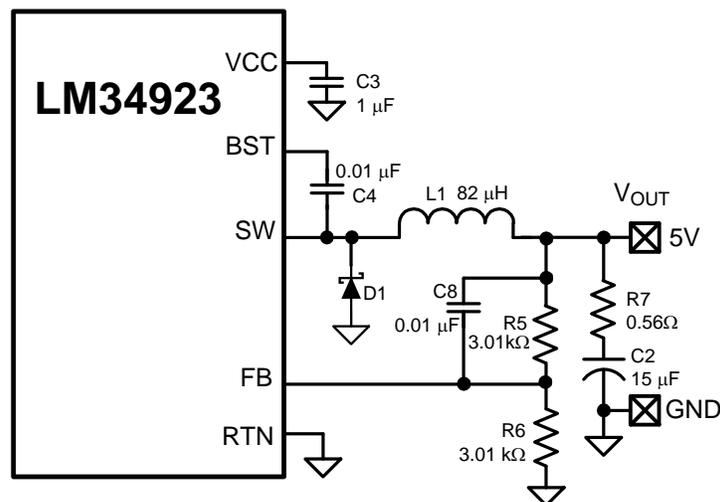


Figure 3. Reduced Ripple Configuration

Since the output ripple is passed by C8 to the FB pin with little or no attenuation, R7 can be reduced so the minimum ripple at V_{OUT} is ≈ 25 mVp-p. The minimum value for Cff is calculated from:

$$C8 \geq \frac{3 \times t_{ON(max)}}{(R5//R6)} \quad (2)$$

where $t_{ON(max)}$ is the maximum on-time (at minimum V_{IN}), and $R5//R6$ is the parallel equivalent of the feedback resistors. The ripple at V_{OUT} ranges from 28 mVp-p to 159 mVp-p over the input voltage range, see Figure 8.

5.3 Option C) Minimum Ripple Configuration

To obtain minimum ripple at V_{OUT} , R7 is set to 0Ω , and R8, C6, and C7 are added to generate the required ripple for the FB pin. In this configuration, the output ripple is determined primarily by the characteristics of the output capacitance and the inductor's ripple current, see [Figure 8](#).

The ripple voltage required by the FB pin is generated by R8, and C6 since the SW pin switches from $-0.1V$ to V_{IN} , and the right end of C6 is a virtual ground. The values for R8 and C6 are chosen to generate a 30-100 mVp-p triangle waveform at their junction. That triangle wave is then coupled to the FB pin through C7. The following procedure is used to calculate values for R8, C6 and C7:

1) Calculate the voltage V_A :

$$V_A = V_{OUT} - (V_{SW} \times (1 - (V_{OUT}/V_{IN}))) \tag{3}$$

where V_{SW} is the absolute value of the voltage at the SW pin during the off-time, and V_{IN} is the minimum input voltage. For this circuit, V_A calculates to 4.98V. This is the approximate DC voltage at the R8/C6 junction, and is used in [Equation 4](#).

2) Calculate the R8 x C6 product:

$$R8 \times C6 = \frac{(V_{IN} - V_A) \times t_{ON}}{\Delta V} \tag{4}$$

where, t_{ON} is the maximum on-time, V_{IN} is the minimum input voltage, and ΔV is the desired ripple amplitude at the R8/C6 junction, 40 mVp-p for this example.

$$R8 \times C6 = \frac{(6V - 4.98V) \times 4.38 \mu s}{0.04} = 1.12 \times 10^{-4} \tag{5}$$

R8 and C6 are then chosen from standard value components to satisfy the above product. Typically, C6 is 3000 to 10000 pF, and R8 is 10 k Ω to 300 k Ω . C7 is chosen large compared to C6, typically 0.1 μF . The ripple at V_{OUT} is typically less than 10 mVp-p, see [Figure 4](#) and [Figure 8](#).

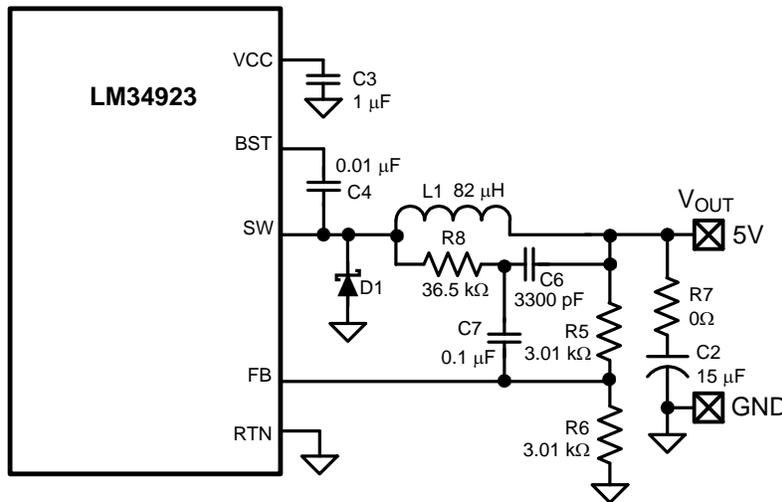


Figure 4. Minimum Output Ripple Configuration

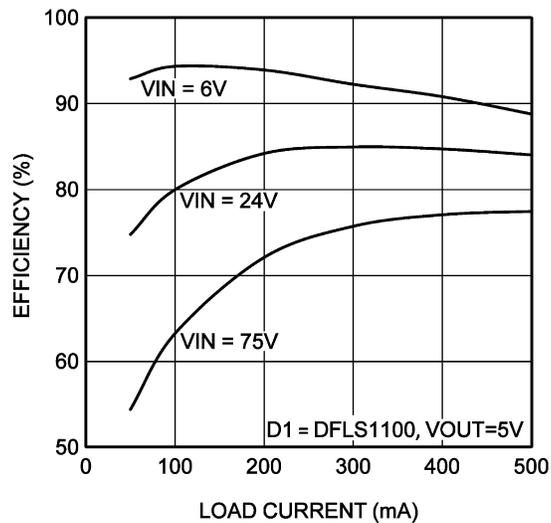


Figure 5. Efficiency at 200 kHz

6 Under-Voltage Detector

The under voltage detector can be used to monitor the input voltage, or any other system voltage as long as the voltage at the UV pin does not exceed its maximum rating. On this evaluation board, the input voltage is monitored via resistors R2 and R3.

An appropriate pull-up voltage less than 10 volts must be connected to test point TP2-UVO on this evaluation board. R4 is the pull-up resistor for the UVO output. The under-voltage status can then be monitored at the TP3-Status test point.

On this evaluation board the UVO output switches low when the input voltage exceeds 12V, and it switches high when the input voltage is less than 11V. If it is desired to change the thresholds, the equations for determining the resistor values are:

$$R2 = \frac{V_{UVH} - V_{UVL}}{5 \mu A} = \frac{V_{UV(HYS)}}{5 \mu A} \quad (6)$$

$$R3 = \frac{R2 \times 2.5V}{V_{UVL} - 2.5V} \quad (7)$$

where, V_{UVH} is the upper threshold at VIN, and V_{UVL} is the lower threshold. The threshold at the UV pin is 2.5V.

The UVO output is high when the VCC voltage is below its UVLO threshold, or when the LM34923 is shutdown by grounding the TP1-SD test point, regardless of the voltage at the UV pin.

8.1 Bill of Materials (BOM)

Table 1. Bill of Materials (BOM)

Item	Description	Mfg., Part Number	Package	Value
C1	Ceramic Capacitor	TDK C3225X7R2A225M	1210	2.2 μ F, 100V
C2	Ceramic Capacitor	TDK C3225X7R1C156M	1210	15 μ F, 16V
C3	Ceramic Capacitor	TDK C1608X7R1C105K	0603	1 μ F, 16V
C4	Ceramic Capacitor	TDK C1608X7R2A103K	0603	0.01 μ F, 100V
C5	Ceramic Capacitor	TDK C2012X7R2A104M	0805	0.1 μ F, 100V
C6	Ceramic Capacitor	TDK C1608X7R2A332K	0603	3300 pF, 100V
C7	Ceramic Capacitor	TDK C2012X7R2A104M	0805	0.1 μ F, 100V
C8	Unpopulated			
C9	Ceramic Capacitor	TDK C1608X7R2A102K	0805	1000 pF, 100V
L1	Inductor	Coiltronics DR74-820-R or Wurth Electronics 744771182		82 μ H, 1A
D1	Schottky Rectifier	Diodes Inc DFSL1100	Power DI123	100V, 1.0A
R1	Resistor	Vishay CRCW0603191KF	0603	191k Ω
R2	Resistor	Vishay CRCW0603200KF	0603	200k Ω
R3	Resistor	Vishay CRCW060359KOF	0603	59 k Ω
R4	Resistor	Vishay CRCW0603100KF	0603	100 k Ω
R5	Resistor	Vishay CRCW06033KO1F	0603	3.01 k Ω
R6	Resistor	Vishay CRCW06033KO1F	0603	3.01 k Ω
R7	Resistor	Vishay CRCW06030000Z	0603	0 Ω jumper
R8	Resistor	Vishay CRCW060336K5F	0603	36.5 k Ω
R9	Resistor	Vishay CRCW06030000Z	0603	0 Ω jumper
U1	Switching Regulator	LM34923	VSSOP-10	

9 Circuit Performance

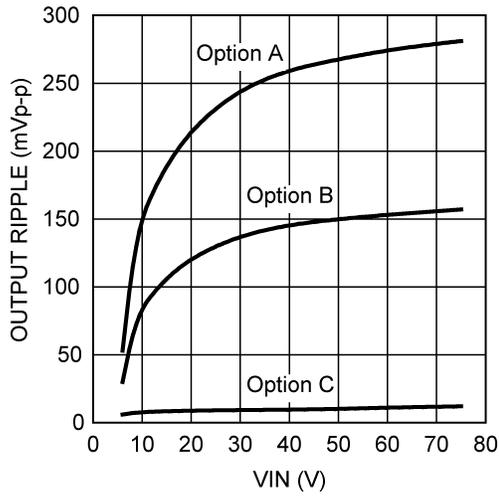


Figure 7. Output Voltage Ripple

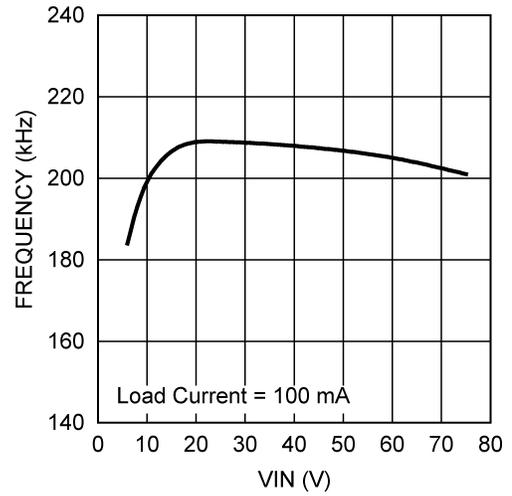


Figure 8. Switching Frequency vs. Input Voltage

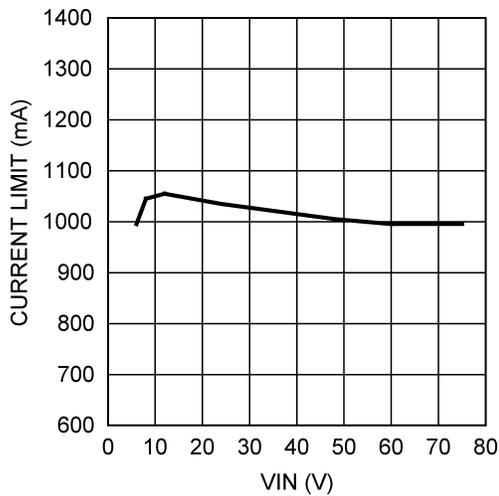


Figure 9. Current Limit vs. Input Voltage

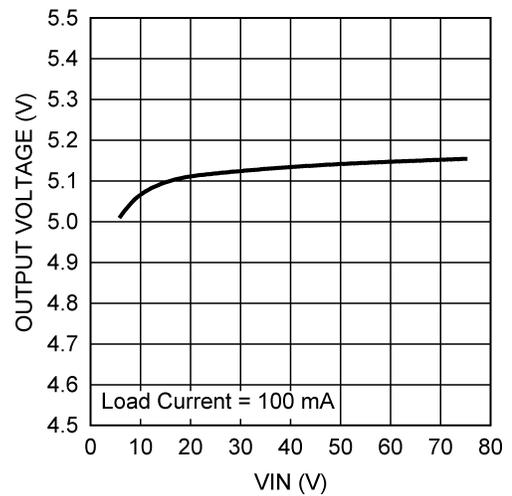


Figure 10. Line Regulation


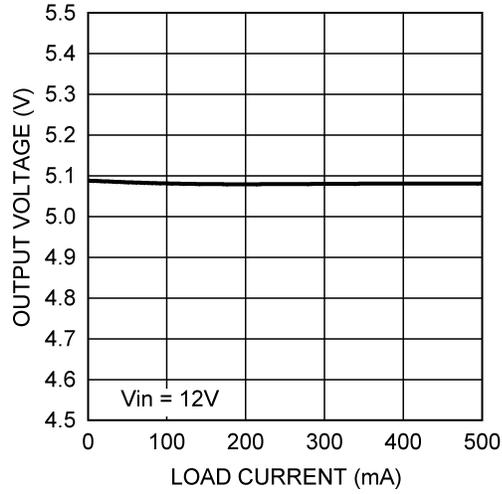


Figure 11. Load Regulation

10 Typical Waveforms

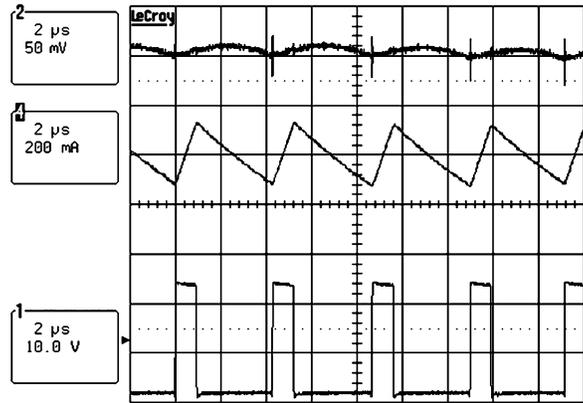

Trace 1 = SW Pin
 Trace 2 = V_{OUT}
 Trace 4 = Inductor Current
 $V_{in} = 12V$, $I_{out} = 200 mA$

Figure 12. Typical Waveforms

11 PC Board Layout

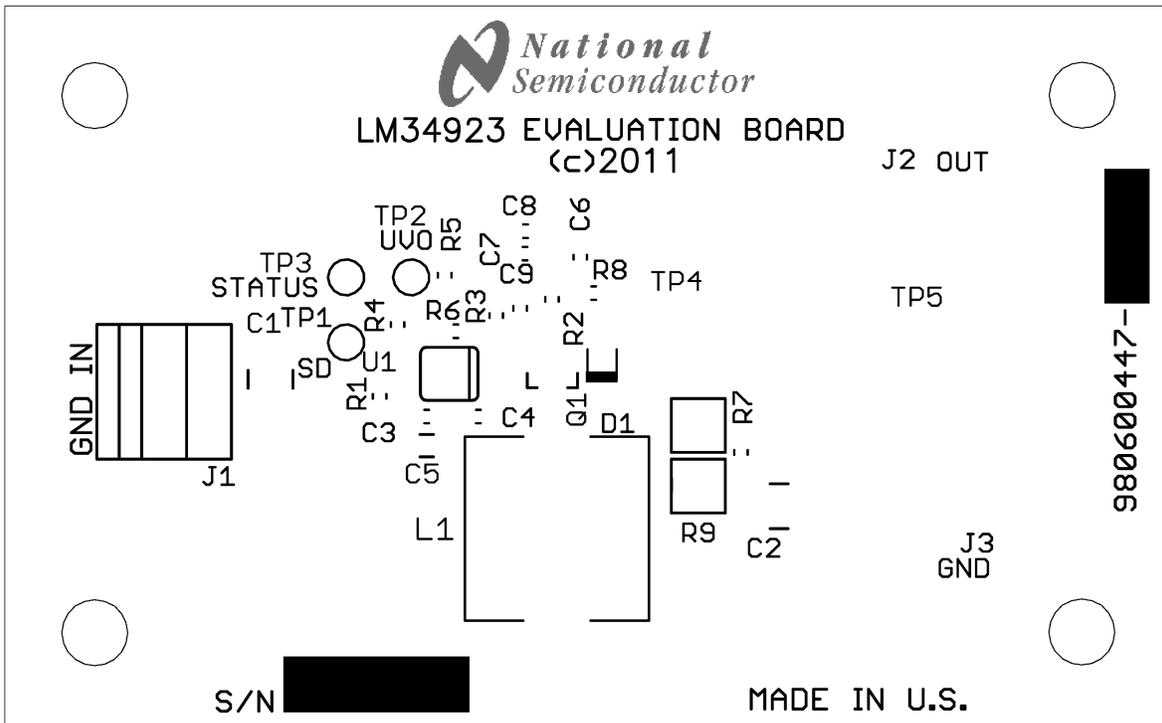


Figure 13. Board Silkscreen


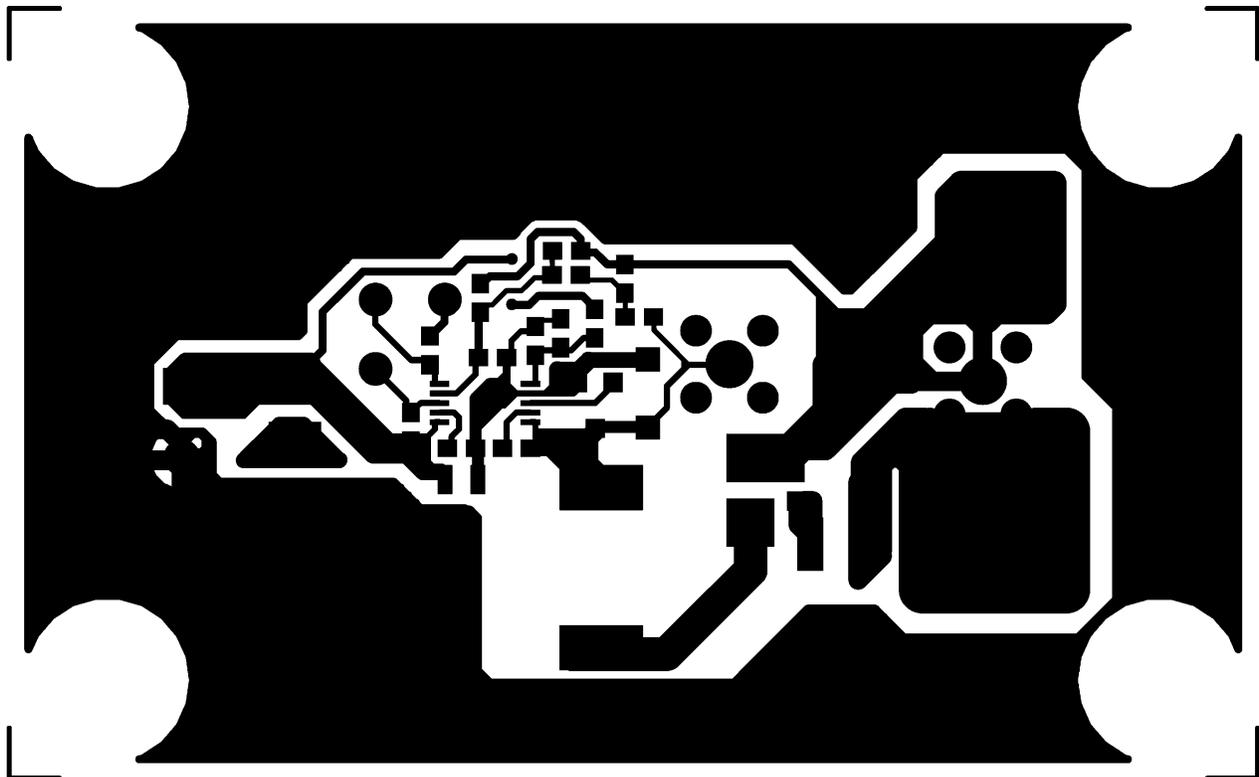


Figure 14. Board Top Layer

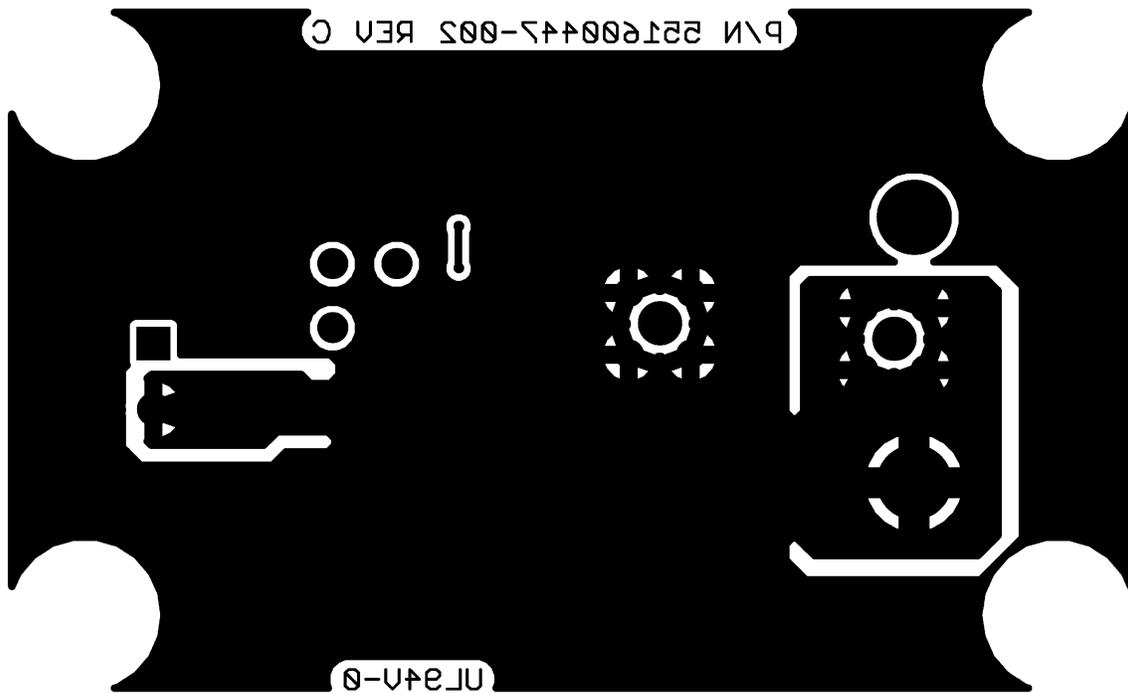

BOTTOM LAYER (.SOL) AS VIEWED FROM TOP

Figure 15. Board Bottom Layer (Viewed from Top)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com