

How To Improve Speed and Reliability of Isolated Digital Inputs in Motor Drives

Anant Kamath, Systems Engineer, Isolation Products, Interface Group



Digital Input Receivers in Motor Drives

Digital Input receivers are used in AC and servo motor control to interface various 24-V signals to the control module of the drive. These signals include inputs from field sensors and switches, position and speed feedback encoded as 24-V signals, clock or PWM inputs for speed control, and emergency stop signals, such as Safe Torque Off (STO). Isolation is used to manage ground potential differences.

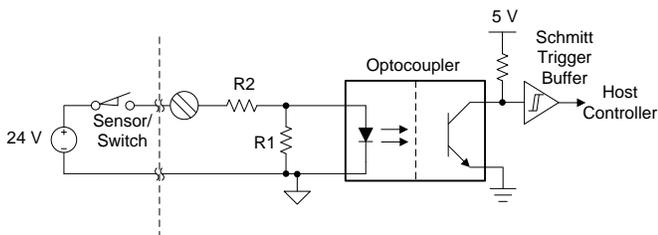


Figure 1. Traditional implementation of Digital Input Receivers in Motor Drives

Common Implementations


Figure 1 shows the most common implementation of Digital Input receivers in motor drive applications in use today. The voltage thresholds and the receiver input current are set by the resistors R1 and R2, in combination with the optocoupler's input characteristics. A Schmitt trigger buffer is usually needed after the optocoupler to provide hysteresis for noise immunity.

New Digital Input Solutions for Motor Drive Applications

Texas Instruments' ISO1211 and ISO1212 devices are high-speed isolated digital input receivers with integrated current limit, voltage comparator with hysteresis and reverse polarity protection. The ISO1211 can be used for channel-to-channel isolation and the ISO1212 is ideal for multichannel designs.

Figure 2 shows the implementation of one channel of a Digital Input receiver with ISO1211. The resistor R_{SENSE} controls the current limit, and the resistor R_{THR} , the voltage transition thresholds. This allows the systems

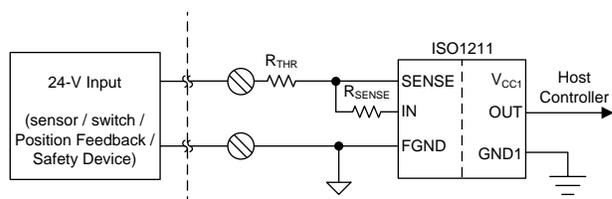designer to independently adjust these parameters. The ISO121x can reduce power dissipation by a factor of 5x compared to traditional approaches, as shown in the [How To Simplify Isolated 24-V PLC Digital Input Module Designs](#) TI Tech Note.



Copyright © 2017, Texas Instruments Incorporated

Figure 2. Digital Input Module with ISO1211

A CMOS based integrated solution such as the ISO121x offers several advantages over traditional optocoupler solutions for motor drive digital inputs.

Higher Speed and Lower Response Times

Standard optocouplers have a response time of tens of micro-seconds, and are not capable of high speed operation. ISO121x devices offer much higher speed and response time, and are ideal for high speed digital inputs such as for position and speed feedback and control signals in motor drives.

Device	Max. Response Time / Propagation Delay	Maximum Clock Frequency
Optocoupler	20 μ s	20 kHz
ISO121x	140 ns	2 MHz

Controlled Thresholds and Noise Immunity

Motor drives are noisy systems, and it is imperative to design interfaces including digital inputs for noise immunity. Optocoupler input response and current transfer ratio varies greatly from device to device, and with temperature. Over a period of time, the LEDs used in the optocoupler also age, resulting in a further shift in input and transfer characteristics. Keeping these factors in mind, digital inputs designed with optocouplers have a wide variation in input voltage transition thresholds. To keep the current draw low, often the system designer is forced to design the digital input receiver to draw the minimum required current at a higher input voltage (i.e. the maximum threshold is pushed higher, beyond the desired

specification). In comparison, as shown in Figure 3, an ISO121x based solution has controlled thresholds and hysteresis, and sufficient margin to the low and high levels, to account for noise, variation in the 24-V supply and voltage drop in the input wiring.

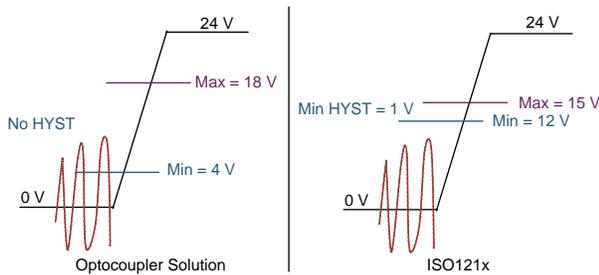


Figure 3. ISO121x Based Receivers Have Higher Noise Margin to the High and Low Levels

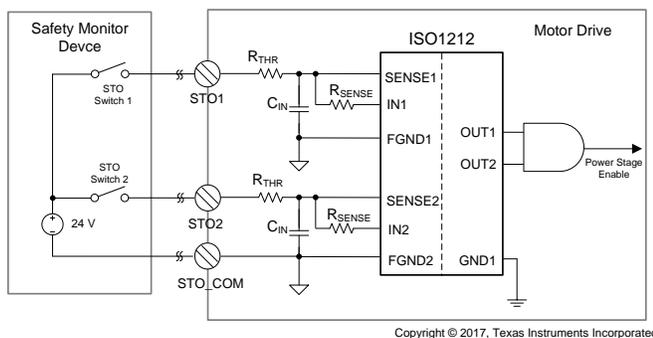


Figure 4. Safe Torque Off (STO) Signals Implemented with ISO1212

Increased Reliability

The ISO121x devices, like other digital isolation products from Texas Instruments are manufactured using a well-controlled CMOS semiconductor manufacturing process. These devices have a very low Failure in Time (FIT) rate of <0.3 per 1 billion hours of operation. In comparison, optocouplers have a FIT rate of 10 to 30 per 1 billion hours of operation, orders of magnitude worse. The ISO121x devices also do not age with time, unlike optocouplers.

Device	FIT rate	Aging
Optocoupler	20	Significant
ISO121x	0.3	Negligible

Critical signals such as Safe Torque Off (STO) that are active-low, and hence operate at a continuous high-level in normal operation can cause accelerated aging in optocouplers. Safe Torque Off (STO) when implemented with ISO121x as shown in Figure 4 benefits from a lower FIT rate, and negligible impact from aging.

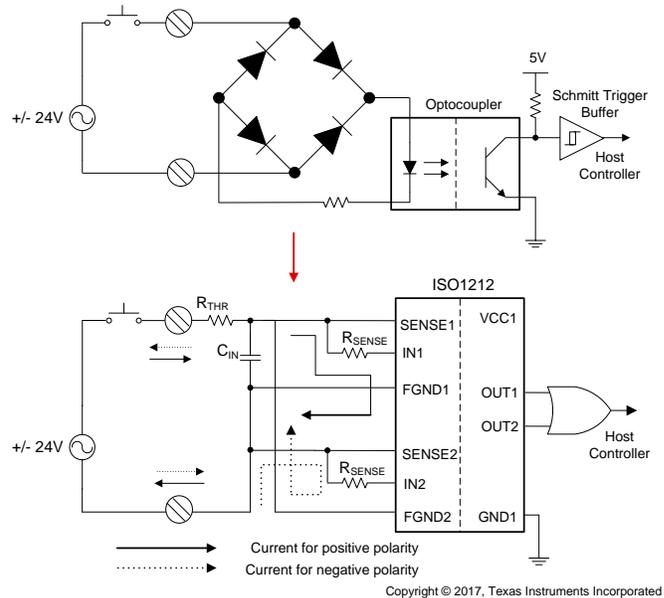


Figure 5. Implementing Bipolar, AC or Sink-Source Configuration using ISO1212

Bipolar, AC or Sink-Source Operation

Digital inputs for motor drives are sometimes implemented in bipolar or sink-source configuration. To implement bipolar operation, usually a full-bridge rectifier using four diodes is used ahead of an optocoupler. The ISO1212 device can be used to create an input module that can be used for bipolar, AC or sink-source operation, as shown in Figure 5, resulting in a compact solution, while maintaining the benefits of current limit, and precise voltage thresholds.

Conclusion

The ISO1212 and ISO1211 devices bring a modern solution for Digital Input receivers in motor drive applications offering higher speed, well controlled voltage thresholds, better noise immunity and increased reliability and longevity compared to traditional solutions with optocouplers.

Table 1. Alternative Device Recommendations

Device	Optimized Parameters	Performance Trade-Off
ISO1211	Single-channel isolated digital input receiver	For channel to channel isolation
ISO1212	Dual-channel isolated digital input receiver	For group isolated inputs. Lower cost per channel
SN65HVS880	8-channel digital input serializer	Non-isolated, Lower Speed, Needs field side supply

Table 2. Adjacent Tech Notes

SLLA370	How To Simplify Isolated 24-V PLC Digital Input Module Designs
---------	--

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated