

Dual-Channel VCAs: Methods for Powering Down One Channel

Sean Cline
High-Speed Data Products

ABSTRACT

Texas Instruments offers several product groups of highly-integrated voltage-controlled amplifiers (VCAs), originally designed for ultrasound applications. These product families include the VCA2611/12/13/16, with an integrated Low-Noise Preamplifier (LNP), and the VCA2614/18/19, without an LNP. Both the VCA2611 and the VCA2614 families feature two channels. Recently, a question has arisen regarding whether it is possible to power only one channel of the VCA while powering down the other. This application note outlines two possible approaches to this question and describes the steps needed to assure the greatest chance of success. Additional methods to accomplish this task are also suggested. Unless otherwise specified, this application report applies to any member of the VCA2611 and VCA2614 families.

Contents

Powering Down A Single Channel	2
Alternate Power-Down Methods	5
Conclusion	7

List of Figures

Figure 1. Typical Power Supply Connection of the VCA2614 Family	3
Figure 2. Typical Power Supply Connection of the VCA2611 Family	4
Figure 3. Example LDO Connection to the VCA261x	5
Figure 4. Example Relay Connection to the VCA261x	6
Figure 5. Example Transistor Connection to the VCA261x	6


Powering Down A Single Channel

This report addresses the fundamental issue of whether or not it is possible to power only one channel of a VCA while powering down the other. The VCA2614 family features a dedicated power-down pin that powers down the entire device. However, this report will show that it is possible to power-down one channel of either family of VCAs.

The VCA2614 and VCA2611 families are dual-channel devices with separate power-supply pins for each channel. Separate supply pins make it possible for a user to apply power to one channel and not the other. The two channels of the device share some internal functions (such as the MGS settings) because of the internal circuitry of the VCAs.


NOTE: *Powering down one channel will reduce the overall power consumed by the VCA, but it will not reduce the power consumption by half. This limited power consumption is a result of the shared circuitry architecture.*

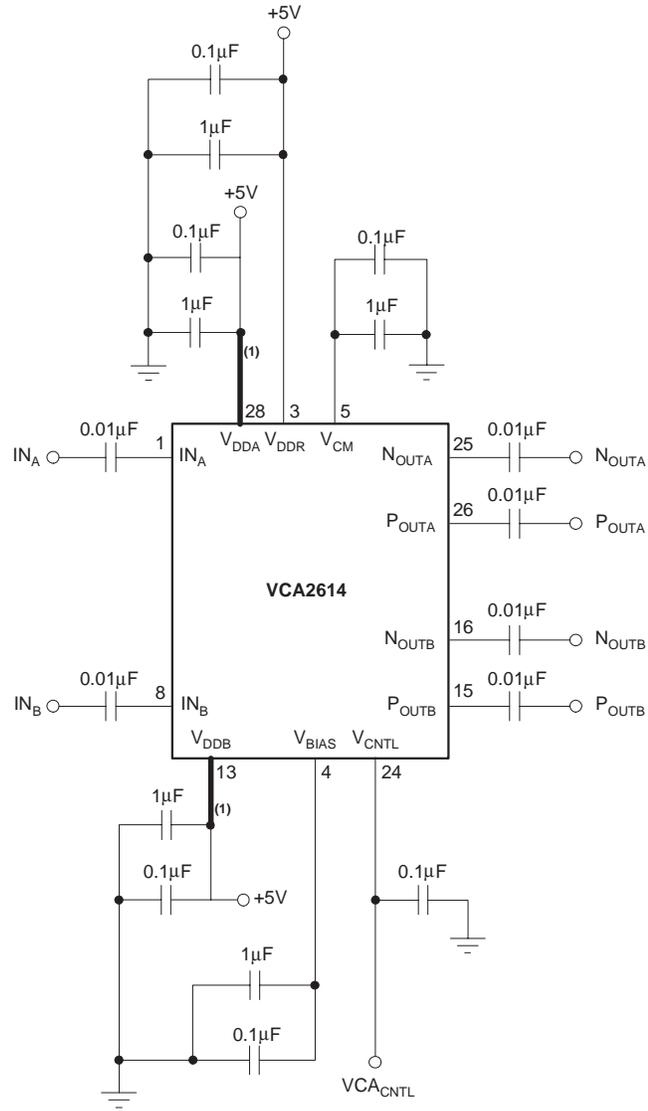Once the user has determined which channel will not be powered, the V_{DD} supply pin can be left disconnected from the power-supply. Figure 1 and Figure 2 show the locations of the connection to the supplies, with respect to each channel.



NOTE: (1) When powering down a single channel, one or the other supply pins (V_{DDX}) must be disconnected.

Figure 1. Typical Power Supply Connection of the VCA2614 Family

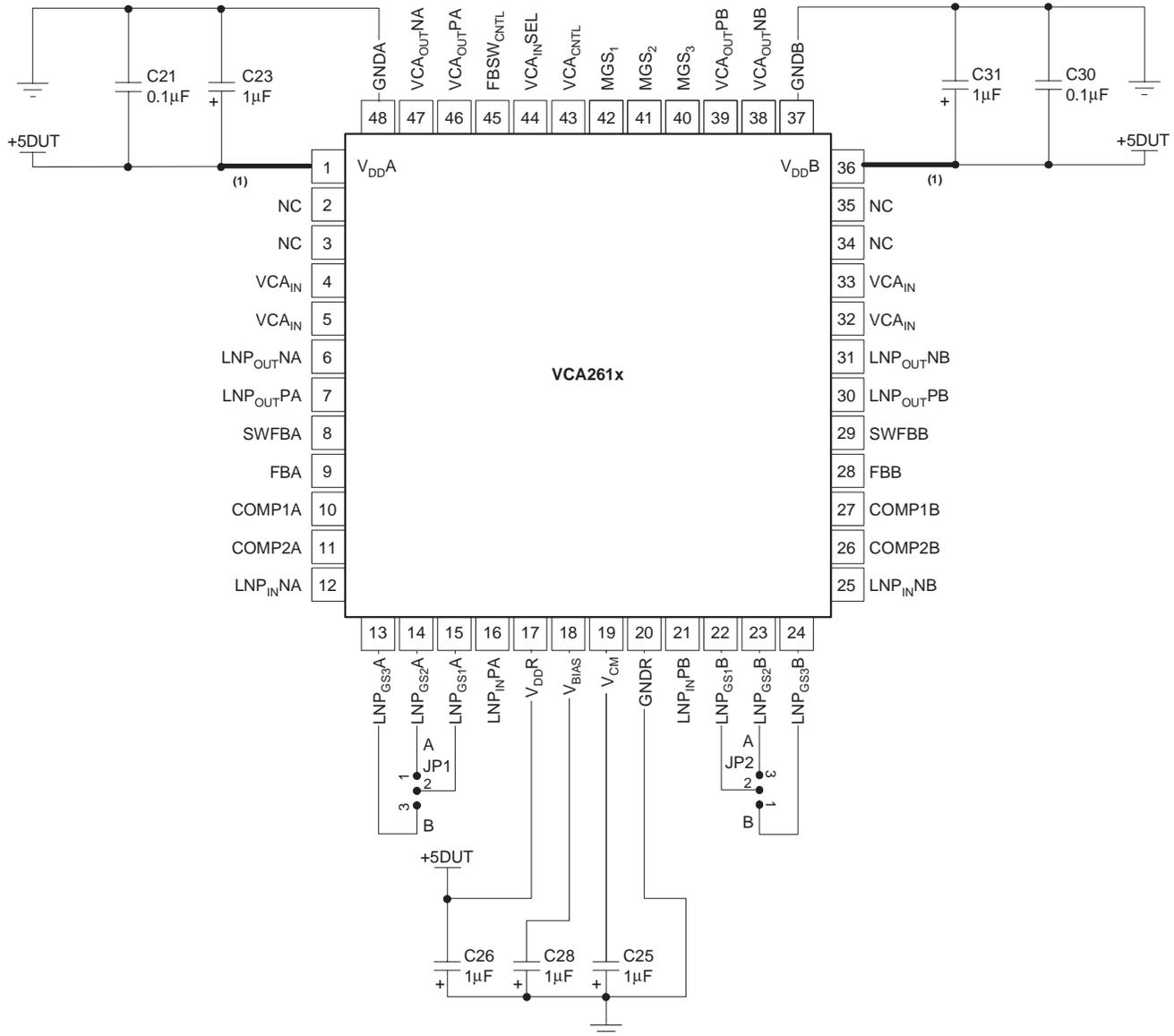

NOTE: (1) When powering down a single channel, one or the other supply pins (V_{DDX}) must be disconnected.

Figure 2. Typical Power Supply Connection of the VCA2611 Family

The ground pin (GNDA or GNDB) for the selected channel that will be powered down must be connected to ground. This requirement is a consequence of the shared internal circuitry. The reference supply pin and its associated ground pin (V_{DDR} and GNDR) must be connected, as well. Even though the reference circuit is shared, it is still important to connect these pins. These are all that is necessary to power down a single channel of the VCA.

Other possible methods of powering down a VCA channel include the use of a relay, as shown in Figure 4, or a transistor switch, as shown in Figure 5 (both a FET and a BJT are shown as examples). As noted earlier, turn-on delays will be associated with each setup; these characteristics would have to be considered for the actual devices used in either case. Other factors to be evaluated in the turn-on delay would also be the amount of capacitance on the power supply, the on-resistance of the device used, and the resistance and inductance of the printed circuit board trace connecting to the VCA.

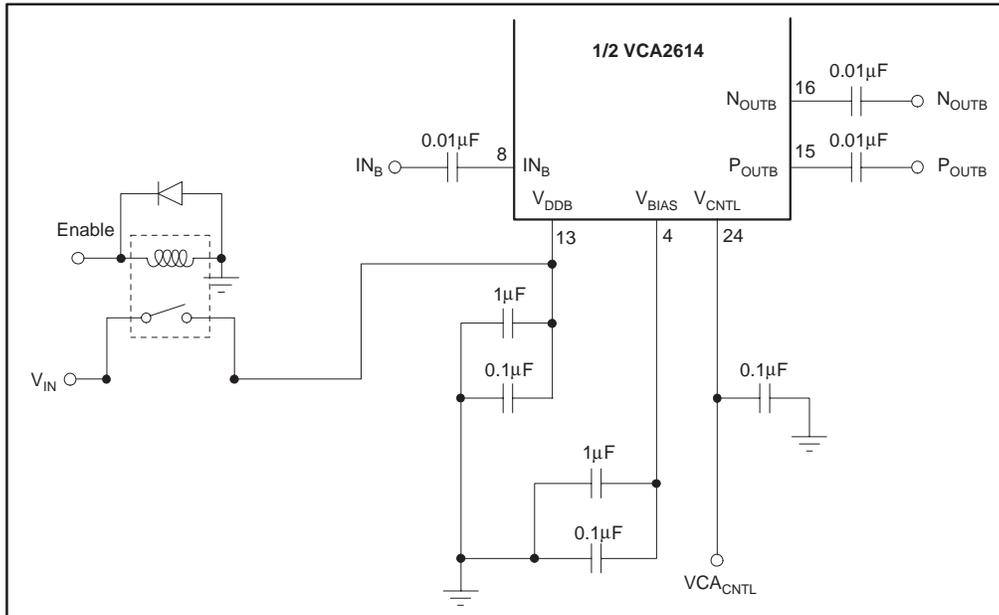


Figure 4. Example Relay Connection to the VCA261x

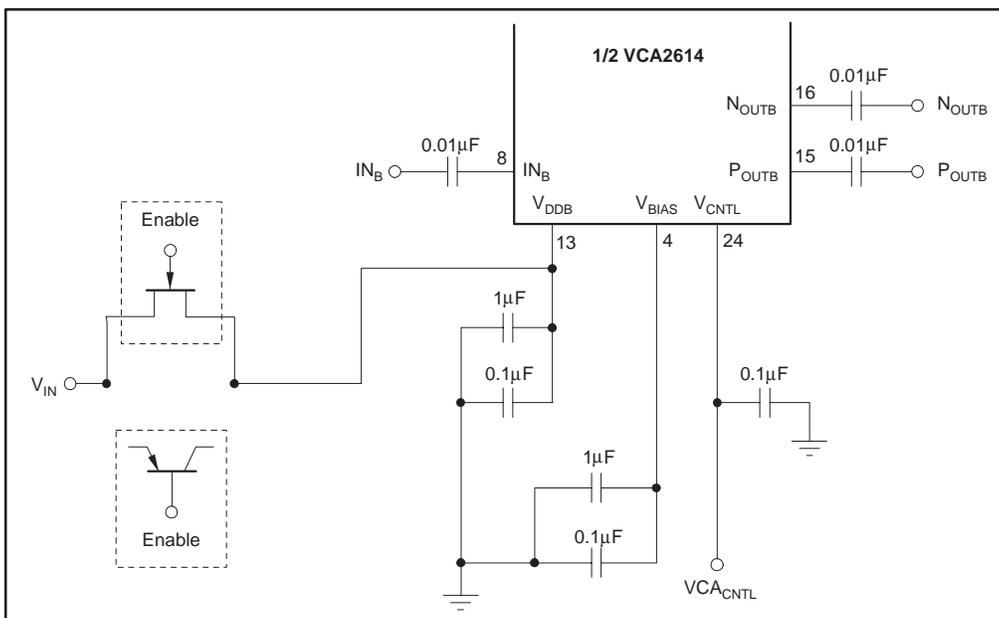


Figure 5. Example Transistor Connection to the VCA261x

Conclusion

Several different methods were presented here to accomplish the powering down of one channel of a VCA device. The concept of this process is simple if the power-down state is to be static; when the power-down state becomes dynamic, however, one must take into account additional variables, such as power-on delay and on-resistance.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265