

LF HDX System Parameter Calculation for TMS37157 (PaLFI)


K. Aslanidis, J. Wyatt

MCU-RF Systems

ABSTRACT

The Texas Instruments low frequency half-duplex (HDX) transponder technology allows the possibility to improve the communication distance between the transponder and reader. This application report provides information for the calculation of the basic system parameters.

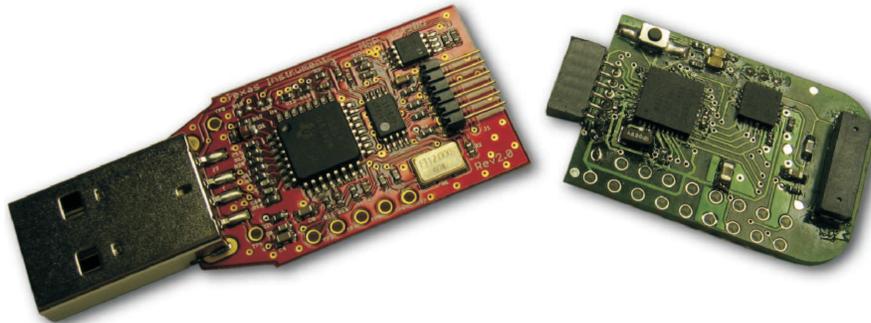The TMS37157 TI transponder IC is based on the TI HDX RFID concept. Using the given formulas, the performance and component parameters can be simulated and adjusted according to the application requirements.



Contents

1	TMS37157 Dual Interface RFID IC	2
2	TMS37157 System Description	4
3	Reference	10

List of Figures

1	TMS37157 PaLFI Block Diagram	2
2	TMS37157 PaLFI EVM.....	3
3	TMS37157 PaLFI Application Example	4
4	Demo Reader Antenna	5
5	Calculated Reader Field Strength Over Distance	6
6	Transponder Antenna Dimension	7
7	Coupling Factor Over Distance	8
8	Simulation Model for Charge Voltage	8
9	Typical Charge Voltage Over Distance	9

List of Tables

1	Abbreviations	3
2	Parameter of Demo Reader Antenna	5
3	Typical Parameter of a LF Transponder Antenna	7
4	Parameter for VCL Calculations	9

1 TMS37157 Dual Interface RFID IC

The TMS37157 TI RFID transponder IC passive low-frequency interface (PaLFI) is designed to work in the low-frequency band (134.2 kHz) and uses the HDX RFID communication protocol.

The IC provides a dual communication interface: one interface is used for the communication over the RF interface and one for the communication over the SPI interface.

The IC fully operates as a passive RFID transponder without any need for external power supply. For additional functionality, the IC can be directly connected to a MSP430 microcontroller via the SPI interface.

Depending on the system parameters and antennas used on both reader and tag side, the PaLFI can supply current derived from the magnetic field from the reader to the connected microcontroller over various distances.

This application report shows how to design the parameters to meet the system performance requirements (see [Figure 1](#)).

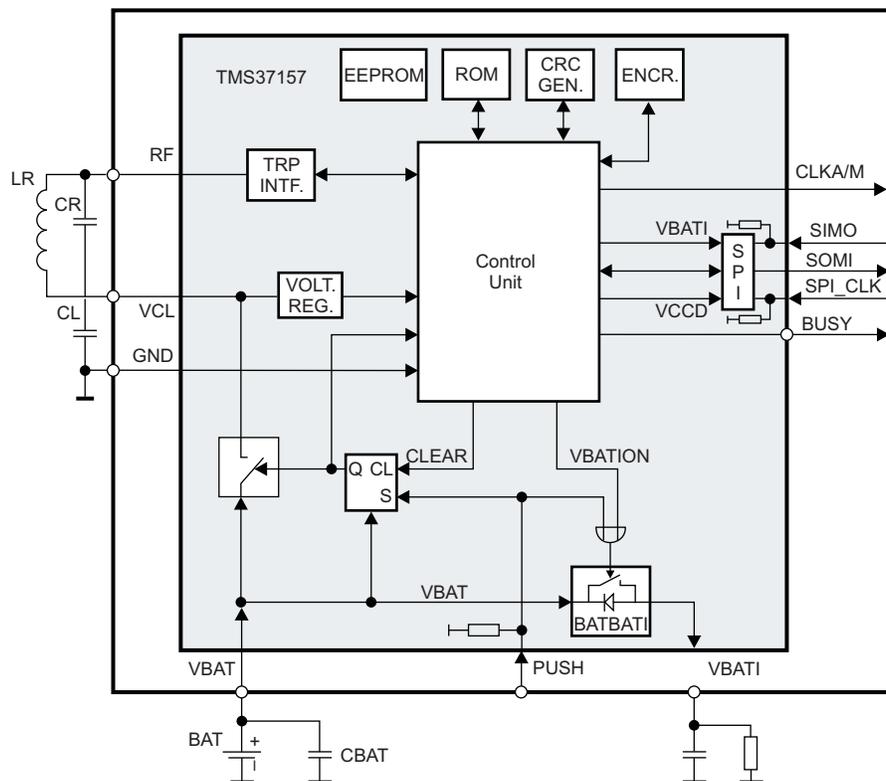


Figure 1. TMS37157 PaLFI Block Diagram

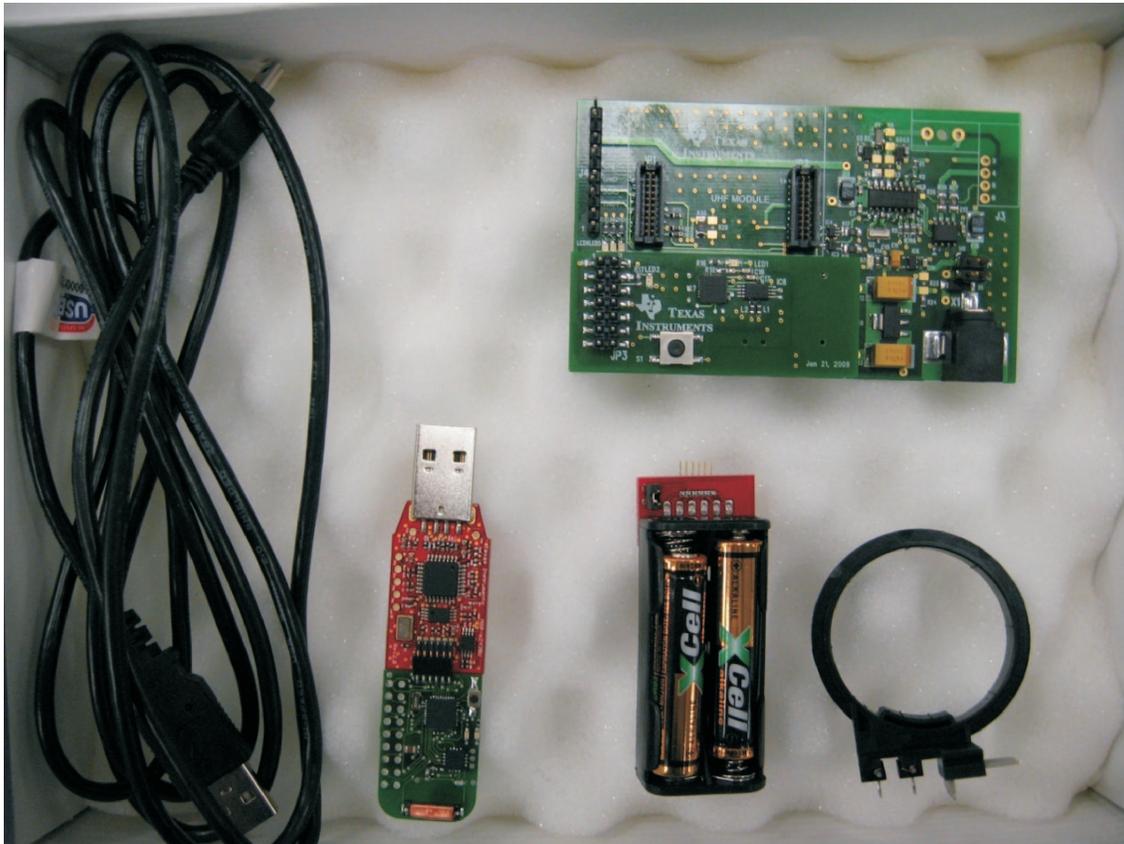


Figure 2. TMS37157 PaLFI EVM

Table 1. Abbreviations

Abbreviation	Description
Atrp	Transponder antenna area
CL	Charge capacitor
d	Distance from the reader antenna
dw	Transponder antenna wire diameter
fres	Transponder resonance frequency
ftx	Operating frequency (134.2 kHz)
H(d)	Reader field strength over distance
H	Reader field strength
ICL	Medium DC standby current of the IC during charge
Itx	Reader antenna current
k	Coupling factor between reader and transponder antenna
Ltrp	Transponder antenna Inductance
Ltx	Reader antenna inductance
Ntrp	Transponder antenna number of turns
Ntx	Reader antenna number of turns
Qant	Reader antenna quality factor
Qant'	Reader antenna total Q (including Rdms)
QRX	Antenna circuit quality factor during receive
Qtrp	Transponder antenna quality factor
QTX	Antenna circuit quality factor during transmit

Table 1. Abbreviations (continued)

Abbreviation	Description
Rant	Reader antenna resistance
Rant'	Reader antenna total resistance (including Rdms)
Rdmp	Parallel resistor to the antenna (damping)
Rdms	Serial resistor to the antenna (damping)
Ron	Driver on resistance
rtx	Medium radius of reader antenna $((A+B)/2)/2$
rtp	Medium radius of transponder antenna
Usup	Driver supply voltage
Utx	Reader antenna peak to peak voltage
VCL	Charge voltage
VCL_50	Charge voltage after 50 ms charge time

2 TMS37157 System Description

A typical RFID system consists basically of two main components:

- Reader
- Transponder

The right definition and design of the transponder and reader system parameters will provide the best possible system performance.

The TMS37157 operates as a typical RFID system, but offers additional functionality that can be executed using the MSP430 microcontroller connected directly to the PaLFI via the SPI interface.

A typical application can be seen in [Figure 3](#).

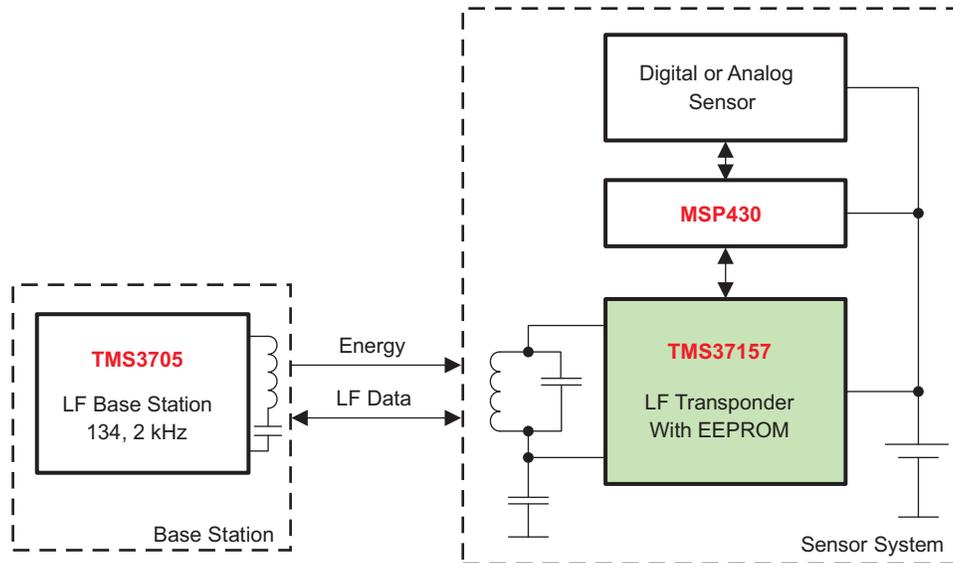


Figure 3. TMS37157 PaLFI Application Example

2.1 RFID Reader

2.1.1 Reader Field Strength

The typically reader (demo reader) using the ASIC TMS3705A [2] uses a circular air coil antenna with the following typical parameter (see Table 2 and Figure 4):

Table 2. Parameter of Demo Reader Antenna

Parameter	Symbol	Value (typ)	Unit
Inner diameter of transmit antenna	A	36	mm
Outer diameter of transmit antenna	B	39	mm
Medium radius of transmit antenna ((A+B)/2)/2	rtx	0.01875	m
Inductance	Ltx	442	μH
Turns	Ntx	72	
Antenna quality factor	Qant	25	

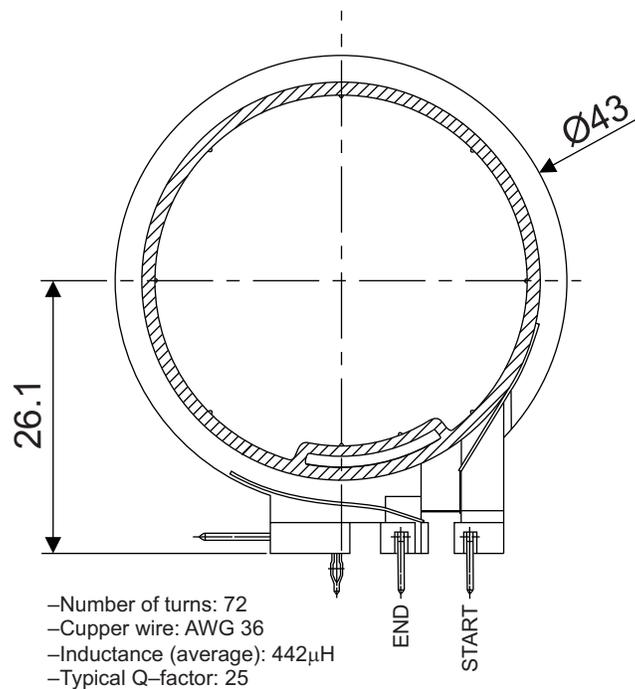


Figure 4. Demo Reader Antenna

2.1.2 Antenna Current and Voltage Calculation

The antenna current (I_{tx}) needed for field strength calculation can be measured with either a current probe or be calculated after a measurement of antenna peak-to-peak voltage (U_{tx}) and antenna quality factor (Q_{ant}):

$$I_{tx} = \frac{1}{2 \cdot \pi \cdot f_{tx} \cdot L_{tx} \cdot \left(\frac{1}{Q_{ant}} + 1 \right)} \cdot \frac{U_{tx}}{2 \cdot \sqrt{2}} = \frac{1}{(R_{ant} + 2 \cdot \pi \cdot f_{tx} \cdot L_{tx})} \cdot \frac{U_{tx}}{2 \cdot \sqrt{2}} \quad (1)$$

$$R_{ant} = \frac{2 \cdot \pi \cdot f_{tx} \cdot L_{ant}}{Q_{ant}} \quad (2)$$

The maximum peak-to-peak antenna voltage U_{tx} is:

$$U_{tx}[V_{pp}] = I_{tx} \cdot 2 \cdot \sqrt{2} \cdot (R_{ant} + (2 \cdot \pi \cdot f_{tx} \cdot L_{ant})) \tag{3}$$

2.1.3 Reader Field Strength Calculation

The field strength H generated by the reader in the distance d in case of a certain antenna current I_{tx} , is calculated with the following formula:

$$H[d] = \frac{N_{tx} \cdot r_{tx}^2 \cdot I_{tx}}{2 \cdot (d^2 + r_{tx}^2)^{1.5}} \tag{4}$$

$$H[dB\mu V/m] = 20 \cdot \log(H[A/m] \cdot 10^6) + 51.5 \tag{5}$$

Figure 5 shows a typical calculated and measured field strength over distance.

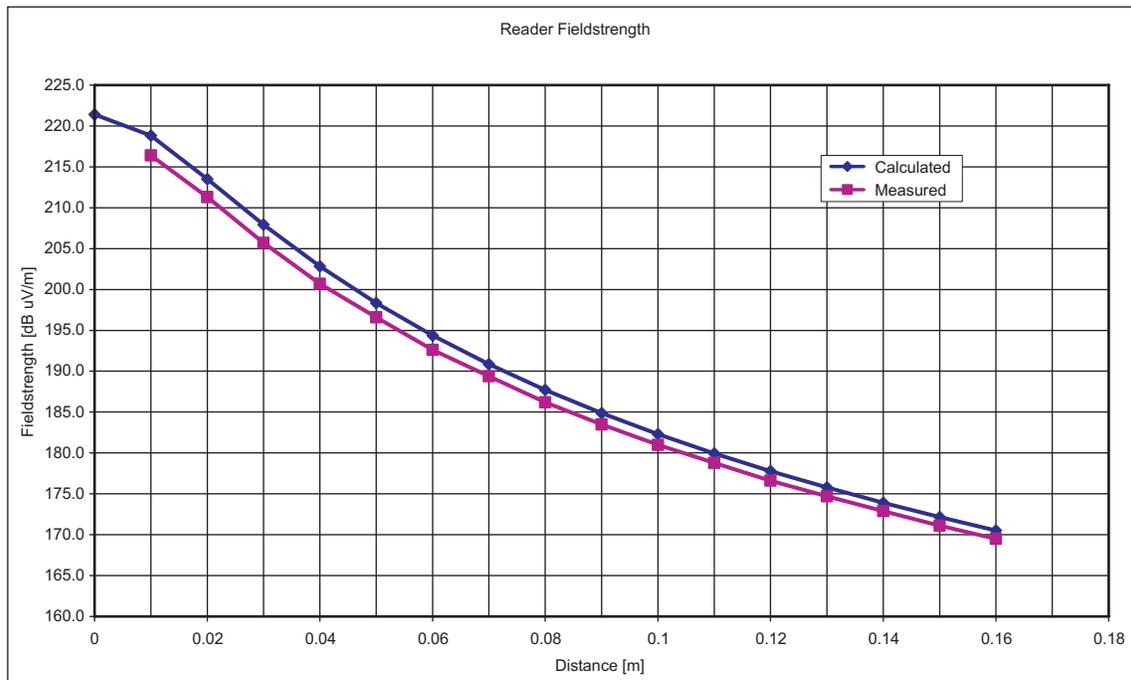


Figure 5. Calculated Reader Field Strength Over Distance

2.2 Transponder Parameter

2.2.1 Typical LF Transponder Antenna

A typical LF transponder antenna has the following typical parameter (see Table 3):

Table 3. Typical Parameter of a LF Transponder Antenna

Parameter	Symbol	Value (typ)	Unit
Magnetic field constant	μ_0	$1.25664 \cdot 10^{-6}$	Vs/Am
Height of transponder antenna	htrp	0.04	m
Width of transponder antenna	wtrp	0.07	m
Equivalent radius	rtrp	0.03	m
Area of loop	Atrp	2.827e-3	m ²
Inductance	Ltrp	2.66	mH
Typical transponder quality factor	Qtrp	35	
Turns	Ntrp	146	
Diameter of wire	dw	0.2	mm

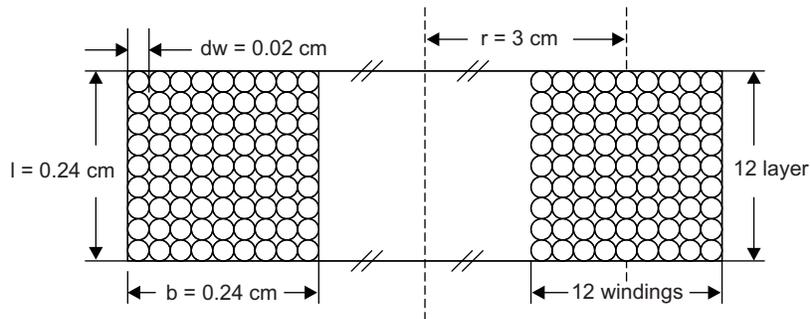


Figure 6. Transponder Antenna Dimension

Calculation of the resulting inductance of the antenna:

$$L_{trp}[\mu H] = \frac{0.8 \cdot (r_{trp} \cdot N_{trp})^2}{(6 \cdot r_{trp} + 9 \cdot l + 10 \cdot b) \cdot 2.56} \tag{6}$$

Calculation of the number of windings if the antenna inductance is known:

$$N_{trp} = \sqrt{\frac{L_{trp} \cdot (6 \cdot r_{trp} + 9 \cdot l + 10 \cdot b) \cdot 2.56}{0.8 \cdot r_{trp}^2}} \tag{7}$$

2.3 Coupling Between Reader and Transponder

The coupling factor (k) over distance (d) between the reader and the transponder antenna is calculated by the following formula:

$$k = \frac{\mu_0 \cdot N_{tx} \cdot N_{trp} \cdot r_{tx}^2 \cdot A_{trp}}{2 \cdot (d^2 + r_{tx}^2)^{1.5} \cdot \sqrt{L_{tx} \cdot L_{trp}}} \tag{8}$$

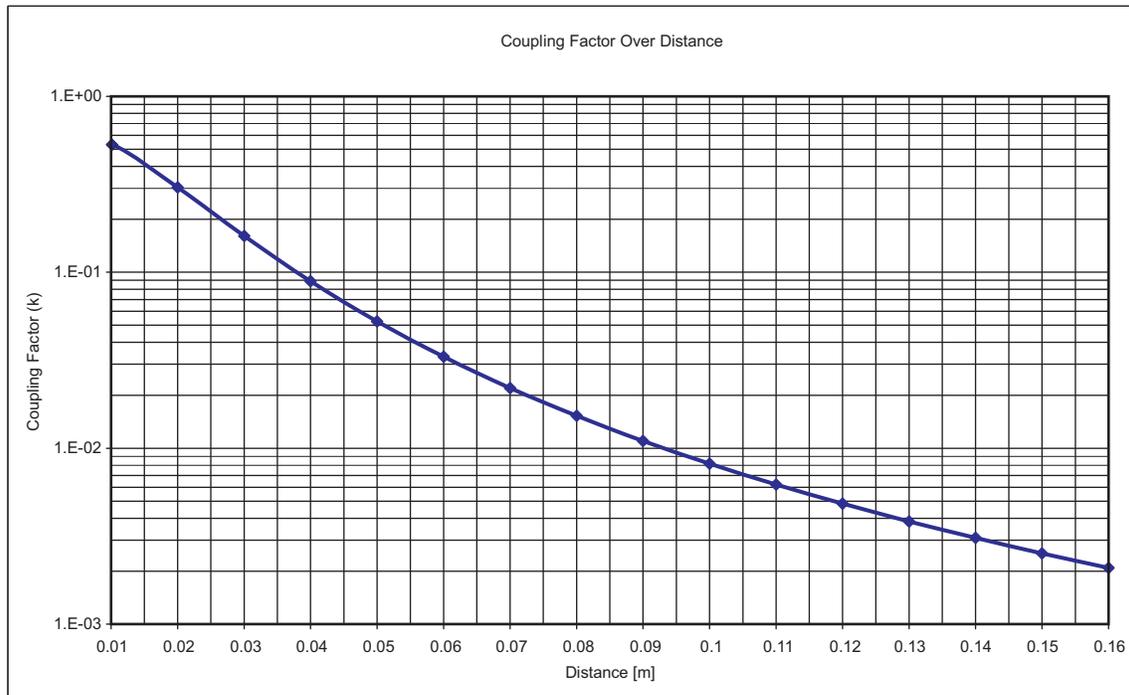


Figure 7. Coupling Factor Over Distance

2.4 Calculation and Simulation of Charge Voltage for HDX Systems

Figure 8 shows the simulation model for determination of charge voltage VCL.

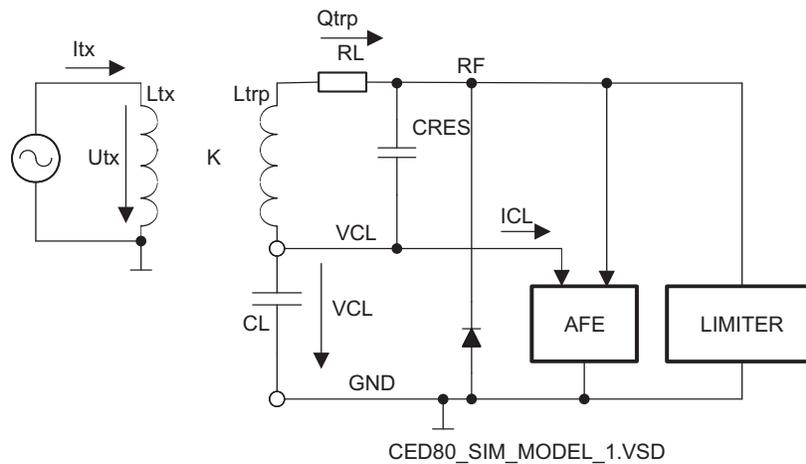


Figure 8. Simulation Model for Charge Voltage

The final charge voltage VCL can be calculated with the following formula:

$$VCL = \left(I_{tx} \cdot k \cdot \sqrt{L_{tx} \cdot L_{trp}} - ICL \cdot \sqrt{2} \cdot L_{trp} \right) \cdot 2 \cdot \pi \cdot f_{res} \cdot Q_{trp} \cdot \sqrt{2} + \frac{ICL}{I_{tx} \cdot k \cdot \sqrt{2}} \cdot \sqrt{\frac{L_{trp}}{L_{tx}}} - 0.5$$

(Assuming... $f_{res} = f_{tx} = 134.2 \text{ kHz}$)

(9)

ICL is the medium DC standby current of the IC during charge and Qtrp is the total transponder quality factor, represented by RL in the simulation model:

$$Q_{trp} = \frac{2 \cdot \pi \cdot f_{RES} \cdot L_{trp}}{RL}$$

(10)

The charge voltage without limitation after 50 ms can be calculated by:

$$VCL_{50} = VCL \cdot \left(1 - e^{\frac{-0.05}{4 \cdot \pi \cdot f_{res} \cdot Q_{trp} \cdot L_{trp} \cdot CL}} \right)$$

(11)

For the chart shown in Figure 9, the parameters shown in Table 4 are assumed.

Table 4. Parameter for VCL Calculations

Parameter	Symbol	Value (typ)	Unit
Transponder Quality Factor	Qtrp	35	
Standby Current During Charge	ICL	5	μA
Charge Capacitor	CL+CBAT	100	μF

Figure 9 shows the typical charge voltage (limited) over distance for a 50 ms charge burst.

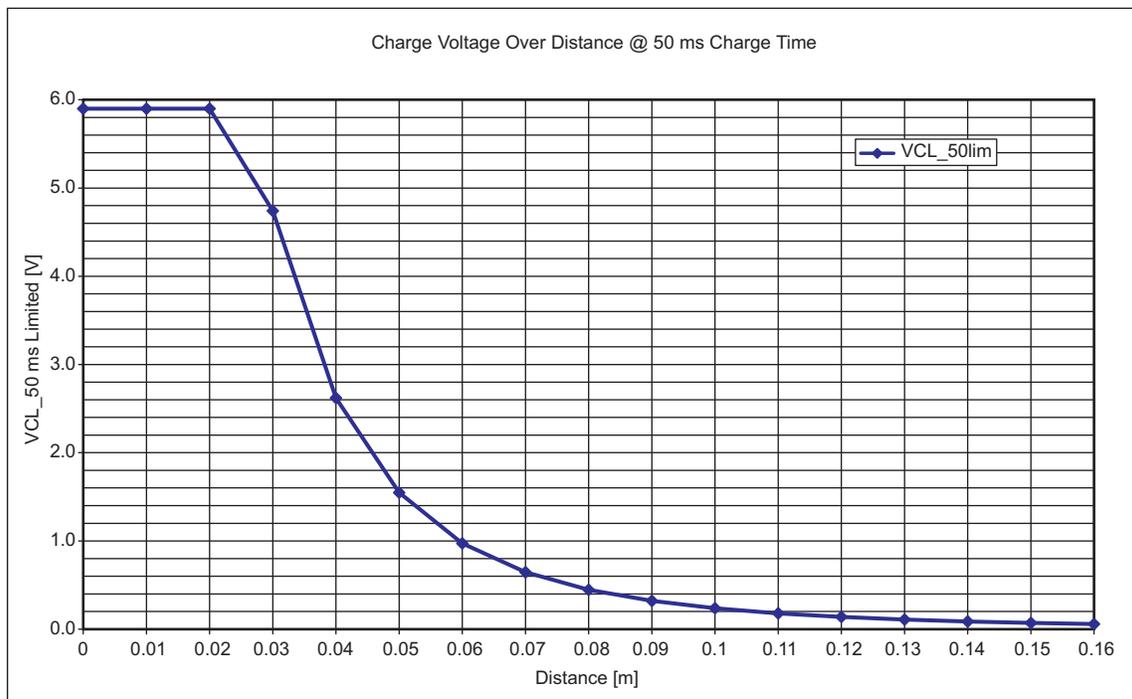


Figure 9. Typical Charge Voltage Over Distance

3 Reference

1. *TMS37157 Passive Low Frequency Interface Device With EEPROM and 134.2 kHz Transponder Interface Data Sheet* ([SWRS083](#))
2. *TMS3705 Transponder Base Station IC Data Sheet* ([SCBS881](#))
3. *UCC27423, UCC27424, UCC27425 Dual 4-A High Speed Low-Side MOSFET Drivers With Enable Data Sheet* ([SLUS545](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated