

Texas Instruments Robotics System Learning Kit





Module 2


Lecture: Voltage, Current and Power



Voltage, Current and Power

You will learn in this module

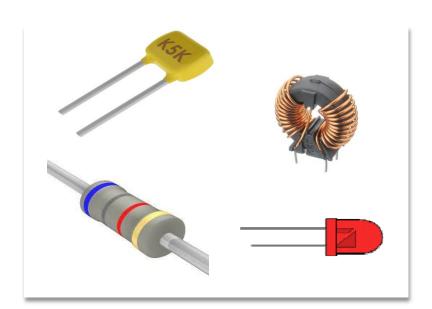- Electrical Engineering Terms
 - Voltage, V (volts)
 - Current, I (amps)
 - Energy, E (joules)
 - Power, P (watts)
- Electrical Engineering Devices
 - Resistors
 - Capacitors
 - Inductors
 - LEDs
- Test Equipment
 - Voltmeter, ohmmeter, current meter
 - Oscilloscope





Current


- Definition of Current
 - Current is caused by motion of electrons
 - Symbol is I, measurement unit is Ampere or Amps
 - 1 ampere (A) is 6.241×10¹⁸ electrons per second
 - Current of 1A = one coulomb of charge per second

Properties

- Directional, along a path or wire
- Stimulates muscles and nerves
- Drive motors of your robot
- Follows Ohm's Law (V= IR)

Measurements

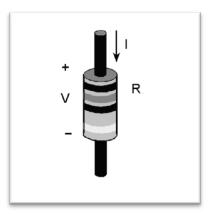- Current inside a circuit can be measured with a meter
- Voltage across a know resistor V = I*R



MSP432 can source/sink up to 6 mA



Voltage


- Definition of voltage
 - Voltage is caused by potential difference between two points
 - Symbol is V and is measured in Volts
 - Electromotive force or potential to produce current

Properties

- · Always measured as a difference
- Signed, directional causes current to flow
- Battery used to drive motors of your robot
- Follows Ohm's Law

Measurements

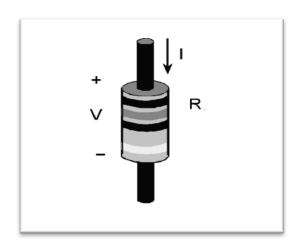- Voltmeter measures DC and AC voltage
- Oscilloscope measures voltage changes as function of time (V v/s t)



MSP432 can output 0V or 3.3V



Energy and Power

- Definition of energy
 - Amount of storage, for battery specification
 - Units of energy are joules(J=volts*amps*time)
 - E=1J delivers 1V at 1A for 1 second
- Batteries
 - · Constant voltage
 - Rated in amp-hour
- Power
 - · Rate of change of energy
 - P = V*I
 - Units of power are watts=J/sec = volts*amps
 - Conversions: electrical, optical, mechanical, thermal, acoustic

MSP432 requires 5mA at 3.3 V

AA alkaline battery has 2 A-h at 1.5V


Power budget:


Two AA alkaline batteries will power an MSP432 for 16 days, 2000 mA-h = 5mA*400h




Resistor

- Definition of resistor
 - Passive device with a linear V-I relationship
 - Resistance is measured in R, in Ohms (Ω)
 - Follow's Ohm's Law
- Parameters
 - Tolerance, e.g., 5% (1000 $\Omega \pm 5$ %)
 - Maximum power, wattage (¼ watt = 250 mW)
 - For a V= 2 V, I= 2 mA, P= 2 * 2 mA = 4 mW
- Applications
 - Used to limit or control current
 - Used in circuits to effect gain, offset, frequency response

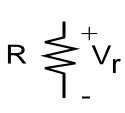

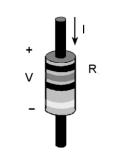


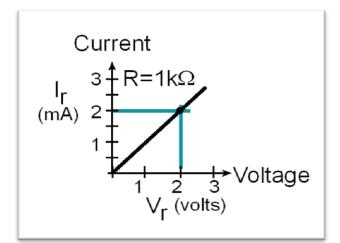



Analogy

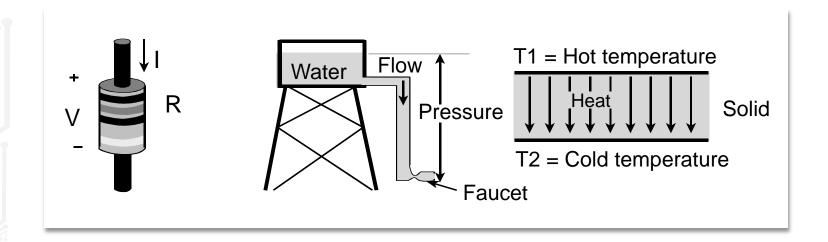
- Current = Voltage/Resistance
- Fluid Flow = Pressure/Resistance
- Heat Flow = Temperature/Resistance





Capacitor

- Definition of capacitor
 - Passive device that can store charge
 - Complex impedance, Z = 1/(j2πfC)
 - Open circuit at DC
 - Allows current at AC
 - Reactance, $|V|/|I| \equiv X = 1/(2\pi fC)$
- Parameters
 - Capacitance, C, in farads (F)
 - Tolerance, e.g., 5%
 - Maximum voltage
 - Type, e.g., ceramic, tantalum
- Applications
 - Used as temporary storage of energy
 - Used in circuits to effect frequency response
 - Used to reduce noise in circuits

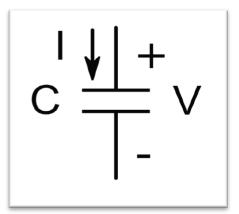






Inductor

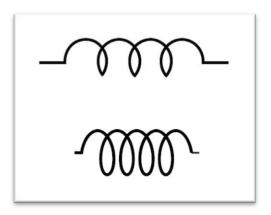- Definition of inductor
 - Passive device build with coiled wire
 - Complex impedance $V/I \equiv Z = j2\pi fL$
 - Closed circuit at DC
 - Resists current at AC
- Parameters
 - Inductance, L, in Henries (H)
- Applications
 - Used as to build DC motors









Light Emitting Diode

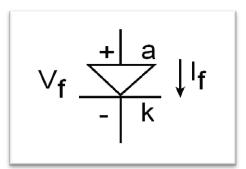- Definition of LED
 - Semiconducting device that can emit light
 - Electrical power => optical power
 - Conducts in one direction only
- Parameters
 - Voltage, current
 - Efficiency, brightness
 - Size
- Applications
 - Lights, displays, sensors
 - Isolation circuits, fiber optics



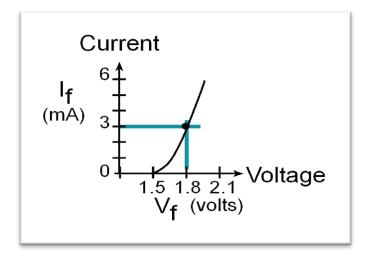



DC motor


- Definition of DC Motor
 - Electromechanical device
 - Electrical power => mechanical power
 - Spins in both directions



- Voltage, current
- Efficiency, torque
- Size, weight
- Applications
 - Robot actuator



Electrical Model

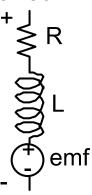


- Resistance, R
- Inductance, L
- emf, V



Voltage, Current, Power

Summary

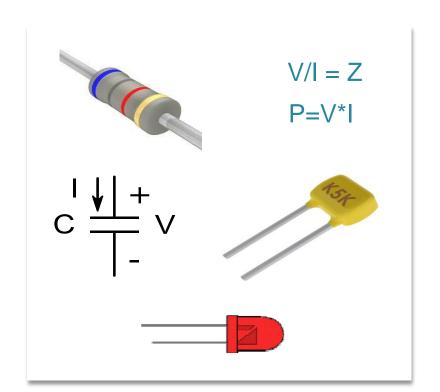- Resistors
 - Voltage, current, power
 - Ohm's Law, V=I*R
- Capacitors
 - Voltage, current
 - Reactance, $X = 1/(2\pi fC)$
 - Impedance, $Z = 1/(j2\pi fC)$
- Inductors
 - Voltage, current
 - Impedance, $Z = j2\pi fL$
- LEDs
 - Voltage, current, power
 - Unidirectional
 - Nonlinear






Lecture: Introduction to Circuits



Introduction to Circuits

You will learn in this module

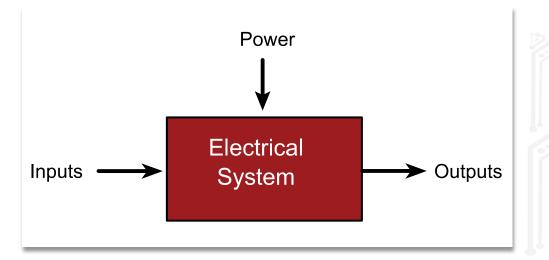- Electrical systems combine
 - Power
 - Inputs
 - Components
 - Connections
 - Outputs
- Simple DC circuit
 - Battery, switch, resistor, and LED
 - Voltmeter, current meter
- Simple AC circuit
 - Sine wave input, resistor, capacitor
 - Signal generator, oscilloscope
- Motor Drive Circuit
 - Microcontroller input, motor output
 - Logic analyzer





An electrical circuit includes


- Power
- Electrical components
- Interconnection of the components
- Mechanisms for testing





Electrical Components

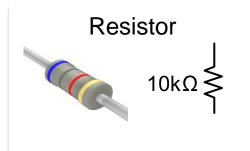


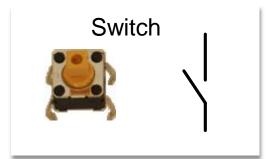

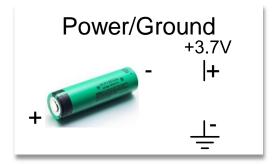


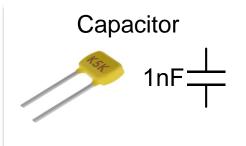

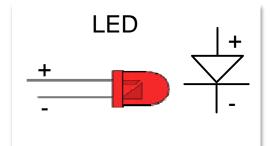

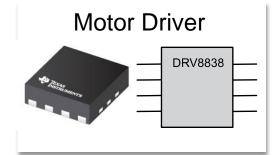


Interconnection Rules

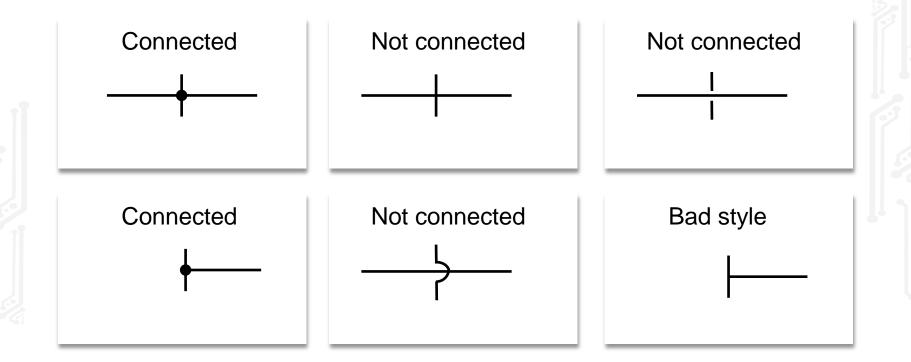



Switch-controlled LED

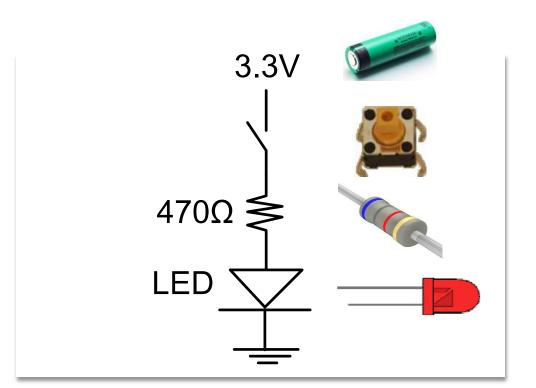
- Input
 - SPST switch
- Power
 - 3.3V supply
 - Ground
- Output
 - Light from LED





Switch-controlled LED

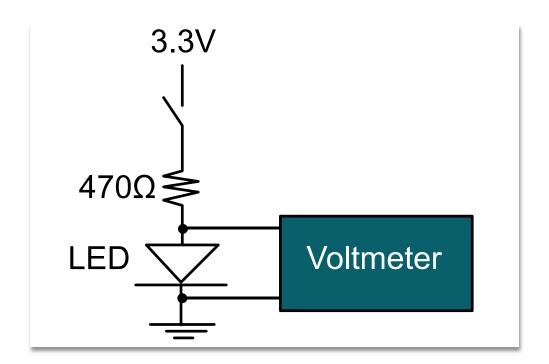
- Input
 - SPST switch
- Power
 - 3.3V supply
 - Ground
- Output
 - Light from LED
- Testing
 - Voltmeter





Switch-controlled LED

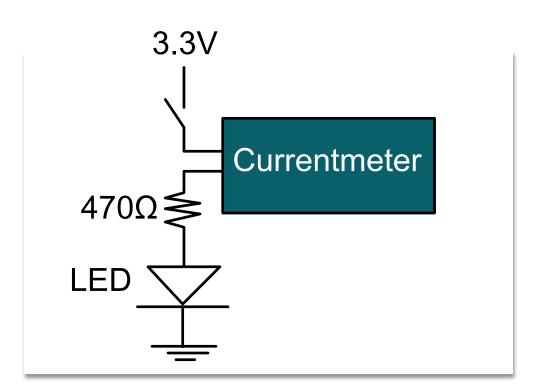
- Input
 - SPST switch
- Power
 - 3.3V supply
 - Ground
- Output
 - Light from LED
- Testing
 - Voltmeter
 - Current meter





Analog Low Pass Filter

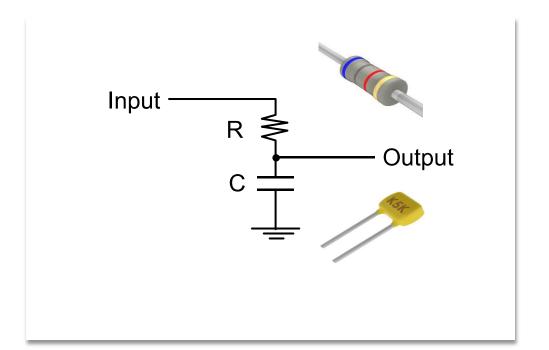
- Input
 - Signal from other circuit
- Power
 - Ground
- Output
 - Signal to other circuit





Analog Low Pass Filter

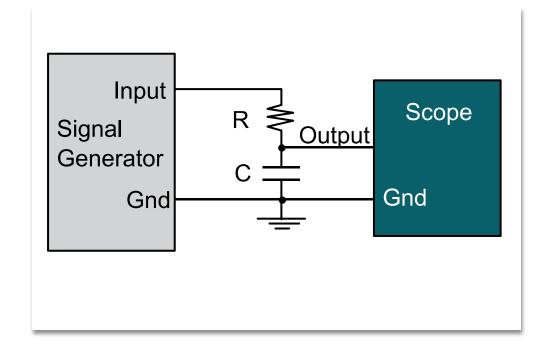
- Input
 - Signal from other circuit
- Power
 - Ground
- Output
 - Signal to other circuit
- Testing
 - Signal Generator
 - Oscilloscope





Motor Driver

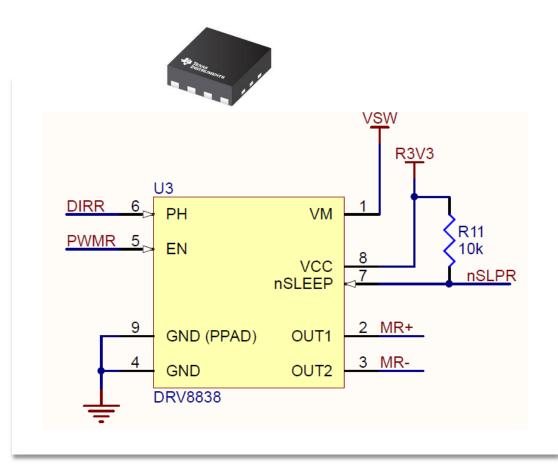
- Input
 - Signals from microcontroller
- Power
 - VSW = 7.2V
 - R3V3 = 3.3V
 - Ground
- Output
 - Signals to motors





Motor Driver

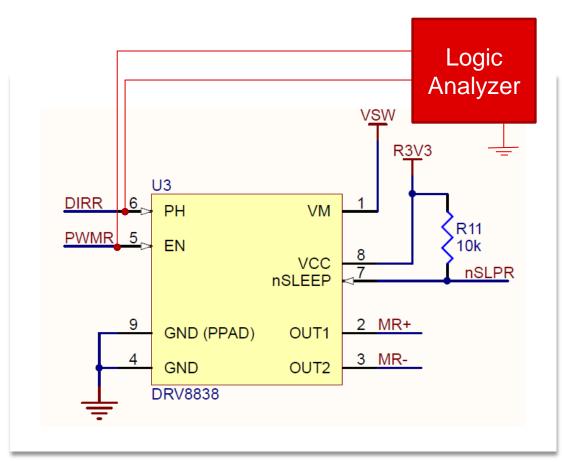- Input
 - Signals from microcontroller
- Power
 - VSW = 7.2V
 - R3V3 = 3.3V
 - Ground
- Output
 - Signals to motors






Introduction to Circuits

Summary

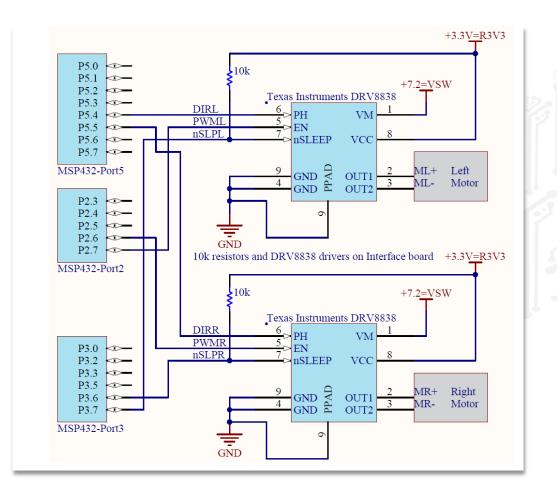- Electrical Systems have
 - Inputs
 - Electrical Circuits
 - Outputs
- Electrical Circuits
 - Power Source
 - Components
 - Interconnections
- Mechanisms for Testing
 - Voltmeter
 - Current meter
 - Signal generator
 - Oscilloscope
 - Logic Analyzer



ti.com/rslk



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2019, Texas Instruments Incorporated