

# DRV3201 Boost Converter

Motor Drive Business Unit - Advanced Protection Motor Drivers

## ABSTRACT

The DRV3201 boost converter is used to drive the external power MOSFETs. This type of converter allows the DRV3201 to continue full operation of the external bridges down to a lower voltage than other DC-DC converters. It is important to understand the requirements of the external components to power the boost to ensure proper operation. This application report describes the boost converter for the DRV3201.

### Contents

1	Boost Converter .....	1
2	Application Circuit for Boost Converter .....	3
3	Boost Converter Noise Reduction .....	4

### List of Figures

1	Coil Current Waveforms in Steady State for Nominal, High and Low Battery Voltage .....	2
2	Boost Waveforms Showing Burst Pulsing Controlled by Hysteretic Comparator Levels .....	3
3	Recommended Application Circuit for Boost Converter .....	3
4	Boost Output and Current Sense O1 Output, Before and After Bypass Capacitor .....	4
5	High Current Path During Boost FET 'On' State .....	5
6	High Current Path During Boost FET 'Off' State .....	5
7	High Switching Transient Current Return Paths .....	6

### List of Tables


## 1 Boost Converter

The output current capability of the Boost Converter can be configured with the external *Rshunt\_boost* resistor to  $0.1 V/Rshunt\_boost$  (please note that this resistor needs to be able to conduct the boost switching current). In this way, the output current capability can be dimensioned to the needed current determined by the PWM switching frequency and the gate-charge of the external power FETs. TI recommends choosing a coil having a current saturation level of at least 30% above the current limit level set with the resistor *Rshunt\_boost*.

The operation principle of the Boost Converter is based on a burst-mode fixed-frequency controller. During the on-time, the internal low-side boost FET turned on until the current limit level is detected; the off-time is calculated proportionally from a 2.5-MHz time-reference by sensing the supply voltage (VS) and the output voltage (VBOOST). The formula for the calculated off-time is given in [Equation 1](#), with  $f_{boost} = 2.5$  MHz.

$$t_{off} = \frac{VS}{V_{BOOST} \times f_{BOOST}} \quad (1)$$

For steady-state, the current in the coil will look as illustrated in [Figure 1](#).

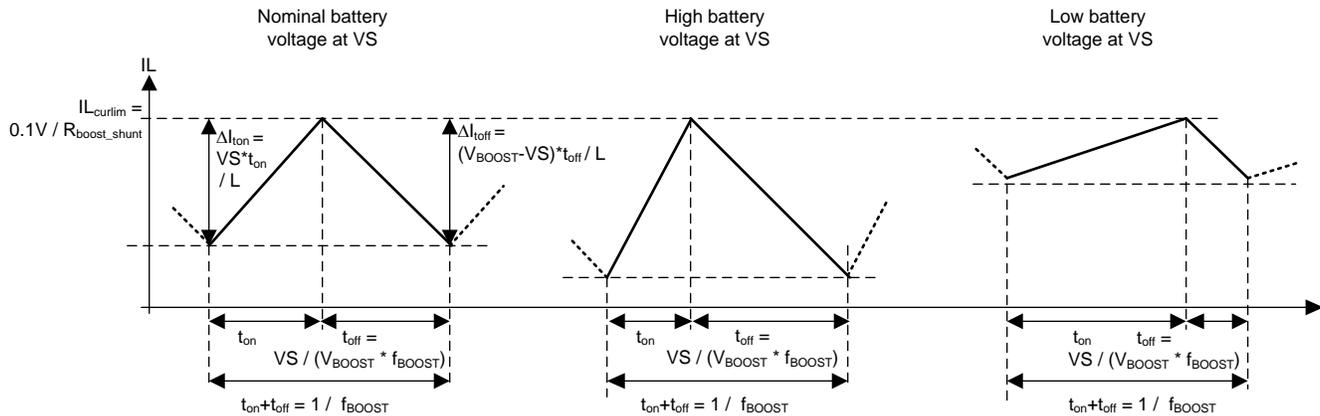

**Figure 1. Coil Current Waveforms in Steady State for Nominal, High and Low Battery Voltage**

From this figure, the ripple current and the boost output current can be calculated as follows:

$$I_{L\_ripple} = \frac{VS}{L \times f_{BOOST}} \times \left(1 - \frac{VS}{V_{BOOST}}\right) = \frac{(V_{BOOST} - VS) \times VS}{L \times f_{BOOST} \times V_{BOOST}} \quad (2)$$

$$I_{BOOST} = \frac{VS}{V_{BOOST}} \times I_{L\_curlim} - \frac{1}{2} \times \left(\frac{(V_{BOOST} - VS) \times VS}{L \times f_{BOOST} \times V_{BOOST}}\right) \quad (3)$$

$$f_{BOOST} = 2.5 \text{ MHz}; \quad (V_{BOOST} - VS) = 15 \text{ V}; \quad I_{L\_curlim} = \left(\frac{0.1 \text{ V}}{R_{shunt\_boost}}\right) \quad (4)$$

As Equation 3 shows, the boost output current capability for a given  $I_{L\_curlim}$  is the lowest for the minimum supply voltage  $VS$ . So the boost output current capability needs to be dimensioned (by setting  $I_{L\_curlim}$  with external  $R_{shunt\_boost}$ ) such that the needed output current (based on PWM frequency and gate-charge of the external power FETs) can be delivered at the needed minimum supply voltage for the application. Equation 5 gives  $I_{L\_curlim}$  as a function of  $I_{BOOST}$  and  $VS$ :

$$I_{L\_curlim} = I_{BOOST} \times \frac{V_{BOOST}}{VS} + \frac{1}{2} \times \left(\frac{V_{BOOST} - VS}{L \times f_{BOOST}}\right) \quad (5)$$

For setting the  $I_{L\_curlim}$ , the minimum application supply needs to be used in this equation and  $I_{BOOST}$  according to Equation 5. The minimum application supply voltage which the DRV3201 can support is 4.75 V.

As shown by Equation 3, the boost output current capability increases for higher supply voltage  $VS$ . In case the boost output current capability is dimensioned such that it can deliver the necessary output current for the minimum supply voltage, it actually will deliver more current than needed for nominal supply voltage. This will cause the boost voltage to increase. Therefore, a hysteretic comparator (low-level  $V_{BOOST} - VS = 14 \text{ V}$ , high level  $V_{BOOST} - VS = 16 \text{ V}$ ) determines starting/stopping the burst pulsing, as Figure 2 illustrates.

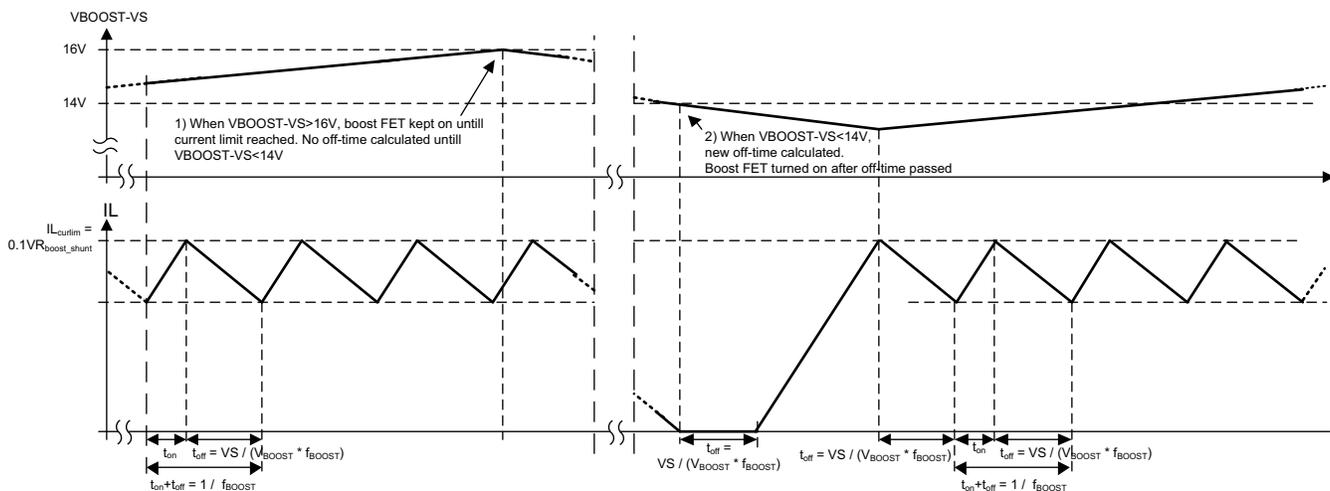


Figure 2. Boost Waveforms Showing Burst Pulsing Controlled by Hysteretic Comparator Levels

## 2 Application Circuit for Boost Converter

The recommended application for the Boost Converter is given in Figure 3. For the best performance a Schottky diode and a 22- $\mu$ H coil is required. The current limit for the internal FET (and hence the maximum current in the coil) can be adjusted and is set to  $0.1 V / 0.33 \Omega = 303 \text{ mA}$  in the recommended application.

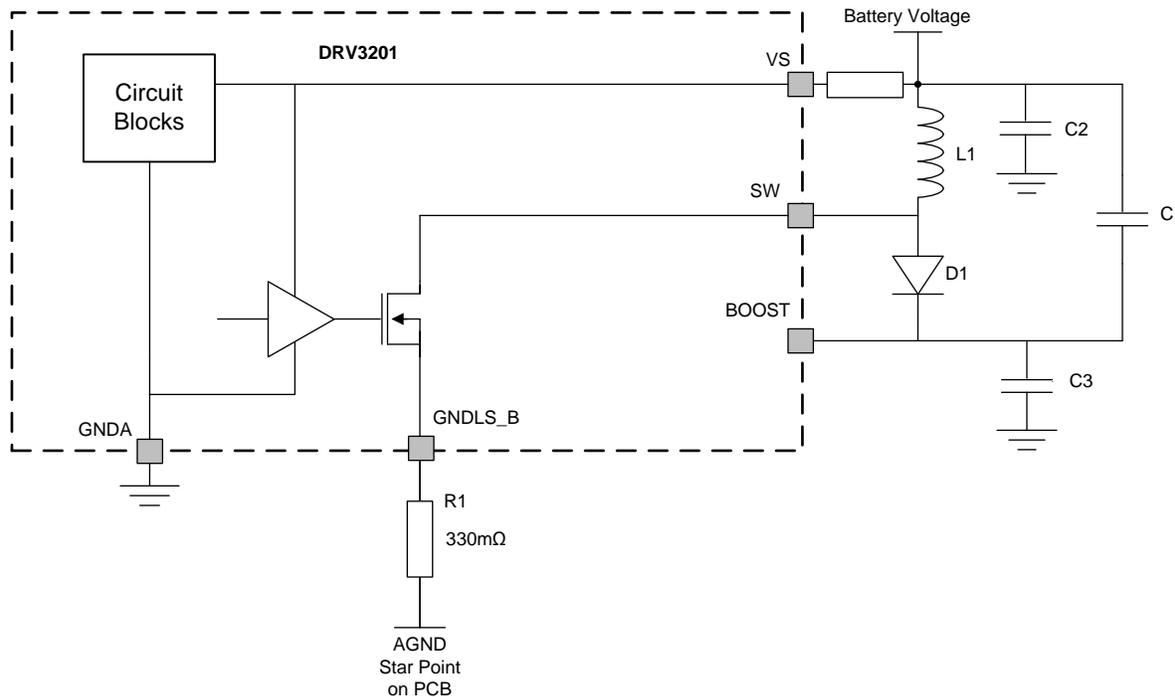



Figure 3. Recommended Application Circuit for Boost Converter

All capacitors must be appropriately sized to handle the boost voltage. The following list shows the part numbers for the primary components:

- L1 = B82442A1223K000
- D1 = SS28
- C1 = 1  $\mu$ F

### 3 Boost Converter Noise Reduction

In addition to the boost capacitor C1, two bypass capacitors, C2 and C3, are placed to reduce the ringing effect from the converter switching. [Figure 4](#) shows the effect of adding two 0.1- $\mu$ F bypass capacitors to the boost ripple. The red trace is the rising edge of the boost ripple while the converter is switching. The green trace shows the current sense output O1 to illustrate the possible coupling on the system. The first diagram is taken from our DRV3201EVM without any bypass components and shows the coupling from the converter switching to the boost output and the O1 current sense output. The addition of the bypass capacitors in the second diagram show a decrease in the transient spikes on the boost output, and show no coupling on the current sense output O1.

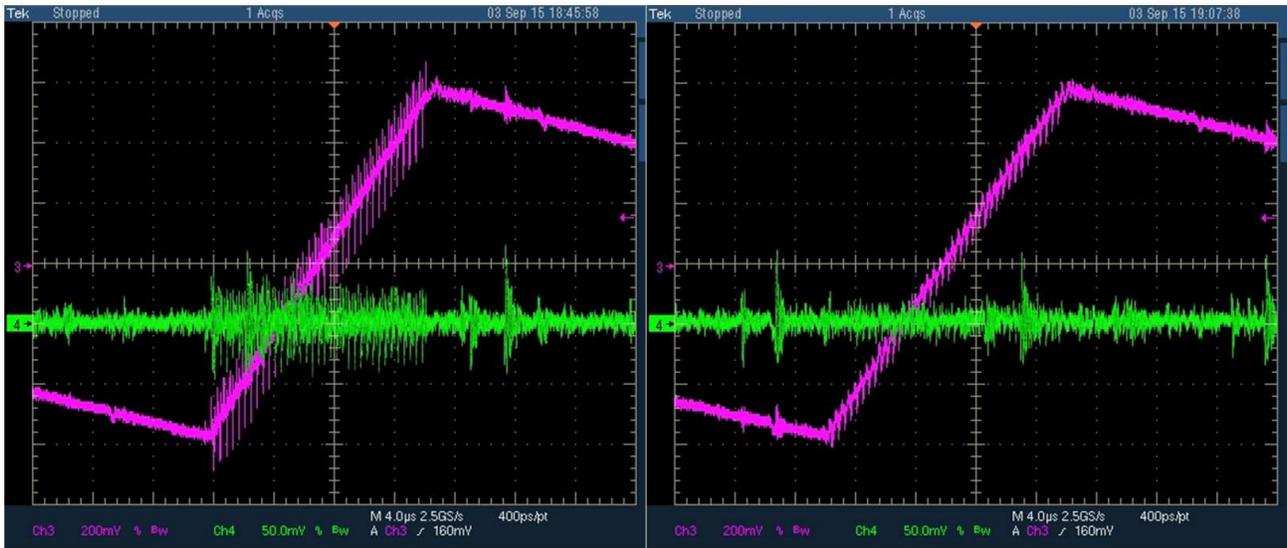

**Figure 4. Boost Output and Current Sense O1 Output, Before and After Bypass Capacitor**

The layout for the boost converter is critical to the device performance for both regulation and noise suppression. The most important consideration when laying out the boost converter is to keep all high current loops small. [Figure 5](#) and [Figure 6](#) show the high current paths during the on and off states of the boost MOSFET during regulation.

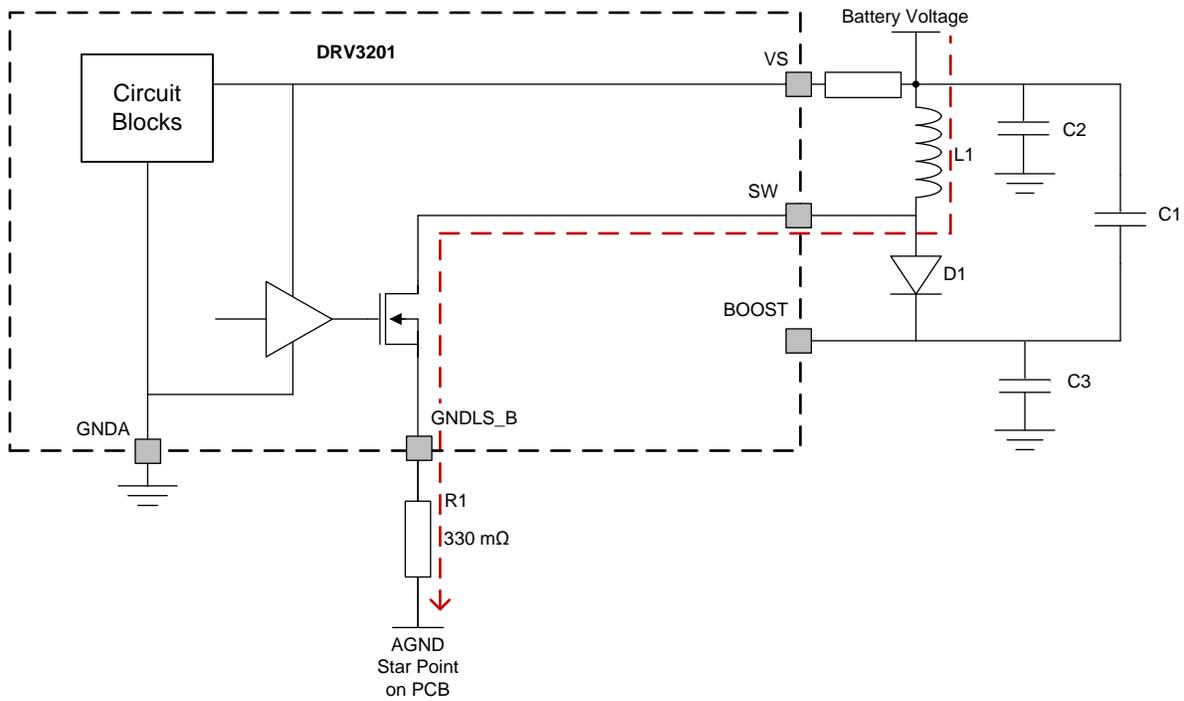


Figure 5. High Current Path During Boost FET 'On' State


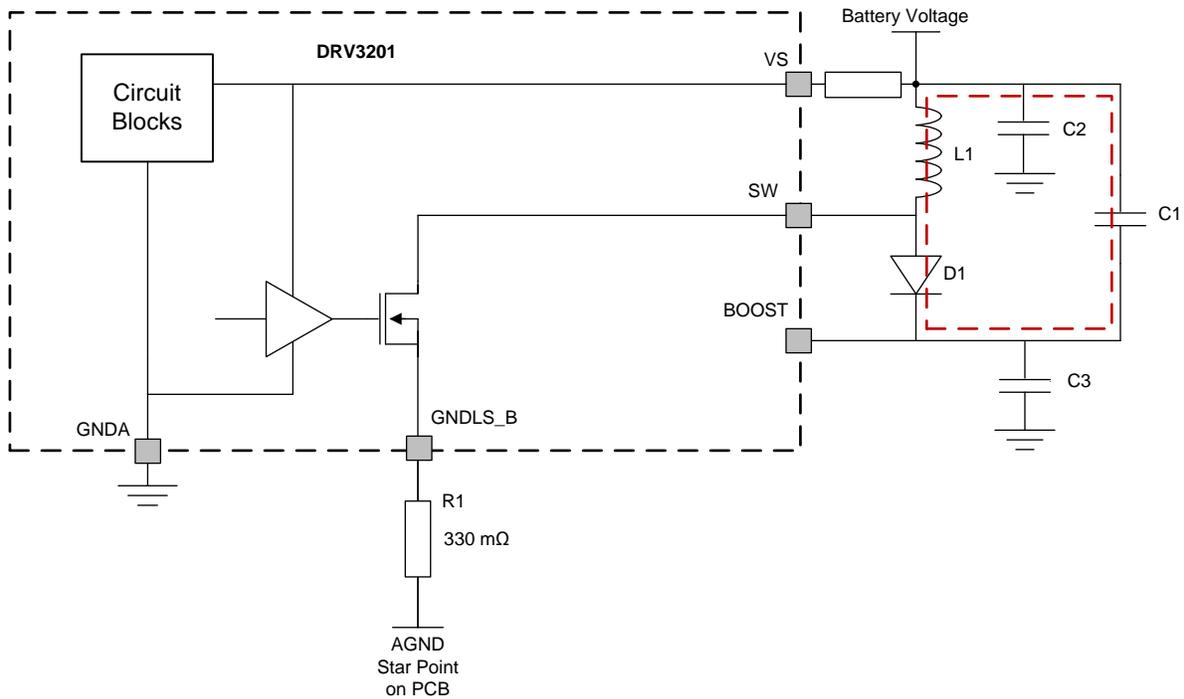


Figure 6. High Current Path During Boost FET 'Off' State

In addition to these high current paths, the loops for high current transients must be kept small. [Figure 7](#) illustrates the high current transient loops that exist when at the instant the boost FET is switched on or off.

### High Switching Transient Current Return Paths

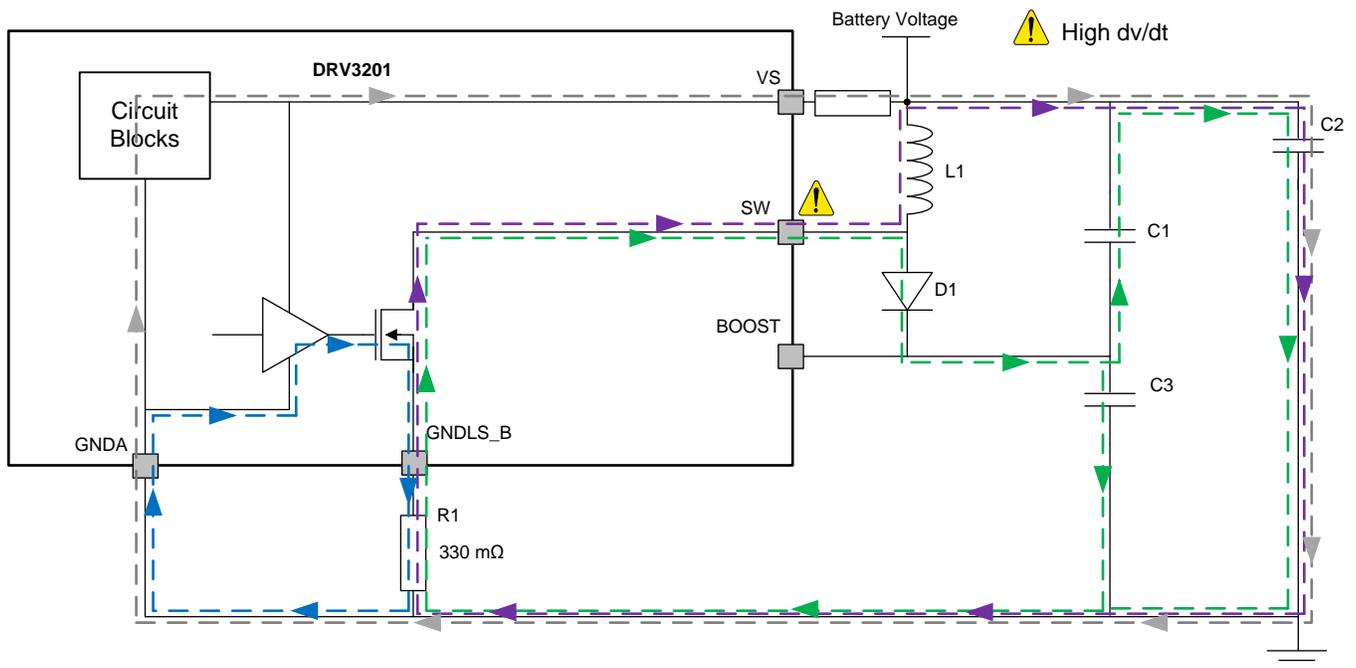

**Figure 7. High Switching Transient Current Return Paths**

If required, an additional series RC snubber circuit can be added to the switch pin to further reduce noise due to the effects of parasitic inductance and capacitance. For additional details on selection of snubber components, refer to *Minimizing Ringing at the Switch Node of a Boost Converter* ([SLVA255](#)).

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)