

Estimating available application power for Power-over-Ethernet applications*

By **Martin Patoka** (Email: mpatoka@ti.com)

Systems Engineer

Introduction

Many existing Ethernet devices are being converted from wall-adaptor power sources to utilize the newly released IEEE 802.3af Power-over-Ethernet (PoE) standard. Power-system efficiency formerly was not much of an issue with a wall adapter—but PoE changes that. Applications whose functional circuits begin to draw power in the 10-W range need close control of their power usage. This article helps the designer determine how much power is available when an application operates from a PoE source.

First we will determine the net power available once the functions required by the 802.3af standard are performed. Then a method of modeling the usual DC/DC converters to compute the power available for the applications circuits will be presented, with two example topologies for comparison. The modeling process allows the designer to identify topology and technology issues before the first circuit is designed. In this discussion, application circuits are considered to be everything in the powered device (PD) except the PoE front end and DC/DC converters.

PoE front-end losses

Figure 1 is a basic block diagram that shows the interconnection of the power-source equipment (PSE) through the

DC/DC converter and application circuits. Calculations yielding the results in Table 1 assume that the PSE output (44 V minimum) is connected through 20 Ω of cable into a PD. The PD front end has a transformer (1 Ω total, with

Table 1. Analysis of PoE distribution and front-end losses


PARAMETERS	MIN	TYP	MAX
PSE output (V)	44	—	57
Distribution resistance (Ω)	—	—	20
Source power (W)	—	—	15.4
PD average current (A)	—	—	0.35
Constants			
Diode forward drop (V)	—	0.8	—
Transformer resistance (Ω)	—	—	1
PD-controller switch resistance (Ω)	—	1	—
PD-controller bias power (A)	—	0.0012	—

LOSS SOURCE	LOSS (W)	AVAILABLE POWER (W)
		15.40**
Distribution	2.45	12.95
Input diode	0.56	12.39
Input transformer	0.06	12.33
PD-controller switch	0.12	12.21
PD-controller bias	0.04	12.16

**Total PoE power available

*An edited version of this article was published December 3, 2003, on PlanetAnalog.com, an *EE Times* online community.

Figure 1. Basic PoE block diagram

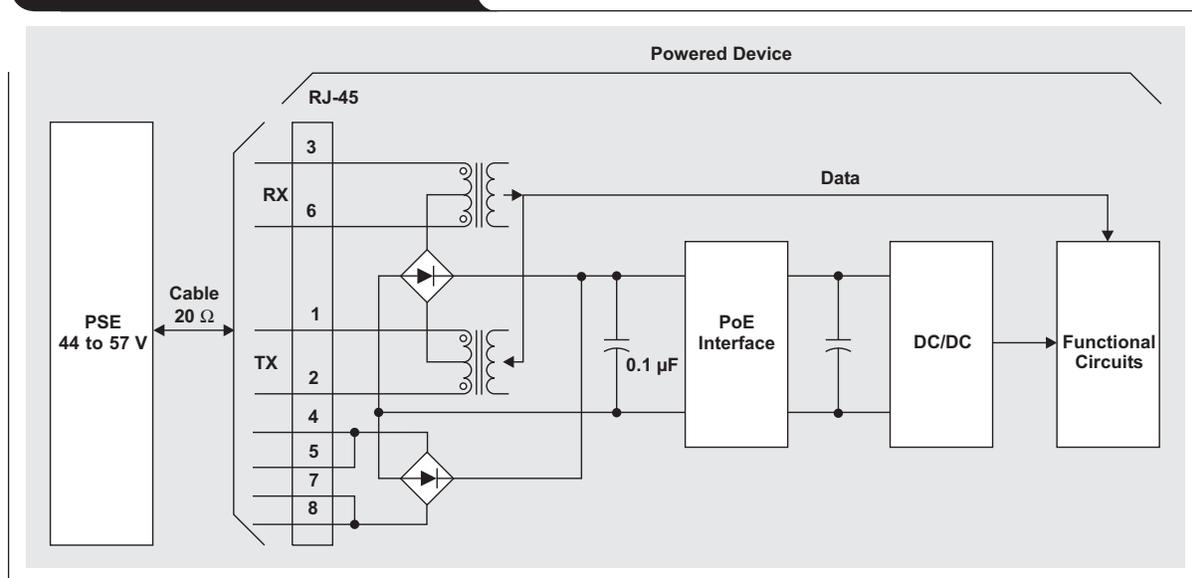

0.5 Ω each side to the center tap), a full-wave bridge, and a hot-swap controller (or PD controller) with a 1- Ω switch (FET) in series.

There is a maximum of 12.16 W available for PD functional circuits. The 802.3af standard defines the 2.45-W worst-case cable loss, and the input diode bridge dominates the additional front-end losses of 0.78 W.

Modeling of power-conversion stage

Simple modeling techniques allow the designer to understand the effects of different topology and technology choices before an actual design is done. Simple efficiency assumptions give quick, qualitative results to allow topology comparison and optimization. The end results will be only as good as the assumptions, so the designer should always allow some margin by specifying the available power below these results.

First, let's look at the baseline of a single-stage conversion to one output voltage. A single 3.3-V output converter at 90% efficiency will yield an available output power of $0.9 \times 12.16 = 10.9$ W. Although the 90% efficiency may be viewed as optimistic, it does provide a baseline for comparison to other topologies.

Next we will estimate the output power available from a more complex power supply. A simple modeling technique is used to study how the topology and technology for each regulator affect output power. Output voltages of +5 V at 0.2 A, 3.3 V at 2 A, 2.5 V at 0.25 A, and 1.8 V at 0.25 A are assumed. These add up to a reasonable 9.6 W.

Figure 2 shows two possible supply architectures and technology choices. Topology 1 represents adaptation of an

existing appliance design that had a 12-V wall adapter, which was replaced with a 48-V to 12-V front end.

Topology 2 attempts to maximize the available power.

To evaluate the model, start at the right-most regulators, calculating their loss and total input power, and then use these results to evaluate the next regulator to the left. For simplification, assume 90% efficiency for a switcher and no bias current for linear regulators. These calculations are summarized for the regulator types as follows.

Definitions

I_{OUT} = application load current

$P_{IN_Next_Stage}$ = power drawn by a downstream converter or linear regulator

Linear regulator stage

$$P_{OUT} = (V_{OUT} \times I_{OUT}) + P_{IN_Next_Stage}$$

$$P_{IN} = V_{IN} \times \frac{P_{OUT}}{V_{OUT}}$$

$$P_{Loss} = P_{IN} - P_{OUT}$$

Switching regulator stage

$$P_{OUT} = (V_{OUT} \times I_{OUT}) + P_{IN_Next_Stage}$$

$$P_{IN} = \frac{P_{OUT}}{\text{Efficiency}}$$

$$P_{Loss} = P_{IN} - P_{OUT}$$

Figure 2. Alternative supply topologies

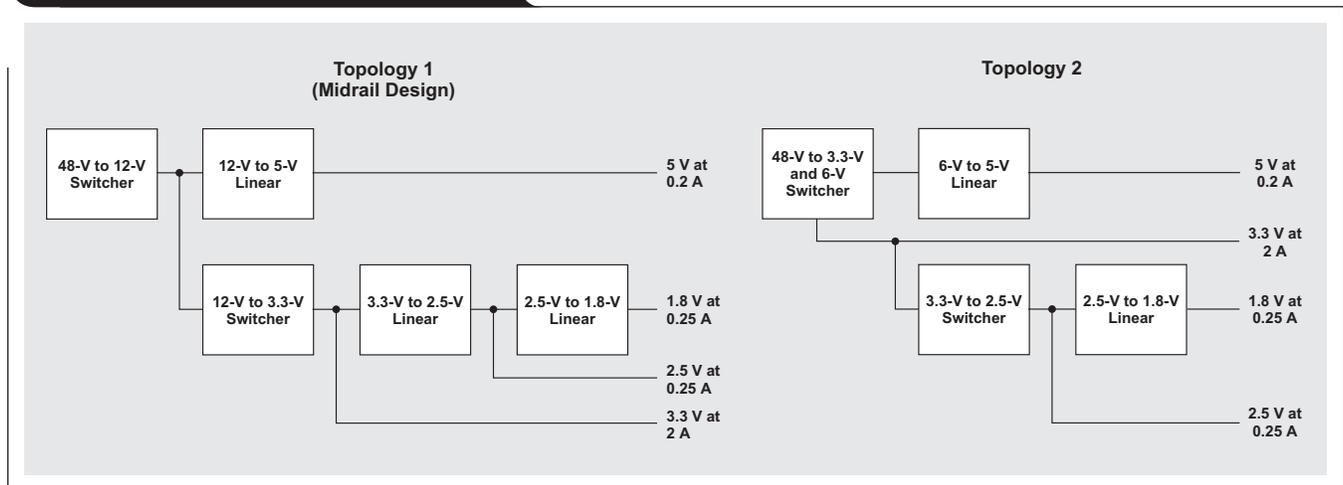


Table 2. Topology 1 model

MODEL COMPONENTS	OUTPUT VOLTAGE (V)	REGULATOR TYPE	INPUT VOLTAGE (V)	REGULATOR EFFICIENCY (%)	APPLICATION CURRENT (A)	ADDITIONAL OUTPUT LOAD (W)	COMPUTED INPUT POWER (W)	STAGE LOSS (W)
Chain 1	1.8	Linear	2.5	—	0.25	0.00	0.63	0.18
	2.5	Linear	3.3	90	0.25	0.63	1.65	0.40
	3.3	Switcher	12	90	1.83	1.65	8.54	0.85
Chain 2	5	Linear	12	—	0.2	0.00	2.40	1.40
First-stage input power	—	Switcher	48	90	0	10.94	12.16	1.22
Total loss								4.05
Apparent efficiency = 67%								
Available output power = 8.11 W								

Table 3. Topology 2 model

MODEL COMPONENTS	OUTPUT VOLTAGE (V)	REGULATOR TYPE	INPUT VOLTAGE (V)	REGULATOR EFFICIENCY (%)	APPLICATION CURRENT (A)	ADDITIONAL OUTPUT LOAD (W)	COMPUTED INPUT POWER (W)	STAGE LOSS (W)
Chain 1	1.8	Linear	2.5	—	0.25	0.00	0.63	0.18
	2.5	Switcher	3.3	90	0.25	0.63	1.39	0.14
	3.3	—	—	100	2.532	1.39	9.74	0.00
Chain 2	5	Linear	6	—	0.2	0.00	1.20	0.20
First-stage input power	—	Switcher	48	90	0	10.94	12.16	1.22
Total loss								1.73
Apparent efficiency = 86%								
Available output power = 10.43 W								

Using data in Table 2, let's go through the calculations for the Topology 1 model shown in Figure 2. Looking at the lower branch, Chain 1, data in Table 2, start with the 1.8-V regulator's input power and loss; notice that there is no next-stage power. The 2.5-V regulator is computed similarly, with the output power now comprised of the 0.25 A to the load multiplied by 2.5 V, plus the 1.8-V regulator's input power previously computed. The 3.3-V switching regulator's input power is the total output power divided by the efficiency of this stage (0.9%). The power loss of the 3.3-V regulator is still the input power minus the output power. The upper branch is computed in a like manner with the Chain 2 data. The 48-V to 12-V regulator's parameters are calculated like those of the 3.3-V regulator, where the total output power is the sum of the upper- and lower-branch input powers. To get a handle on the topology's performance, the individual losses are summed and the apparent efficiency is computed as

$$\text{Efficiency} = 1 - \frac{\text{Total_Losses}}{\text{Input_Power}}$$

The available output power in Table 2 is the input power minus all the computed individual losses.

Topology 1's input power exceeds the amount available. To provide a more interesting result, the 3.3-V load shown was adjusted until the input power was 12.16 W. Bold values in Table 2 reflect the reduction of the 3.3-V supply load from 2 A to 1.83 A.

Topology 2 is modeled with data in Table 3 much as Topology 1, with a small wrinkle. A dummy 3.3-V regulator is modeled with an efficiency of 1 for proper totaling of the power and loss.

The efficiency of 90% used for the 48-V to 3.3-V converter in Topology 2 is a fairly optimistic number for a practical, synchronous output-rectifier circuit.

Conclusion

After the 802.3af standard functions are considered, 12.16 W is the maximum power available for other electronics, including regulator losses.

The effects of topology and technology choices for PoE applications are quite startling. Topology 1 makes only 8.11 W available to the application's circuits, while Topology 2 makes 10.43 W available. This is an increase of 28%. The baseline single-output converter provided 10.9 W, so all the processing represented by the additional three outputs in Topology 2 cost only 0.47 W! Using a diode output converter (85% efficiency) instead of a synchronous rectifier for the 3.3-V converter drops the available power by 0.61 W.

This modeling technique allows the designer to calculate available output power rapidly based on topology and technology choices. The designer can use this information to trade off available power, complexity, and cost.

Related Web site

analog.ti.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		ti-china@ti.com

C011905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLY085