
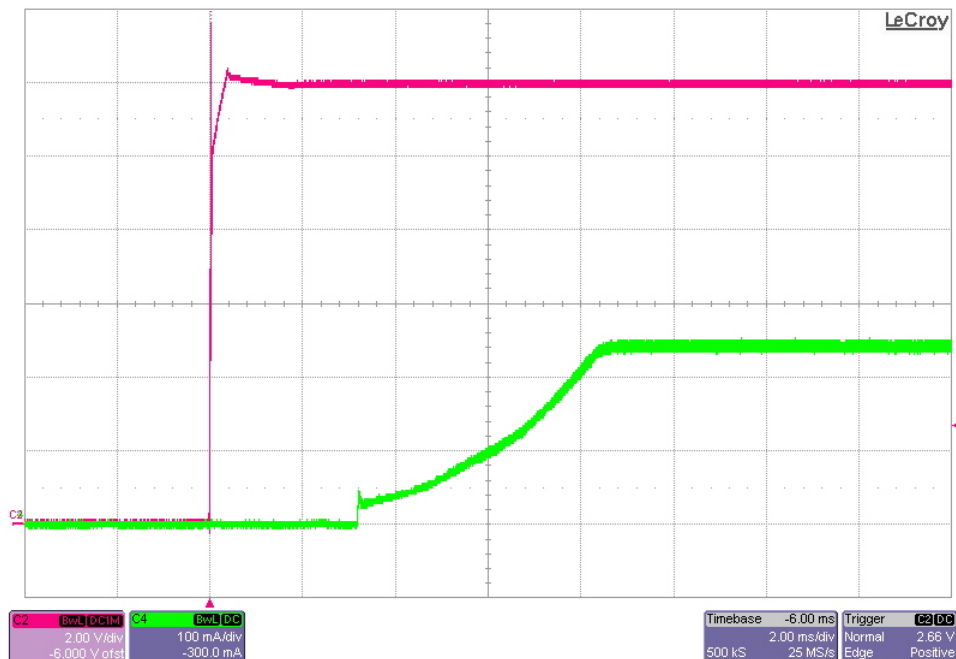

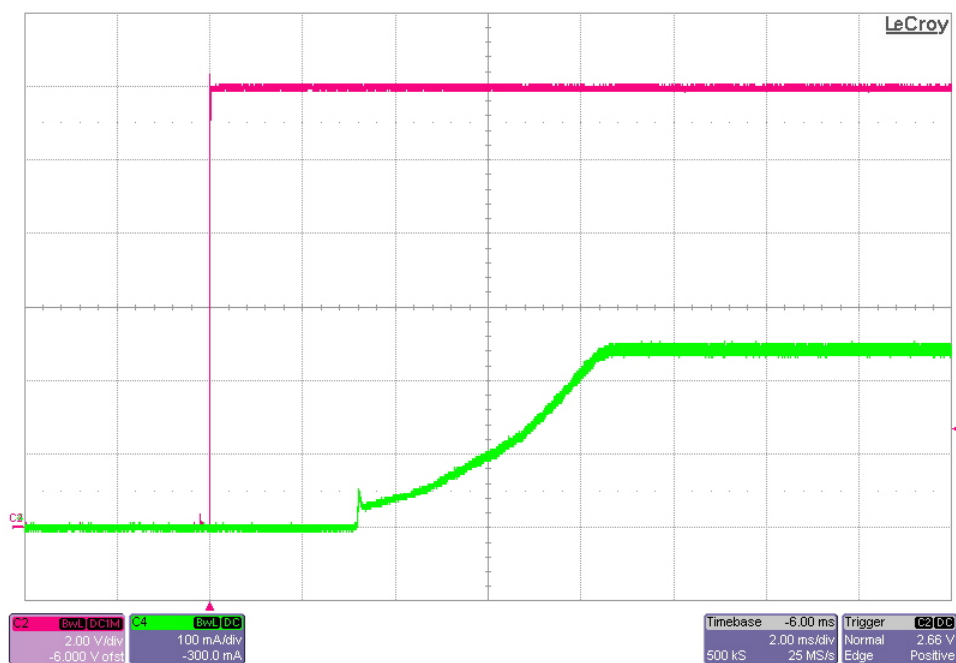
## 1 Startup

The LED current startup waveform (GREEN) is shown after the input voltage (RED) is applied. The CTRL signal was connected to Vin. Vin = 12V and I\_LED = 0.24A. (2V/DIV, 100mA/DIV, 2mS/DIV)




The LED current startup waveform (GREEN) is shown after the CTRL voltage (RED) is applied. The input voltage (Vin = 12V) was applied prior to enabling. I\_LED = 0.24A. (2V/DIV, 100mA/DIV, 2mS/DIV)



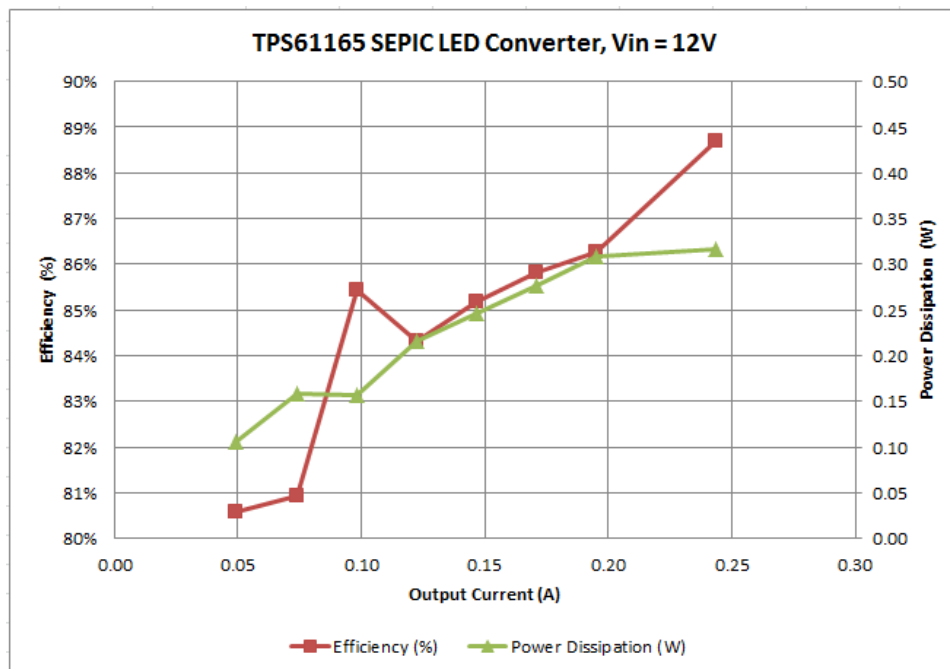
## 2 Efficiency

The converter's efficiency is shown in the figure below. An external 0-5V, 50KHz PWM input signal was connected to the CTRL input and duty cycle modulated between 20% - 80% to adjust the LED current.




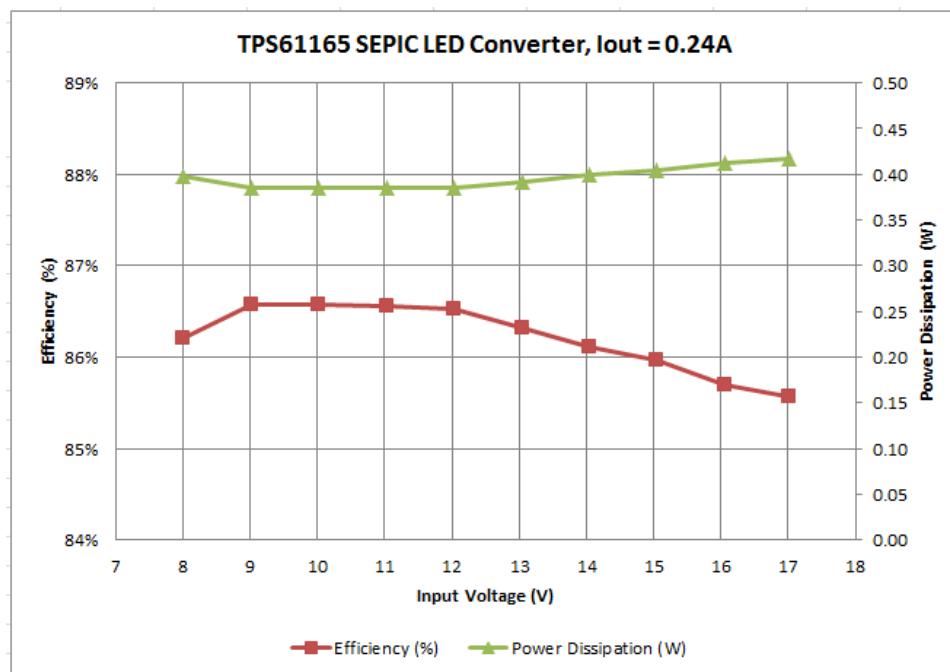The converter's efficiency is shown in the figure below. The CTRL input was connected to VIN for max LED current.



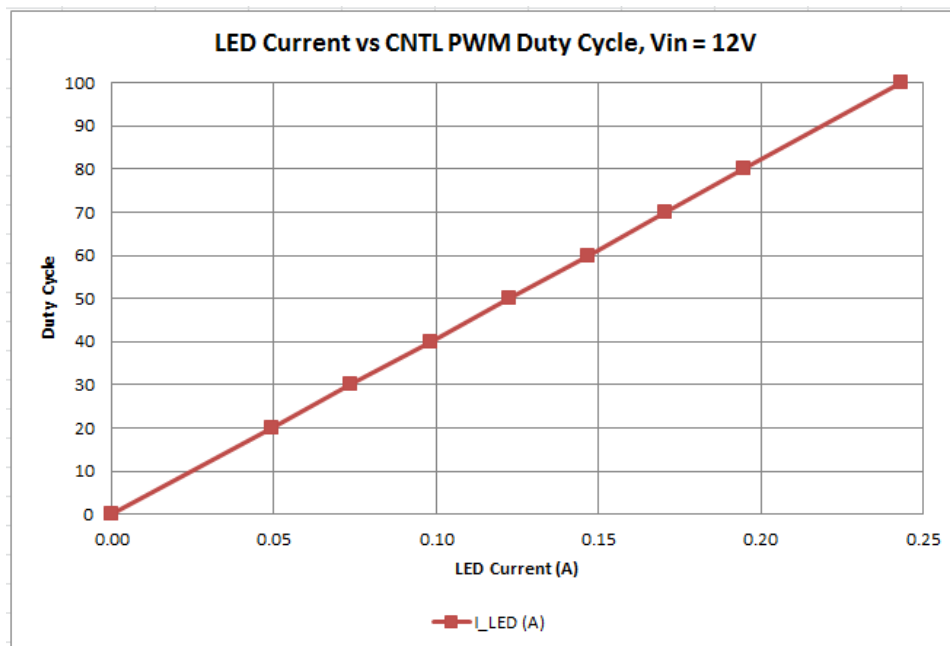
### 3 LED Current Linearity versus CTRL input signal Duty Cycle

An external 0-5V, 50KHz PWM input was duty cycle modulated between 20% - 80% to adjust the LED current.



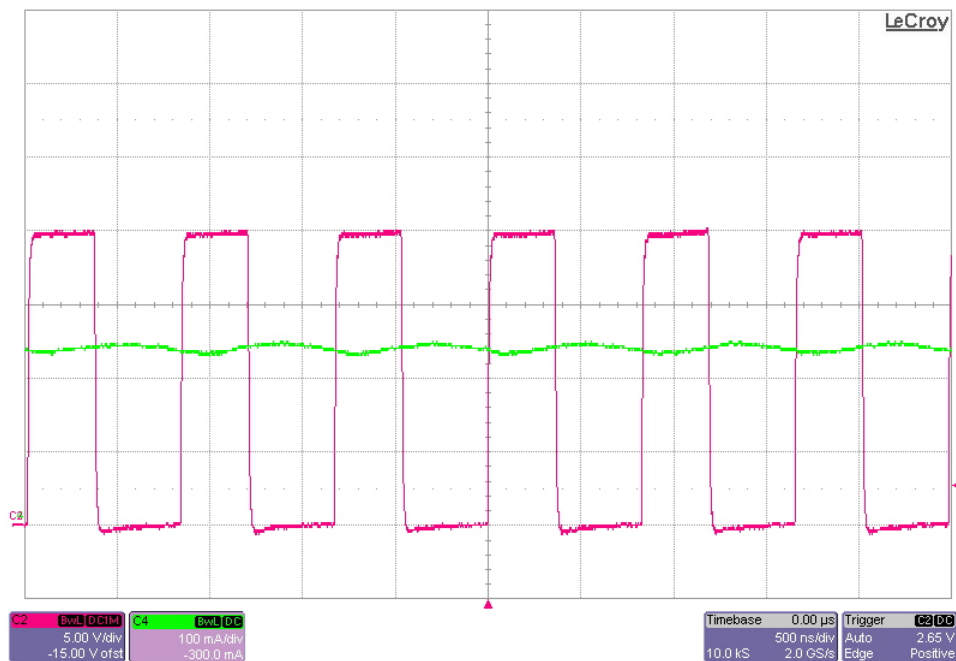
## 4 Switch Node Waveforms


The waveform below shows the switch node voltage at TP1 and the LED current. The input voltage is 8.7V and the LED output is 0.24A. (5V/DIV, 100mA/DIV, 500nS/DIV)



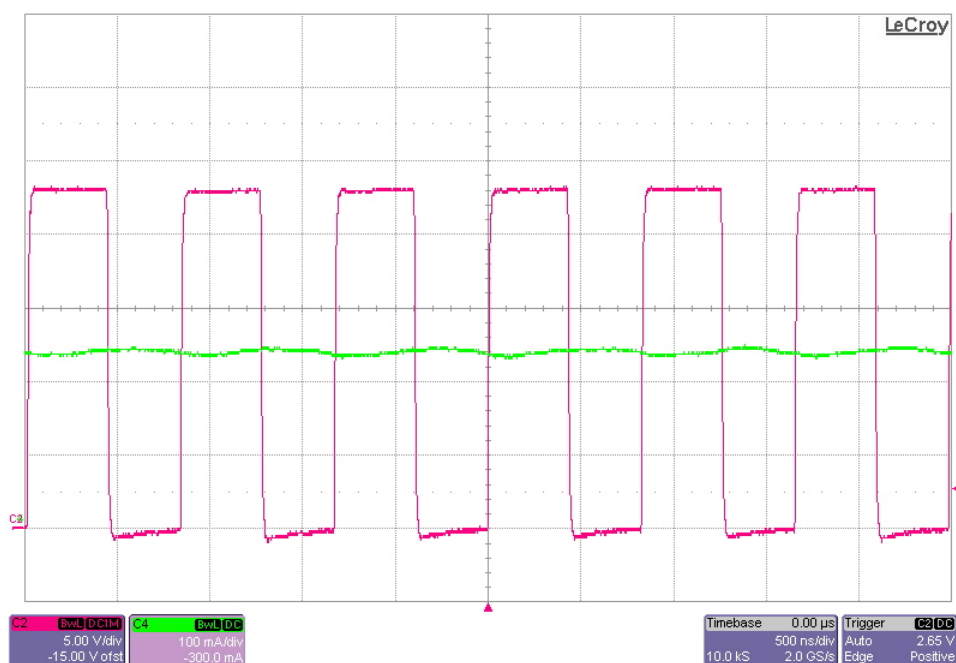
The waveform below shows the switch node voltage at TP1 and the LED current. The input voltage is 12V and the LED output is 0.24A. (5V/DIV, 100mA/DIV, 500nS/DIV)



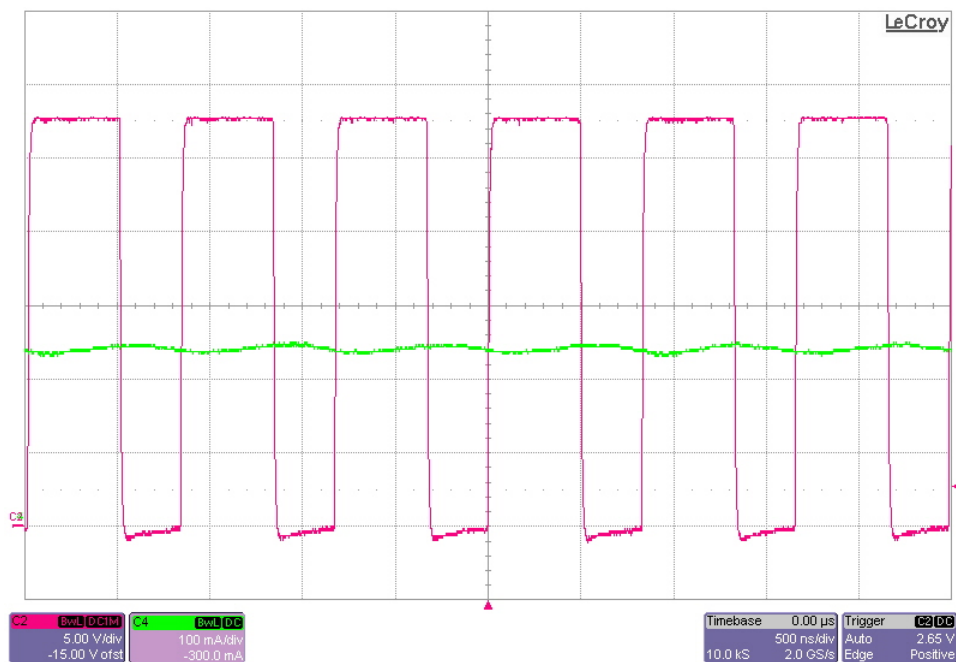
The waveform below shows the switch node voltage at TP1 and the LED current. The input voltage is 16.5V and the LED output is 0.24A. (5V/DIV, 100mA/DIV, 500nS/DIV)



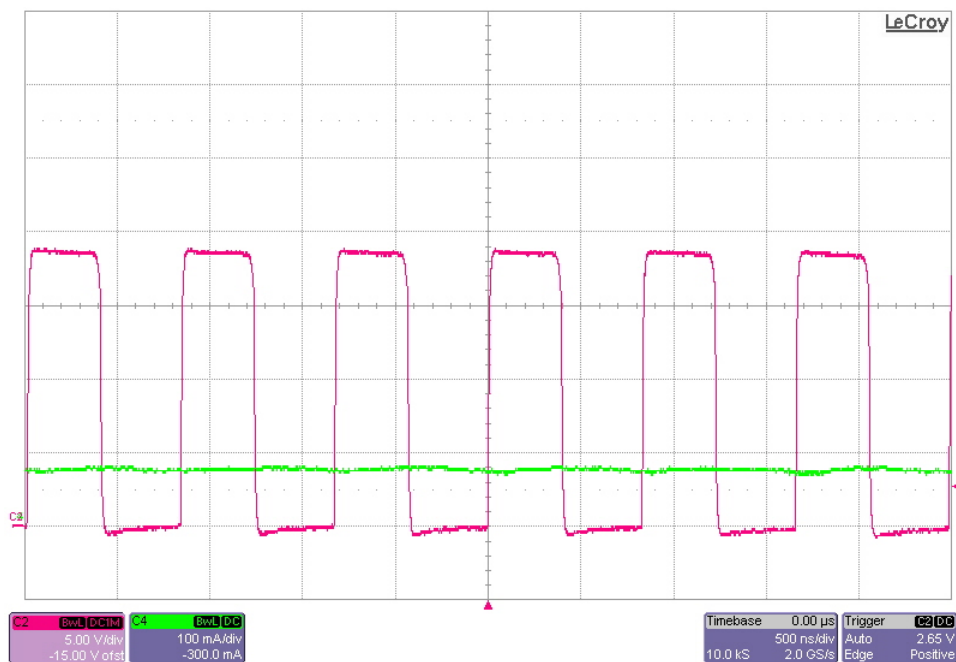The waveform below shows the switch node voltage at TP1 and the LED current. An external 0-5V, 50KHz PWM input signal was connected to the CTRL input with the duty cycle set to 32% to adjust the LED current to 0.079A. The input voltage was set to 8.7V. The converter is in DCM operation at this LED current and below. (5V/DIV, 100mA/DIV, 500nS/DIV)




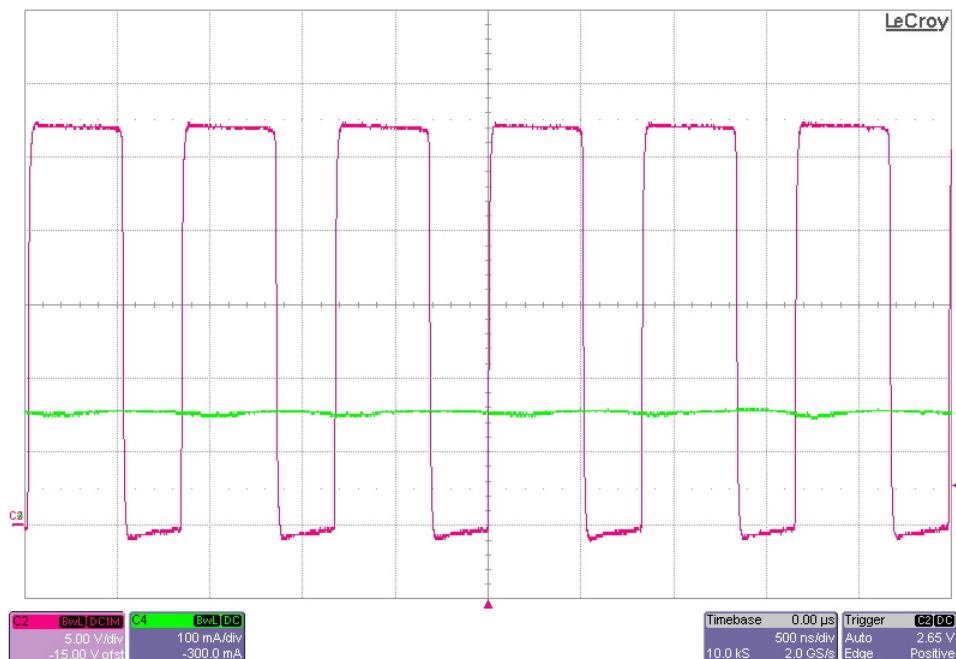The waveform below shows the switch node voltage at TP1 and the LED current. An external 0-5V, 50KHz PWM input signal was connected to the CTRL input with the duty cycle set to 64% to adjust the LED current to 0.156A. The input voltage was set to 16.5V. The converter is in DCM operation at this LED current and below. (5V/DIV, 100mA/DIV, 500nS/DIV)


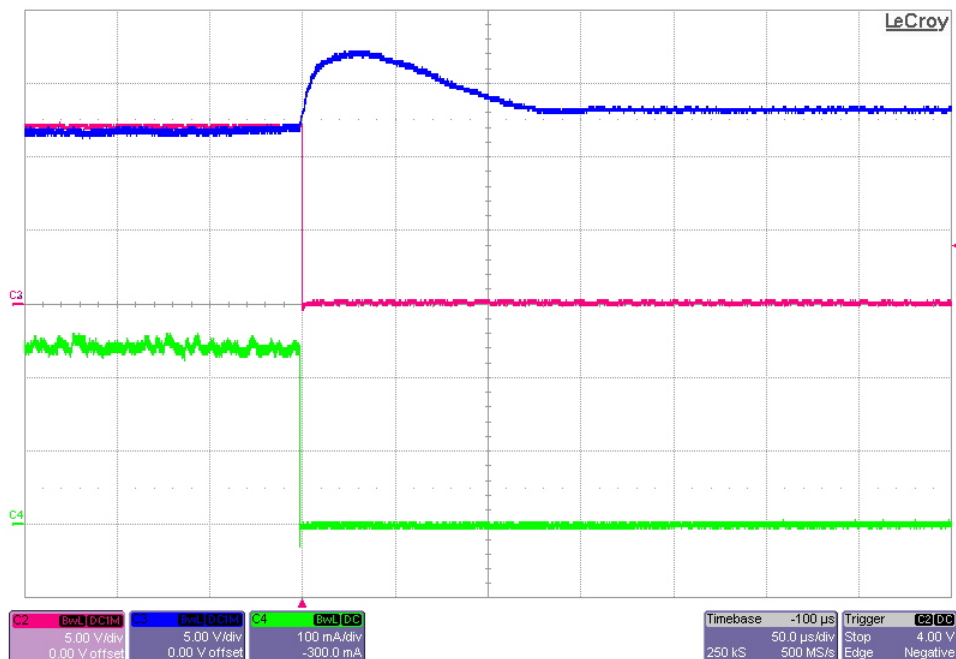
## 5 Open LED Test

The waveform below shows the LED current (GREEN), Output Voltage (BLUE), and the /OPENLED signal after the LED is removed. The input voltage is 12V and the LED output is 0.24A. (5V/DIV, 100mA/DIV, 50uS/DIV)




## 6 Control Loop Gain / Stability

The plot below shows the converter's gain and phase margin when the LED current is 0.24A.

Vin = 8.7V  
Vin = 16.5V

Band Width = 8.59KHz  
Band Width = 12.8KHz

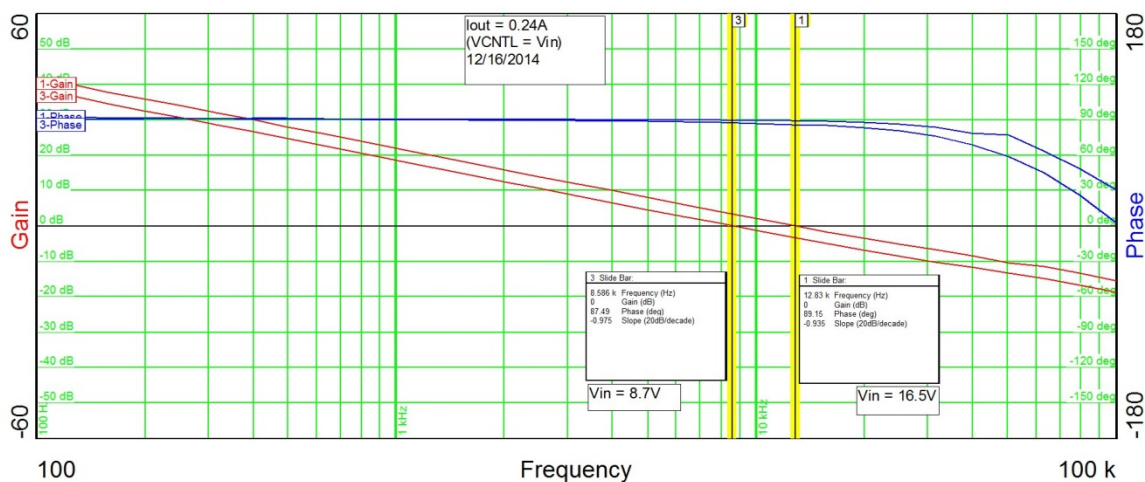Phase Margin = 87 degrees  
Phase Margin = 89 degrees




The plot below shows the converter's gain and phase margin for Vin = 12V. An external 0-5V, 50KHz PWM input signal was connected to the CTRL input with the duty cycle adjusted to vary the LED current.

I LED = 0.048A  
I LED = 0.120A  
I LED = 0.192A

Band Width = 3.52KHz  
Band Width = 6.41KHz  
Band Width = 9.44KHz

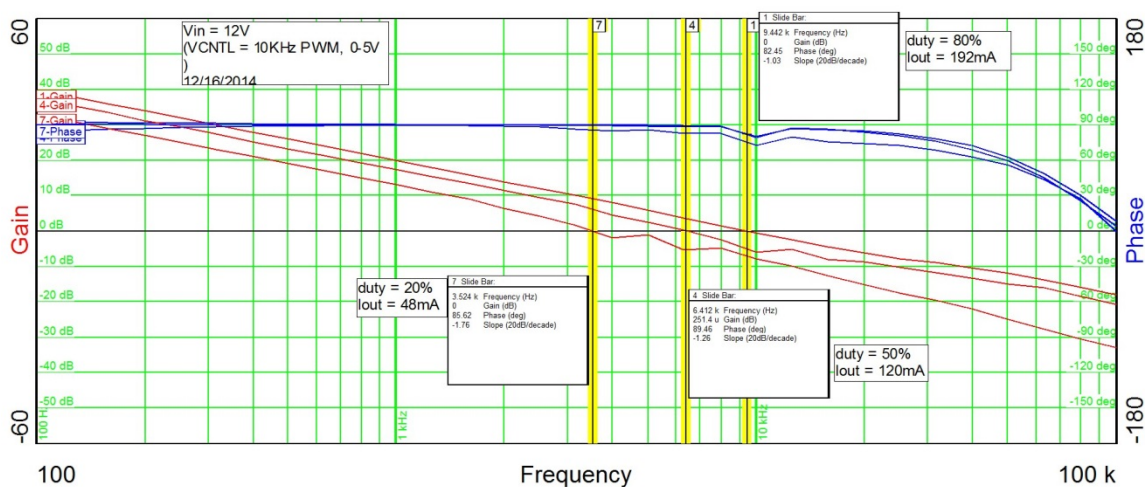
Phase Margin = 86 degrees  
Phase Margin = 89 degrees  
Phase Margin = 82 degrees





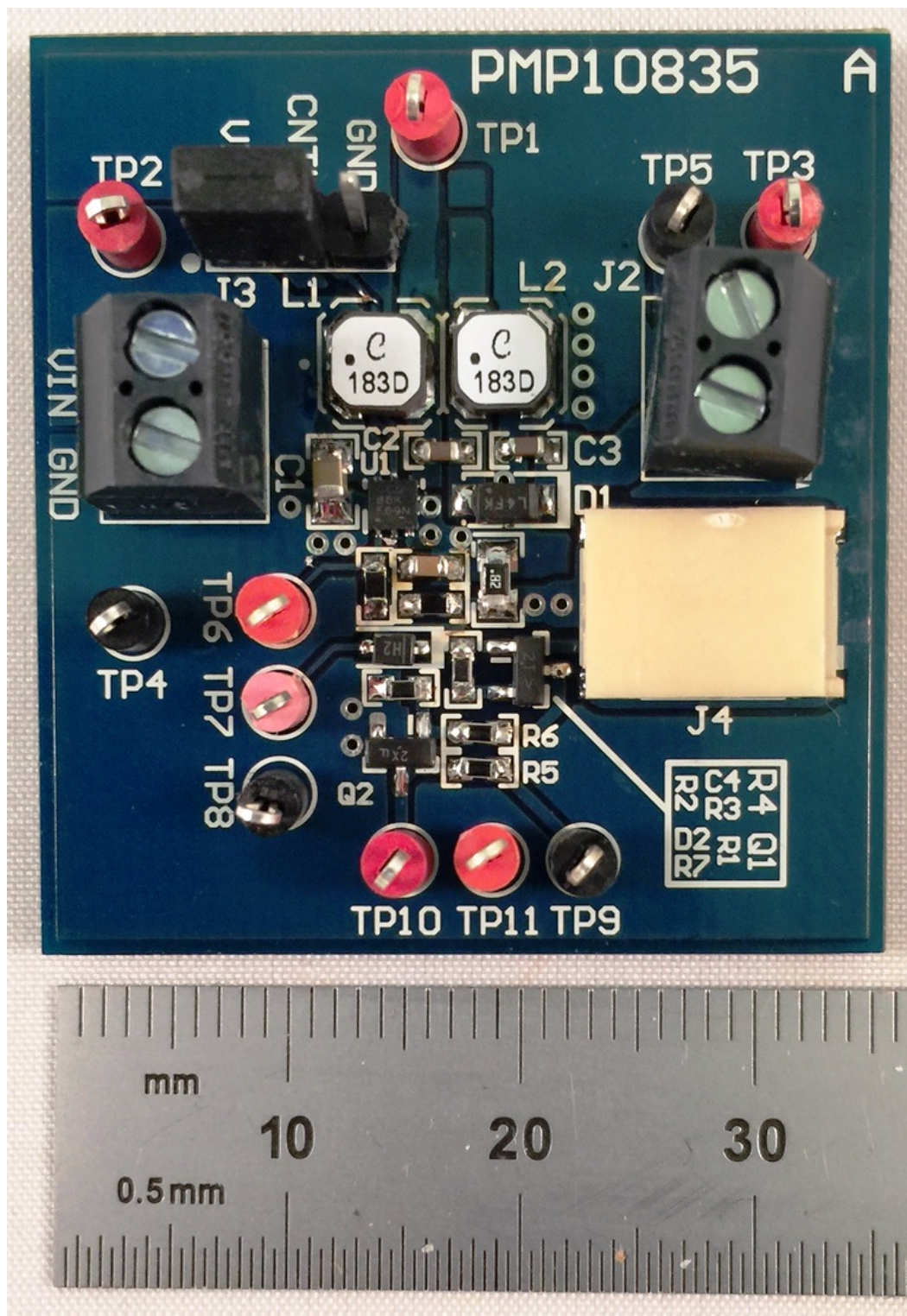
## 7 Photo

The photo below shows the PMP10835 REVB assy built on the REVA PWB.


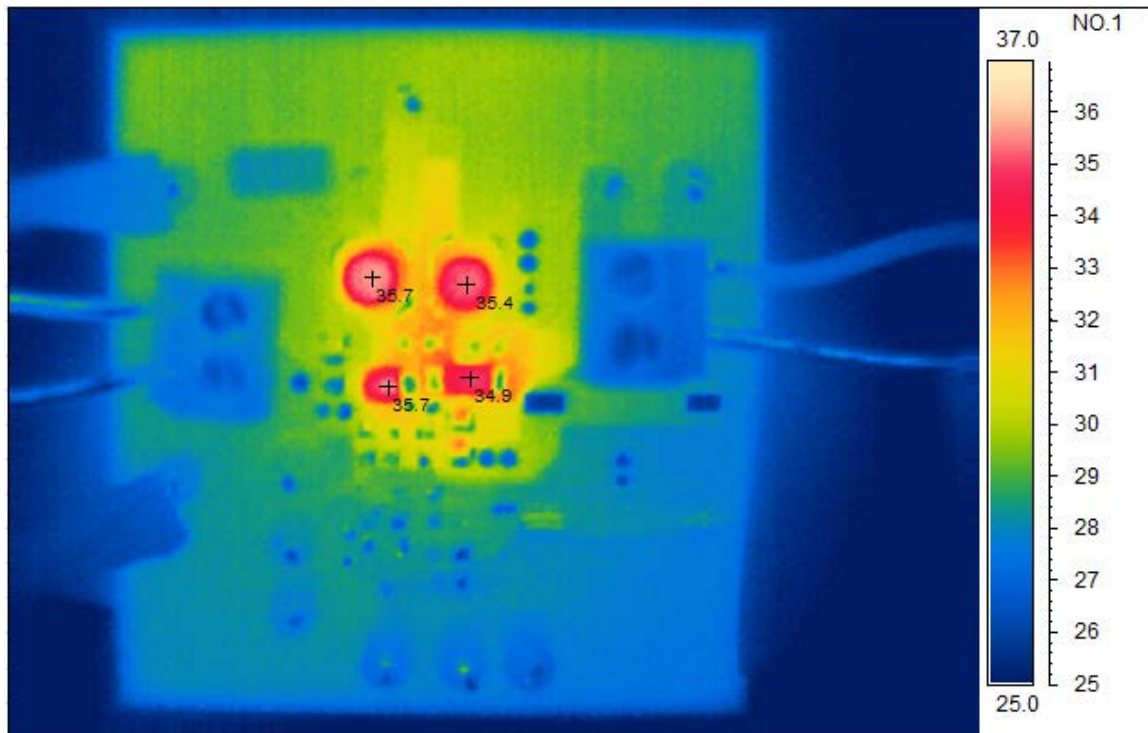
## 8 Thermal Image

The thermal image below shows operation at 12V input and an LED current of 0.24A, with no airflow.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated