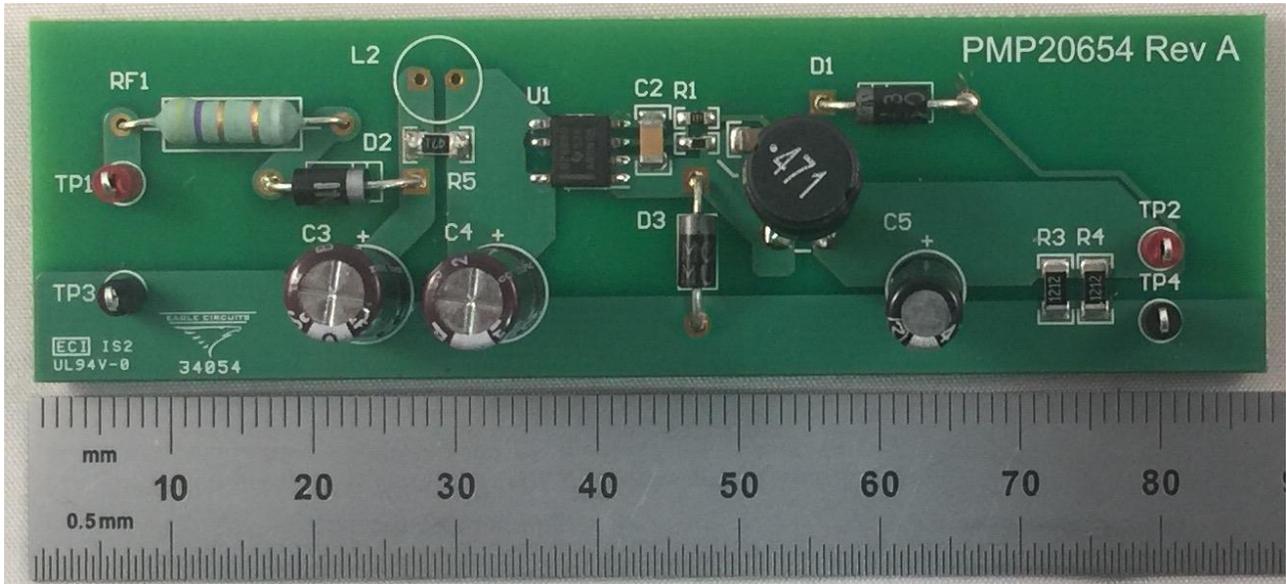



## 1 Photo

The photographs below show the PMP20654 Rev A assembly. This circuit was built on a PMP20654 Rev A PCB.


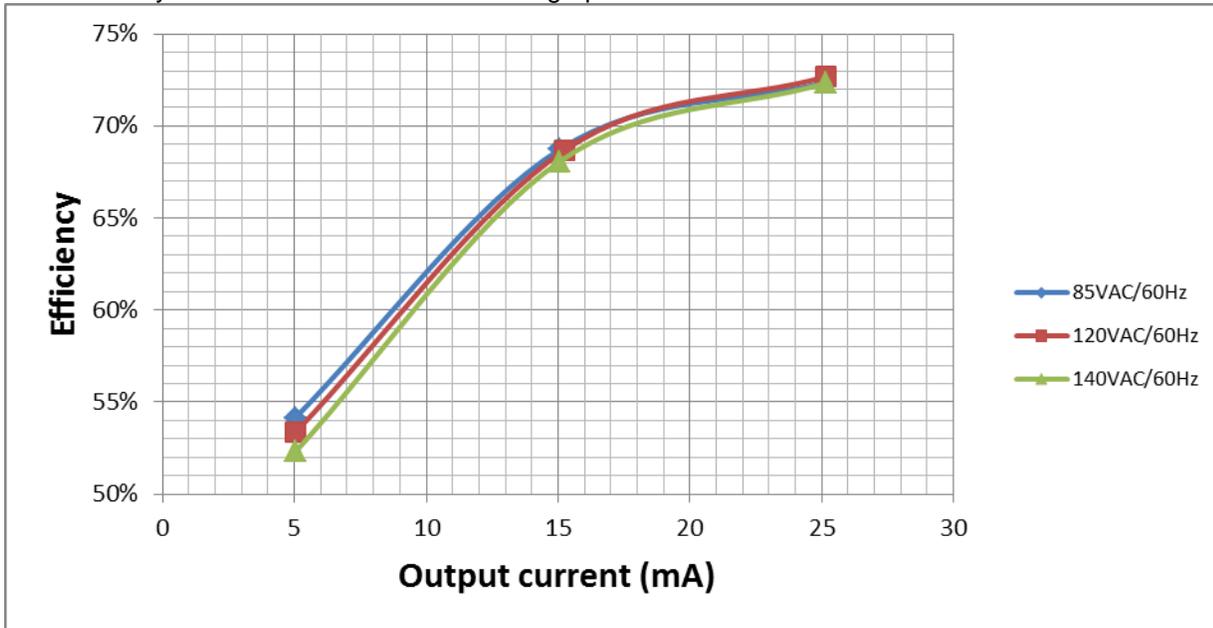
## 2 Converter Efficiency

The efficiency data is shown in the tables and graph below. R5=4.7Ω in this test.




Vin(V)	Iin(mA)	Pin(W)	Vout(V)	Iout(mA)	Pout(W)	Losses(W)	Efficiency (%)
85.05	12.462	0.4001	11.5	25.18	0.28957	0.11053	72.37%
85.06	8.632	0.2541	11.59	15.07	0.174661	0.0794387	68.74%
85.06	4.417	0.10942	11.78	5.03	0.059253	0.0501666	54.15%
85.07	1.921	0.03768	12.25	0	0	0.03768	0.00%
120.06	10.054	0.3976	11.49	25.15	0.288974	0.1086265	72.68%
120.06	7.144	0.2572	11.58	15.26	0.176711	0.0804892	68.71%
120.07	3.7	0.11154	11.77	5.06	0.059556	0.0519838	53.39%
120.07	1.663	0.04049	12.27	0	0	0.04049	0.00%
140.09	9.236	0.399	11.48	25.14	0.288607	0.1103928	72.33%
140.09	6.506	0.2562	11.58	15.06	0.174395	0.0818052	68.07%
140.09	3.463	0.11341	11.77	5.04	0.059321	0.0540892	52.31%
140.09	1.564	0.004224	12.29	0	0	0.004224	0.00%

### 3 Thermal Images

The thermal images below show a top view and bottom view of the board under 120V<sub>AC</sub>/60Hz input condition. The ambient temperature was 20°C with no forced air flow. The output was at full load: 12V/25mA. R5=4.7Ω in this test.

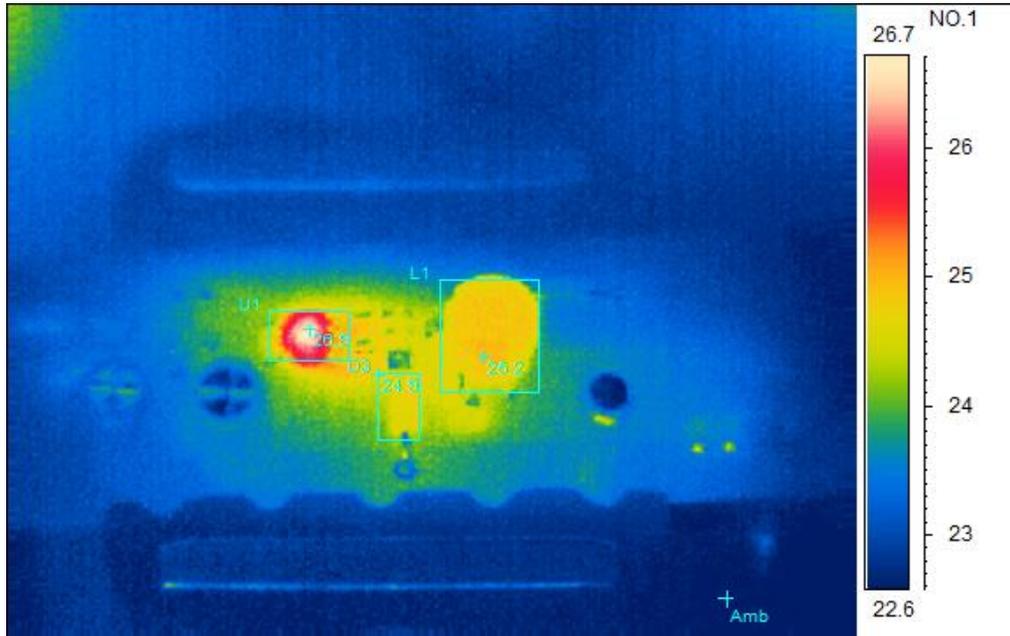**V<sub>in</sub>=120V<sub>AC</sub>/60Hz**




Spot analysis	Value
Amb Temperature	22.4°C
Area analysis	Value
U1Max	26.9°C
D3Max	24.9°C
L1Max	25.2°C


## 4 Startup Waveforms

The output voltages at startup are shown in the images below.  $R_5=4.7\Omega$  in this test.

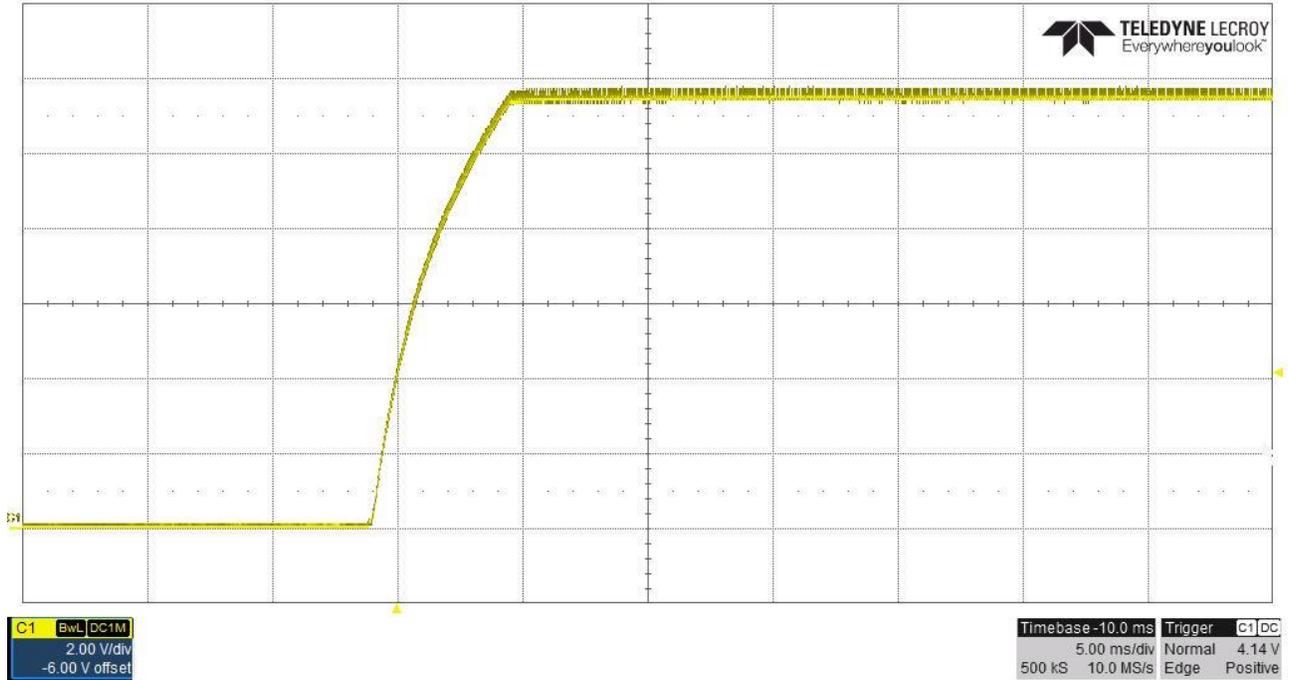
### 4.1 Start Up @ 85V<sub>AC</sub>: 12V/25mA.



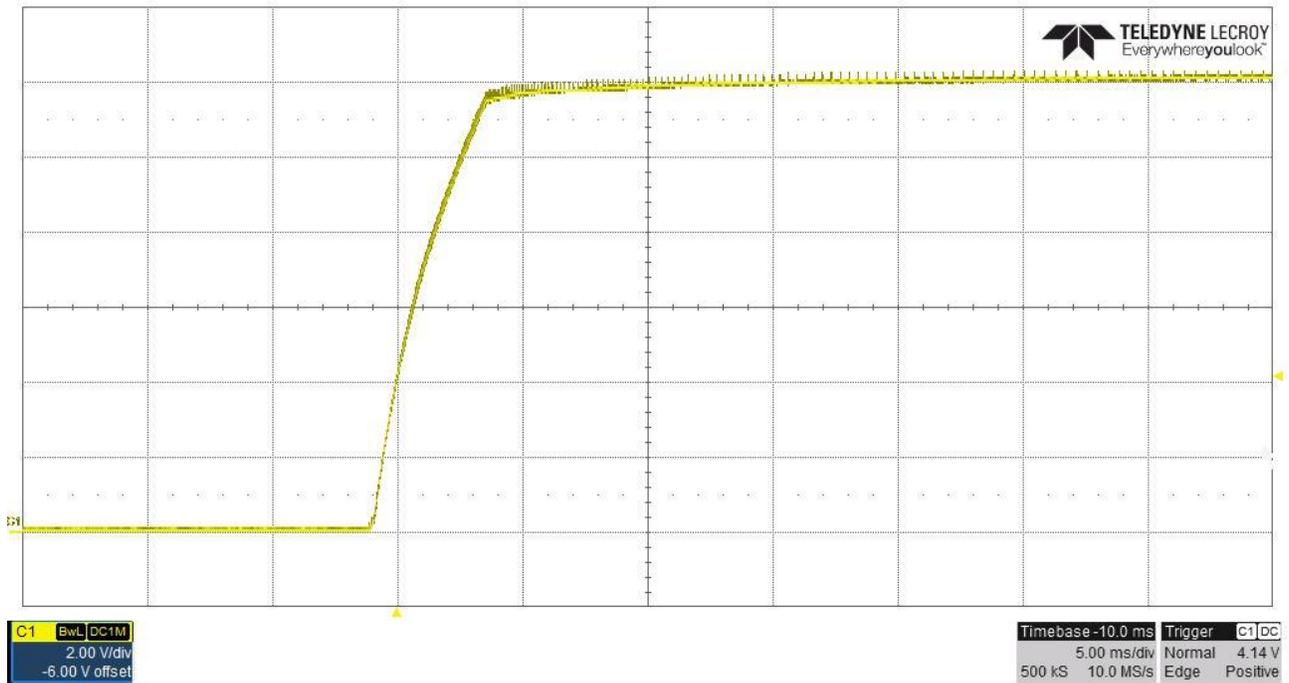
### 4.2 Start Up @ 85V<sub>AC</sub>: no load.



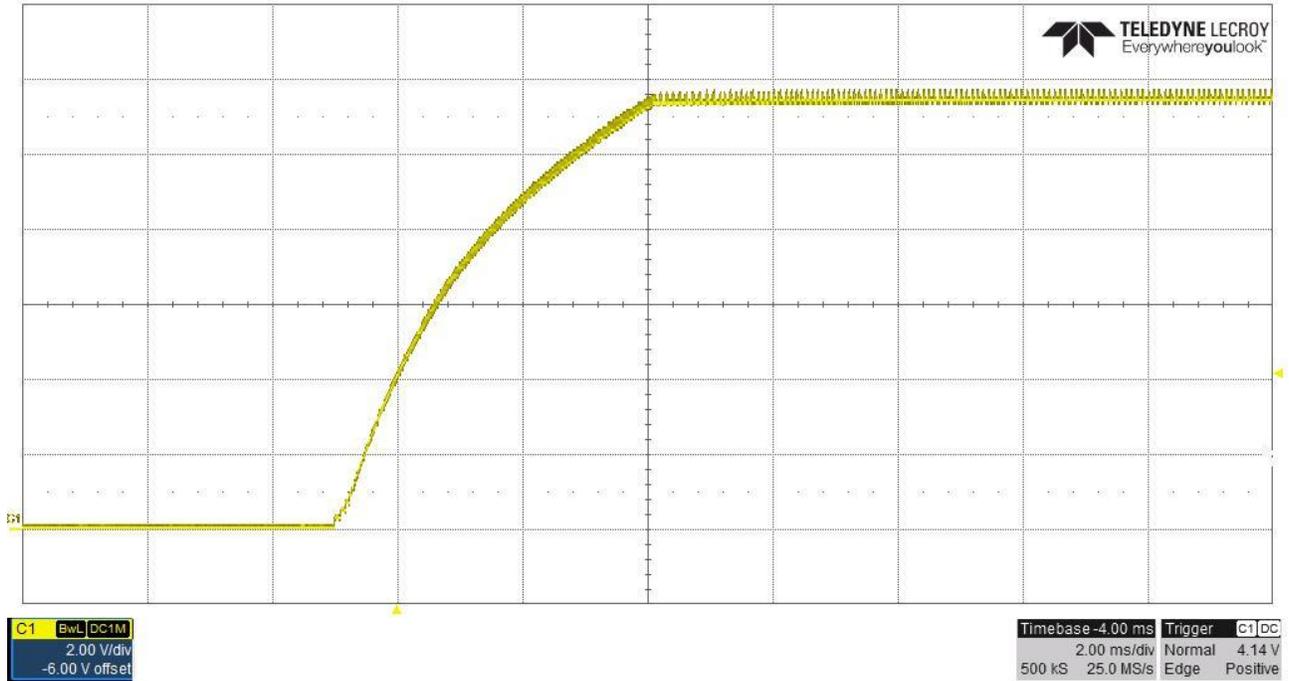
### 4.3 Start Up @ 120V<sub>AC</sub>: 12V/25mA.



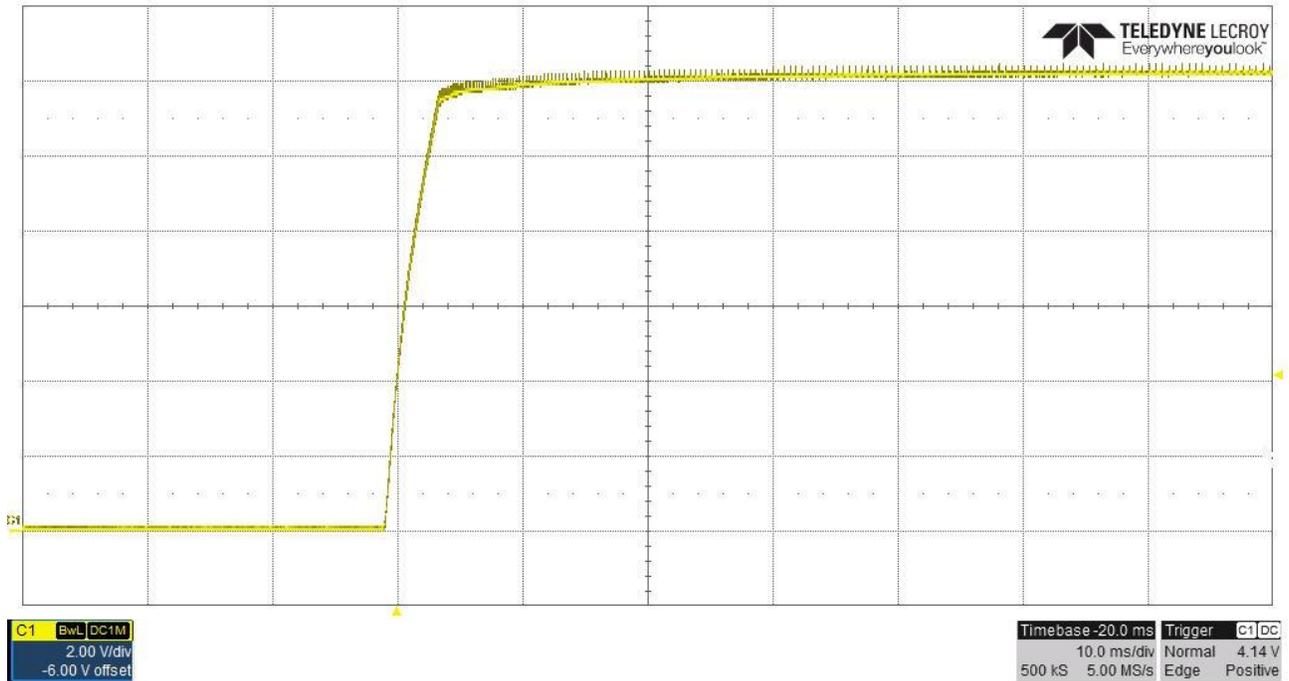
### 4.4 Start Up @ 120V<sub>AC</sub>: no load.


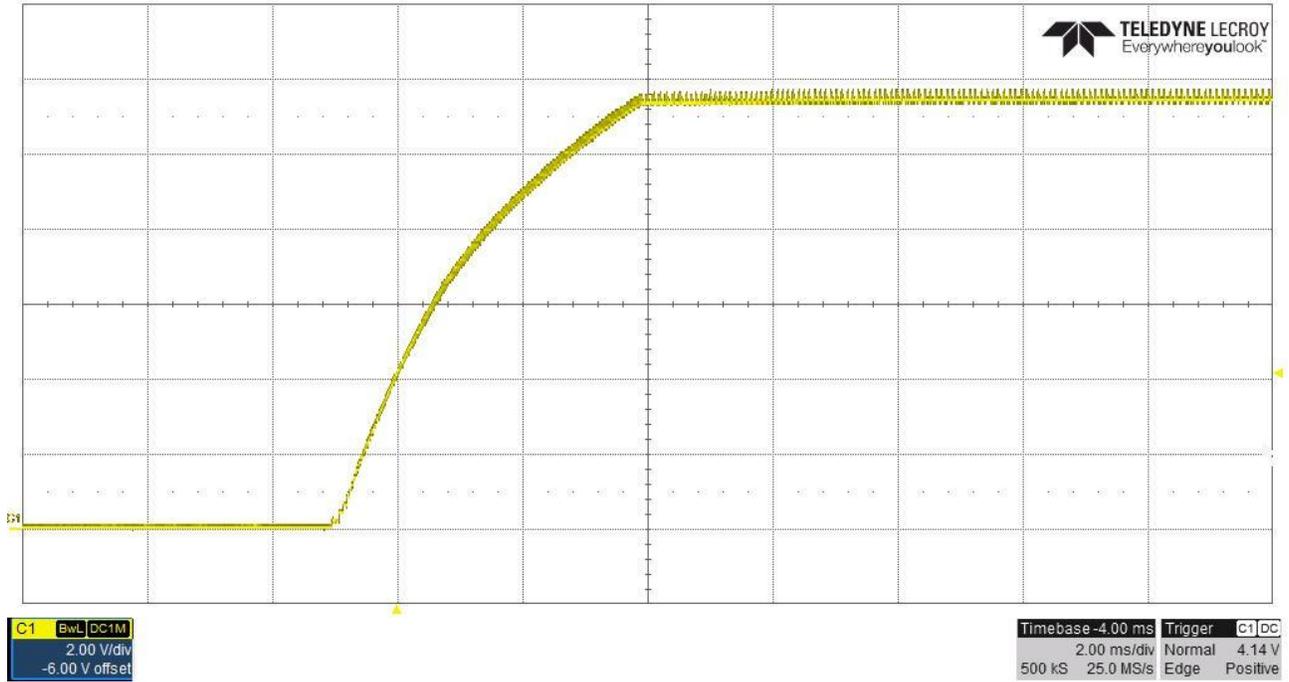
### 4.5 Start Up @ 140V<sub>AC</sub>: 12V/25mA.



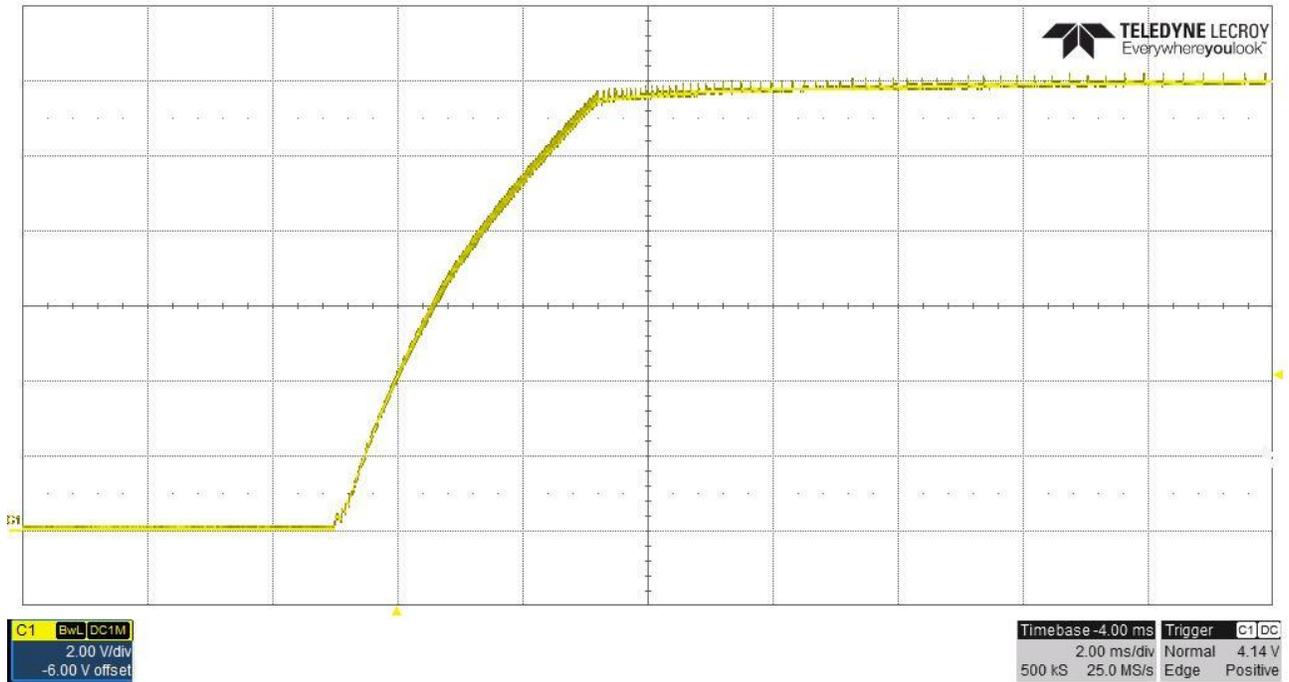
### 4.6 Start Up @ 140V<sub>AC</sub>: no load.



## 5 Turn off

The output voltage at turn off transient is shown in the image below at full load (12V/25mA). R5=4.7Ω in this test.

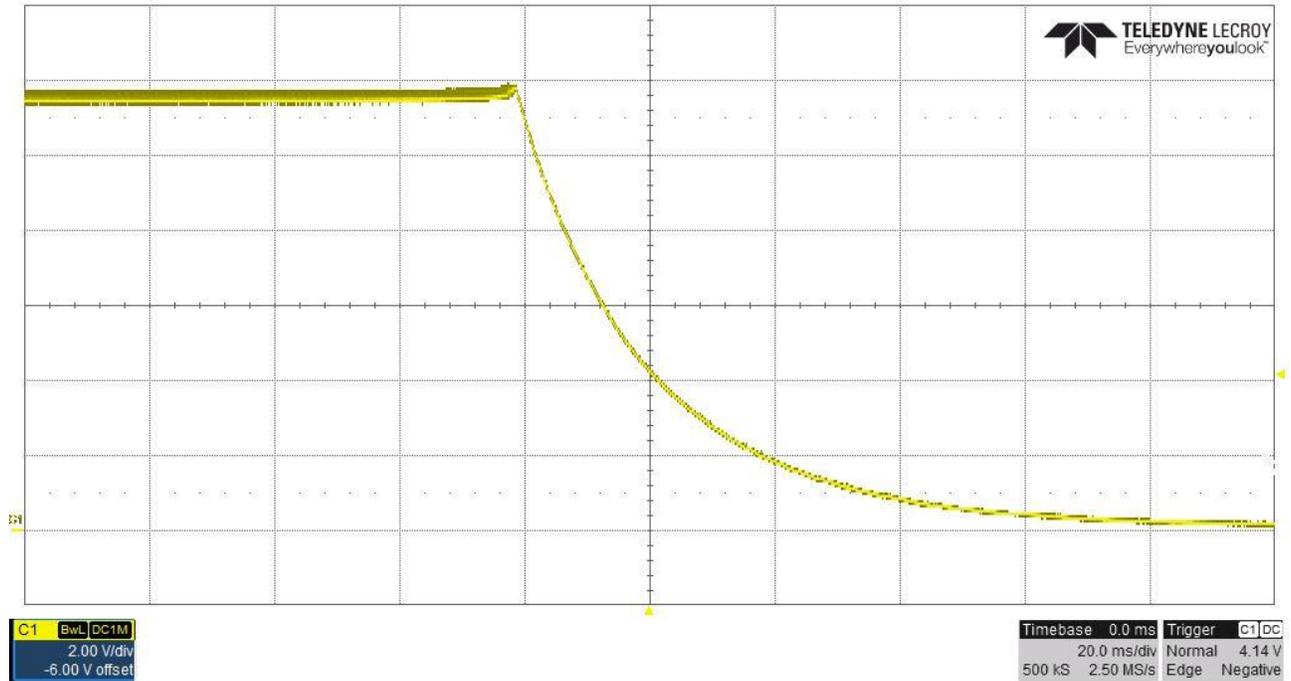
### 5.1 Turn off @ 120V<sub>AC</sub>: 12V/25mA.




## 6 Output Ripple Voltages

The output ripple voltages are shown in the plots below.  $R5=4.7\Omega$  in this test.


### 6.1 85V<sub>AC</sub>: 12V/25mA:

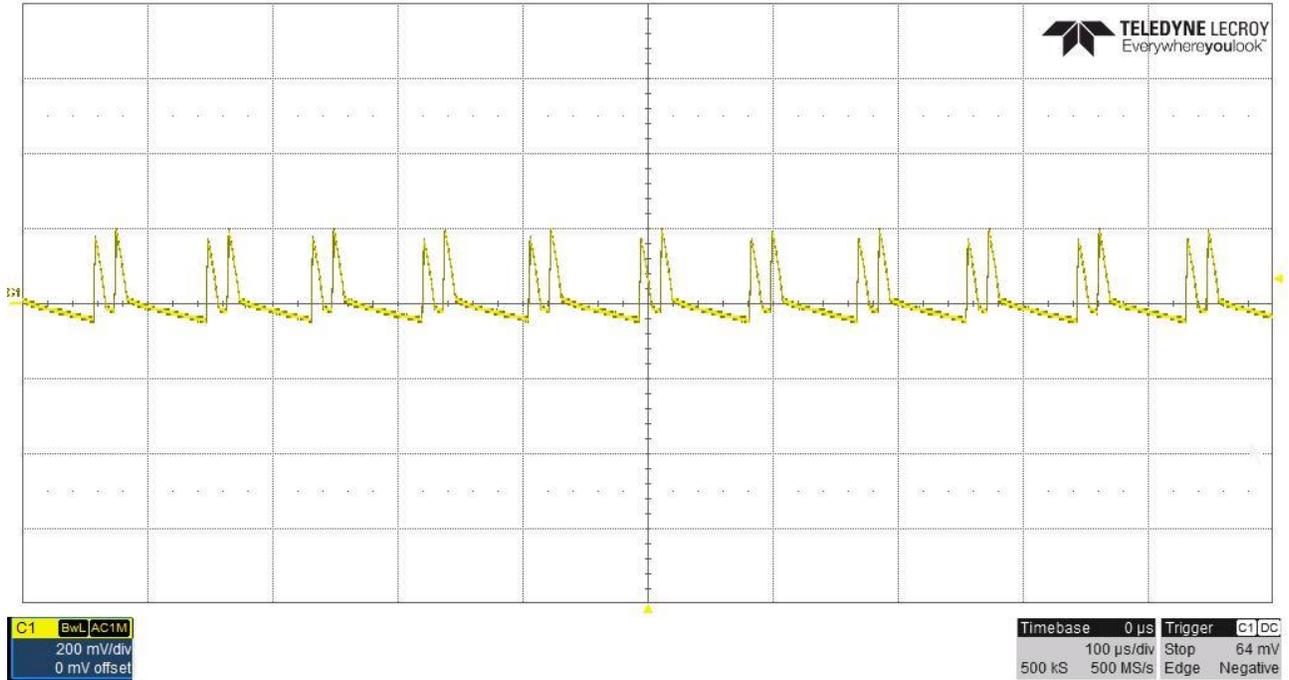


### 6.2 85V<sub>AC</sub>: no load:

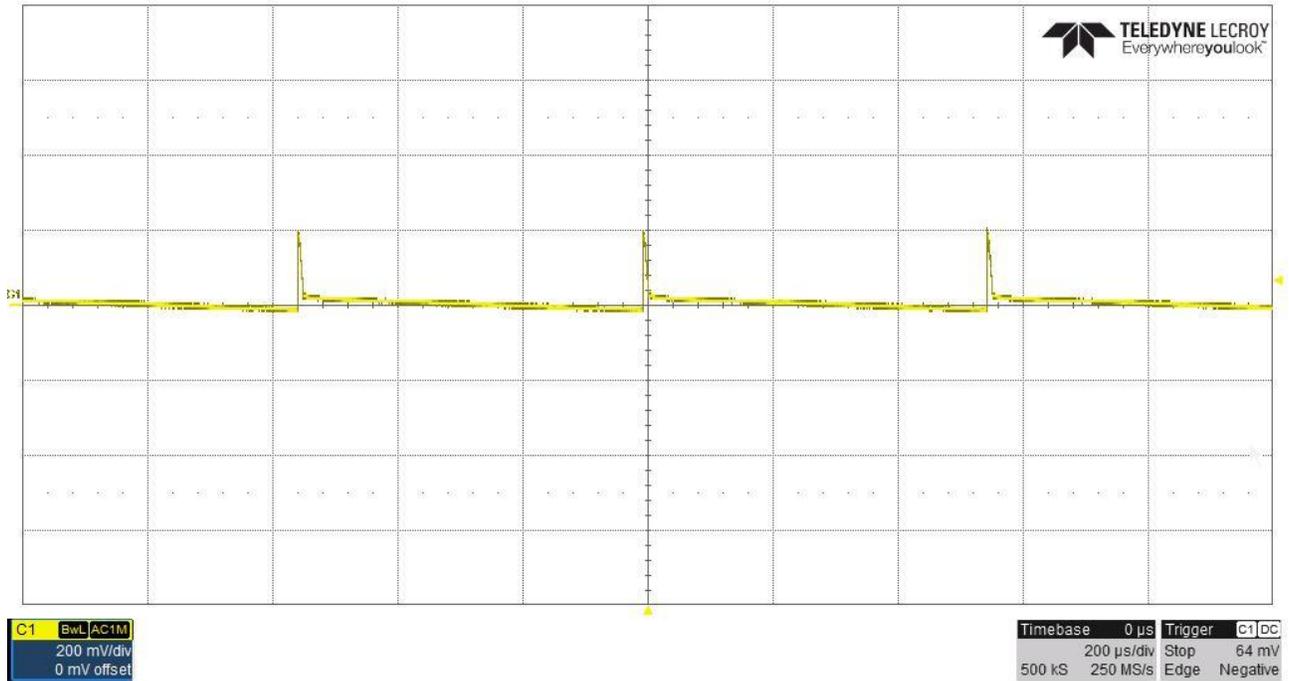


### 6.3 120V<sub>AC</sub>: 12V/25mA:

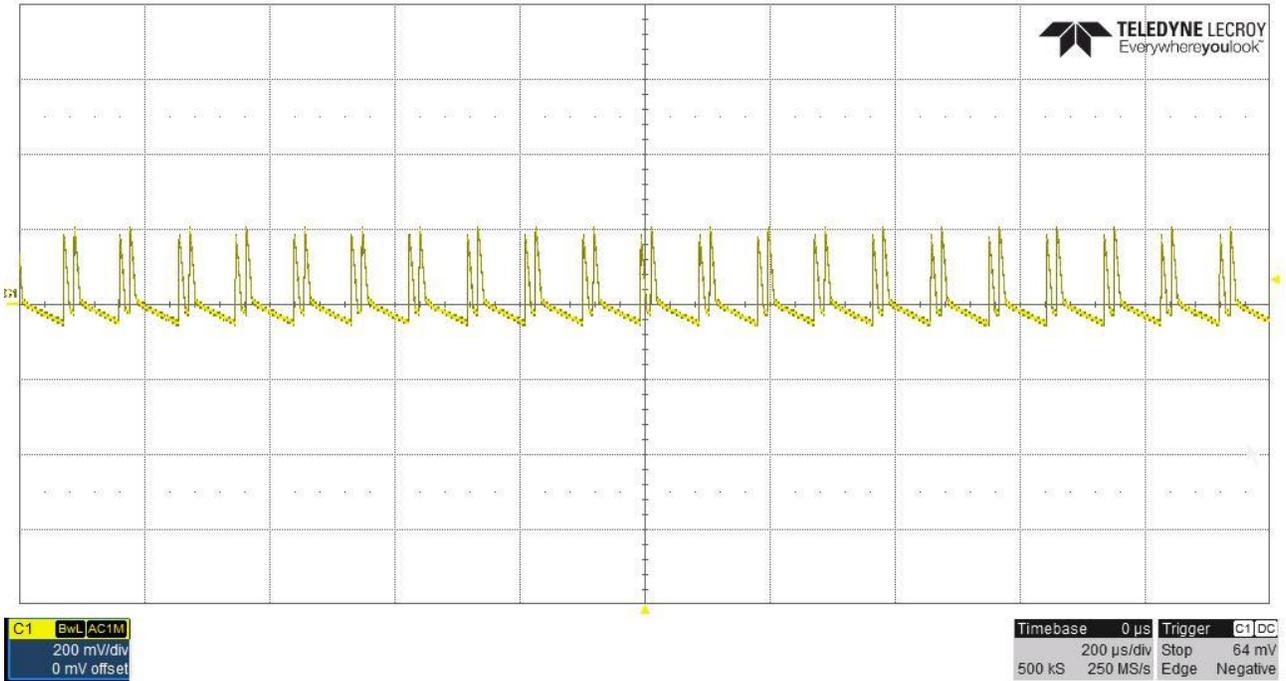


### 6.4 120V<sub>AC</sub>: no load:

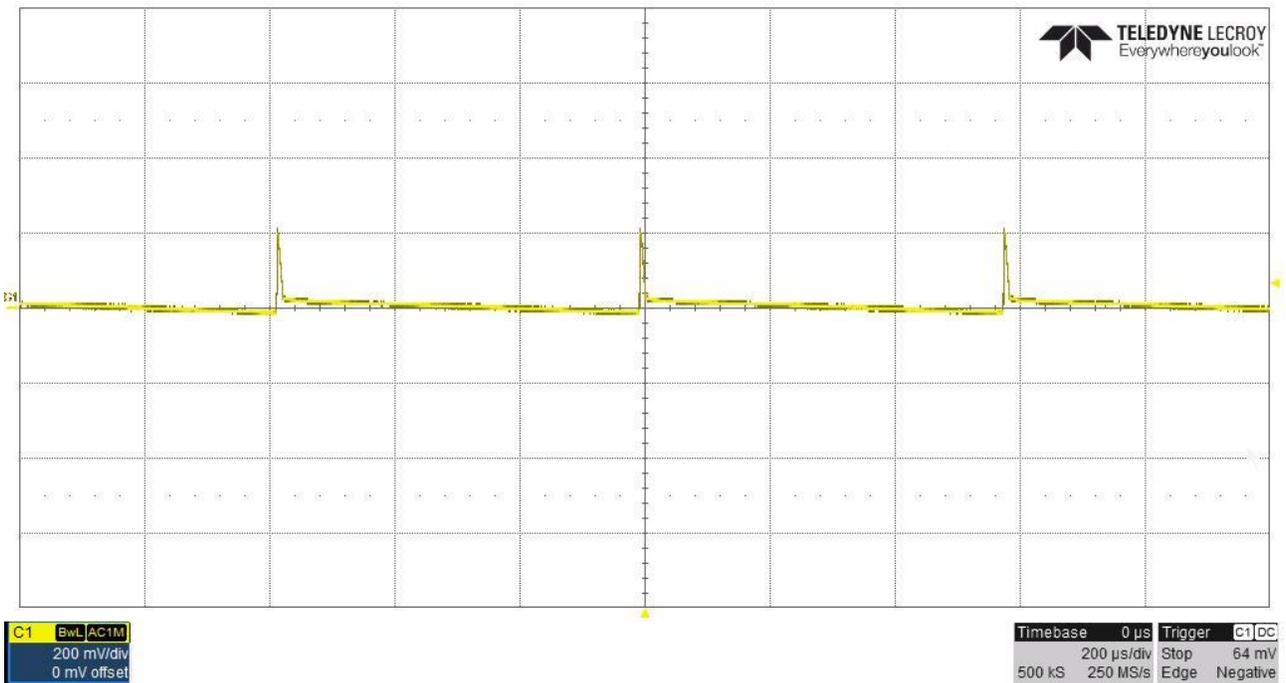

## 6.5 140V<sub>AC</sub>: 12V/25mA:

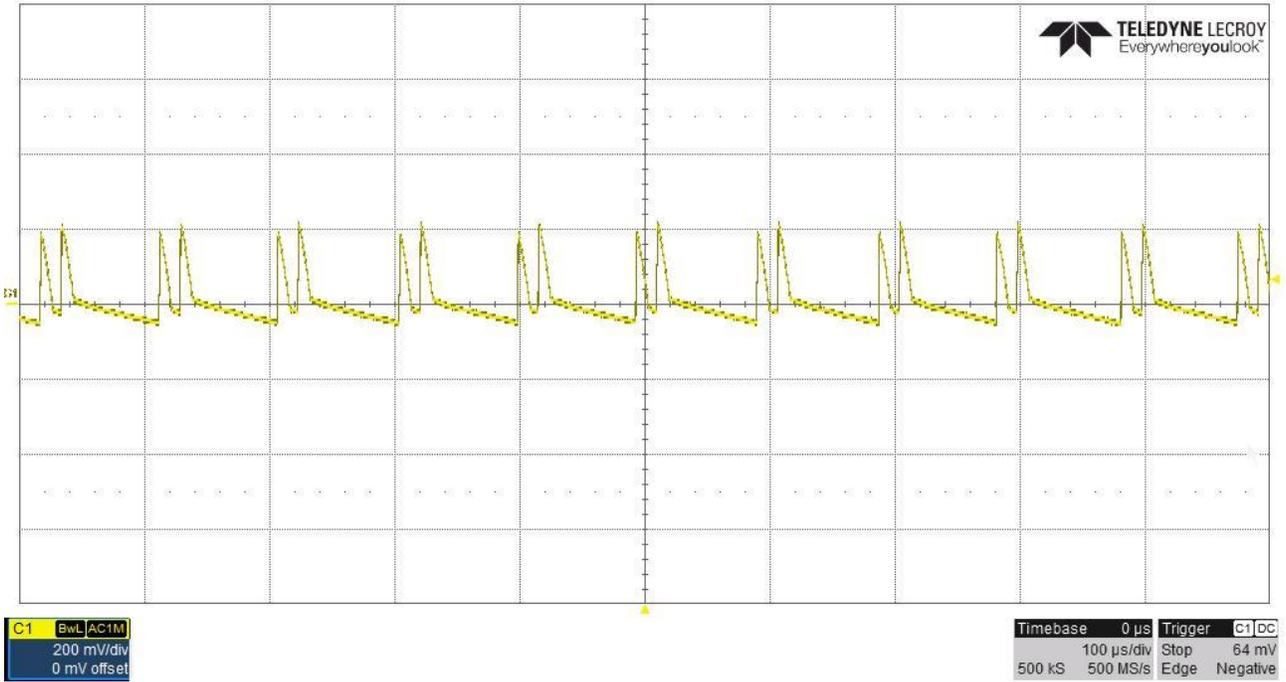


## 6.6 140V<sub>AC</sub>: no load:

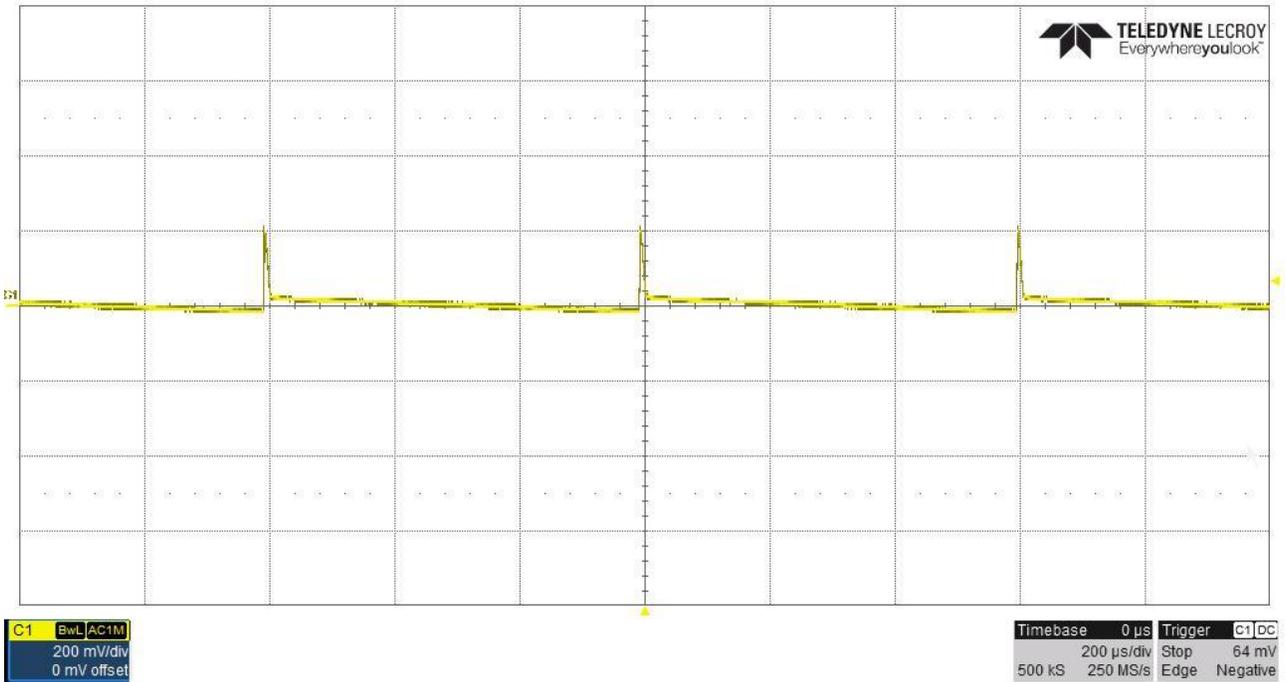


## 7 Switching Waveforms

The images below show key switching waveforms of PMP20654RevA. The waveforms are measured with 25mA full load. R5=4.7Ω in this test.

### 7.1 Diode D3 @ 85V<sub>AC</sub>/60Hz

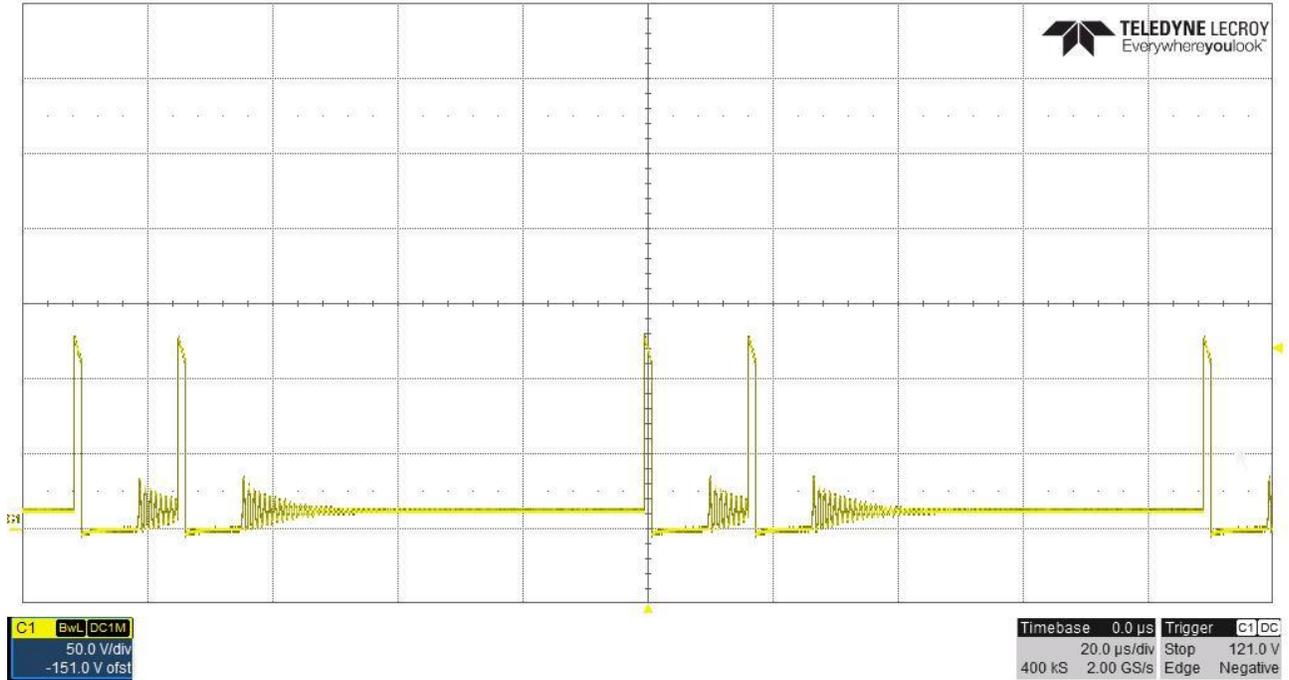
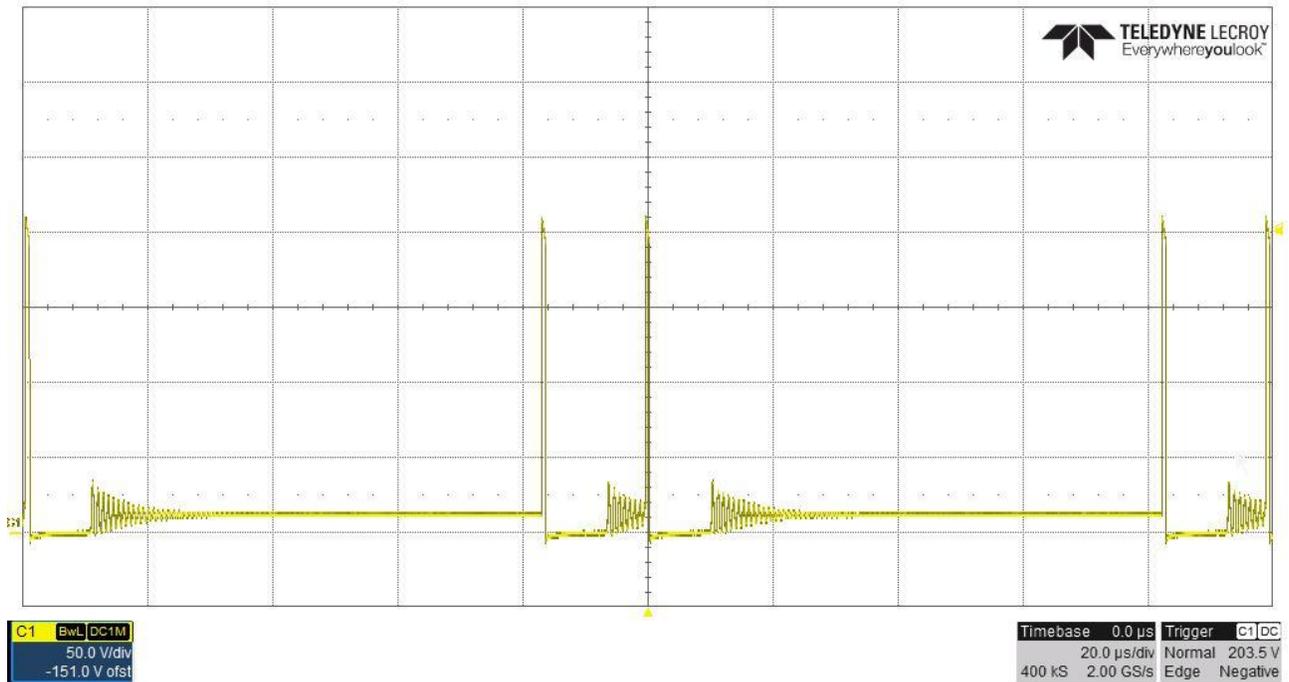
### 7.2 Diode D3 @ 140V<sub>AC</sub>/60Hz







## 8 Conduction EMI

Conducted EMI of PMP20654 Rev A was tested at the condition of  $V_{IN}=120V_{AC}$  and 12V/25mA output. The following curves show the peak scan results with maximum hold. **R5=470Ω** in this test.

### Line 1

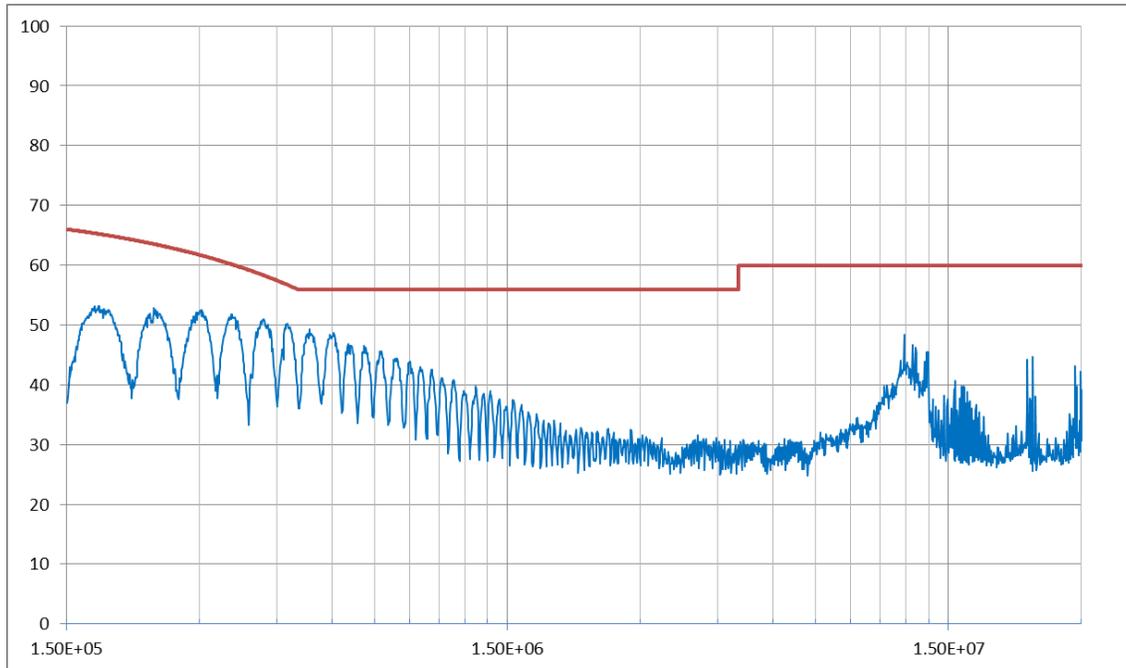

### Line 2

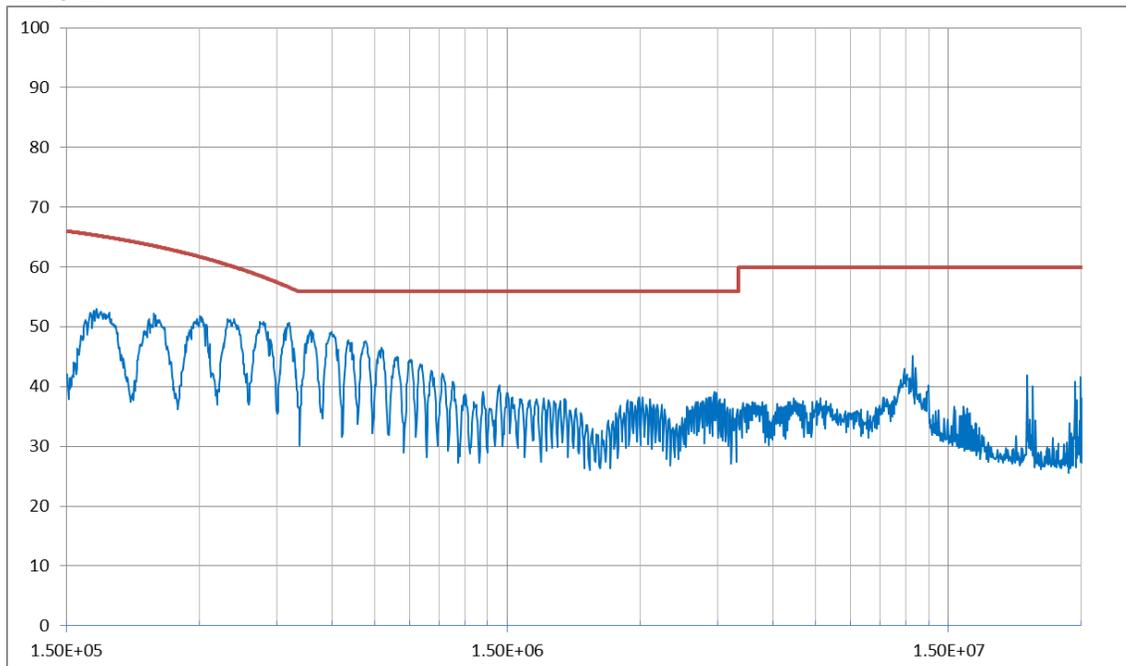

Trace073csv

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated