

Save power with a soft Zener clamp

By John Betten


Applications Engineer and
Senior Member, Technical Staff

Flyback converters are wildly popular due to their low cost, their isolation, and the ease with which additional output voltages can be implemented. For multiple-output flybacks, one output voltage—typically the highest-power output—is tightly regulated by means of feedback to the control circuit. Additional outputs are usually added by tightly coupling transformer windings to the main regulated winding. Linear regulators or DC/DC switchers may be added, or the outputs can be left unregulated. This last option is the most efficient, but many times voltage regulation suffers when the outputs are heavily or lightly loaded while the main output voltage has the opposite load level. This cross-regulation problem is highly dependent on the transformer leakage and winding structure, as well as on other parasitic circuit components. One of the worst scenarios is when the main output is heavily loaded and the unregulated winding is completely unloaded. Any voltage ringing present on the transformer's secondary winding is often peak-detected by the output rectifier, causing the unregulated output voltage to greatly increase. It is not uncommon for the output voltage to rise to twice its nominal voltage in this situation. This can be catastrophic to any downstream load that cannot tolerate a higher voltage or that does not present minimal loading at all times to dissipate the leakage energy.

Several solutions can remedy this no-load overvoltage condition. The simplest solution would be to add a preload to the unregulated output in the form of a resistor. This will load the output enough to dissipate the leakage energy and to lower the output voltage to an acceptable level. Unfortunately, this load will always be present and causes a loss of efficiency that is often considered unacceptable.

A second option is to simply add a Zener diode to the unregulated output. The diode's voltage rating must be set higher than the nominal output voltage after the typical 5% or 10% part tolerance is included. This means the diode won't conduct or dissipate power until the output voltage rises high enough. While this may seem like an ideal solution, several potential problems exist. Once the Zener diode conducts, its impedance drops significantly and provides little resistance to current flow. The current flow into the diode, and hence the power dissipated in it, is determined by parasitic circuit components and thus is

Figure 1. Zener diode with resistor provides soft clamp for no-load output voltage

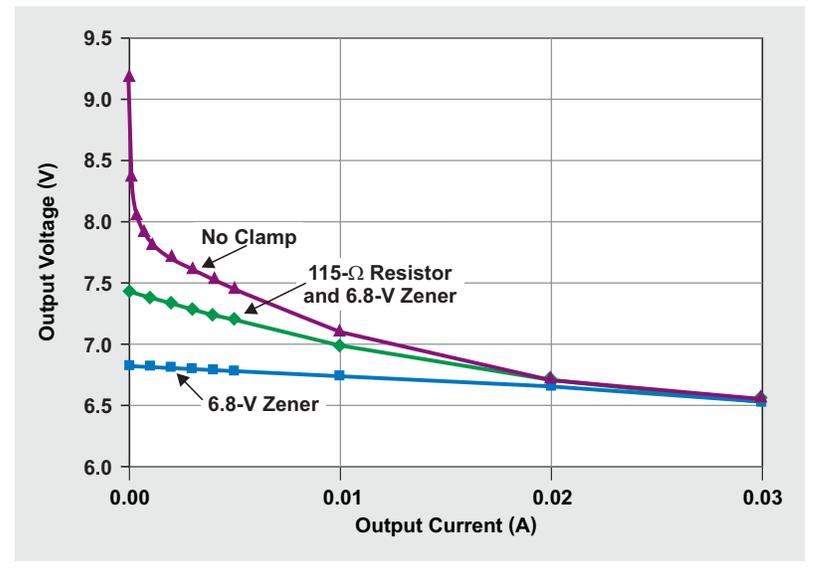

hard to control. Higher-power converters can potentially source a large current and easily destroy a Zener diode. For this reason, it is risky to add a small Zener diode and difficult to calculate the power dissipated.

Another option is to use a snubber to dissipate the leakage energy. This generally dissipates more power than using a preload resistor and does not always provide as much no-load voltage reduction on the output.

A soft Zener clamp, which consists of a resistor in series with a Zener diode, can provide a good compromise. It can clamp the unregulated output voltage to a level that is lower than that of the unclamped output voltage but higher than that of a Zener diode alone. To determine the resistor's value, the output can be loaded with just enough current to reduce the high output voltage to the desired safe level. Figure 1 shows an example where the desired no-load output voltage is 7.4 V. The series resistor's value can be calculated by subtracting the Zener diode's nominal voltage from this voltage and dividing the result by the preload current. The benefit of this circuit is that it does not dissipate power at loads that would typically be seen in operation. Under extreme cross-load conditions, this circuit clamps the "runaway" output voltage to a much more predictable level.

Related Web site

power.ti.com

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A042210

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps