

Digitally-isolated ADS8689 circuit design

Reed Kaczmarek


Input	ADC Input	Digital Output ADS7042
VinMin = -12.288V	AIN_P = -12.288V, AIN_N = 0V	8000 _H or -32768 ₁₀
VinMax = 12.288V	AIN_P = 12.288V, AIN_N = 0V	7FFF _H or 32767 ₁₀

Power Supplies		
AVDD	Vee	Vdd
5 V	6.5 V	5 V

Design Description

This design shows a digitally isolated high-voltage SAR ADC that is capable of full AC performance at maximum throughput. This design is intended for channel-to-channel isolated analog input modules as well as measuring a signal with a very large common mode. Programmable logic controller, analog input modules, and many 4- to 20-mA signal applications will benefit from this design. See [Isolated Power Supply Low-Noise, 5V, 100mA](#) for details on the isolated power supply design suitable for these applications. This cookbook includes links to design files.

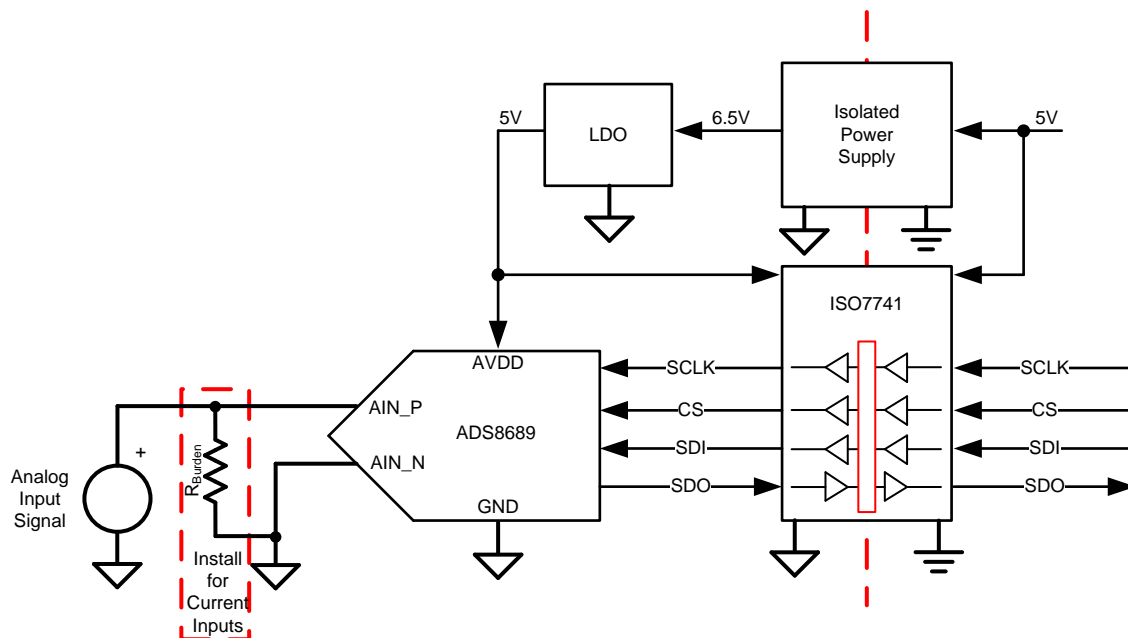This circuit implementation is applicable in applications such as [Analog Input Modules](#), [Electrocardiogram \(ECG\)](#), [Pulse Oximeter](#), and [Bedside Patient Monitors](#).



Copyright © 2018, Texas Instruments Incorporated

Specifications

Specification	Calculated	Measured
SCLK Frequency	6.66MHz	6.67MHz
Sampling Rate	100ksps	100ksps
Signal-to-Noise Ratio (SNR)	92dB	Min: 92.29dB Max: 92.46dB
Total Harmonic Distortion (THD)	-112dB	Min: -108.8dB Max: -111.38dB

Design Notes

1. Select a SAR ADC that will meet the input voltage range, sampling rate, and resolution for the system. This is covered in the *component selection* section.
2. Select a digital isolator that will allow for the required isolation specification as well as the correct number of channels and channel directions. This is covered in the *component selection* section.
3. Install the burden resistor for current inputs. This design will remove any common mode limitation of the inputs due to the channel-to-channel isolation. The burden resistor should be selected so that the maximum current input will stay within the full scale range of the SAR ADC.

Component Selection

1. Select a SAR ADC that meets the input voltage range, sampling rate, and resolution for the system:
 - Desired input range: $\pm 12V$
 - Desired effective number of bits (ENOB): 14 bits
 - Desired sampling rate: 100ksps
 - ADS8689 input range: $\pm 12.228V$
 - ADS8689 ENOB: 14.8 bits
 - ADS8689 maximum sampling rate: 100ksps

NOTE: There is a wide selection of TI SAR ADCs that match the specifications in the previous list.


2. Select a digital isolator that will allow for the required isolation specification as well as the correct number of bidirectional channels:
 - TI offers digital isolators with isolation rating ranging from $2.5kV_{RMS}$ to $5.7kV_{RMS}$.
 - Choose isolation ratings based on the system requirements.
 - For a standard SPI interface, the digital isolator needs to be 4-channels with 3 channels in the same direction and 1 channel in the opposite direction.
 - The ISO774x is a digital isolator family for 4-channel devices with all combinations of channel directions and the ability to select a $2.5kV_{RMS}$ or a $5.0kV_{RMS}$ isolation rating.
3. Understand the expected delays to the digital signal from the digital isolator:
 - The ISO7741 has a typical propagation delay of 10.7ns with a maximum of 16ns.
 - Round trip isolation delay is 21.4ns typical or 32ns maximum.
 - SCLK is running at 6.66MHz resulting in a period of 150ns.
 - The typical roundtrip delay is 14% of the SCLK period.
 - The maximum roundtrip delay is 21% of the SCLK period.

NOTE: The delay from the isolator results in a delay between the ideal SDO read relative to SCLK and the actual SDO read. This delay can be adjusted for by adding an SCLK return signal that travels through the digital isolator to all for the SDO to be read at exactly the correct time. Adding a return clock requires another channel of isolation.

Measured FFT

This performance was measured on a custom 4-channel, channel-to-channel isolated ADS8689 PCB. The input signal is a 24Vpp, 1-kHz sine wave. The AC performance indicates minimum SNR = 92.2dB and minimum THD = -108.8dB, which matches well with the specified performance of the ADC of SNR = 92dB and THD = -112dB.

Channel	SNR(dB)	THD (dB)
1	92.29	-109.95
2	92.38	-108.82
3	92.46	-109.53
4	92.42	-111.38

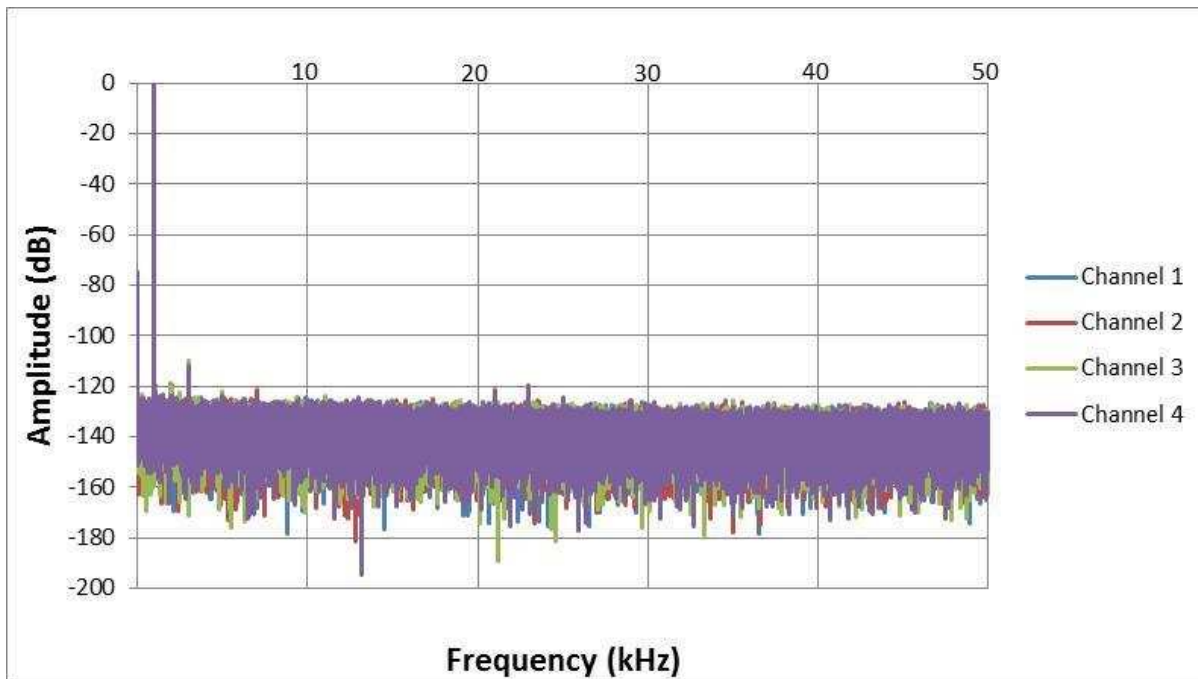

TVS Diode Performance Degradation

A 14-V bidirectional TVS diode was used in this design to protect the input of the SAR ADC. The TVS diode actually degrades total harmonic distortion (THD) due to the added capacitance. The THD was seen to be around 6dB worse with the TVS diode installed versus uninstalled.

Design Featured Devices

Device	Key Features	Link	Similar Devices
ADS8689⁽¹⁾	16 bit resolution, SPI, 100-ksps sample rate, single-ended input, and ± 12.288 -V input range.	www.ti.com/product/ADS8689	www.ti.com/adcs
ISO7741⁽²⁾	High-speed, robust-EMC reinforced quad-channel digital isolator	www.ti.com/product/iso7741	www.ti.com/iso

⁽¹⁾ The ADS8689 has an internal attenuator and programmable gain amplifier that allows for a wide input voltage range.

⁽²⁾ The ISO7741 is used to isolate the digital input signals.

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Link to Key Files

Source files for Digitally-Isolated ADS8689 – <http://www.ti.com/lit/zip/sbac179>.

Revision History

Revision	Date	Change
A	March 2019	Downstyle the title and changed title role to 'Data Converters'. Added link to circuit cookbook landing page.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated