

Circuit for driving high-voltage SAR ADC with a buffered instrumentation amplifier


Dale Li

Input	ADC Input	Digital Output ADS7042
VinDiffMin = -10V	CH_x = -10V	8000H
VinDiffMax = +10V	CH_x = +10V	7FFFH

Power Supplies			
AVDD	DVDD	HVDD (V _{CC})	HVSS(V _{EE})
5.0V	3.3V	+15V	-15V

Design Description

Instrumentation amplifiers are optimized for low noise, low offset, low drift, high CMRR and high accuracy but these instrument amplifiers may not be able to drive a precision ADC to settle the signal properly during the acquisition time of ADC. This design will show how a wide bandwidth buffer (OPA827) can be used with an instrumentation amplifier to achieve good settling at higher sampling rate. This INA828 instrumentation amplifier with the buffer drives the ADS8568 SAR ADC to implement data capture for a high voltage fully differential signal which may have a wide common-mode voltage range or a bipolar single-ended signal up to $\pm 10\text{V}$. A related cookbook circuit shows a simplified approach that does not include the wide bandwidth buffer ([Driving High Voltage SAR ADC with an Instrumentation Amplifier](#)), this simplified approach has limited sampling rate as compared to the buffered design in this document. This circuit implementation is applicable to [Industrial Transportation](#) and [Analog Input Modules](#) that require Precision Signal-Processing and Data-Conversion.

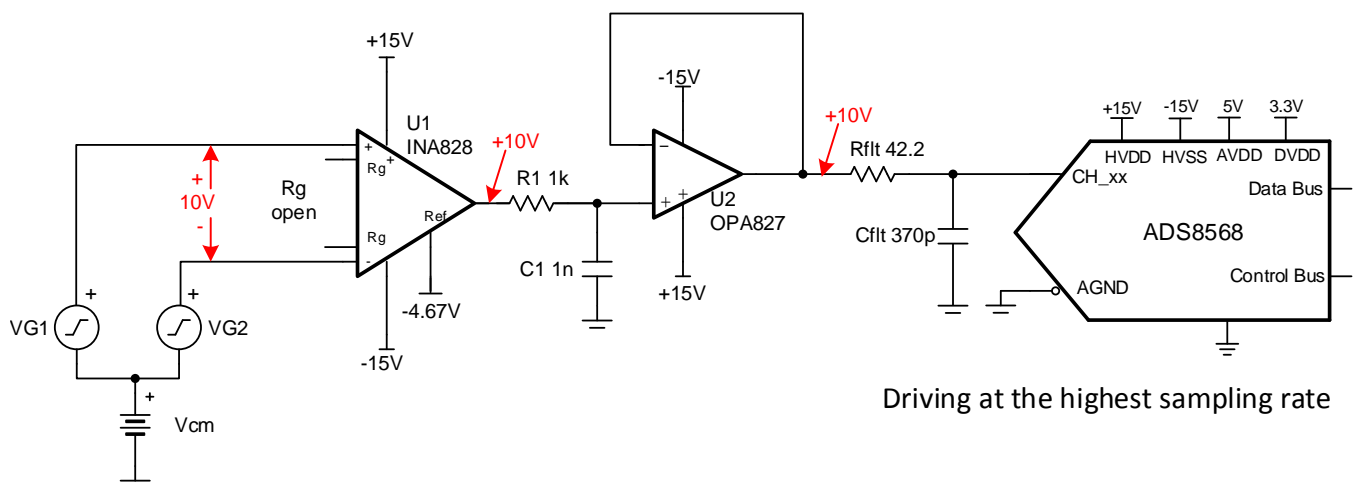

Specifications


Specification	Goal	Calculated	Simulated
Transient Settling Error	< 1/2LSB (< 152 μ V)	NA	-346nV
Noise (at ADC Input)	<20 μ V _{RMS}	47.2 μ V _{RMS}	46 μ V _{RMS}

Design Notes

1. The bandwidth of instrumentation amplifiers is typically not enough to drive SAR data converters at higher data rate, so a wide bandwidth driver is needed because the SAR ADC with switched-capacitor input structure has an input capacitor that needs to be fully charged during each acquisition time. The [OPA827](#) buffer is added to allow the ADC to run at full sampling rate ([ADS8568](#) 510kSPS for parallel interface).
2. The [ADS8568](#) can accept a ± 10 -V single-ended input signal. The [INA828](#) is used to translate a ± 10 -V differential signal to a ± 10 -V single-ended signal. So the [INA282](#) is in unity gain for this example, and no external gain set resistor R_g is needed. Refer to [Circuit for Driving an ADC with an Instrumentation Amplifier in High Gain](#) in cases where the input signal range is small and gain is required.
3. Check the common mode range of the amplifier using the [Common-Mode Input Range Calculator for Instrumentation Amplifiers](#) software tool.
4. Select COG capacitors for C_1 and C_{filt} to minimize distortion.
5. Precision labs video series covers the method for selecting driver amplifier and the charge bucket circuit R_{filt} and C_{filt} . For details, see the [Selecting and Verifying the Driver Amplifier](#) and [Introduction of SAR ADC Front-End Component Selection](#) videos.
6. Set the cutoff of the filter between the op amp and instrumentation amplifier for anti aliasing and to minimize noise. See [Aliasing and Anti-aliasing Filters](#) for more details on aliasing and anti-aliasing filters.

Component Selection

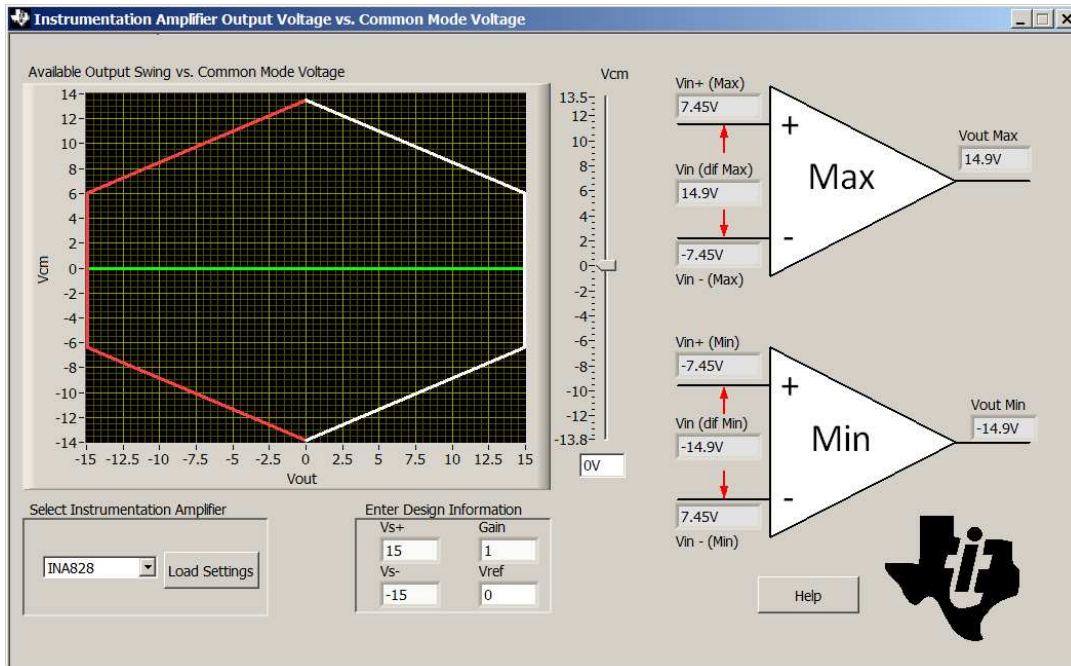1. Find the gain based on differential input signal and ADC full-scale input range. The input signal in this design is ± 10 -V high voltage signal, so the Gain of [INA828](#) should be set to 1 and no gain resistor (R_g) is needed.
2. Use the [Common-Mode Input Range Calculator for Instrumentation Amplifiers](#) to determine if the [INA828](#) is violating the common mode range. The common mode calculator in the following figure indicates that the output swing is ± 14.9 V for a 0-V common-mode input.




3. Find the value for C_{filt} , and R_{filt} using [TINA SPICE](#) and the methods described in [SAR ADC Front-End Component Selection](#). The value of R_{filt} and C_{filt} shown in this document will work for these circuits; however, if you use different amplifiers you will have to use TINA SPICE to find new values.
4. Select the RC filter between the [INA828](#) and [OPA827](#) based on your system requirements ($f_{cRC} = 15.9$ kHz in this example). Set the cutoff of this filter for anti aliasing and to minimize noise.

$$f_{cRC} = \frac{1}{2\pi \cdot R_1 \cdot C_1} = \frac{1}{2\pi \cdot (1k\Omega) \cdot (1pF)} = 159kHz$$


DC Transfer Characteristics

The following graph shows a linear output response for inputs from differential -12.2V to $+12.2\text{V}$. The input range of the ADC is $\pm 10\text{V}$, so the amplifiers are linear well beyond the required range. Refer to [Determining a SAR ADC's Linear Range when using Instrumentation Amplifiers](#) for detailed theory on this subject. The full-scale range (FSR) of the ADC falls within the linear range of the Instrumentation Amplifier.

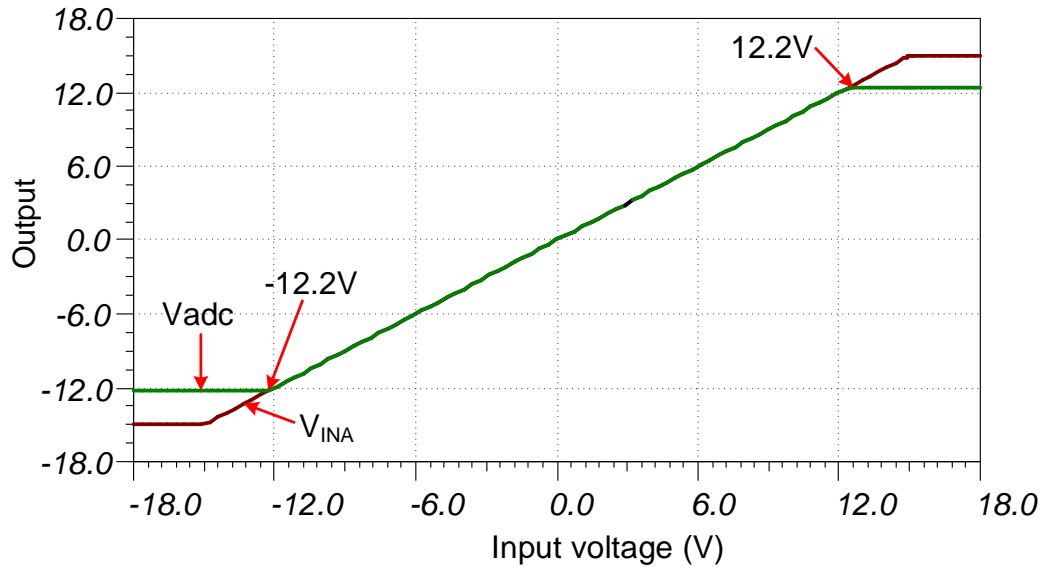


AC Transfer Characteristics

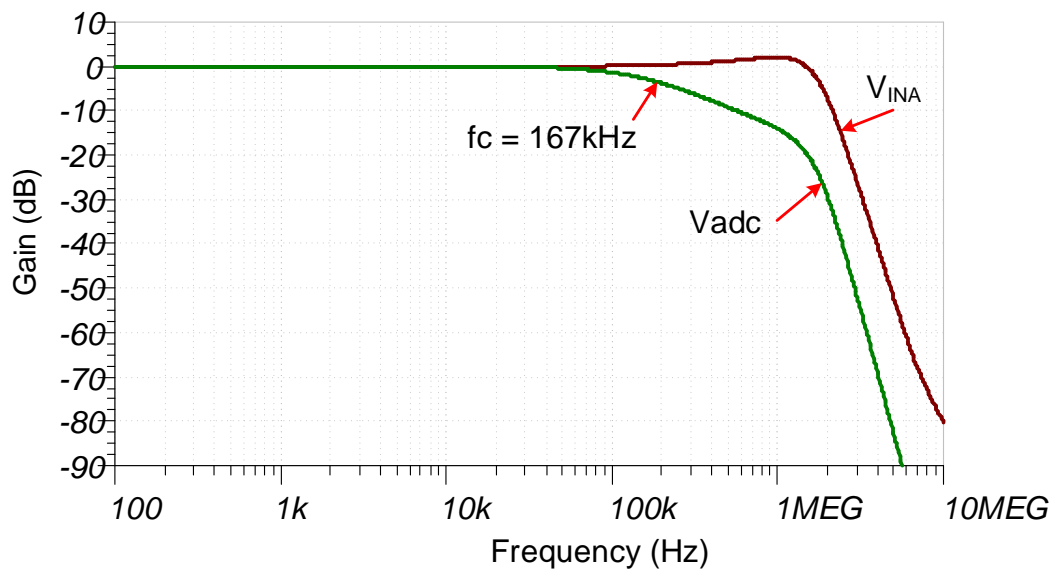The bandwidth for this system is simulated to be 167kHz and the gain is 0dB . The filter between the [OPA827](#) and [INA828](#) limits the bandwidth to about 167kHz .



Transient ADC Input Settling Simulation (510kSPS)

The [OPA827](#) buffer (22MHz GBW) is used because it is capable of responding to the rapid transients from the [ADS8568](#)'s charge kickback. The op amp buffer allows the system to achieve the [ADS8568](#) maximum sampling rate of 510kSPS. The following simulation shows settling to a full scale DC input signal with [INA828](#) and [OPA827](#) buffer, and [ADS8568](#). This type of simulation shows that the sample and hold kickback circuit is properly selected to meet desired $\frac{1}{2}$ of a LSB (152 μ V). Refer to the [Introduction to SAR ADC Front-End Component Selection](#) training video series for detailed theory on this subject.

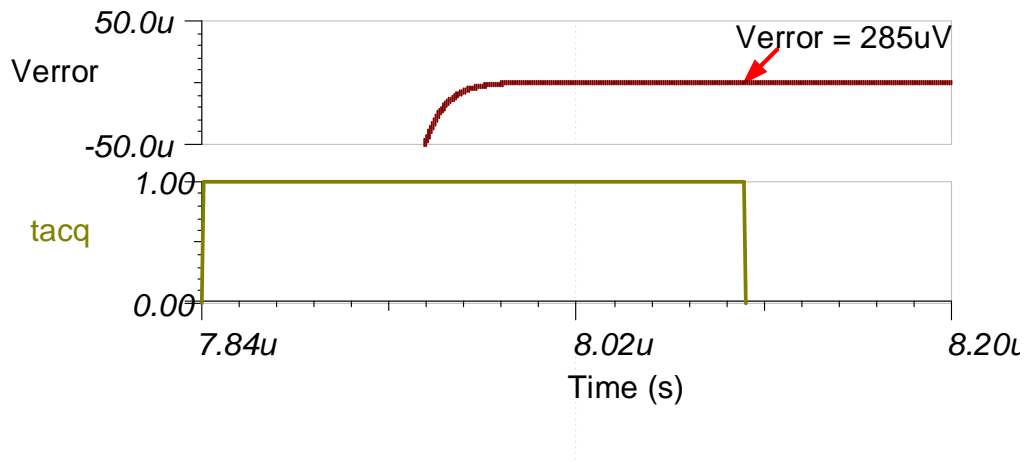

Noise Simulation

The section walks through a simplified noise calculation for a rough estimate. We include both the [INA828](#), and [OPA827](#) noise. Note that the RC filter between the instrumentation amplifier and op amp significantly reduces the total noise. The output filter pole is estimated as a second order filter because the [OPA827](#) (22MHz) bandwidth limit and charge bucket filter cutoff frequency (10.2MHz) is close.

$$E_{n-INA} = G \sqrt{e_{n-in}^2 + \left(\frac{e_{n-out}}{G}\right)^2} \cdot \sqrt{K_n \cdot f_{cRC}}$$


$$E_{n-INA} = 1 \sqrt{\left(4 \text{ nV}/\sqrt{\text{Hz}}\right)^2 + \left(\frac{90 \text{ nV}/\sqrt{\text{Hz}}}{1}\right)^2} \cdot \sqrt{(1.57) \cdot (159 \text{ kHz})} = 45.1 \mu\text{Vrms}$$

$$f_{c-adcFilter} = \frac{1}{2\pi \cdot R_{filt} \cdot C_{filt}} = \frac{1}{2\pi \cdot (42.2\Omega) \cdot (370 \text{ pF})} = 10.2 \text{ MHz}$$

$$E_{opa} = e_{n-opa} \sqrt{K_n \cdot f_c} = (4 \text{ nV}/\sqrt{\text{Hz}}) \sqrt{(1.22) \cdot (10.2 \text{ MHz})} = 14.1 \mu\text{Vrms}$$

$$E_{n-total} = \sqrt{E_{n-INA}^2 + E_{opa}^2} = \sqrt{(45.1 \mu\text{V})^2 + (14.1 \mu\text{V})^2} = 47.2 \mu\text{Vrms}$$

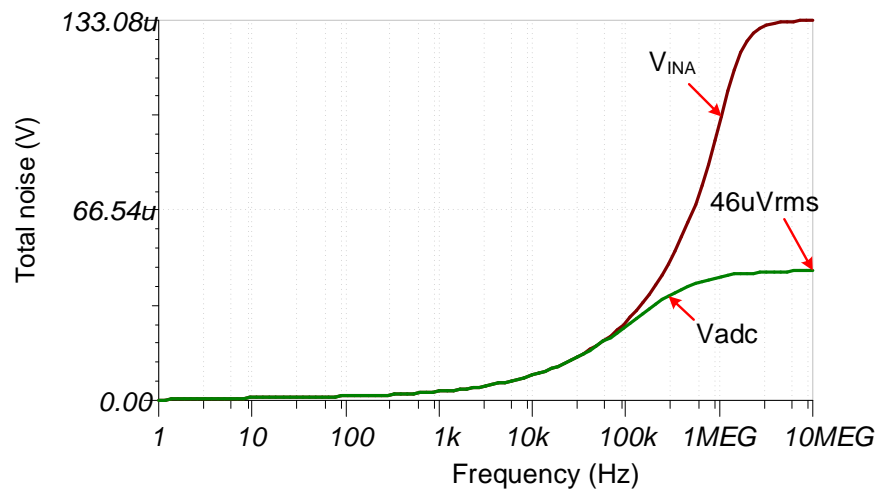Note that calculated and simulated match well (calculated = 47.2μV, Simulated = 46μV). See [TI Precision Labs - Noise 4](#) for detailed theory on amplifier noise calculations, and [Calculating Total Noise for ADC Systems](#) for data converter noise.



Design Featured Devices

Device	Key Features	Link	Similar Devices
ADS8568	16-bit, 8 Channel Simultaneous-Sampling, Bipolar-Input SAR ADC	http://www.ti.com/product/ADS8568	www.ti.com/adcs
INA828	Bandwidth 1MHz (G=1), low noise 18nV/rtHz, low offset $\pm 40\mu\text{V}$, low offset drift $\pm 0.4\mu\text{V}/^\circ\text{C}$, low gain drift 0.1ppm/ $^\circ\text{C}$. (Typical values)	http://www.ti.com/product/INA828	www.ti.com/inas
OPA827	Gain bandwidth 22MHz, low noise 4nV/rtHz, low offset $\pm 75\mu\text{V}$, low offset drift $\pm 0.1\mu\text{V}/^\circ\text{C}$ (Typical values)	http://www.ti.com/product/OPA827	www.ti.com/opamp

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Links to Key Files

Source files for this circuit - <http://www.ti.com/lit/zip/SBAC216>.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated