

SYNCHRONIZATION OF ISO120/121 ISOLATION AMPLIFIERS

By Rod Burt and R. Mark Stitt (602) 746-7445

Internal clock circuitry in the ISO120/121 precision isolation amplifier (ISO amp) can be synchronized to an external clock signal. Synchronization to an external clock can be used to eliminate beat frequencies in multichannel systems or for rejection of specific AC signals and their harmonics—see the ISO120/121 product data sheet, PDS-820.

The external clock signal can be directly connected to the ISO120/121 if it is a sine or triangle wave of the proper amplitude. At clock frequencies above 400kHz, a square wave external clock can also be directly connected to the ISO120/121. Other clock signals can be used with the addition of the signal conditioning circuit shown in Figure 2.

SYNCHRONIZING TO A SINE OR TRIANGLE WAVE EXTERNAL CLOCK

The ideal external clock signal for the ISO120/121 is a $\pm 4V$ sine wave or $\pm 4V$, 50% duty-cycle triangle wave. The *ext osc* pin of the ISO120/121 can be driven directly with a $\pm 3V$ to $\pm 5V$ sine or 25% to 75% duty-cycle triangle wave and the ISO amp's internal modulator/demodulator circuitry will synchronize to the signal.

EXTERNAL CLOCK FREQUENCY RANGE	C ₁ , C ₂ ISO120/121 MODULATOR, DEMODULATOR EXTERNAL CAPACITOR
400kHz to 700kHz	none
200kHz to 400kHz	500pF
100kHz to 200kHz	1000pF
50kHz to 100kHz	2200pF
20kHz to 50kHz	4700pF
10kHz to 20kHz	0.01 μ F
5kHz to 10kHz	0.022 μ F

TABLE I. Recommended ISO120/121 External Modulator/Demodulator Capacitor Values vs External Clock Frequency.

EXTERNAL CLOCK FREQUENCY RANGE	C _x
400kHz to 700kHz	30pF
200kHz to 400kHz	180pF
100kHz to 200kHz	680pF
50kHz to 100kHz	1800pF
20kHz to 50kHz	3300pF
10kHz to 20kHz	0.01 μ F
5kHz to 10kHz	0.022 μ F

TABLE II. Recommended C_x Values vs Frequency for Figure 2 Circuit.

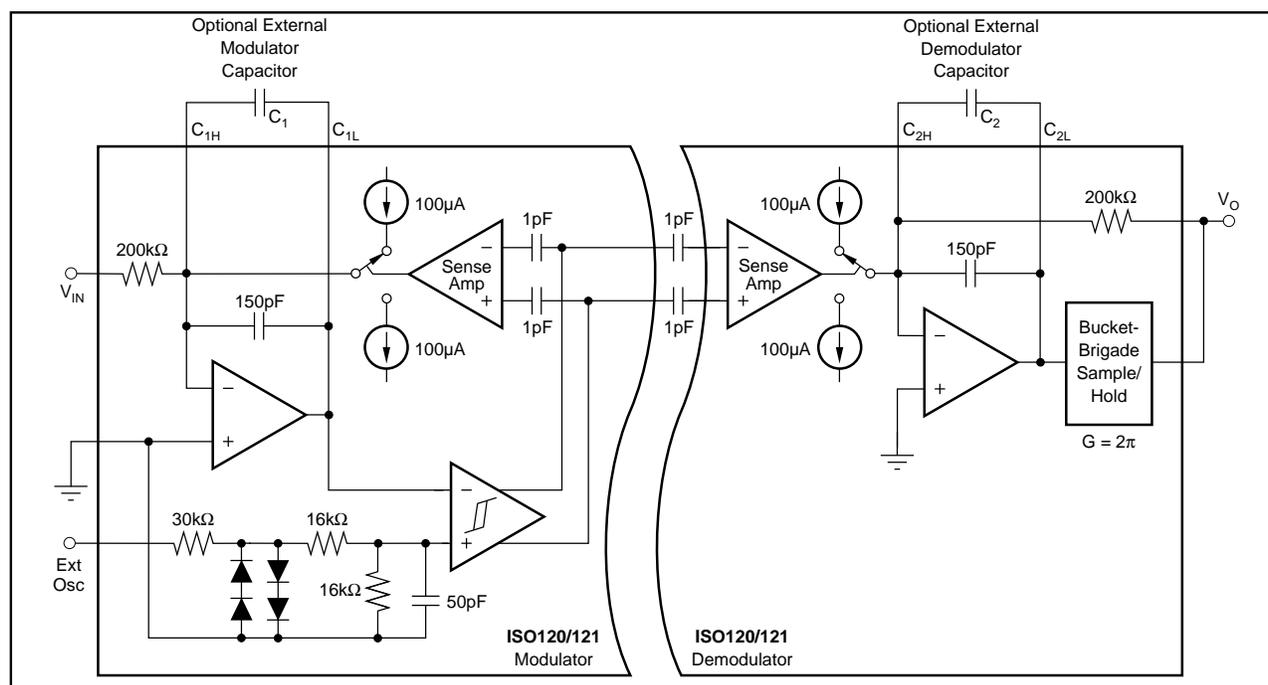


FIGURE 1. ISO120/121 Block Diagram Showing Internal Clamp and Filter Circuitry at the Ext Osc Pin.

Synchronizing to signals below 400kHz requires the addition of two external capacitors to the ISO120/121. Connect one capacitor in parallel with the internal modulator capacitor and connect the other capacitor in parallel with the internal demodulator capacitor as shown in Figure 1.

The value of the external modulator capacitor, C_1 , depends on the frequency of the external clock signal. Table I lists recommended values.

The value of the external demodulator capacitor, C_2 , depends on the value of the external modulator capacitor. To assure stability, C_2 must be greater than $0.8 \cdot C_1$. A larger value for C_2 will decrease bandwidth and improve stability:

$$f_{-3dB} \approx \frac{1.2}{200k\Omega (150pF + C_2)}$$

Where:

$f_{-3dB} \approx$ -3dB bandwidth of ISO amp with external C_2 (Hz)
 $C_2 =$ External demodulator capacitor (F)

For example, with $C_2 = 0.01\mu F$, the f_{-3dB} bandwidth of the ISO120/121 is approximately 600Hz.

SYNCHRONIZING TO A 400kHz TO 700kHz SQUARE-WAVE EXTERNAL CLOCK

At frequencies above 400kHz, an internal clamp and filter provides signal conditioning so that a square-wave signal can be used to directly drive the ISO120/121. A square-wave external clock signal can be used to directly drive the ISO120/121 *ext osc* pin if: the signal is in the 400kHz to 700kHz frequency range with a 25% to 75% duty cycle, and $\pm 3V$ to $\pm 20V$ level. Details of the internal clamp and filter circuitry are shown in Figure 1.

SYNCHRONIZING TO A 10% TO 90% DUTY-CYCLE EXTERNAL CLOCK

With the addition of the signal conditioning circuit shown in Figure 2, any 10% to 90% duty-cycle square-wave signal can be used to drive the ISO120/121 *ext osc* pin. With the values shown, the circuit can be driven by a 4Vp-p TTL signal. For a higher or lower voltage input, increase or decrease the $1k\Omega$ resistor, R_x , proportionally. e.g. for a $\pm 4V$ square wave (8Vp-p) R_x should be increased to $2k\Omega$.

The value of C_x used in the Figure 2 circuit depends on the frequency of the external clock signal. Table II shows recommended capacitor values.

Note: For external clock frequencies below 400kHz, external modulator/demodulator capacitors are required on the ISO120/121 as before.

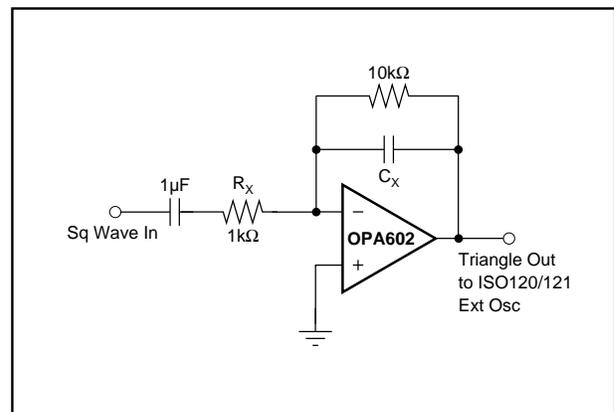


FIGURE 2. Square Wave to Triangle Wave Signal Conditioner for Driving ISO120/121 Ext Osc Pin.

The information provided herein is believed to be reliable; however, BURR-BROWN assumes no responsibility for inaccuracies or omissions. BURR-BROWN assumes no responsibility for the use of this information, and all use of such information shall be entirely at the user's own risk. Prices and specifications are subject to change without notice. No patent rights or licenses to any of the circuits described herein are implied or granted to any third party. BURR-BROWN does not authorize or warrant any BURR-BROWN product for use in life support devices and/or systems.

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.