

Monitoring Current for Multiple Out-of-Range Conditions



Dennis Hudgins, Current Sensing Products

One of the first parameters engineers look at when determining proper operation of a PCB design is the operating current. By examining the operating current, an engineer can immediately tell if something on the board is shorted, whether any of the devices are damaged, and in some cases detect if the software is running as expected. The traditional approach of using a current sense amplifier + ADC to monitor current for out-of-range conditions does not provide the required alert response time. Also, use of an ADC to monitor over current alert thresholds requires constant communication between the ADC and host processor which can unnecessarily burden the system.

Being able to quickly know when a current level is out of range allows improved safety, improved system intelligence/diagnostics and reduced downtime.

To address the response time required for out-of-range current conditions, analog comparators are needed to detect when the current exceeds a given reference threshold. However, in many cases having only one alert level is insufficient to determine the system status and provide appropriate system responses to out-of-range currents. To handle this requirement the circuit shown in Figure 1-1 can be used to monitor multiple out-of-range current conditions.

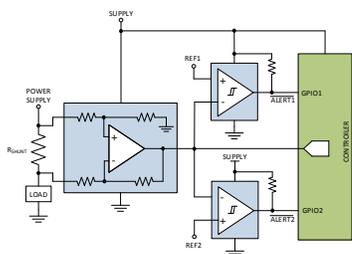


Figure 1-1. Discrete Implementation to Detect Multiple Over-current Events

This circuit is composed of 5 devices: a current sense amplifier, two comparators, and two references. The discrete implementation, shown in Figure 1-1 requires careful selection of the comparators to get the desired alert response time. Slow response times may not allow enough time for the system to take action; while

too fast of a response time can trigger false alerts, possibly resulting in system shutdown.

Figure 1-2 shows a simpler circuit that addresses the design issues present in the discrete implementation.

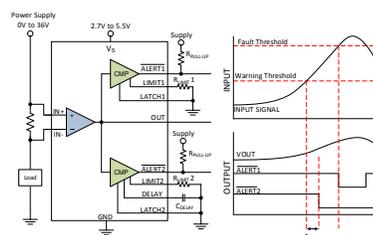


Figure 1-2. INA302 Multi-Alert Over-Current Comparator

The INA302 incorporates the ability to detect two out-of-range conditions. The lower out-of-range condition is referred to as the over current warning threshold, while the higher out-of-range condition is referred to as the over current fault threshold. The over current warning threshold allows detection when the current is starting to get too high but has not yet reached the fault threshold where system shutdown may be initiated. When the current exceeds the warning threshold, the system may opt to reduce the system power consumption by disabling sub-circuits, controlling supply voltages, or reducing clocking frequencies to lower the total system current to prevent a fault condition. If an over-current fault condition does occur, it is important to respond quickly to prevent further system damage or malfunctioning behavior.

To minimize the component count and facilitate ease of use, the alert thresholds of the INA302 are set with single external resistors. The fault threshold should be set higher than the worst case current the system could be expected to consume. When the current exceeds this threshold, the alert pin of the INA302 will respond within 1 μ s. The value for the warning threshold is application dependent, but is usually higher than the nominal operating current. The response time of the warning threshold is adjustable with an external capacitor from 3 μ s to 10 s.

By setting the warning threshold delay time appropriately, it is possible to set the over-current

warning threshold closer to the maximum DC operating current while still avoiding false trips due to brief current spikes or noise. Wider separation between the fault and warning thresholds provides the system additional time for preventative action before the fault threshold is exceeded.

Some systems allow operation above the warning threshold for a period of time before triggering an alert. One such application is monitoring the supply current to a processor. The processor may be allowed to operate above the normal maximum current level for a brief period of time to maximize computing throughput during critical operations. If the current is above the warning threshold when the set delay expires the alert output will pull low to notify the host processor so the voltage or clocking frequency can be decreased before overheating occurs.

In some systems it is beneficial to detect when the current is too low. For these applications, the [INA303](#), shown in [Figure 1-3](#) provides both over and under current detection.

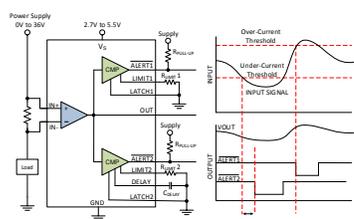


Figure 1-3. INA303 Over and Under Current Detection

When the current exceeds the over current fault threshold, the ALERT1 output will respond within 1 μ s. However, if the current goes below the under current threshold, the ALERT2 response time is set by the delay capacitor. Undercurrent situations may briefly occur in normal operation; however, if this condition persists, it could be due to a damaged device or system that is about to fail.

In this case, the alert output can notify the system of this condition and fault handling procedures can be implemented before system failure.

Another use of under-current detection is to provide confirmation of proper system status. Some systems go into low power modes where the current is below the normal operating range. In this case, the under-current alert output can be used to notify the host that the system has indeed entered the shutdown state.

Some designs may only care to get notified if the current is outside of expected operating bounds. For these cases, the [INA303](#) can be configured to run in window mode by connecting the two alert outputs together as shown in [Figure 1-4](#). In this mode, the single alert output will be high as long as the current is with-in the normal operating window.

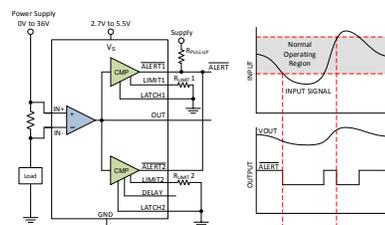


Figure 1-4. INA303 Window mode Operation

Alternate Device Recommendations

The [INA226](#) can be used in applications that require digital current monitoring. If only a single digital alert output is needed, the [INA300](#) provides an optimal solution in a tiny 2mm x 2mm QFN package. For applications that only require a single alert output in addition to the analog current signal, the [INA301](#) provides excellent current monitoring accuracy with an alert response less than 1 μ s. For cost sensitive applications and added flexibility, the [INA381](#) provides an current sense amplifier with an internal comparator with accessible inputs.

Table 1-1. Alternate Device Recommendations

Device	Optimized Parameter	Performance Trade-off
INA301	MSOP-8 package, single alert with analog monitor.	Single alert
INA300	2mm x 2mm QFN package	Alert only
INA381	Cost effective, accessible comparator inputs	Single alert
INA226	Digital current monitor	N/A

Table 1-2. Related TI Application Briefs

Device	Measuring Current To Detect Out-of-Range Conditions
SBOA162	High-Side Motor Current Monitoring for Over-Current Protection
SBOA163	Integrating The Current Sensing Signal Path
SBOA167	Safety and Protection for Discrete Digital Outputs in a PLC System
SBOA193	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated