


## Overcurrent Event Detection Circuit

### Design Goals

Input		Overcurrent Conditions		Output		Supply	
$I_{load\ Min}$	$I_{load\ Max}$	$I_{OC\_TH}$	$I_{Release\_TH}$	$V_{out\_OC}$	$V_{out\_release}$	$V_S$	$V_{REF}$
1.5A	40A	35A	32A	2.8V	2.61V	3.3V	2.8V
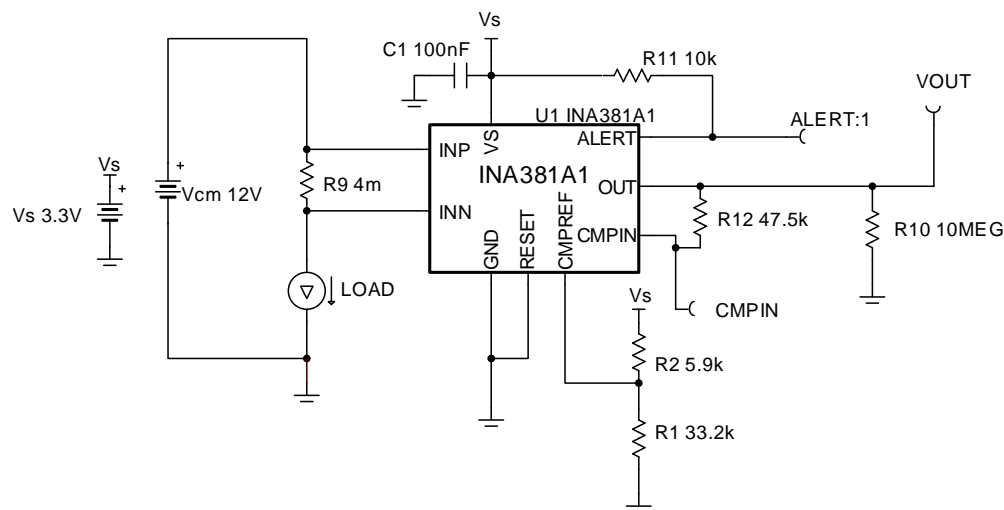
### Design Description

This is a unidirectional current sensing solution generally referred to as overcurrent protection (OCP) that can provide an overcurrent alert signal to shut off a system for a threshold current and re-engage the system once the output drops below a desired voltage ( $V_{out\_release}$ ) lower than the overcurrent output threshold voltage ( $V_{out\_OC}$ ). In this particular setup, the sensing range is from 1.5A to 40A, with the overcurrent threshold defined at 35A ( $I_{OC\_TH}$ ). The system re-asserts the ALERT to high once the current has dropped below 32A ( $I_{Release\_TH}$ ). The current shunt monitor is powered from a 3.3-V supply rail. OCP can be applied to both high-side and low-side topologies. The solution presented in this article is a high-side implementation.



### Design Notes

1. Use low-tolerance, high-precision resistors if using a voltage divider for CMPREF and consider buffering the voltage. Otherwise consider using a low-dropout regulator (LDO), reference or buffered reference voltage circuit to supply the CMPREF.
2. Use decoupling capacitors to ensure the device supply is stable, such as C1. Also place the decoupling capacitor as close to the device pin as possible.

### Design Steps

1. Calculate the  $R_{\text{shunt}}$  value given 20V/V gain. Use the nearest standard value shunt, preferably lower than the calculated shunt to avoid railing the output prematurely .

$$R_{\text{shunt}} = \frac{V_{\text{out max}}}{\text{gain} \times I_{\text{max}}} = \frac{V_S - 0.02V}{\text{gain} \times I_{\text{max}}} = \frac{3.3V - 0.02V}{20V/V \times 40A} = 0.0041\Omega$$

$$R_{\text{standard shunt}} = 4\text{m}\Omega \text{ (standard 1\% value)}$$

2. Determine the voltage at the current shunt monitor output for the overcurrent threshold.

$$V_{\text{out}_35A} = I_{\text{OC\_TH}} \times R_{\text{standard shunt}} \times \text{gain} = 35A \times 4\text{m}\Omega \times 20V/V = 2.8V$$

3. Choose a standard resistor value for  $R_1$  and solve for  $R_2$ .

A resistor with kilo-ohm resistance or higher is desired to minimize power loss. Through calculation, 33.2k $\Omega$  and 5.9k $\Omega$  were chosen for resistances  $R_1$  and  $R_2$ .

$$R_2 = \left( \frac{V_S}{V_{\text{out}_35A}} - 1 \right) \times R_1 = \left( \frac{3.3V}{2.8V} - 1 \right) \times 33.2\text{k}\Omega = 5.9\text{k}\Omega$$

4. Calculate the resistance ( $R_{\text{Hyst}}$ ) required for the proper hysteresis.

$$R_{\text{Hyst}} = \frac{V_{\text{out}_35A} - (I_{\text{Release\_TH}} \times R_{\text{standard shunt}} \times \text{gain} + V_{\text{Hyst\_def}})}{I_{\text{Hyst}}}$$


$$R_{\text{Hyst}} = \frac{2.8V - (32A \times 4\text{m}\Omega \times 20V/V + 50\text{mV})}{4\mu A} = 47.5\text{k}\Omega$$

## Design Simulations

### Transient Simulation Results

Considering **error**,  $V_{out\_OC}$  is expected to be approximately 2.8V, while  $V_{out\_release}$  is expected to be approximately 2.61V.

### High-Side OCP Simulation Results

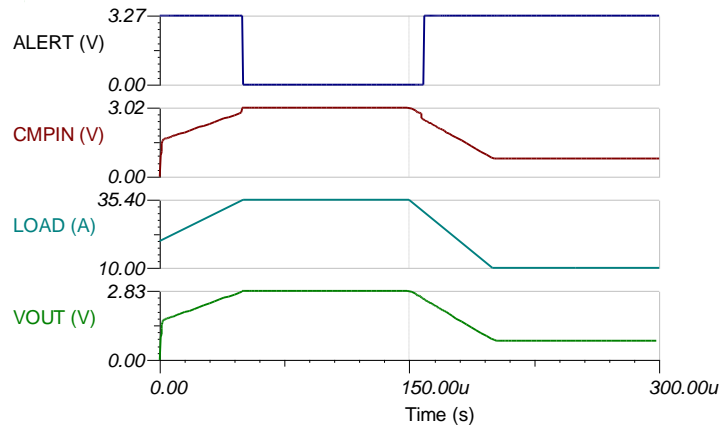

The device exhibits an active low on the Alert pin when the load reaches 35A and re-asserts Alert to high when the load drops below 32A. If the user zooms in and looks at the VOUT voltage, and accounts for an expected propagation delay of 0.4 $\mu$ s, the device output is 2.69V at  $I_{OC\_TH}$ , which only has an error of 0.39% with respect to the ideal output of 2.8V. At  $I_{release\_TH}$ , the alert re-asserts to high when the output dropped to 2.58V, which only has an error of 1.15% with respect to the ideal output of 2.61V.

## Design References

### Key files for Overcurrent Protection Circuit:

Source files for this design:

[High-Side OCP Tina Model](#)

[Low-Side OCP Tina Model](#)

### Getting Started with Current Sense Amplifiers video series:

<https://training.ti.com/getting-started-current-sense-amplifiers>

### Design Featured Current Sense Amplifier

INA381	
$V_S$	2.7V to 5.5V
$V_{CM}$	GND-0.3V to 26V
$V_{OUT}$	GND+5 $\mu$ V to $V_S$ -0.02V
$V_{OS}$	$\pm$ 100 typical
$I_q$	250 $\mu$ A typical
$I_B$	80 $\mu$ A typical
<a href="http://www.ti.com/product/INA381">http://www.ti.com/product/INA381</a>	

### Design Alternate Current Sense Monitor

	INA301	INA302	INA303
$V_S$	2.7V to 5.5V	2.7V to 5.5V	2.7V to 5.5V
$V_{CM}$	GND-0.3V to 40V	-0.1V to 36V	-0.1V to 36V
$V_{OUT}$	GND+0.02 to $V_S$ -0.05V	GND+0.015 to $V_S$ -0.05V	GND+0.015 to $V_S$ -0.05V
$V_{OS}$	Gain Dependent	Gain Dependent	Gain Dependent
$I_q$	500 $\mu$ A typical	850 $\mu$ A typical	850 $\mu$ A typical
$I_B$	120 $\mu$ A typical	115 $\mu$ A typical	115 $\mu$ A typical
Comparator	Single Comparators	Dual Comparators	Window Comparators
	<a href="http://www.ti.com/product/INA301">http://www.ti.com/product/INA301</a>	<a href="http://www.ti.com/product/INA302">http://www.ti.com/product/INA302</a>	<a href="http://www.ti.com/product/INA303">http://www.ti.com/product/INA303</a>

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated