


Overcurrent event detection circuit

Design Goals

Input		Overcurrent Conditions		Output		Supply	
$I_{load\ Min}$	$I_{load\ Max}$	I_{OC_TH}	$I_{Release_TH}$	V_{out_OC}	$V_{out_release}$	V_S	V_{REF}
1.5A	40A	35A	32A	2.8V	2.61V	3.3V	2.8V

Design Description

This is a unidirectional current sensing solution generally referred to as overcurrent protection (OCP) that can provide an overcurrent alert signal to shut off a system for a threshold current and re-engage the system once the output drops below a desired voltage ($V_{out_release}$) lower than the overcurrent output threshold voltage (V_{out_OC}). In this particular setup, the sensing range is from 1.5A to 40A, with the overcurrent threshold defined at 35A (I_{OC_TH}). The system re-asserts the ALERT to high once the current has dropped below 32A ($I_{Release_TH}$). The current shunt monitor is powered from a 3.3-V supply rail. OCP can be applied to both high-side and low-side topologies. The solution presented in this article is a high-side implementation.

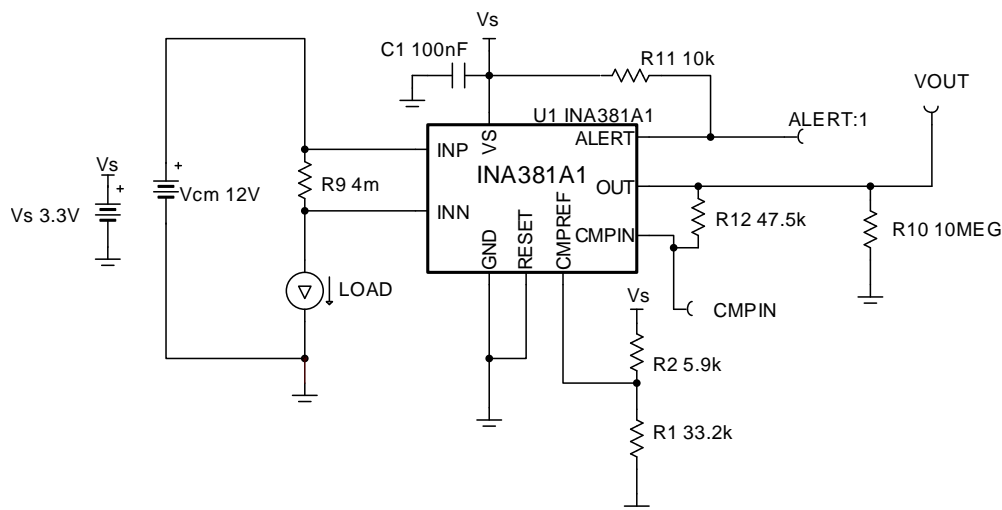

Design Notes

1. Use low-tolerance, high-precision resistors if using a voltage divider for CMPREF and consider buffering the voltage. Otherwise consider using a low-dropout regulator (LDO), reference or buffered reference voltage circuit to supply the CMPREF.
2. Use decoupling capacitors to ensure the device supply is stable, such as C1. Also place the decoupling capacitor as close to the device pin as possible.

Design Steps

1. Calculate the R_{shunt} value given 20V/V gain. Use the nearest standard value shunt, preferably lower than the calculated shunt to avoid railing the output prematurely .

$$R_{\text{shunt}} = \frac{V_{\text{out max}}}{\text{gain} \times I_{\text{max}}} = \frac{V_S - 0.02V}{\text{gain} \times I_{\text{max}}} = \frac{3.3V - 0.02V}{20V/V \times 40A} = 0.0041\Omega$$

$$R_{\text{standard shunt}} = 4m\Omega \text{ (standard 1\% value)}$$

2. Determine the voltage at the current shunt monitor output for the overcurrent threshold.

$$V_{\text{out}_35A} = I_{\text{OC_TH}} \times R_{\text{standard shunt}} \times \text{gain} = 35A \times 4m\Omega \times 20V/V = 2.8V$$

3. Choose a standard resistor value for R_1 and solve for R_2 .

A resistor with kilo-ohm resistance or higher is desired to minimize power loss. Through calculation, 33.2k Ω and 5.9k Ω were chosen for resistances R_1 and R_2 .

$$R_2 = \left(\frac{V_S}{V_{\text{out}_35A}} - 1 \right) \times R_1 = \left(\frac{3.3V}{2.8V} - 1 \right) \times 33.2k\Omega = 5.9k\Omega$$

4. Calculate the resistance (R_{Hyst}) required for the proper hysteresis.

$$R_{\text{Hyst}} = \frac{V_{\text{out}_35A} - (I_{\text{Release_TH}} \times R_{\text{standard shunt}} \times \text{gain} + V_{\text{Hyst_def}})}{I_{\text{Hyst}}}$$


$$R_{\text{Hyst}} = \frac{2.8V - (32A \times 4m\Omega \times 20V/V + 50mV)}{4\mu A} = 47.5k\Omega$$

Design Simulations

Transient Simulation Results

Considering **error**, V_{out_OC} is expected to be approximately 2.8V, while $V_{out_release}$ is expected to be approximately 2.61V.

High-Side OCP Simulation Results

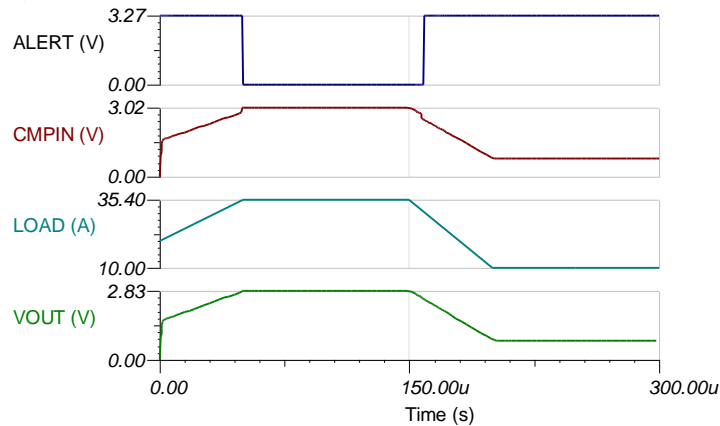

The device exhibits an active low on the Alert pin when the load reaches 35A and re-asserts Alert to high when the load drops below 32A. If the user zooms in and looks at the VOUT voltage, and accounts for an expected propagation delay of 0.4 μ s, the device output is 2.69V at I_{OC_TH} , which only has an error of 0.39% with respect to the ideal output of 2.8V. At $I_{release_TH}$, the alert re-asserts to high when the output dropped to 2.58V, which only has an error of 1.15% with respect to the ideal output of 2.61V.

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Key files for Overcurrent Protection Circuit:

Source files for this design:

[High-Side OCP Tina Model](#)

[Low-Side OCP Tina Model](#)

Getting Started with Current Sense Amplifiers video series:

<https://training.ti.com/getting-started-current-sense-amplifiers>

Design Featured Current Sense Amplifier

INA381	
V_S	2.7V to 5.5V
V_{CM}	GND-0.3V to 26V
V_{OUT}	GND+5 μ V to V_S -0.02V
V_{OS}	\pm 100 typical
I_q	250 μ A typical
I_B	80 μ A typical
http://www.ti.com/product/INA381	

Design Alternate Current Sense Monitor

	INA301	INA302	INA303
V_S	2.7V to 5.5V	2.7V to 5.5V	2.7V to 5.5V
V_{CM}	GND-0.3V to 40V	-0.1V to 36V	-0.1V to 36V
V_{OUT}	GND+0.02 to V_S -0.05V	GND+0.015 to V_S -0.05V	GND+0.015 to V_S -0.05V
V_{OS}	Gain Dependent	Gain Dependent	Gain Dependent
I_q	500 μ A typical	850 μ A typical	850 μ A typical
I_B	120 μ A typical	115 μ A typical	115 μ A typical
Comparator	Single Comparators	Dual Comparators	Window Comparators
	http://www.ti.com/product/INA301	http://www.ti.com/product/INA302	http://www.ti.com/product/INA303

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated