

Flexible Voltage-Level Translation With CBT Family Devices

SCDA006
July 1999



IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.

Abstract

Voltage translation between buses with incompatible logic levels can be accomplished using Texas Instruments (TI™) translation-voltage clamps (TVC) or standard crossbar technology (CBT) devices. CBT devices in this application offer flexibility in designs, protection of circuits that are sensitive to high-state voltage-level overshoots, and cost efficiency.

Introduction

In designing electronics systems, proper interfaces between buses with incompatible logic levels must be provided. Voltage-level translation is necessary to allow the interconnection with flexibility to provide a future migration path to lower-voltage input/output (I/O) levels (see Figure 1). TI offers I/O voltage translation solutions with two device families.

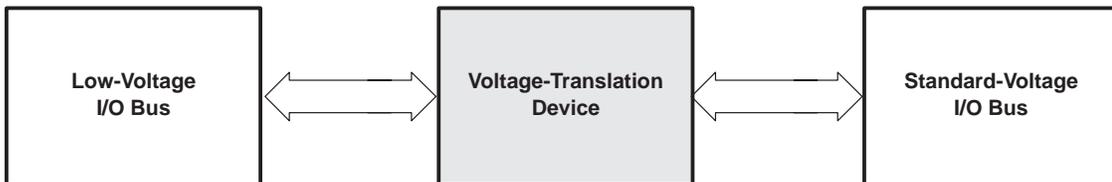


Figure 1. Flexible Voltage-Translation Application

One possible solution for flexible voltage translation is the TI translation-voltage clamp (TVC) family that has been designed specifically for protecting sensitive I/Os (see Figure 2). The information in the data sheet for each TVC-family device describes the I/O protection application of the TVC family and should enable the design engineer to successfully implement an I/O protection circuit utilizing the TI TVC solution.

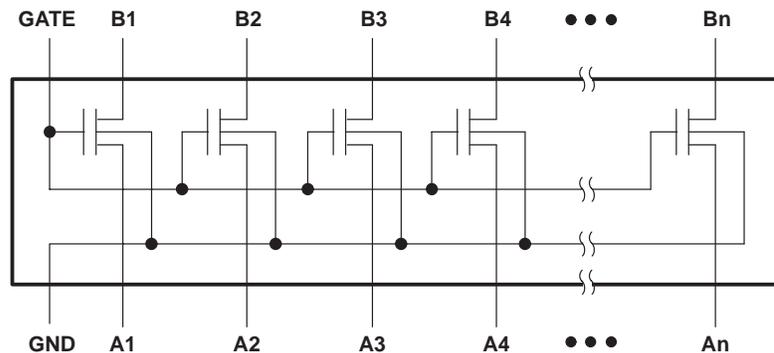


Figure 2. Simplified Schematic of a Typical TVC-Family Device

A comparable solution, allowing cost-effective and flexible voltage translation implemented with standard crossbar technology (CBT) family devices is described in this application report.

Device Description

The CBT family of devices provides an array of n-type metal-oxide semiconductor (NMOS) field-effect transistors (FETs) with the gates cascaded together to a control circuit (see Figure 3). Within a CBT device, all of the transistors are fabricated at the same time on one integrated die. This leads to a very small fabrication-process variation in the characteristics of the transistors. Because, within the device, the characteristics from transistor-to-transistor are the same, there is minimal deviation from one output to another. This is a large benefit of the CBT solution over discrete devices.

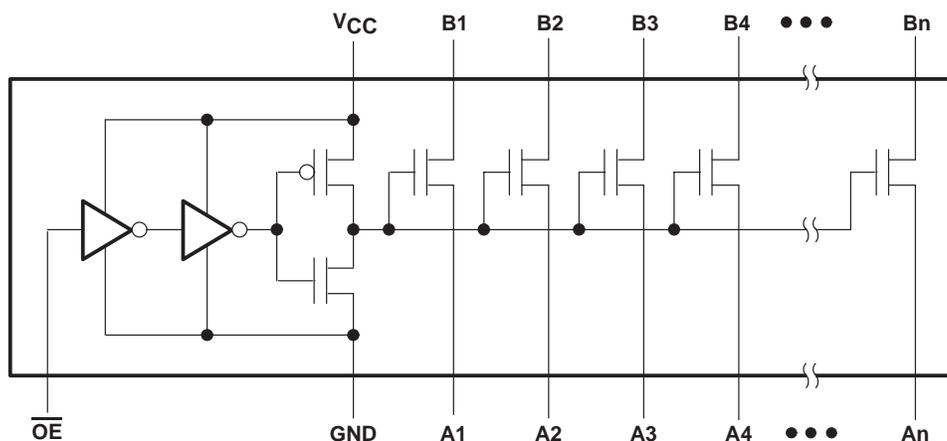


Figure 3. Simplified Schematic of a Typical CBT-Family Device

A CBT device can be used as a voltage limiter or voltage translator by connecting one of the FETs as a reference transistor, and the remainder as pass transistors. The most positive voltage on the low-voltage side of each pass transistor is limited to a voltage set by the reference transistor. All of the transistors in the array have the same electrical characteristics; therefore, any one of them can be used as the reference transistor. Because the transistors are fabricated symmetrically and the I/O signals are bidirectional through each FET, either port connection of each bit can be used as the low-voltage side.

Application

When the active-low, output-enable (\overline{OE}) input is connected directly to ground, the gate of the p-channel FET in the final inverter of the control circuitry is grounded. This saturates the p-channel, turning the FET on hard, and effectively connects the V_{CC} input directly to the gates of the n-channel pass transistors, thus providing external control of the gate voltage.

For the example in Figure 4, the ASIC has an open-drain interface that is sensitive to high-state voltages. For the voltage-limiting configuration, the CBT \overline{OE} input must be grounded. The V_{CC} input must be connected to one side (A or B) of any one of the transistors. This connection determines the V_{BIAS} input of the reference transistor. The V_{BIAS} input is connected through a pullup resistor (typically 200 k Ω) to the V_{DD} supply. A filter capacitor on V_{BIAS} is recommended. The opposite side is used as the reference voltage (V_{REF}) connection. The V_{REF} input must be less than $V_{BIAS} - 1$ V to bias the reference transistor into conduction. The reference transistor regulates the V_{BIAS} , thus gate voltage (V_G) of all the pass transistors. The gate voltage is determined by the characteristic gate-to-source voltage difference (V_{GS}) because $V_G = V_{REF} + V_{GS}$. The low-voltage side of the pass transistors has a high-level voltage limited to a maximum of $V_G - V_{GS}$, or V_{REF} . A weak pulldown resistor on open-drain outputs ensures that when the output switches off (logic high), overshoots do not cause the voltage to exceed the maximum voltage rating.

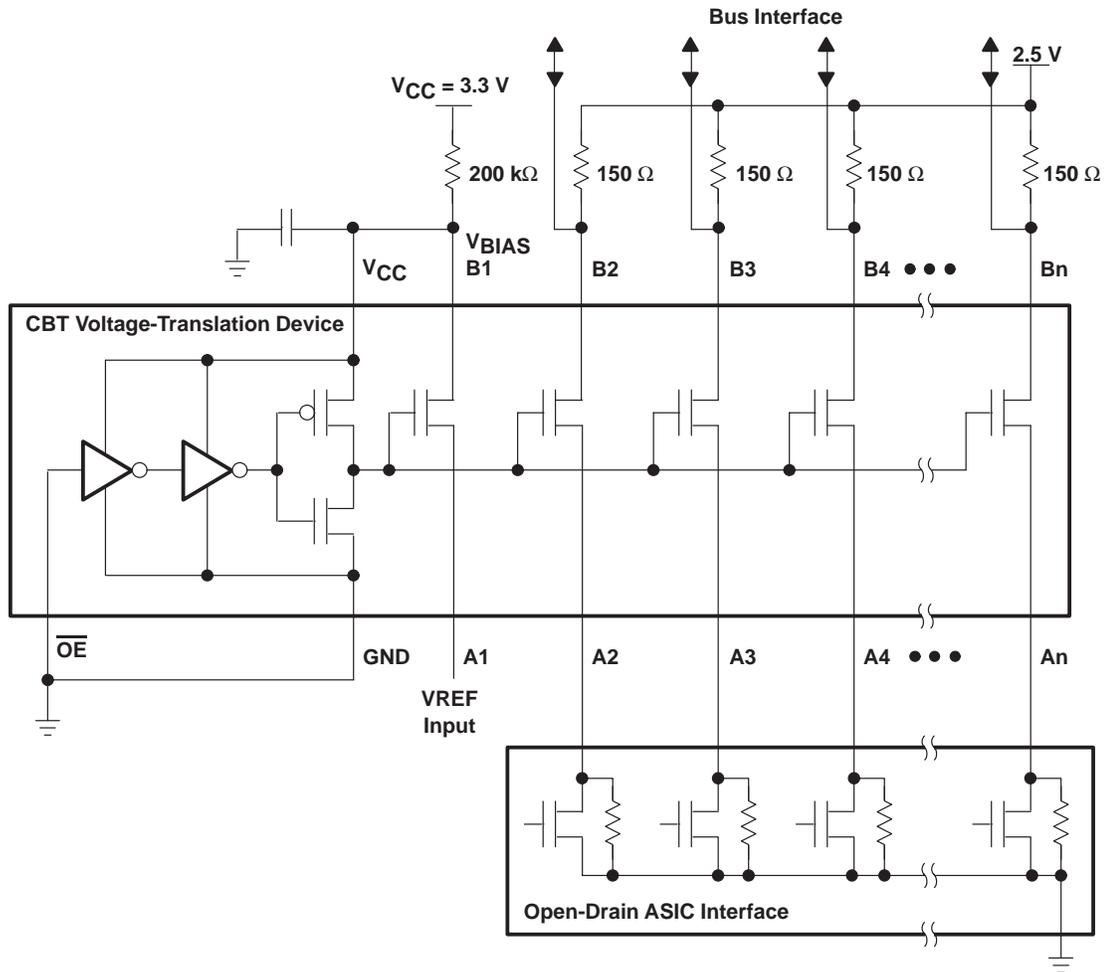


Figure 4. Typical Application of CBT as a Voltage-Translation Device

Conclusion

TI offers a line of CBT devices, including standard, Widebus™, dual-bit, and single-bit functions. The flexibility of CBT enables a low-voltage migration path for advanced designs to align with existing industry standards. The TI CBT family provides the designer with a solution for voltage-level translation and protection of circuits with I/Os that are sensitive to high-state-voltage-level overshoots.

Acknowledgment

The authors of this application report are Thomas V. McCaughey, Stephen M. Nolan, and John D. Pietrzak.