

Factors Affecting V_{OL} for TXS and LSF Auto-bidirectional Translation Devices

Shreyas Rao, Adrian Ozer

ABSTRACT

The TXS and LSF families of translators differ from other translator families, because their outputs are not driven by buffers. Instead, the TXS and LSF families use internal or external pullup resistors to drive logic high, and an internal pass transistor that lets the host device to drive logic low. This results in a V_{OL} (Logic low output voltage) level that is a function of V_{IL} (Logic low Input voltage), the resistance of the internal pass transistor, and the current through the pass transistor. In [Section 1](#) and [Section 2](#), the relationship between V_{OL} , V_{IL} , pass transistor resistance and the pass transistor current are examined in detail for the TXS and LSF families of passive auto-bidirectional translators.

Contents

1	V_{OL} Versus V_{IL} of TXS Type Translators	2
1.1	Summary for V_{OL} Versus V_{IL} of TXS Type Translators	3
2	V_{OL} Versus V_{IL} of LSF Type Translators	4
2.1	Summary for V_{OL} Versus V_{IL} of LSF-Type Translators	5
3	References	5

List of Figures

1	Simplified TXS Architecture	2
2	TXS0101 V_{OL} Versus V_{IL}	3
3	TXS0108E V_{OL} Versus V_{IL}	3
4	LSF010x Simplified Architecture.....	4
5	LSF0108 V_{OL} Versus V_{IL}	4

1 V_{OL} Versus V_{IL} of TXS Type Translators

The internal architecture of the TXS family of translators contains a pass transistor, internal pullup resistors on both the I/O ports, and One-shot edge accelerator circuitry. Figure 1 shows a simplified diagram of this internal architecture. For more information, see the [A Guide to Voltage Translation With TXS-Type Translators](#) application report.

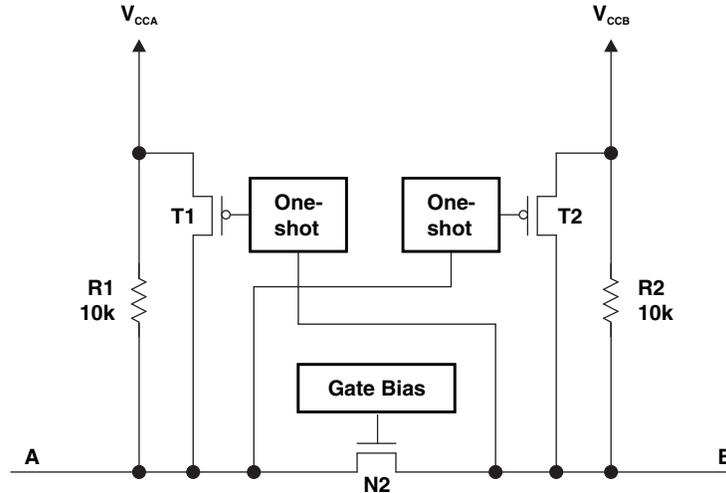


Figure 1. Simplified TXS Architecture

The pass transistor bias voltage, V_{BIAS} , is referenced to V_{CCI} , the input side supply voltage. When the voltage on one of the I/O lines drops below the threshold of the gate bias voltage, V_{BIAS} , the pass transistor turns on and the input tracks the output. In general, when the pass transistor stops conducting the voltage is roughly equal to [Equation 1](#).

$$\frac{V_{CCI}}{2} \quad (1)$$

When the pass transistor is on, the output voltage is equal to the input voltage plus the voltage drop across the pass transistor. Therefore, as the current increases, the output voltage also increases, even with a constant input voltage. Likewise, if the input voltage increases, the output voltage also increases, even with a constant current. This implies that the V_{OL} voltage level is a function of the V_{IL} voltage level and the current flowing through the pass transistor.

Figure 2 and Figure 3 show this relationship, where V_{OL} is plotted against V_{IL} at various current levels for the TXS0108E and TXS0101 voltage translators.

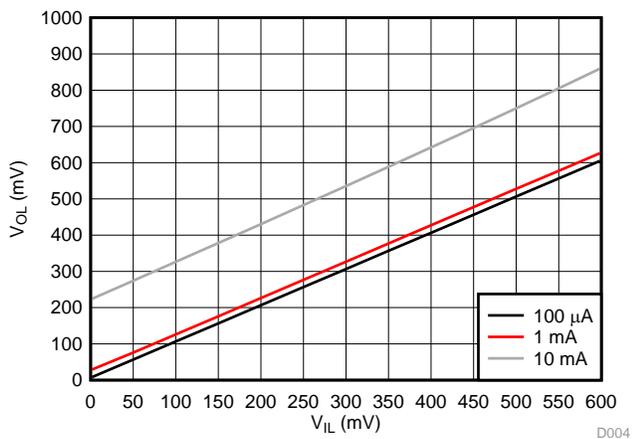


Figure 2. TXS0101 V_{OL} Versus V_{IL}

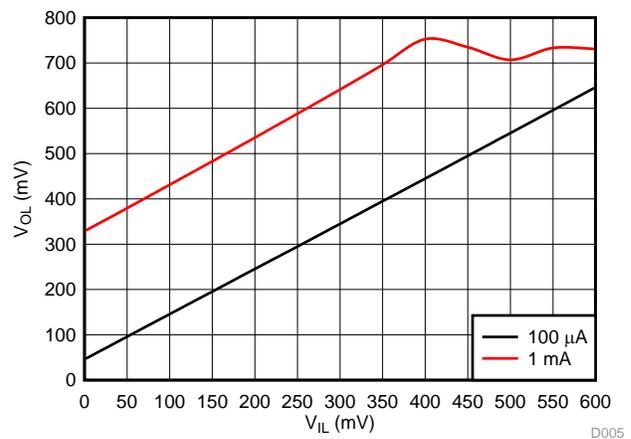


Figure 3. TXS0108E V_{OL} Versus V_{IL}

As shown in Figure 2 and Figure 3, there is a linear relationship between V_{OL} and V_{IL} as long as the current remains constant and the voltage at the output does not exceed the threshold voltage of the pass transistor. The TXS0101 can maintain a reasonable V_{OL} , with up to 10 mA of current through the pass transistor with the input at 0 V. However, the TXS0108E device cannot maintain a reasonable V_{OL} for current levels above 1 mA. With 1 mA through the pass transistor, the TXS0108E device also begins to oscillate at the output as the input voltage reaches 400 mV, because the output voltage begins to exceed the threshold voltage of the pass transistor. At 100 μ A, the TXS0101 and TXS0108E devices can both maintain a V_{OL} under 50 mV with V_{IL} at 0 V.

1.1 Summary for V_{OL} Versus V_{IL} of TXS Type Translators

When driving the line low, the voltage at the output is equal to Equation 2.

$$V_{OL} = V_{IL} + I_{OL} \times R_{pass}$$

where

- R_{pass} is the on-state resistance of the pass transistor.
- I_{OL} is the current flowing through the pass transistor.

Therefore, to maintain the lowest possible V_{OL} two practices must be observed. First, the V_{IL} must be kept as close as possible to 0 V, and second, the current through the pass transistor must be kept as low as possible. To prevent excessive current through the pass transistor, strong external pullup resistors of less than 50 k Ω must be avoided. The effects of external resistors are described in the [Effects of External Pullup and Pulldown Resistors on TXS and TXB Devices](#) application report.

2 V_{OL} Versus V_{IL} of LSF Type Translators

Like the **TXS** family, the **LSF** family also contains a pass transistor that conducts when driving the line low. The LSF family differs in that there are no internal pullup resistors; however, the behavior of the pass transistor is identical with the exception of the pass transistor gate reference, which is supplied by the EN pin, as shown in **Figure 4**. See the [Voltage Translation With the LSF Family](#) application report, watch the [LSF Logic Minute](#) videos to understand more about the LSF device operation and its applications.

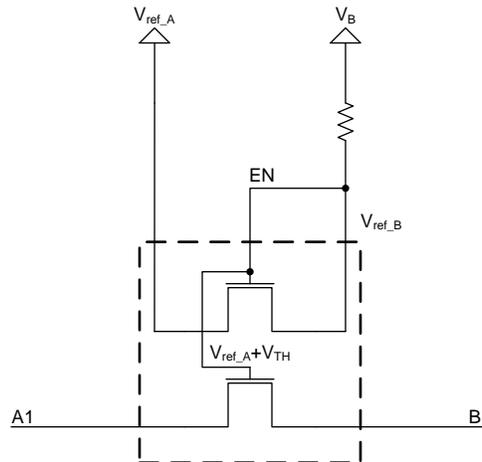


Figure 4. LSF010x Simplified Architecture

When the pass transistor is on, the output voltage is equal to the input voltage plus the voltage drop across the pass transistor. Therefore, as the current increases, the output voltage also increases, even with a constant input voltage. Likewise, if the input voltage increases, the output voltage also increases, even with a constant current. This implies that the V_{OL} voltage level is a function of the V_{IL} voltage level and the current flowing through the pass transistor. **Figure 5** shows this relationship, where V_{OL} is plotted against V_{IL} at various current levels for the **LSF0108** device.

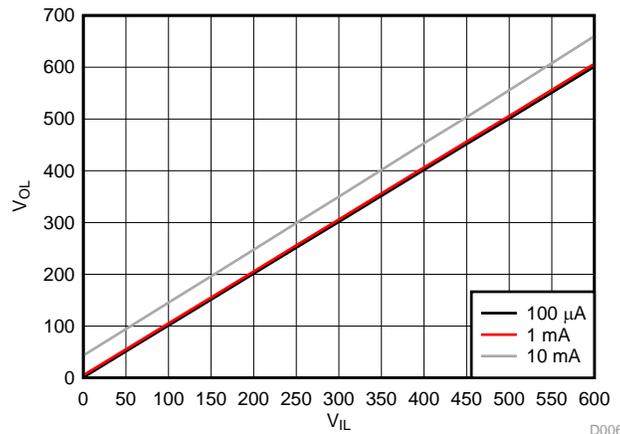


Figure 5. LSF0108 V_{OL} Versus V_{IL}

As shown in **Figure 5**, there is a linear relationship between V_{OL} and V_{IL} , given a constant current. The LSF translators can maintain a V_{OL} less than 100 mV, even at 10 mA, indicating a lower on-state resistance of the pass transistor when compared to the TXS family of translators.

2.1 Summary for V_{OL} Versus V_{IL} of LSF-Type Translators

When driving the line low, the voltage at the output is equal to [Equation 3](#).

$$V_{OL} = V_{IL} + I_{OL} \times R_{pass}$$

where

- R_{pass} is the on-state resistance of the pass transistor.
- I_{OL} is the current flowing through the pass transistor. (3)

Therefore, to maintain the lowest possible V_{OL} two practices must be observed. First, V_{IL} must be kept as close as possible to 0 V. Second, the current through the pass transistor must be kept as low as possible.

3 References

- Texas Instruments, [Basics of Voltage-Level Translation](#), application report
- Texas Instruments, [Voltage Translation With the LSF Family](#), application report
- Texas Instruments, [A Guide to Voltage Translation With TXB-Type Translators](#), application report
- Texas Instruments, [A Guide to Voltage Translation With TXS-Type Translators](#), application report
- Texas Instruments, [Effects of External Pullup and Pulldown Resistors on TXS and TXB Devices](#), application report

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated