

Loop-powered 4- to 20-mA transmitter circuit


Garrett Satterfield

Design Goals

Loop Supply Voltage	DAC Output Voltage	Output Current	Error
12V–36V	0V–3V	4mA–20mA	<1% FSR

Design Description

The loop powered current transmitter regulates the current in series loop consisting of the power supply, transmitter, and load resistance. The active circuitry in the transmitter derives power from the loop current, meaning the current consumption of all devices must be less than the zero-scale current, which can be as low as 3.5mA in some applications. A regulator steps down the loop voltage to supply the DAC, op amp and additional circuitry. The op amp biases the transistor to regulate the current flowing from Loop+ to Loop-. The circuit is commonly used in [2-wire field sensor-transmitters](#) such as [Flow Transmitters](#), [Level Transmitters](#), [Pressure Transmitters](#), and [Temperature Transmitters](#).

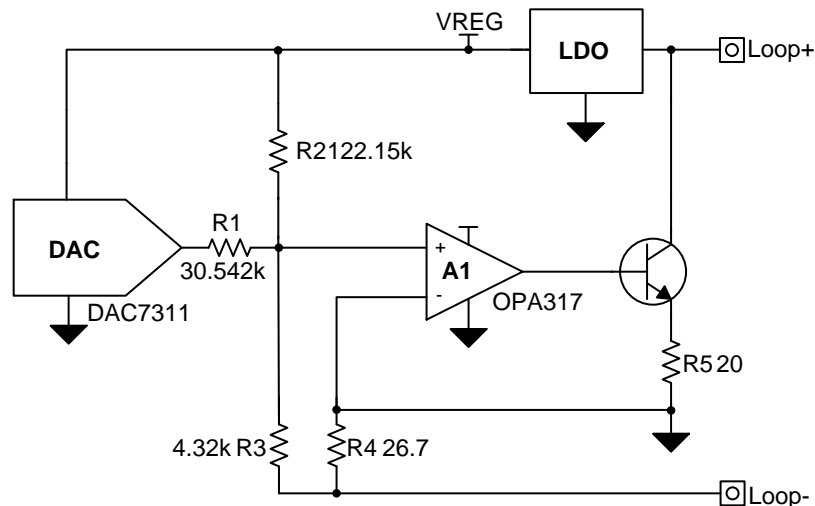

Design Notes

1. Select a single channel DAC with the required resolution and accuracy for the application. Use an op amp with low offset and low drift to minimize error.
2. Select a low power DAC, op amp, and voltage regulator to ensure a total sensor-transmitter quiescent current of less than 4mA.
3. Minimize current flow through R1, R2, and R3 by selecting a large ratio of R3/R4 to minimize thermal drift of the resistors.
4. Use precision low drift resistors for R1-R4, R7-R8 to minimize error.
5. Use a voltage regulator with a wide input voltage range and low dropout voltage to allow for a wide range of loop supply voltages.

Design Steps

The output current transfer function is:

$$I_{OUT} = \left(\frac{V_{DAC}}{R1} + \frac{V_{REG}}{R2} \right) \left(\frac{R3}{R4} + 1 \right)$$

1. Select a large ratio of R3/R4:

$$\frac{R3}{R4} = \frac{4.32k\Omega}{26.7\Omega}$$

2. Calculate R2 based on the zero-scale current (4mA), regulator voltage, and gain ratio (R3/R4).

$$R2 = \frac{V_{REG}}{I_{OUT,ZS}} \left(\frac{R3}{R4} + 1 \right) = \frac{3V}{4mA} \left(\frac{4.32k\Omega}{26.7\Omega} + 1 \right) = 122.10k\Omega$$

3. Calculate R1 to set the full-scale current based on the full-scale DAC voltage and current span of 16mA.

$$R1 = \frac{V_{DAC,FS}}{I_{OUT,SPAN}} \left(\frac{R3}{R4} + 1 \right) = \frac{3V}{16mA} \left(\frac{4.32k\Omega}{26.7\Omega} + 1 \right) = 30.524k\Omega$$


4. Calculate the zero-scale output current based on the chosen resistance values.

$$I_{OUT,ZS} = \frac{V_{REG}}{R2} \left(\frac{R3}{R4} + 1 \right) = \frac{3V}{122.15k\Omega} \left(\frac{4.32k\Omega}{26.7\Omega} + 1 \right) = 3.9983mA$$


5. Calculate the full-scale current based on the chosen resistor values.

$$I_{OUT,FS} = \left(\frac{V_{DAC}}{R1} + \frac{V_{REG}}{R2} \right) \left(\frac{R3}{R4} + 1 \right) = \left(\frac{3V}{30.542k\Omega} + \frac{3V}{122.15k\Omega} \right) \left(\frac{4.32k\Omega}{26.7\Omega} + 1 \right) = 19.9891mA$$

DC Transfer Characteristic

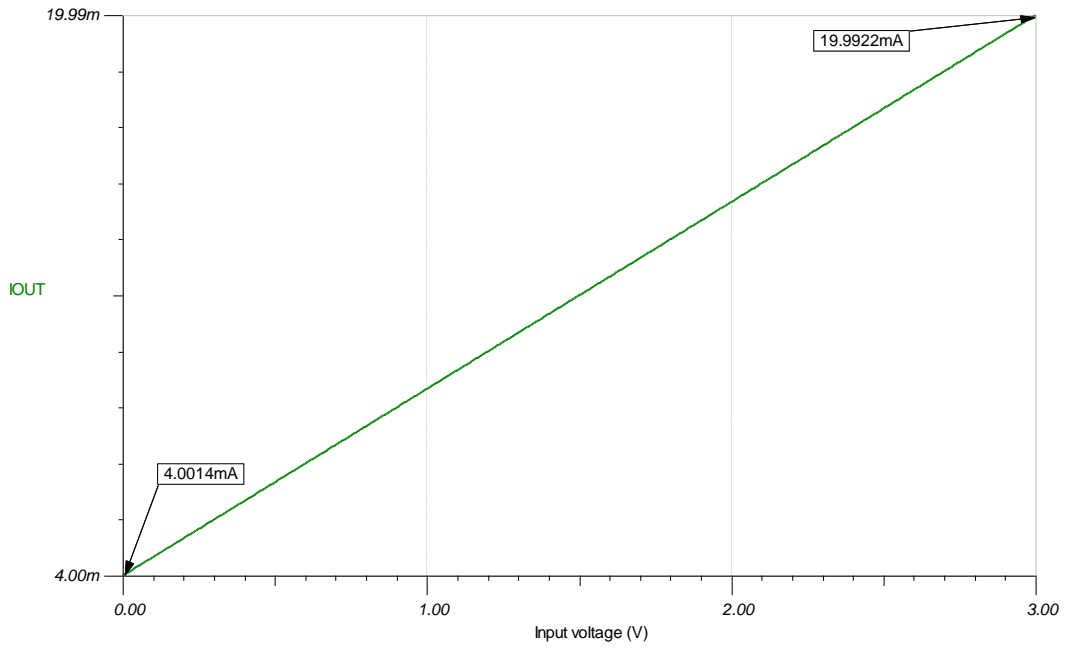

Small Signal Step Response

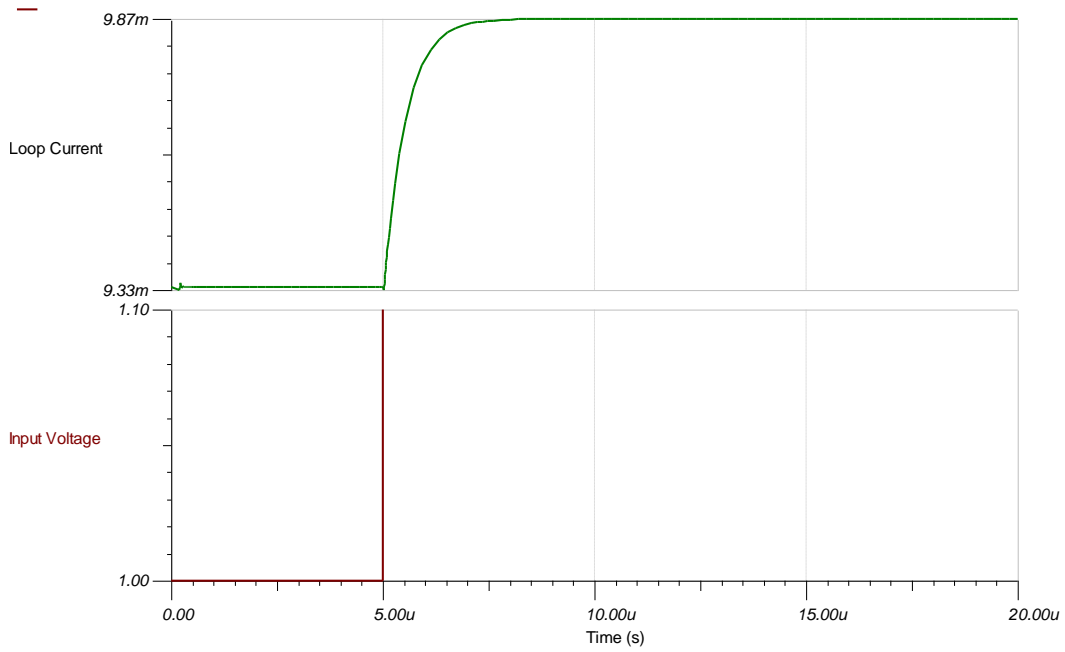

Devices

Device	Key Features	Link	Other Possible Devices
DACs			
DAC7311	12-bit resolution, single channel, ultra-low power, 1 LSB INL, SPI, 2V to 5.5V supply	http://www.ti.com/product/DAC7311	http://www.ti.com/dacs
DAC8560	16-bit resolution, single channel, internal reference, low power, 4 LSB INL, SPI, 2V to 5.5V supply	http://www.ti.com/product/DAC8411	http://www.ti.com/dacs
DAC8830	16-bit resolution, single channel, ultra-low power, unbuffered output, 1 LSB INL, SPI, 2.7V to 5.5V supply	http://www.ti.com/product/DAC8830	http://www.ti.com/dacs
DAC161S997	16-bit, 4-20mA current output, 100uA supply current, SPI, 2.7V to 3.3V supply	http://www.ti.com/product/DAC161S997	http://www.ti.com/dacs
Amplifiers			
TLV9001	Low-Power, 0.4mV Offset, Rail-to-Rail I/O, 1.8V to 5.5V supply	http://www.ti.com/product/TLV9001	http://www.ti.com/opamps
OPA317	Zero-Drift, Low-Offset, Rail-to-Rail I/O, 35uA supply current max, 2.5V to 5.5V supply	http://www.ti.com/product/OPA317	http://www.ti.com/opamps
OPA333	microPower, Zero-Drift, Low Offset, Rail-to-Rail I/O, 1.8V to 5.5V supply	http://www.ti.com/product/OPA333	http://www.ti.com/opamps

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

Links to Key Files

TI Designs TIPD158, [Low Cost Loop-Powered 4-20mA Transmitter EMC/EMI Tested Reference Design](#)

TI Designs TIDA-00648, [4-20mA Current Loop Transmitter Reference Design](#)

TI Designs TIDA-01504, [Highly-Accurate, Loop-Powered, 4mA to 20mA Field Transmitter with HART Modem Reference Design](#)

[Source Files for Loop-Powered 4- to 20-mA Transmitter](#) – <http://www.ti.com/lit/zip/slac782>.

For direct support from TI Engineers use the E2E community:

e2e.ti.com

Other Links:

[Precision DAC Learning Center](#)

<http://www.ti.com/data-converters/dac-circuit/precision/overview.html>

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated