

# TPS2350, A High-Negative Voltage ORing Controller

Bob Kando


## ABSTRACT

This application note addresses a method to OR the high side of the power source as well as the low side using N-channel MOSFETs, thus replacing diodes D1 and D2 with more efficient MOSFETs in the high current path. The MOSFET switch of the return current is referred to here as the high side switch. A circuit schematic for high side switching is recommended and component selection discussed. High side switching can be used in ATCA and other Telecom applications.

## 1 Introduction

The TPS2350 is a high-negative voltage ORing controller. Two power supplies are input to the TPS2350 at pins  $-V_{INA}$  and  $-V_{INB}$ , see [Figure 1](#). The more negative voltage is switched to the load by N-channel MOSFETs, Q2 or Q3. The TPS2350 provides hysteric selection of the more negative supply, enabling only one switch, Q2 or Q3. The TPS2350 controls Q1 to ramp the inrush current to the load at power up and provides circuit breaker protection to the load. If the load current exceeds the programmed limit transistor Q1 is disabled.

Diodes, D1 and D2, in the upper left hand side of [Figure 1](#), OR the power supply return currents. These diodes may be replaced with MOSFETs to increase the system's efficiency and eliminate ground loops.

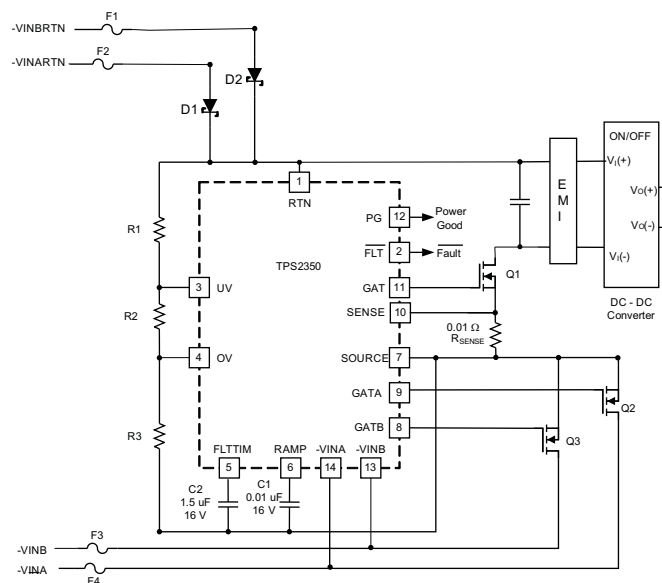

**Figure 1. Typical TPS2350 configuration**


## 2 Description

MOSFET switches, Q4 and Q5, inserted in each return path and controlled by the TPS2490 provide a low resistance current path on the return side. The TPS2350 pins GATA and GATB that select the input power MOSFET, Q2 and Q3 in [Figure 2](#) also select the return path switch, Q4 and Q5, respectively, via the enable pins of the TPS2490 controllers.

### 2.1 High-Side Controller

N-channel MOSFETs, are preferred over P-channel because of the lower  $R_{DS(on)}$  and resultant reduced heat dissipation. The N-channel MOSFET gate requires a positive voltage with respect to its source terminal. The onboard charge pump of the TPS2490 drives the gate voltage well above the source of Q4 and Q5 to fully enhance the MOSFETs. Diodes D1 and D2 provide a low current path to power the TPS2350.

Designed for high-positive voltage systems, the TPS2490 can be used in this application because it doesn't share a ground with external circuits. The hot swap features of the TPS2490 are not used so there is no sense resistor, power limit programming resistors or timing capacitor. [Figure 2](#) shows the TPS2350 ORing controller of [Figure 1](#) modified for high-side switching.

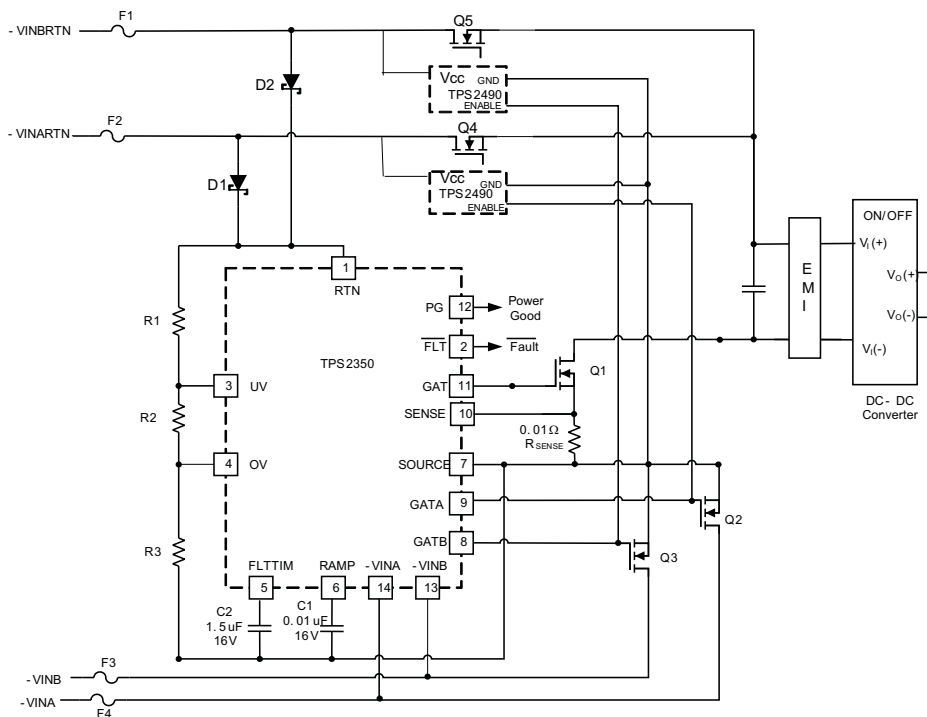

**Figure 2. TPS2350 ORing controller modified for high-side switching**

## 2.2 TPS2490 High-Side Schematic

The detailed schematic of the TPS2490 block in Figure 2 is shown in Figure 3 for the single switch configuration.

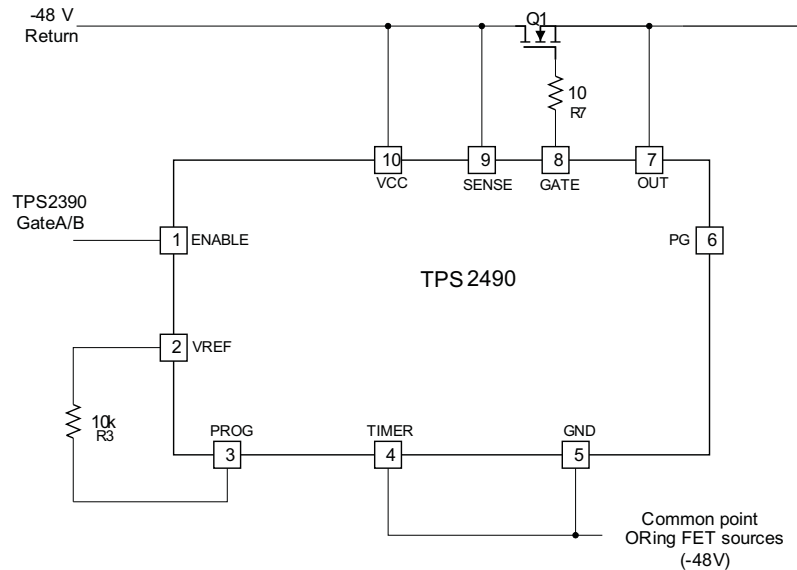


Figure 3. TPS2490 High Side Schematic

### 2.2.1 Back-to-Back MOSFETS

Alternatively, for isolation of the MOSFET body diode, a back-to-back MOSFET configuration may be used, see Figure 4. The TPS2490 OUT pin connects to the MOSFET sources, which allows the TPS2490 to control the MOSFET gate to source voltage.

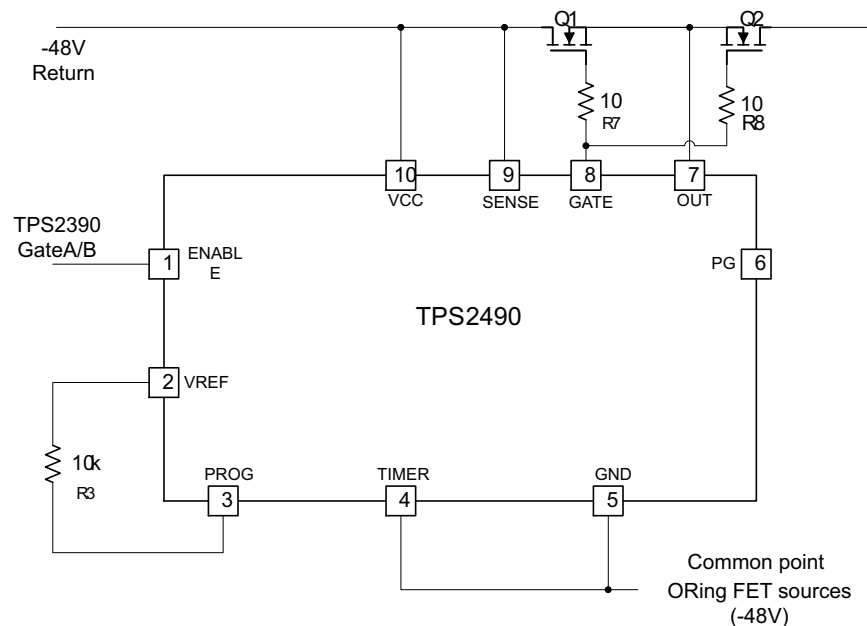


Figure 4. TPS2490 Back-to-Back MOSFET Isolation Schematic

### 3 Electrical Performance

Should the selected power supply fail, the TPS2350 transitions the load to the alternate power supply. During this transition, the voltage across the load drops as the bypass capacitance is discharged by the load current. The longer the time to switchover the power supply the more the load voltage drops. The voltage drop during the switchover time is called a droop. The switchover time can be compensated by bulk or holdup capacitance on the load.

#### 3.1 MOSFET Selection

The MOSFET switch speed is directly related to its gate-to-source charge,  $Q_{GS}$ , listed in the MOSFET datasheet. The switchover time,  $T$ , is the gate to source charge  $Q_{GS}$  divided by the gate drive current,  $I_G$ :

$$T = \frac{Q_{GS}}{I_G} \quad (1)$$

Where the gate to source charge for the IRF530NS is 5.5 nC and the typical gate drive current for the TPS2490 of 22  $\mu$ A, the switchover time  $T$  equals:

$$T = \frac{5.5 \times 10^{-9}}{22 \times 10^{-6}} = 250 \mu s \quad (2)$$

Other factors influencing MOSFET selection are listed in [Table 1](#).

**Table 1. MOSFET Selection Parameters**

PARAMETER	SYMBOL	TYPICAL FOR ATCA
Operating voltage	$V_{DS}$	100 V
Operating current	$I_{DS}$	2 to 3 or more times load current steady state
Gate voltage	$V_{GS}$	+ / - 20 V
Gate threshold	$V_{GS(TH)}$	< 5 V
Gate charge	$Q_{GS}$	As calculated
On resistance	$R_{DS(on)}$	Low to minimize power and heat loss

#### 3.2 Load Bypass Capacitance

Bypass capacitance reduces voltage droop across the load during supply transition. Using the transition time,  $T$ , calculated above, the maximum voltage drop allowed during transition,  $\Delta V$ , and the load current,  $I$ , the required bypass capacitance may be calculated:

$$C \geq \frac{I \times T}{\Delta V} \quad (3)$$

#### 4 Performance Data

The output voltage,  $V_{OUT}$ , at the point where the power supplies transition is shown in Figure 5. In this example, the load is 0.6 A with 300- $\mu$ F bypass capacitance. The IRF530S MOSFET is used in all four switching positions, Q2, Q3, Q4 and Q5, because of its low gate to source charge,  $Q_{GS}$ . The switchover time is less than 0.5 ms and the output droop is about 0.7 V.

Figure 6 shows the output voltage droop for the same load and bulk capacitance as the previous example, however IRFS4710 MOSFETs are used for switching at Q2, Q3, Q4, and Q5. The IRFS4710 gate charge is 43 nC typical. This example is included to demonstrate the importance of  $Q_{GS}$  in MOSFET selection. The 5-ms switchover time for the IRFS4710 allows the load voltage to droop 3.0 V.

Figure 7 and Figure 8 show the IRF530S MOSFET gates when transitioning the power supply between on and standby.

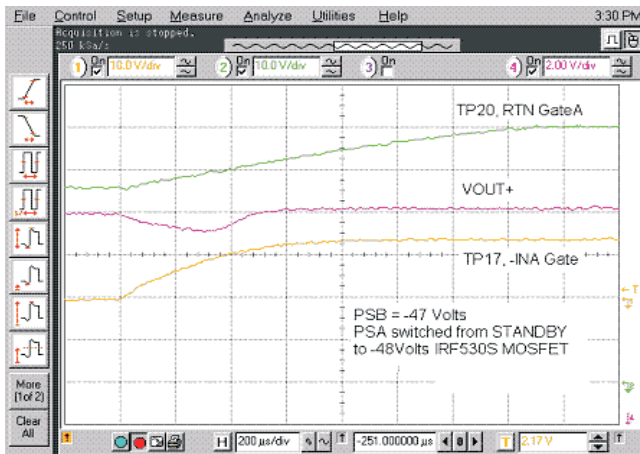


Figure 5.  $V_{OUT}$  at 0.6 A with 300- $\mu$ F bypass capacitance

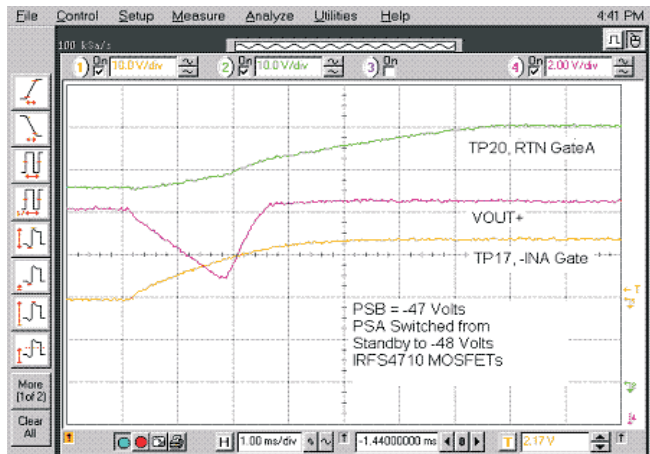


Figure 6. Output Voltage Droop Under Load and Bulk Capacitance

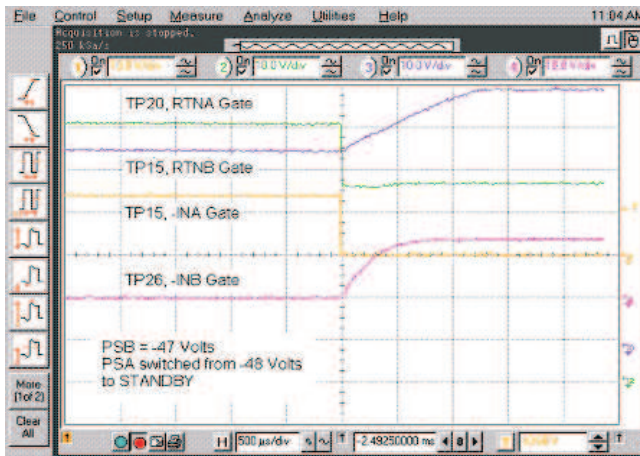


Figure 7. Transitioning the Power Supply Between ON and Standby

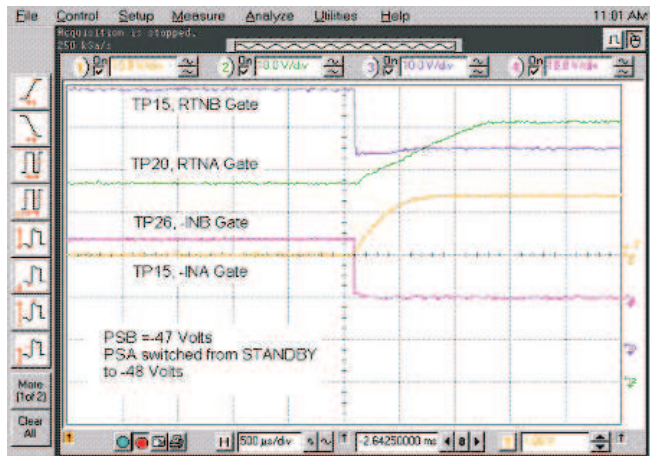


Figure 8. Transitioning the Power Supply Between ON and Standby



## 6 List of Materials

**Table 2. List of Materials**

COUNT	REF DES	DESCRIPTION	MFR	PART NUMBER
2	C1, C3	Capacitor, aluminum, SM, 150 $\mu$ F 20%, 100 V		EEV-FK2A151M
1	C21	Capacitor, ceramic, 1000 pF, 16 V, X7R, 10%		STD
1	C22	Capacitor, ceramic, 1000 pF, 16 V, X7R, 10%		STD
3	C5, C7, C8	Capacitor, ceramic, 0.1 $\mu$ F, 100 V, X7R, 10%,		ECJ-3YB2A104K
1	C6	Capacitor, ceramic, 0.1 $\mu$ F, 16 V, X7R, 10%,		STD
2	D2, D7	Diode, switching, 200 mA, 200 V, 330 mW		BAS21
1	D3	Diode, TVS, 70 V, 600 W		SMBT70A
1	Q3	MOSFET, N-channel, 100 V, 120 A, 0.009 $\Omega$		STB120NF10
4	Q4, Q7, Q14, Q15	MOSFET, N-channel, 100 V, 75 A, 0.014 $\Omega$		IRF530NS
1	R10	Resistor, chip, 10 $\Omega$ , 1/10 W, 1%		Std
2	R11, R16	Resistor, chip, 6.65 k $\Omega$ , 1/10 W, 1%		Std
1	R14	Resistor, chip, 100 $\Omega$ , 1/10 W, 1%		Std
1	R15	Resistor, chip, 0.004 $\Omega$ , W, 1%		WSL-2010.004<1%
1	R2	Resistor, chip, 20 k $\Omega$ , 1 W, 5%, 87		CRCW2512-203J
2	R25, R28	Resistor, chip, 100 k $\Omega$ , 1/10 W, 1%,		Std
1	R3	Resistor, chip, 324 k $\Omega$ , 1/10 W, 1%		Std
2	R33, R37	Resistor, chip, 100 k $\Omega$ , 1/10 W, 1%		Std
1	R5	Resistor, Cchipip, 374 k $\Omega$ , 1/10 W, 1%		Std
1	U1	Device, Hot-Swap Power Manager For Redundant -48 V		TPS2350D
2	U3, U5	Device		TPS2490DGS

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2008, Texas Instruments Incorporated