

LED Driver – Paralleled Outputs Provide High-Current Outputs

Michael Day

PMP - Portable Power DC-DC Applications

ABSTRACT

This application report describes how to use the TLC5922, TLC5923, and TLC5924 to drive high-current LEDs. These ICs are designed to provide 16 individually controllable constant-current sinks. However, the 16 outputs can be connected in parallel to increase the current drive capability. Paralleling the outputs of these ICs allows the TLC5922, TLC5923, and TLC5924 to drive high-power LEDs such as the OSRAM Golden DRAGON™ and LUMILEDS Luxeon series of high-current LEDs.

The Texas Instruments family of TLC5922/23/24 constant-current LED drivers provide up to 80 mA of constant-current sink for driving multiple LEDs. These LED drivers provide features such as a 1% current matching, 7-bit dot correction, controlled inrush current, error detection, and a 30-MHz data bus, and are ideal for applications such as large-screen LED displays, LED signboards, and LED backlighting.

High-current LEDs such as the OSRAM Golden DRAGON™ require up to 500 mA of forward current and provide a high-intensity light output that is used in applications such as automotive lighting, reading lamps, architectural lighting, LCD and TFT backlighting, and marker lights. The TLC5922/23/24 can be configured to provide the higher currents required to drive these types of LEDs. The IC's output stage consists of a current mirror, which closely resembles a constant-current source. As with current sources connected in parallel, the TLC5922/23/24 outputs can be connected in parallel to achieve a higher current drive capability. The total drive current is the sum of the individual drive currents. When connected in parallel, each output can be individually programmed to sink different currents. [Table 1](#) provides examples of the maximum LED drive current with different numbers of paralleled outputs. Note that the maximum LED current is determined by the number of paralleled outputs times 80 mA.

Table 1. Maximum LED Drive Current With Different Numbers of Paralleled Outputs

Paralleled Outputs	LED Current Range (mA)	Number of LEDs per TLC5922/23/24
1	0–80	16
2	0–160	8
3	0–240	5
6	0–480	2
8	0–640	2
16	0–1280	1

Golden DRAGON is a trademark of OSRAM Opto Semiconductors.

Figure 1 shows a TLC5922/23/24 configured to drive four Golden DRAGON white LEDs. Because each output is capable of 80 mA, paralleling four TLC5922/23/24 outputs allows the IC to drive each LED with up to 320 mA. The TLC5923 allows the user to control LED brightness with either analog or PWM dimming. R1 sets the maximum current per channel to 80 mA.

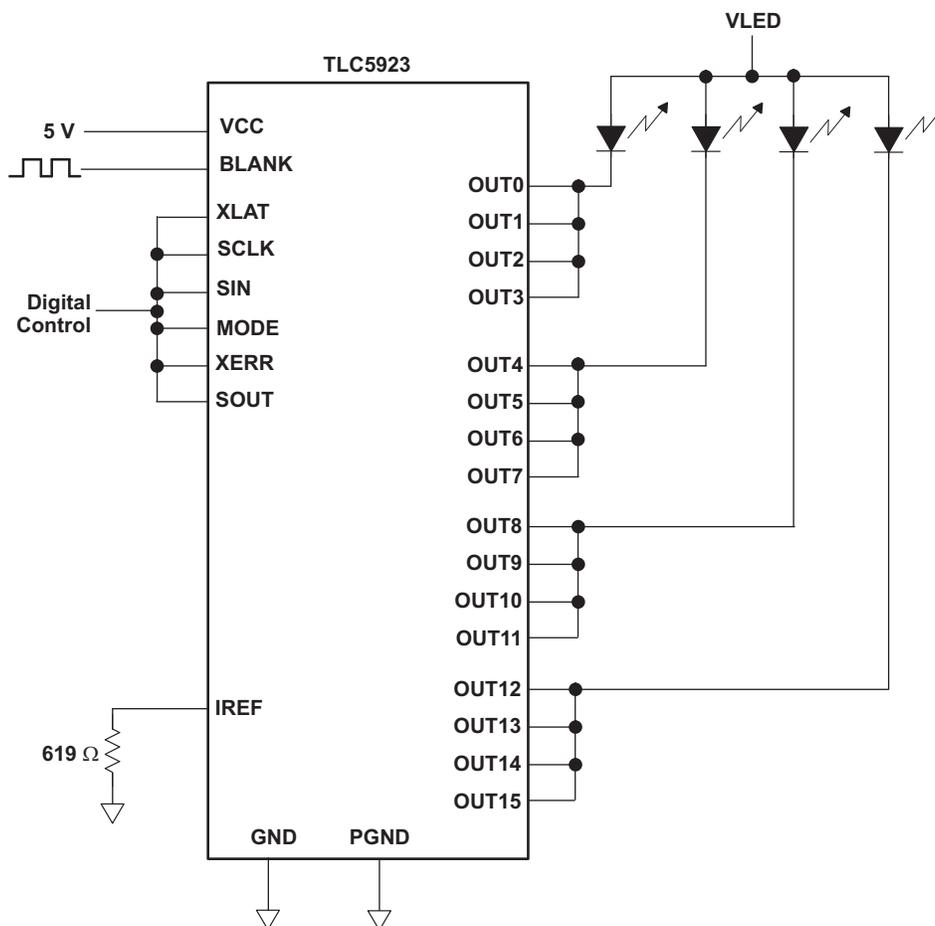


Figure 1. TLC5922/23/24 Configuration Driving Four White LEDs

Figure 2 shows each TLC5922/23/24 output current as well as the total current through D1. The LED current is equal to the sum of the output currents. Each output is programmed with a dot correction value of 127, which drives the full 80 mA per channel. The LED is programmed to full brightness with these settings.

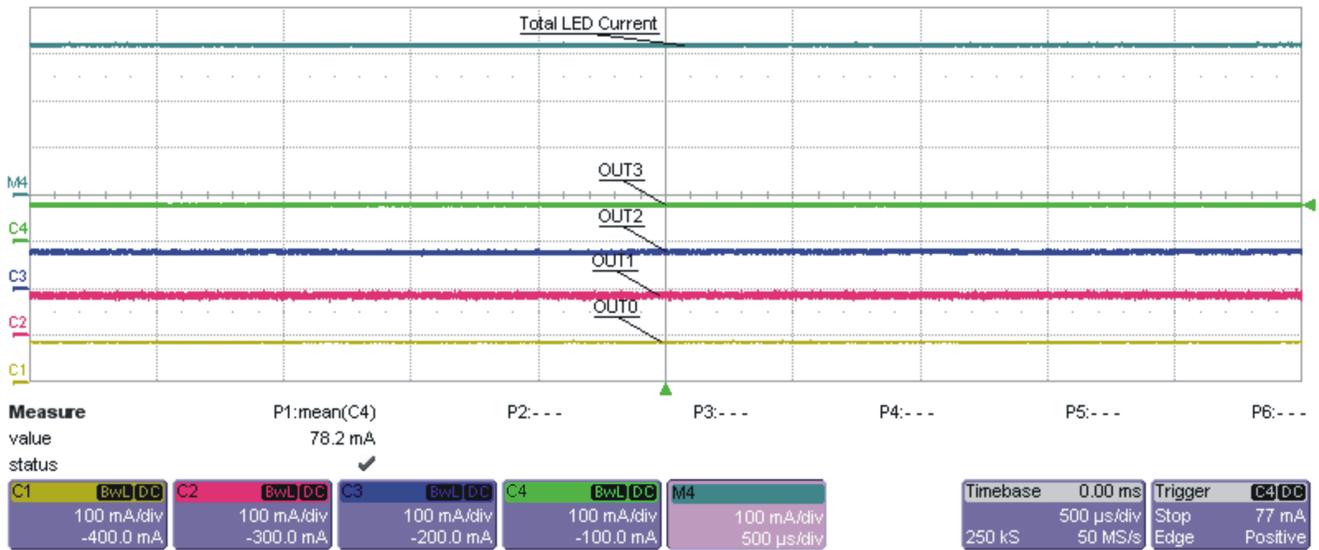


Figure 2. TLC5922/23/24 Output Current and Total Current Through D1

Figure 3 shows the LED programmed to 30% brightness with analog dimming. Using analog dimming, the DC current through the LED is reduced to 30% of the maximum value. Full current is 320 mA; therefore, 30% dimming is achieved by setting the current to $30\% \times 320 \text{ mA} = 96 \text{ mA}$. This is also equivalent to programming each output to 24 mA. Analog dimming with the TLC5922/23/24 is achieved by programming each channel's dot correction to a value less than 127. The correct dot correction value is calculated with Equation 1.

$$\text{Dot Correction} = \frac{I_{\text{out}} \times 127}{I_{\text{max}}} = \frac{24 \text{ mA} \times 127}{80 \text{ mA}} = 38.1 \quad (1)$$

This dot correction value is rounded down to 38.

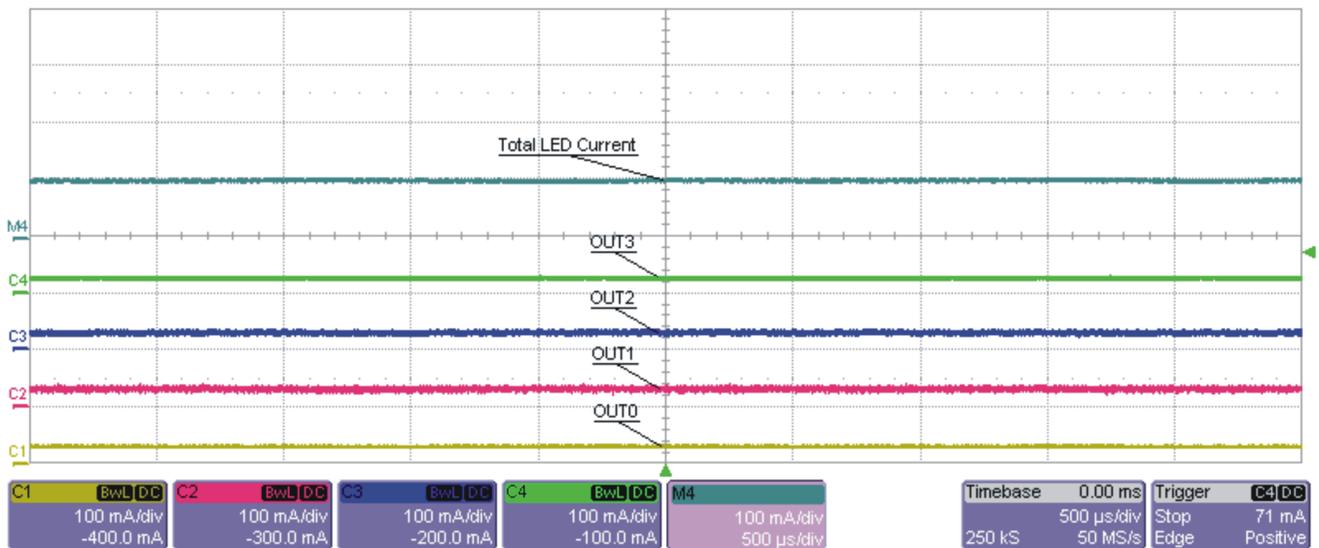


Figure 3. LED Programmed to 30% Brightness

Figure 4 also shows the LED programmed to 30% brightness with analog dimming. In this example, not all output currents are equal: OUT0 = 40 mA, OUT1 = 40 mA, OUT2 = 16 mA, and OUT3 = 0 mA. Each output's dot correction values, which are calculated with Equation 1, are listed as follows.

- OUT0 = 64
- OUT1 = 64
- OUT2 = 25
- OUT3 = 0

This example shows that output currents do not need to be equal to generate the desired LED current. Both analog dimming examples show that the sum of the currents in the paralleled outputs equal the total LED current.

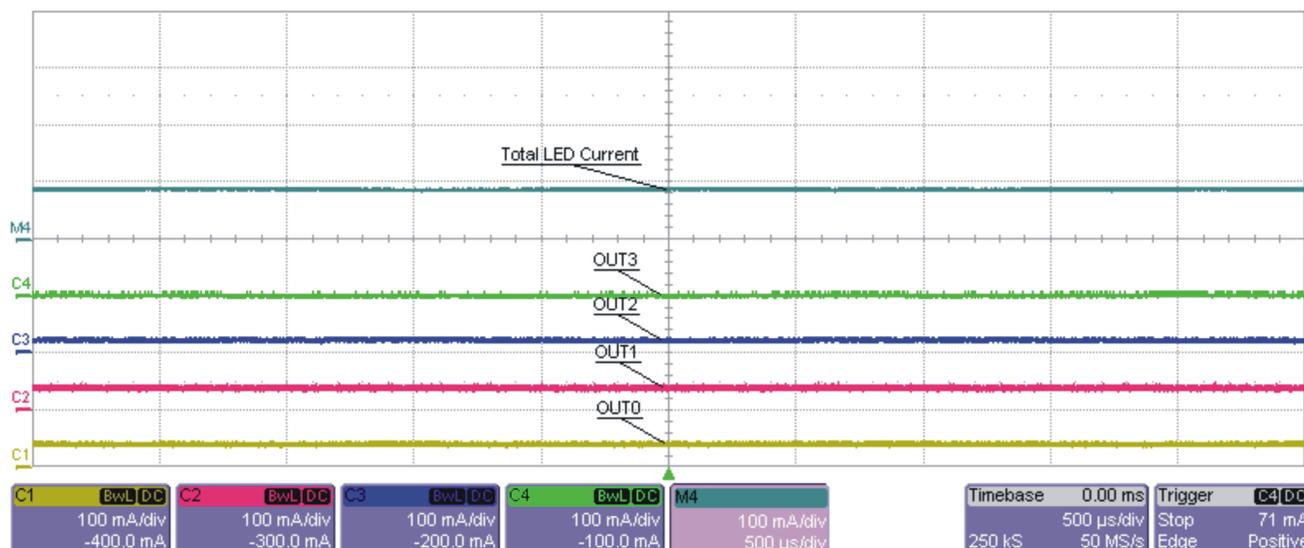


Figure 4. 30% Analog Dimming — Unequal Output Currents

Figure 5 shows the LED programmed to 30% brightness with PWM dimming. PWM dimming is achieved by driving the LED with 100% current for part of the PWM period and with 0% current for the remainder of the period. The ratio of the time with 100% current to the total PWM period is the duty cycle. LED brightness is directly proportional to the duty cycle. PWM dimming with the TLC5922/23/24 is achieved by first programming the dot correction to 127, which sets the outputs to full current. Next, a PWM signal is applied to the BLANK pin to turn the outputs on and off. This drives the LED with 320 mA for part of the time and with 0 mA for the rest of the time. LED brightness is proportional to the duty cycle of the BLANK signal because the human eye averages the pulsed LED brightness. The PWM frequency must be above 60 Hz so that the pulses are not visible to the human eye. Most systems use PWM frequencies between 200 Hz and several kHz. Note that the BLANK signal controls all outputs; so, multiple LEDs cannot be dimmed to a different brightness with PWM dimming. If PWM dimming of multiple LEDs is required, consider using the TLC5940 or TLC5941. These ICs provide both analog and PWM dimming.

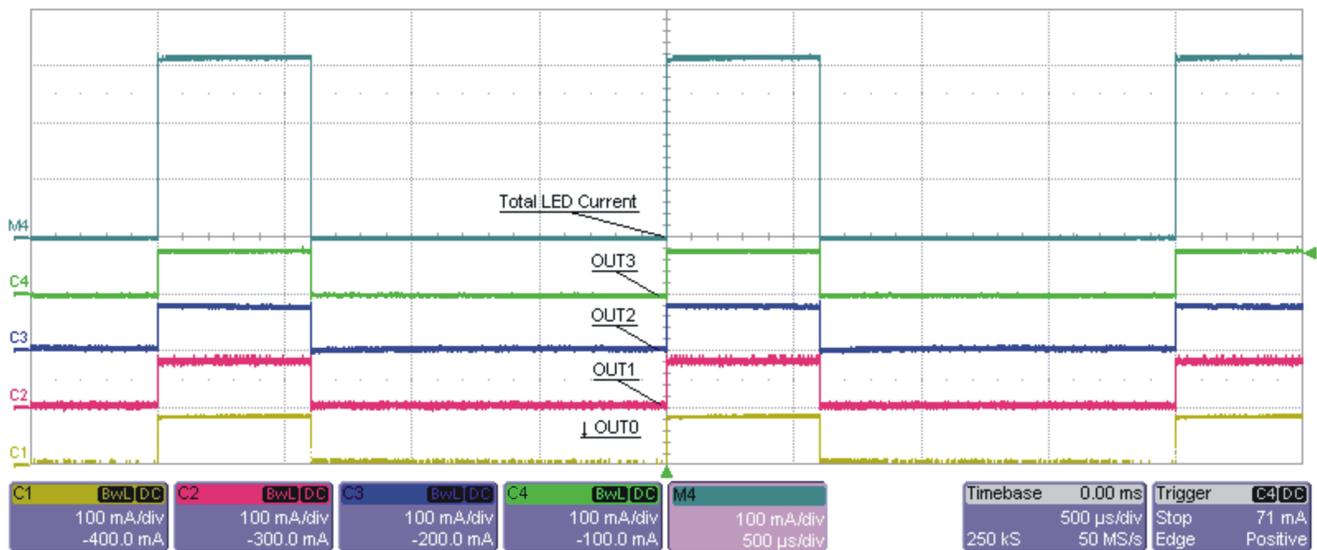


Figure 5. 30% PWM Dimming — 500 Hz

The preceding examples show that the TLC5922/23/24 outputs can be paralleled to achieve higher drive capabilities. They also show the ICs' capability to provide both analog and PWM dimming.

References

1. TLC5922, LED Drive data sheet ([SLVS486](#))
2. TLC5923, 16-Channel LED Driver With Dot Correction data sheet ([SLVS550](#))
3. TLC5924, 16-Channel LED Driver With Dot Correction and Pre-Charge FET data sheet ([SLVS626](#))
4. TLC5924EVM User's Guide ([SLVU187](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265