

Using the bq24650 to Charge a Sealed, Lead-Acid Battery

Jeff Falin, Charles Mauney, Stephen Nortman

PWR - BMS Battery Charge

ABSTRACT

This application report shows how to modify the bq24650 to charge a sealed, lead-acid battery from a solar panel. The circuit uses constant current (CC) charging to reach the bulk battery voltage and then switches to constant voltage (CV) charging until the termination current is reached. The modifications necessary to change the regulated voltage, recharge voltage and regulated current are discussed. The datasheet explains how to configure the MPPSET components, the switching converter active and passive components and other components for the specific application.

Contents

1	Pulse Current Charging	2
2	Circuit to Implement Temperature Compensation	4
3	Design Example	5
4	Test Results	5
5	Circuit to Disable Precharge	6
6	Conclusion	6
7	References	6

List of Figures

1	Algorithm for Pulse Current Charging	2
2	Schematic for Pulse Charging	3
3	Battery Voltage vs Temperature for a 6-cell, Sealed, Lead-Acid Battery	4
4	Measured Results With Circuit Charging a 6-Cell, 2.4-Ahr Battery	6

List of Tables

1	Measured Results using a Source Meter to Simulate a Lead-Acid Battery	6
---	---	---

1 Pulse Current Charging

With some simple modifications, the bq24650 charger, designed specifically for charging Li-ion batteries, can charge lead-acid batteries.

Figure 1 shows the pulse current charging algorithm that is used to charge the sealed lead-acid battery.

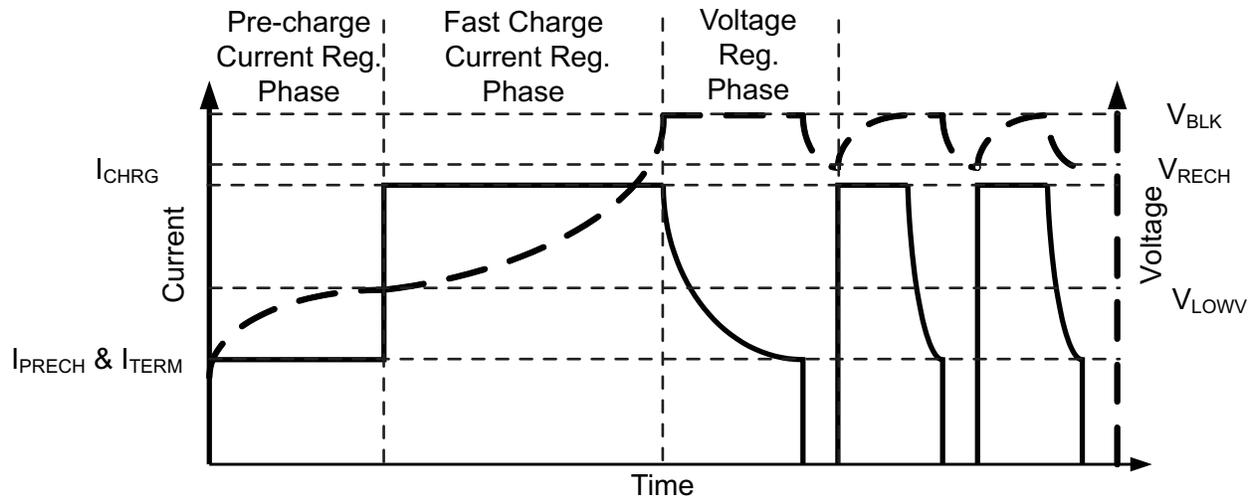


Figure 1. Algorithm for Pulse Current Charging

V_{BLK} is the bulk battery voltage and is the maximum voltage at which the charger regulates. The remaining terms are explained in the bq24650 data sheet ([SLVSA75](#)).

Figure 2 shows the schematic used to implement the algorithm in Figure 1. Five additional components are needed in addition to the typical evaluation module (EVM) circuit. These components, along with the components whose values changed from the EVM circuit, are shown in bold in Figure 2.

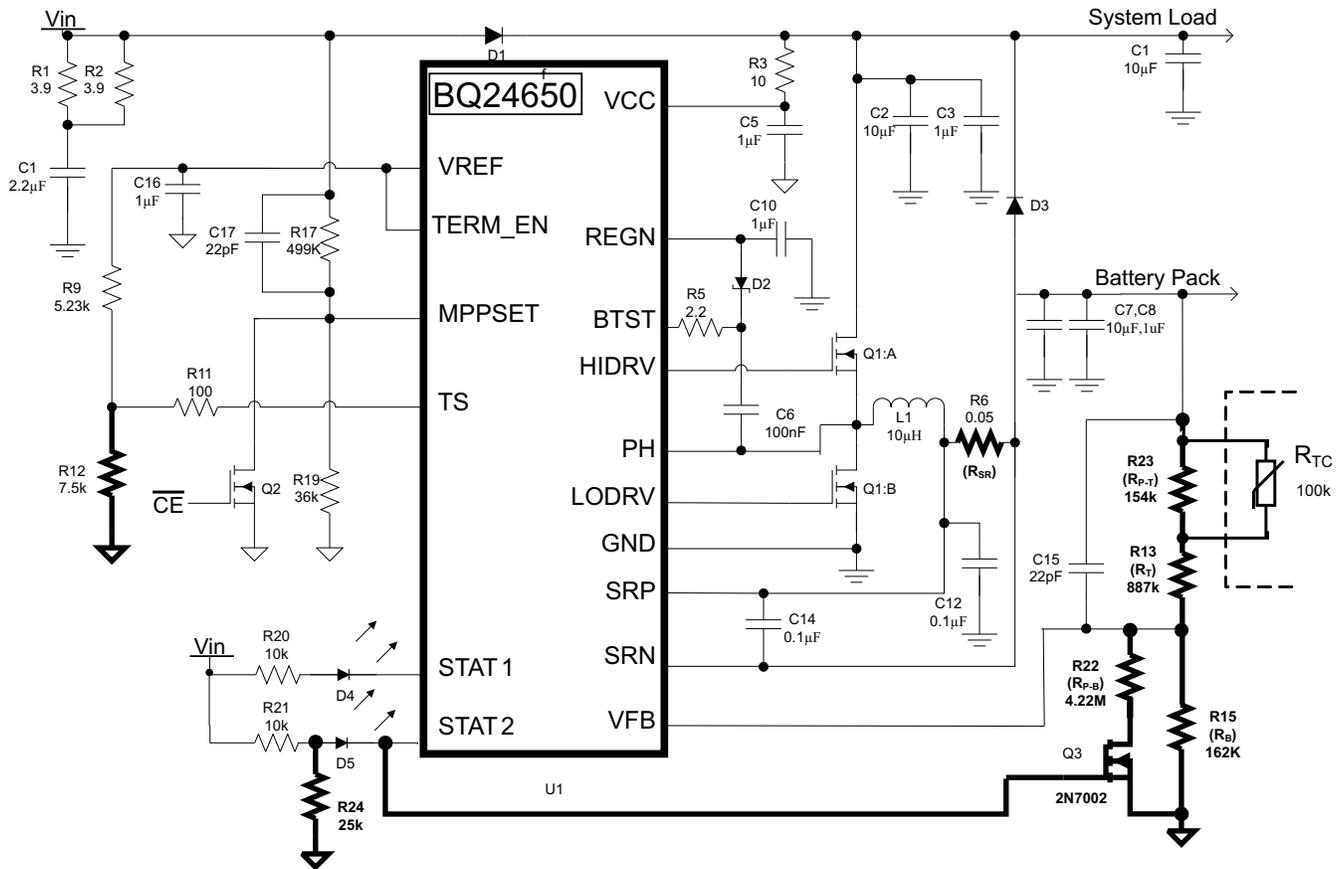


Figure 2. Schematic for Pulse Charging

The charger begins in CC mode and then switches to CV mode. The circuit uses the STAT2 pin, which is pulled high while the battery is charging, to turn on Q3 and increase the charger's CV regulation point to the battery's bulk voltage until the charger senses that the current has tapered off. Normally STAT2 is pulled up to V_{IN} , but to protect the gate of FET Q3, resistor R23 divides down the voltage at STAT2. Once the charging current falls below the termination current threshold, STAT2 goes to low impedance. This causes Q3 to turn off, thus lowering the recharge threshold voltage, V_{RECH} , to the battery's float voltage. When V_{BAT} drops to V_{RECH} , the charger returns to CC charging and sends a pulse of current to recharge the battery to the bulk voltage and the cycle repeats. Equation 1 gives the V_{BULK} regulation voltage:

$$V_{BULK} = V_{REF} \times \left(1 + \frac{R_T + R_{P-T} \parallel R_{TC}}{R_B \parallel R_{P-B}} \right) \quad (1)$$

Equation 2 gives the V_{RECH} threshold voltage.

$$(V_{REF} - 50\text{mV}) = V_{RECH} \times \left(\frac{R_B}{R_B + R_T + R_{TC} \parallel R_{P-T}} \right) \quad (2)$$

Because lead-acid batteries do not typically have built-in thermistors, the charger's over/under temperature regulation features are not used. By changing EVM resistor R12 to 7.5 kΩ, the TS input senses a fixed voltage that is within the normal operating range and does not change any of the regulation parameters with temperature.

2 Circuit to Implement Temperature Compensation

The life span of a lead-acid battery is longer if the charging voltage is adjusted with temperature. For applications where the temperature changes only slightly around 25°C, using a linear negative temperature charging coefficient of approximately -2.5 mV/C per cell is adequate. However, the recommended charging profile over a wider temperature range is not linear. Although not required, for applications where the battery is exposed to a range of ambient temperatures, the regulated bulk and recharge voltages must be adjusted with temperature to maximize battery life. The pink curve in [Figure 3](#) shows the recommended bulk voltage charging profile over temperature, using a 6-cell, lead-acid battery with a bulk voltage of 2.6 V/cell at 25°C. The blue curve is the V_{BULK} regulation value, including the thermistor's resistance variation with temperature, as designed in the following example.

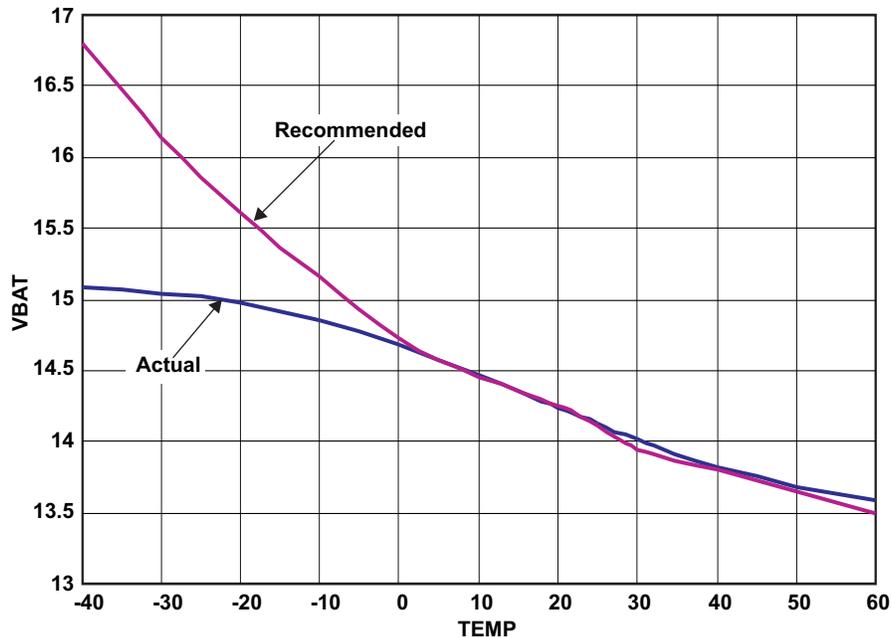


Figure 3. Battery Voltage vs Temperature for a 6-cell, Sealed, Lead-Acid Battery

From [Figure 2](#) and [Equation 1](#), the additional, series feedback resistor ($R_{\text{P-T}}$) in parallel with thermistor R_{TC} , placed close to the battery, alters the charger's bulk regulation and recharge (i.e., float) threshold voltages as the temperature changes. Sizing the resistors to achieve the appropriate negative temperature coefficient and regulation point is a trial and error process. One method for finding the best-fit resistor values is as follows:

1. From the selected thermistor's data sheet, select at least three temperature (e.g., maximum, nominal, and minimum) and corresponding resistance values to compute/plot in a spreadsheet.
2. Initially choose ($R_{\text{B}}||R_{\text{P-B}}$) and $R_{\text{P-T}}$ equal to 1-2 times the thermistor's 25°C value, weighting closer to 2 times as the temperature range goes below zero. Use [Equation 3](#) to estimate R_{T} to give the appropriate bulk battery voltage at nominal temperature.

$$R_{\text{T}} = \left(\frac{V_{\text{BULK@T(NOM)}}}{V_{\text{REF}}} - 1 \right) \times R_{\text{B}}||R_{\text{P-B}} - \frac{R_{\text{P-T}} \times R_{\text{TC@T(NOM)}}}{R_{\text{P-T}} + R_{\text{TC@T(NOM)}}} \quad (3)$$

3. Adjust $R_{\text{P-T}}$ up or down to change the slope of the regulated voltage curve. Increasing $R_{\text{P-T}}$ significantly increases the regulated voltage at low temperatures.
4. Adjust R_{T} up or down to shift the entire curve up or down.

Note that the resistors can only be configured to provide regulation and recharge voltages that match the desired values over a limited temperature range.

3 Design Example

The following design example illustrates how to modify the bq24650EVM so that it can recharge a lead-acid battery. For the 6-cell, 2.4-Ahr sealed lead-acid battery used in this example, the bulk (maximum) battery voltage at 25°C is 14.85 V, and the float voltage, used as the recharge voltage, is 14.1 V. The ambient temperature range is 0°C to 55°C.

- Step 1. Compute the sense resistor, R_{SR} , to provide the maximum charge current (I_{CHARGE}), which also sets the precharge and termination current to one-tenth of the maximum charge current. It is generally recommended to charge lead-acid cells between 0.1-0.3 times the batteries maximum current rating during CC charging. For this example, $I_{CHARGE} = 2.4 \text{ A} \times 0.3 = 0.72 \text{ A}$ rounded up to 0.8 A

$$R_{SR} = \frac{40 \text{ mV}}{I_{CHARGE}} = \frac{40 \text{ mV}}{800 \text{ mA}} = 0.05 \Omega \quad (4)$$

The inductor, L1 and FETS Q1A and Q1B must be sized per the data sheet to accommodate this current.

- Step 2. Select temperature compensation resistors. With a 100-k Ω thermistor having $R_{TC \text{ at } 25^\circ\text{C}} = 100 \text{ k}\Omega$, selecting $R_B || R_{P-B} = 156 \text{ k}\Omega$ and $R_{P-T} = 154 \text{ k}\Omega$ and use Equation 1 to estimate the top feedback resistor, R_T .

$$R_T = \left(\frac{V_{BULK@T(NOM)}}{V_{REF}} - 1 \right) \times (R_B || R_{P-B}) - \frac{R_{P-T} \times R_{TC@T(NOM)}}{R_{P-T} + R_{TC@T(NOM)}} = \left(\frac{14.85\text{V}}{2.1\text{V}} - 1 \right) \times 156\text{k}\Omega - \frac{154\text{k}\Omega \times 100\text{k}\Omega}{154\text{k}\Omega + 100\text{k}\Omega} = 947\text{k}\Omega \quad (5)$$

Lowering R_T to 887-k Ω standard value gives the best fit as shown by the gold curve in Figure 3.

- Step 3. Compute the value for R_B , the bottom feedback resistor that sets V_{RECH} , the recharge voltage threshold. In this example, V_{RECH} at 25°C is 14.1 V.

$$R_B = \frac{R_{P-T} || R_{TC} + R_T}{\frac{V_{RECH}}{V_{REF}} - 1} = \frac{100\text{k}\Omega || 154\text{k}\Omega + 887\text{k}\Omega}{\frac{14.1\text{V}}{2.05\text{V}} - 1} = 161\text{k}\Omega \rightarrow 162\text{k}\Omega \text{ standard value} \quad (6)$$

Note that the temperature compensation circuit shifts V_{RECH} in the same manner that it shifts V_{BULK} .

- Step 4. Compute the value for R_{P-B} , the switched-in resistor that sets $R_B || R_{P-B} = 156 \text{ k}\Omega$.

$$R_B = R_{P-B} = \frac{(R_B || R_{P-B}) \times R_B}{R_B - R_B || R_{P-B}} = \frac{156\text{k}\Omega \times 162\text{k}\Omega}{162\text{k}\Omega - 156\text{k}\Omega} = 4.21\text{M}\Omega \rightarrow 4.22\text{M}\Omega \text{ standard value} \quad (7)$$

- Step 5. NMOS FET Q3 in series with the resistor R_{P-B} can be any low-cost FET. However, few FETs have wider than a $\pm 20\text{-V}$ maximum V_{GS} rating. The 2N7002, with $\pm 20\text{-V}$ maximum V_{GS} rating, was selected. Therefore, a resistor divider, formed by STAT2's pullup resistor, R21, and an additional resistor, R23, to ground is needed to protect the FET from overvoltage if V_{IN} exceeds 20 V. Resistor R23 must be large enough to protect the FET but not too large that it lowers the FET's gate voltage below at least 2 V above its 2.5-V maximum threshold voltage. Equation 8 computes R23 assuming the maximum input voltage is 22 V.

$$R23 > \frac{V_{GS(MAX)} - R21}{V_{IN(MAX)} - V_{GS(MAX)}} = \frac{20 \text{ V} \times 10\text{k}\Omega}{22 \text{ V} - 20 \text{ V}} = 10 \text{ k}\Omega \quad (8)$$

R23 was selected to be 25 k Ω .

4 Test Results

Table 1 shows measured results from using a source meter to simulate the battery compared to minimum and maximum expected results, including resistor and voltage tolerances. Figure 4 shows a scope shot of the circuit as the battery charger moves from precharge mode to CC mode to CV mode and then toward termination.

Table 1. Measured Results using a Source Meter to Simulate a Lead-Acid Battery

	0°C			25°C			55°C		
	Computed Minimum (V)	Measured (V)	Computed Maximum (V)	Computed Minimum (V)	Measured (V)	Computed Maximum (V)	Computed Minimum (V)	Measured (V)	Computed Maximum (V)
V _{LOWV}	11.2	11.4	11.8	10.7	10.9	11.2	10.3	10.6	10.8
V _{BULK}	15.2	15.5	15.9	14.5	14.8	15.2	14.0	14.4	14.6
V _{RECH}	14.7	14.6	15.1	14.1	14.1	14.5	13.5	13.5	13.9

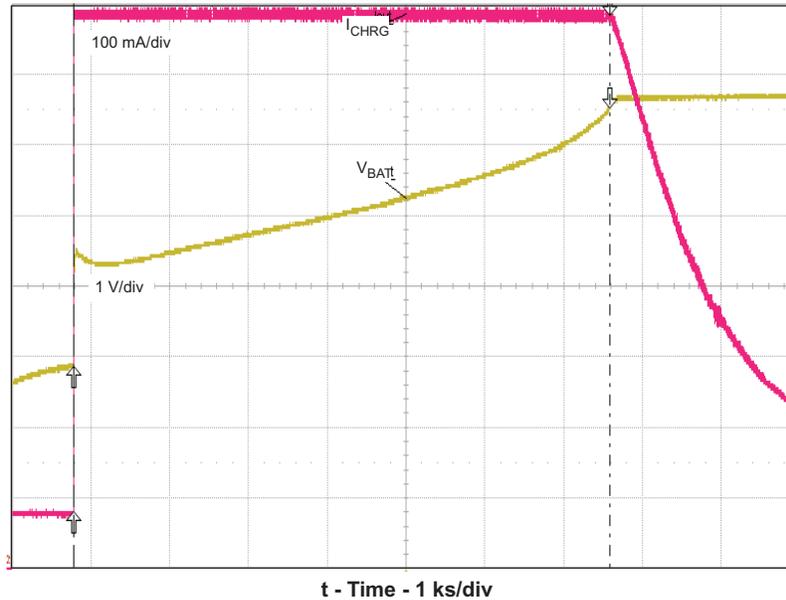


Figure 4. Measured Results With Circuit Charging a 6-Cell, 2.4-Ahr Battery

5 Circuit to Disable Precharge

For an explanation of a circuit to disable Precharge, see the application report *Reducing Precharge Phase Region for bq24650* ([SLVA473](#)).

6 Conclusion

The bq24650 battery charger can be modified to charge a lead-acid battery simply by changing the charger's regulation and recharge voltage set points. The circuit modifications also cause the charger's set points to vary with temperature by placing a thermistor and parallel resistor in series with the top, external feedback resistor. In addition, the modifications cause the charger to "exercise" the battery with pulsing currents during the constant voltage phase of the charge profile. For most lead acid batteries, this charging profile prolongs battery life. However, the user should follow their battery manufacturer's recommended charging profile in order to maximize battery life.

7 References

1. *bq24650, Synchronous Switch-Mode Battery Charge Controller for Solar Power With Maximum Power Point Tracking* data sheet ([SLUSA75](#))

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com