

# ***Voltage-Level Translation With the LSF Family***

Ryan Land

*HVAL – Standard Linear and Logic*

### **ABSTRACT**

This document discusses applications for the LSF family of devices when used as bidirectional voltage translators. It includes theory of operation, example applications, example schematics, component sizing guidelines, and performance plots.

<b>Topic</b>	<b>Page</b>
<b>1 LSF Theory of Operation.....</b>	<b>2</b>
<b>2 Generic Translation Application Using the LSF0101.....</b>	<b>3</b>
<b>3 LSF0101 Translation Application for a PWM Circuit .....</b>	<b>5</b>
<b>4 Design Differences With LSF020X.....</b>	<b>6</b>
<b>5 LSF Translation - Frequently Asked Questions.....</b>	<b>6</b>


## 1 LSF Theory of Operation

This application report discusses the LSF family. This family of devices consists of passive FET switches that use external pullup resistors to translate between voltage levels. The engineer controls the switching threshold of the device by changing Vref\_A. Vref\_B must be  $\geq 0.8$  V higher than Vref\_A, tied to EN (for LSF010x only), and pulled up to its supply voltage through a 200-k $\Omega$  resistor (for LSF010x only). The LSF devices are best suited for translating signals with fast edge rates, and perform well at frequencies up to 200 MHz (down translation) and 100 MHz (up translation).

Applications for the LSF010x family:

- Simple unidirectional voltage translation
- Bidirectional I<sup>2</sup>C translation
- Systems that require multiple levels translated. Example: An LSF0102 can translate from 1.8 to 3.3 V on one channel and 3.3 to 5 V on another channel.

LSF devices work by allowing their FET switches to conduct during the low pulse of an input signal and shutting them off during the high pulse. This allows the pullup resistor on the output to pull up the signal to the user's desired voltage level during the high pulse. Because LSF devices are passive FET switches, they do not have any output current drive strength. The drive strength is determined by external supplies.

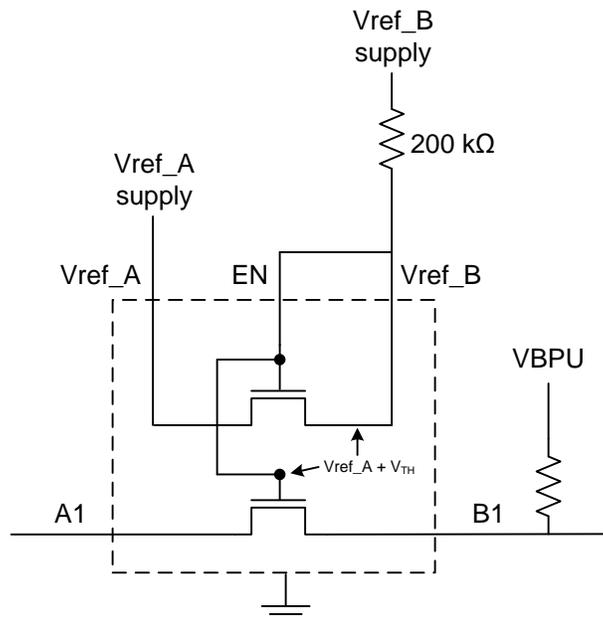

**Figure 1. Basics of LSF010x Theory of Operation**

Remember that the LSF device acts **as a passive switch when the input signal is below Vref\_A – 0.5 V**. In the previous example, suppose the input was a 1-V peak-to-peak square wave centered at 0.5 V. Because that wave never exceeds Vref\_A – 0.5 V, it passes through the switch without translation.

The 200-k $\Omega$  resistor allows Vref\_B to pull the other side of the reference FET to Vref\_A + V<sub>TH</sub>. The EN and Vref\_B pins are required to be tied together on the LSF010x. For LSF020x, this 200-k $\Omega$  is integrated into the device, and the EN pin can be controlled separately from Vref\_B. The connection between the reference FET gates and the channel FET gates allow the gates of every switching FET in the LSF device to have a voltage equal to Vref\_A + V<sub>TH</sub>. When translating down from B to A, this allows the A-side voltage to equal Vref\_A + V<sub>TH</sub> – V<sub>TH</sub> = Vref\_A without any pullups. The reason this is possible is because V<sub>GS</sub> must exceed V<sub>TH</sub> for N-channel MOSFET devices to produce an output. They are said to produce a strong 0 and a weak 1. The presence of output voltage without pullups demonstrates the weak 1. During the weak 1 condition, TI recommends only high-impedance loads because very small amounts of current will cause the output voltage to drop significantly. Pullups to Vref\_A are not required but allow heavier loads on the low side and help with signal integrity issues that may arise. Pullups on the low side (typically A-side) are only required if translating down to a voltage different than Vref\_A.

## 2 Generic Translation Application Using the LSF0101

Designers can test this example using the LSF010xEVM-001 (see [EVM tool page](#)).

**In this example, the goal is to translate a 1.8-V square wave to a 3.3-V square wave.**

Considerations:

- When the input voltage exceeds  $V_{ref\_A} - 0.5\text{ V}$ , the FET turns off and the pullup resistor on the B-side determines the output voltage. Therefore, the designer needs to pull up the B-side to 3.3 V.
- The FET begins to turn off when the input voltage exceeds  $V_{ref\_A} - 0.5\text{ V}$ . As discussed earlier, the FET should be on during the input low pulse and off during the input high pulse. Therefore, set  $V_{ref\_A}$  to 1.8 V.

Figure 2 shows the schematic for our application using the LSF0101. The B-side pullup resistors should be sized according to signal frequency and current limits. In this example, because  $V_{ref\_B}$  and our pullup voltage are both 3.3 V, the designer could have tied VBPU to the supply of  $V_{ref\_B}$ . To translate to 4 V instead, the designer could pull VBPU to 4 V.

Figure 3 shows the input and output voltages of a low-frequency square wave translated by the LSF0101.



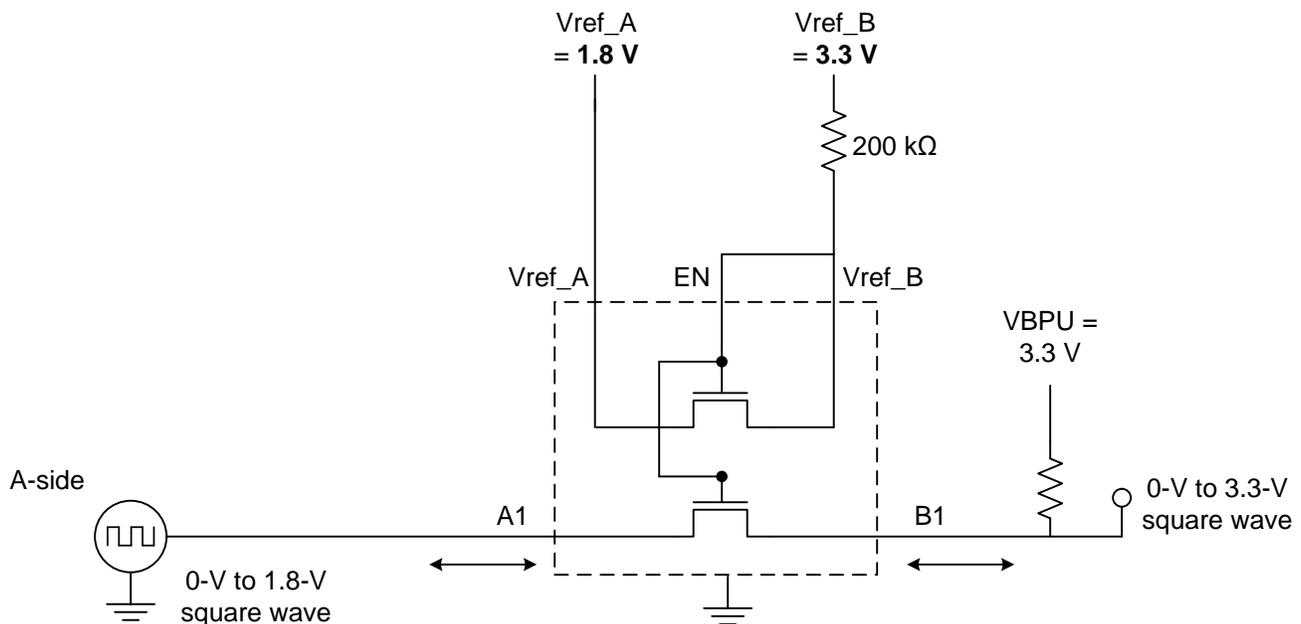


Figure 2. LSF0101 Translation Example Schematic

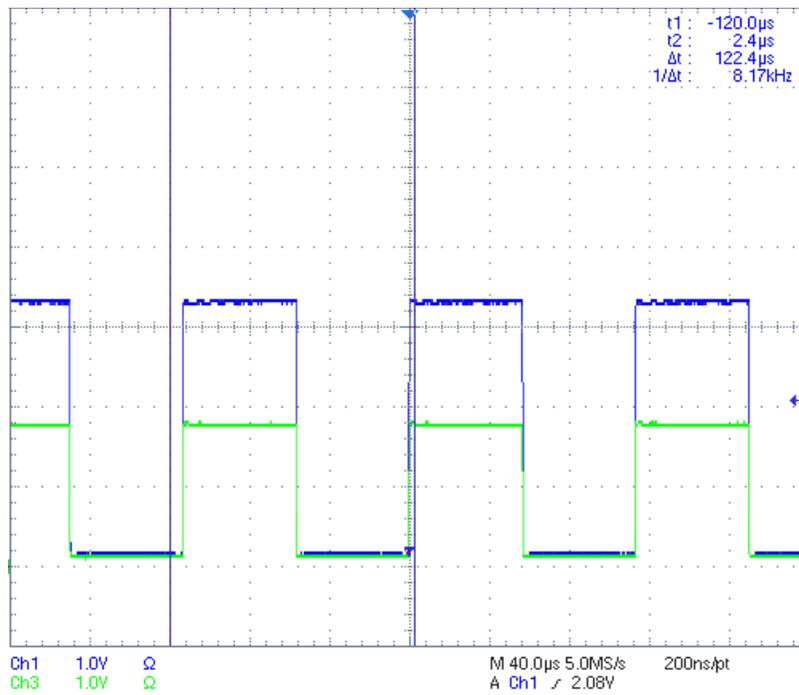

- A CH1 (blue) = B1 output
- B CH3 (green) = A1 input

**Figure 3. Translation from 1.8 to 3.3 V**

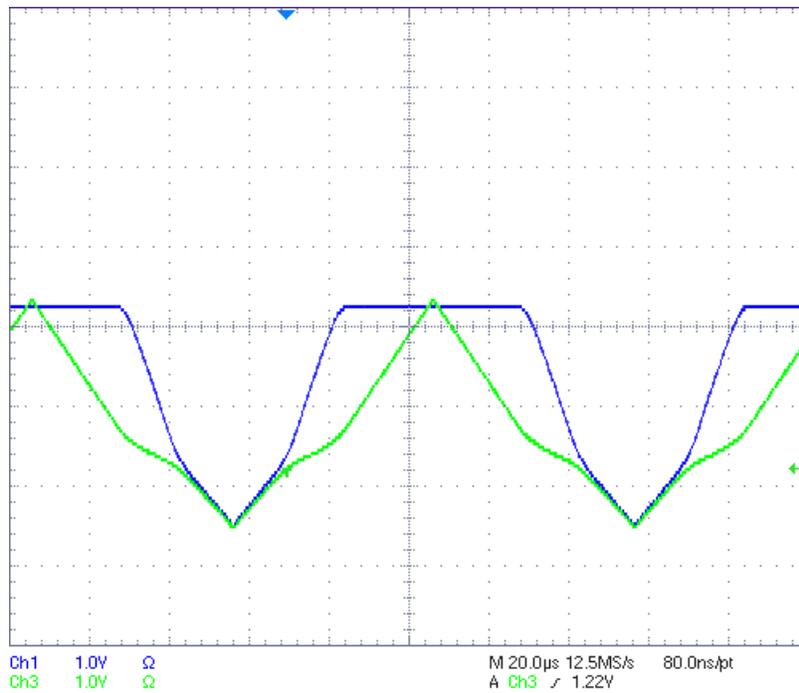

- A CH1 (blue) = Output
- B CH3 (green) = Triangle wave input

**Figure 4. Behavior Across Input Voltage With Vref\_A = 1.8 V**

Figure 4 shows the behavior across input voltage when  $V_{ref\_A} = 1.8\text{ V}$ . Notice that the output starts to rise (FET starts switching off) when the input reaches  $V_{ref\_A} - 0.5\text{ V}$ . This waveform is not a typical input signal for the LSF device. Instead, it illustrates the switching behavior of the LSF across the input voltage range. The waveform shows both states of the LSF device on the same graph: the low-impedance mode during a low input pulse, and the high-impedance mode during a high pulse with the pullup resistor driving the output up to 3.3 V.

### 3 LSF0101 Translation Application for a PWM Circuit

Some systems require an analog input voltage instead of a digital high or low. In these applications, the driving controller (usually a microcontroller) outputs a pulse-width modulated (PWM) signal with a duty cycle percentage equal to the level of analog signal needed between the high and low states. A filter converts these rectangular pulses into a smooth DC signal at a voltage between the MCU's high and low level output voltages.

In this example, consider a MCU which outputs 0 or 3.3 V, but the filter requires a 5-V PWM signal. The LSF0101 translates the 3.3-V PWM signal to a 5-V PWM signal for the filter. See Figure 5 for a PWM application schematic.

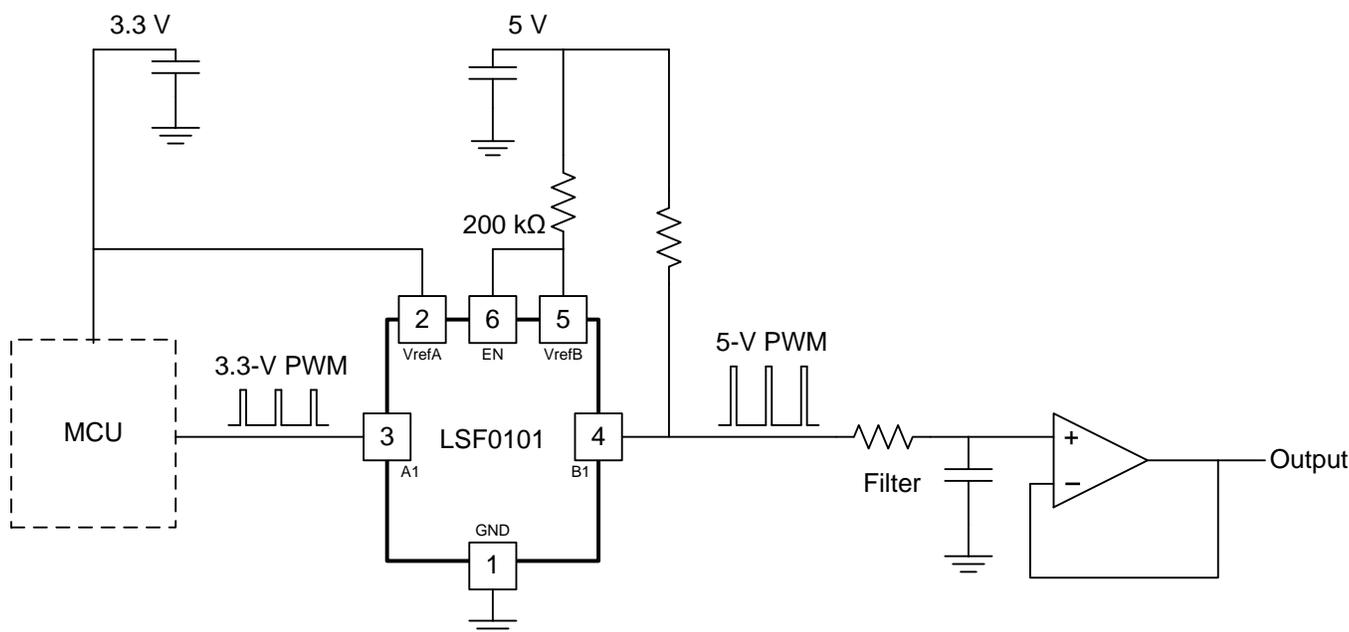


Figure 5. PWM Application With LSF0101

The filter component values can vary depending on the application. If the PWM frequency is very high, the B-side pullup should be small (about 150  $\Omega$ ) to allow for fast edge rates. Designers should test different B-side pullup values to optimize edge rates, overshoot, and power consumption. To limit the current through the FET to 15 mA, select a pullup resistor equal to  $R_{PU} = (V_{PU} - 0.35\text{ V}) / 0.015\text{ A}$ . See the LSF data sheet for more guidance on pullup resistor sizing.

**NOTE:** Consider the  $V_{OL}$  of the output driver when designing a PWM circuit. Example: If the  $V_{OL}$  is 0.2 V in this case, the 0.2 V passes through the LSF0101 because it is lower than  $V_{ref\_A} - 0.5\text{ V}$ . The input and output are 0.2-V to 3.3-V input to the A-side and a 0.2-V to 5-V output on the B-side. If this  $V_{OL}$  is too high for a specific PWM application, consider using a translating logic buffer or CMOS peripheral sink driver instead.

## 4 Design Differences With LSF020X

The LSF0204 and LSF0204D are 4-channel LSF devices, but they are designed in a slightly different way. The following is a list of application considerations for the LSF020X devices:

- There is an integrated 200-k $\Omega$  resistor connected to the Vref\_B pin. An external 200 k $\Omega$  is not needed.
- The EN pin enables/disables the reference FET's gate connection to the channel FETs. EN is not required to be tied to Vref\_B as in the LSF010x. Instead, EN is treated as a logic control input with  $V_{IH}$  and  $V_{IL}$  referenced to Vref\_A. The LSF0204 and LSF0204D have opposite-polarity EN inputs. The EN pin must not be left floating; make sure it is pulled up to Vref\_A or pulled down to GND through a resistor that can be driven high or low by an external GPIO.

## 5 LSF Translation - Frequently Asked Questions

### 5.1 How does the LSF translate?

The LSF family allows external pullups to translate. The LSF acts as a closed circuit during a low input pulse and an open circuit during a high input pulse. When it is an open circuit, the external pullups take over.

### 5.2 When are pullups on the A-side and B-side needed?

TI recommends pullups on the low side (typically the A-side) when one of these conditions is met:

- The low side (typically A-side) is used as an output or a bidirectional port, and it is translating to a voltage not equal to Vref\_A.
- The low side (typically A-side) is used as an output or a bidirectional port, is translating to Vref\_A, and there are signal integrity problems.
- The low side (typically A-side) is used as an input or bidirectional port, and is being driven by an open-drain device.

TI recommends pullups on the high side (typically B-side) when one of these conditions is met:

- The high side (typically B-side) is used as an output or a bidirectional port.
- The high side (typically B-side) is used as an input or bidirectional port, and is being driven by an open-drain device.

Pullups are not required on inputs driven by push-pull devices.

### 5.3 The data sheet says Vref\_B must be 0.8 V higher than Vref\_A. How do I translate across a small range, like 1.2 V to 1.8 V?

Set Vref\_A to 1.2 V and Vref\_B between 2 V and 5.5 V. Add a B-side pullup to 1.8 V. As long as  $V_{ref\_B} \geq V_{ref\_A} + 0.8 \text{ V}$  and Vref\_B is within the *recommended operating conditions* range, the level of Vref\_B does not affect the output signal. Only the B-side pullups affect the output signal level.

### 5.4 What is the frequency range of the LSF?

The LSF family can translate up at 100 MHz and down at 200 MHz with reasonably good signal integrity. Signal integrity for translation depends on many factors, including line capacitance, output load, and pullup resistor sizes. Generally, smaller pullup resistors allow faster translation, but at the expense of power.

### 5.5 What happens if the input signal goes below GND?

If the input goes below GND, the FETs turn on and conduct the negative voltage. If the inputs drop below  $-0.5 \text{ V}$ , there is a risk of turning on a clamp diode and drawing excessive current from GND to the input, damaging the device. See the *Absolute Maximum Ratings* in the data sheet for more details.

### 5.6 What happens if either Vref\_A or Vref\_B is grounded?

If either Vref\_A or Vref\_B are grounded, the switch behaves as an open circuit.

**5.7 What pullup voltages are allowed on the A-side and B-side?**

On either the A-side or B-side, resistors can pull up to any voltage between  $V_{ref\_A}$  and 5 V. Therefore, it is possible to translate down to the B-side.

## Revision B History

<b>Changes from A Revision (February 2015) to B Revision</b>	<b>Page</b>
• Made references to LSF010x, LSF020x, and "LSF" family where appropriate throughout document.....	1
• Updated <a href="#">Section 1</a> with additional information to address down-translation without pullups.....	2
• Updated pullup resistor requirements and recommendations in <a href="#">Section 5.2</a> .....	6

---

## Revision A History

<b>Changes from Original (December 2014) to A Revision</b>	<b>Page</b>
• Added <a href="#">Section 4</a> .....	6
• Updated <a href="#">Section 5.2</a> with additional information .....	6

---

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)