

Prevent Battery Overdischarge with Precise Threshold Enable Pin



Using a buck-boost converter is a convenient way to obtain a fixed supply voltage within the wide voltage range of typical batteries used in low-power devices such as smart meters, wearables or those in the Internet of Things. In order to extract as much energy as possible from the battery, it helps if the converter can operate at low input voltages.

In non-inverting buck-boost devices such as the TPS63802, the minimum operating input voltage is as low as 1.3 V once the device is started. With most rechargeable batteries, however, such a deep discharge can cause irreversible reduction in capacity or even catastrophic failure and damage to the rest of the system. In such situations, it becomes essential to cut off the battery from the rest of the system at a desired voltage value.

Most DC/DC converters have an input pin to enable or disable the device. However, the threshold voltage at this pin can have a huge tolerance, making it difficult to accurately set the desired cutoff voltage. As an example, according to the datasheet, the threshold voltage of the enable (EN) pin for the TPS63020 is within the range listed in Table 1. In this case, the EN pin voltage threshold can be anywhere between 0.4 V and 1.2 V.

Table 1. EN pin voltage levels for TPS63020

Parameter	Min	Typ	Max	Unit
V _{IL} EN input low voltage			0.4	V
V _{IH} EN Input high voltage	1.2			V

This threshold range is fine for on/off control using logic-level signals, but not for setting a precise cutoff voltage derived from the input voltage. To achieve higher accuracy, it is possible to add a comparator and a voltage reference, or a voltage supervisor circuit, but this increases complexity and cost. Instead, it would be more useful if the EN pin has more precisely defined threshold voltages.

The concept of achieving a precise threshold voltage for buck converters was introduced in the application report [Achieving a Clean Startup by Using a DC/DC Converter with a Precise Enable-pin Threshold](#). The new TPS63802 non-inverting buck-boost converter

also has a very precise threshold voltage for the EN pin, with approximately 3% tolerance and 100 mV hysteresis, as listed in Table 2.

Table 2. EN pin threshold voltages for TPS63802

Parameter	Min	Typ	Max	Unit
V _{IT+(EN)} Rising threshold voltage for EN pin	1.07	1.1	1.13	V
V _{IT-(EN)} Falling threshold voltage for EN pin	0.97	1	1.03	V

Having precise voltage thresholds, it is possible to easily set a user-defined minimum supply voltage. This is done using a voltage divider connected to VIN pin, EN pin and ground, as shown in Figure 1.

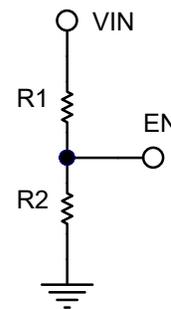


Figure 1. Setting the input cutoff voltage with a voltage divider

Equation 1 calculates the falling threshold supply voltage where the converter is turned off:

$$V_{IT-} = V_{IT-(EN)} \left(1 + \frac{R1}{R2} \right) \quad (1)$$

Equation 2 calculates the rising threshold supply voltage where the converter is turned on:

$$V_{IT+} = V_{IT+(EN)} \left(1 + \frac{R1}{R2} \right) \quad (2)$$

The additional voltage divider will increase the current consumption, therefore, aim for large resistances. Considering that the EN input leakage current for TPS63802 is 0.2 μA maximum, aim for at least 20 μA of current in the voltage divider. The application report

Optimizing Resistor Dividers at a Comparator Input

has more details about how to optimize a resistor divider at a comparator input.

As an example, to set the cutoff input voltage to $V_{IT-} = 2.5\text{ V}$, we can first choose $R1 + R2 = 125\text{ k}\Omega$ to have a $20\text{ }\mu\text{A}$ resistor divider current. Solving [Equation 1](#), we choose $R1 = 75\text{ k}\Omega$ and $R2 = 49.9\text{ k}\Omega$ resistors with 1% tolerance. The turn-on input voltage is now $V_{IT+} = 2.75\text{ V}$ according to [Equation 2](#).

[Figure 2](#) shows that the achieved cutoff and turn-on input voltages are $V_{IT-} = 2.56\text{ V}$ and $V_{IT+} = 2.8\text{ V}$, respectively. This is within the equivalent tolerance of approximately 80 mV (3.1%) caused by the EN pin threshold voltage and resistor tolerances, not taking into account the oscilloscope accuracy. The application report [Method for Calculating Output Voltage Tolerances in Adjustable Regulators](#) has more details on calculating equivalent voltage tolerances.

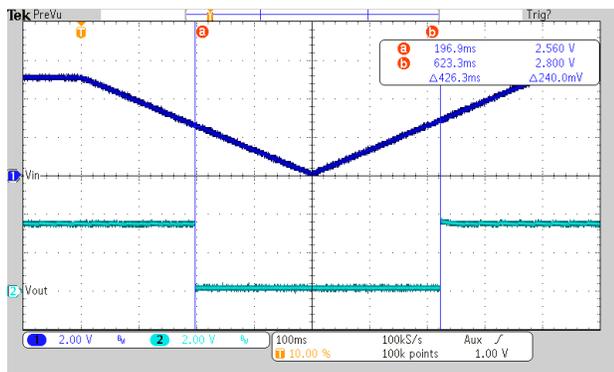


Figure 2. Achieved cutoff and turn-on input voltage thresholds

The previous example shows how simple it is to protect a battery from overdischarge by adding only two resistors. The same solution is applicable not only to buck-boost but also to other buck or boost devices having the precise threshold voltage EN pin.

References

[TPS63802 Datasheet](#)

[TPS63020 Datasheet](#)

[Achieving a Clean Startup by Using a DC/DC Converter with a Precise Enable-pin Threshold](#)

[Optimizing Resistor Dividers at a Comparator Input](#)

[Method for Calculating Output Voltage Tolerances in Adjustable Regulators](#)

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated