

# Calculating noise figure in op amps

By James Karki (Email: j-karki@ti.com)

Member, Group Technical Staff, High-Performance Linear

## Introduction

Noise figure is commonly used in communications systems because it provides a simple method to determine the impact of system noise on sensitivity.

Today, the performance of wide-band op amps is making them viable alternatives to more traditional open-loop amplifiers like monolithic microwave integrated circuits (MMICs) and discrete transistors in communications design.

Recognizing the need to specify wide-band op amps in RF engineering terminology, some manufacturers do provide noise figure, but they seem to be the exception rather than the rule.

Op amp manufacturers typically specify noise performance by giving the input-referred voltage and current noise. The noise figure depends on these parameters, the circuit topology, and the value of external components. If you have all this information, noise figure can be calculated.

## Review of noise figure

Noise figure (NF) is the decibel equivalent of noise factor (F):  $NF \text{ (dB)} = 10\log(F)$ .


Noise factor of a device is the power ratio of the signal-to-noise ratio (SNR) at the input ( $SNR_I$ ) divided by the SNR at the output ( $SNR_O$ ):

$$F = \frac{SNR_I}{SNR_O} \quad (1)$$

The output signal ( $S_O$ ) is equal to the input signal ( $S_I$ ) times the gain:  $S_O = S_I \times G$ . The output noise is equal to the noise delivered to the input ( $N_I$ ) from the source plus the input noise of the device ( $N_A$ ) times the gain:  $N_O = (N_I + N_A) \times G$ . Substituting into Equation 1 and simplifying, we get

$$F = \frac{SNR_I}{SNR_O} = \left[ \frac{\frac{S_I}{N_I}}{G \times \frac{S_I}{G(N_I + N_A)}} \right] = 1 + \frac{N_A}{N_I} \quad (2)$$

Figure 1. Non-inverting noise analysis diagram

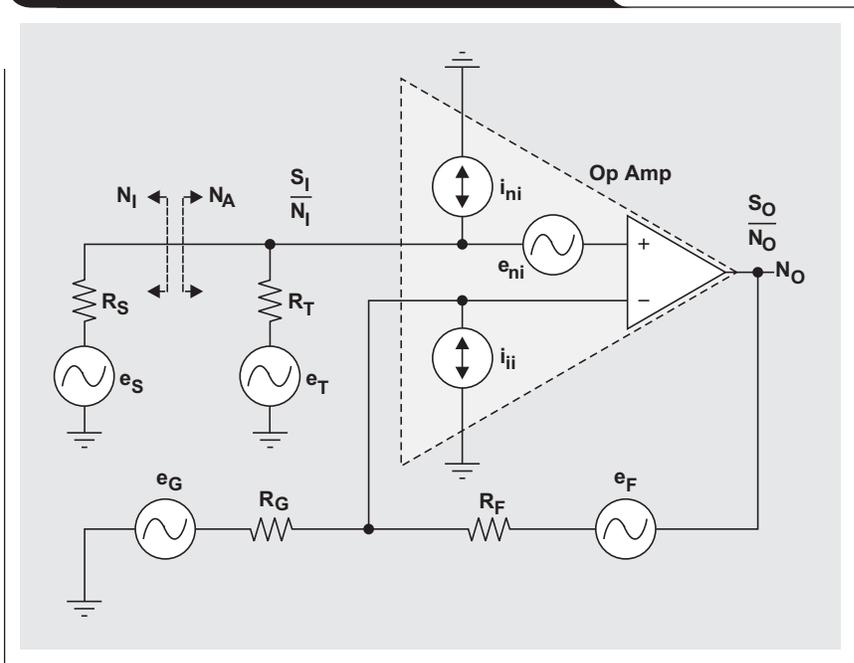

Assuming that the input is terminated in the same impedance as the source,  $N_I = kT = -174 \text{ dBm/Hz}$ , where  $k$  is Boltzman's constant and  $T = 300 \text{ Kelvin}$ ). Once we find the input noise spectral density of the device, it is a simple matter to plug it into Equation 2 and calculate  $F$ .

## NF in op amps

Op amps specify input-referred voltage and current noise. Using these two parameters, adding the noise of the external resistors, and calculating the total input-referred noise based on the circuit topology, we can calculate the input spectral density and use it in Equation 2.

In this discussion, the terms "op amp" and "amplifier" mean different things. "Op amp" refers to only the active device itself, whereas "amplifier" includes the op amp and associated passive resistors that make it work as a usable amplifier stage. In other words, the amplifier is everything shown in Figures 1–3 except  $R_S$ , and the op amp is only the components within the dashed triangles. In this way, the plane marked  $N_A$  and  $N_I$  is the input to the amplifier. This is the point to which the noise sources must be referred so that Equation 2 can be used.

The noise from the source and the input noise of the amplifier are referred to the same point. Because the impedance is the same, expressing the ratio between  $N_A$  and  $N_I$  as a voltage ratio squared is equivalent to the power ratio. An op amp is a voltage-driven device, so using voltage-squared terms makes the calculations easier. In the following discussion, voltage-squared terms are used for  $N_A$  and  $N_I$ .

Op amps use negative feedback to control the gain of the amplifier. One result is that the voltage across the input terminals is driven to zero. This is often referred to as a “virtual short.” It is used in the following analysis\* and referred to as “amplifier action,” since it is a by-product of the op amp doing its job as an amplifier.

Superposition is used throughout the analysis, wherein all sources except the one under consideration are defeated—voltage sources are shorted and current sources are opened.

**Non-inverting amplifier**

Of the three basic op amp circuits, it is easiest to find the input-referred noise for the non-inverting op amp amplifier, so it will be discussed first. Figure 1 shows a noise analysis diagram for a non-inverting op amp amplifier with the noise sources identified.

The source resistance  $R_S$  generates a noise voltage equal to  $\sqrt{4kTR_S}$ . The noise voltage delivered to the amplifier input from the source is divided by the resistors  $R_S$  and  $R_T$ . Therefore,

$$N_I = 4kTR_S \left( \frac{R_T}{R_S + R_T} \right)^2$$

$R_T$  is typically used to terminate the input so that  $R_T = R_S$ , in which case  $N_I = kTR_S$ .

The amplifier’s voltage noise is a combination of  $e_{ni}$ ,  $i_{ni}$ , and  $i_{ii}$  with associated impedances  $e_T$ ,  $e_G$ , and  $e_F$ . These are all referred

Figure 2. Inverting noise analysis diagram


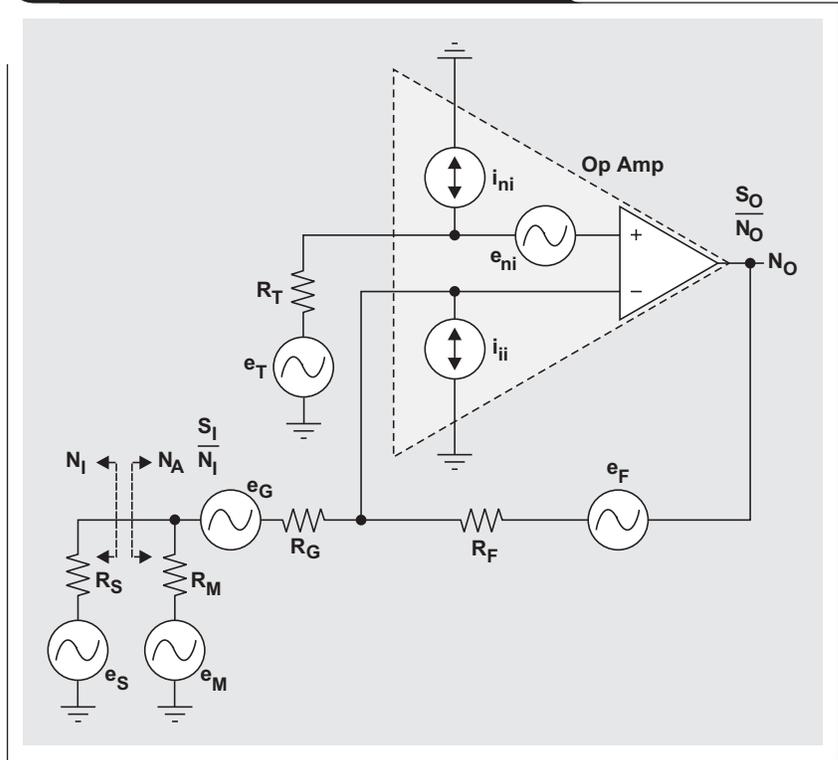


Figure 3. Fully differential noise analysis diagram

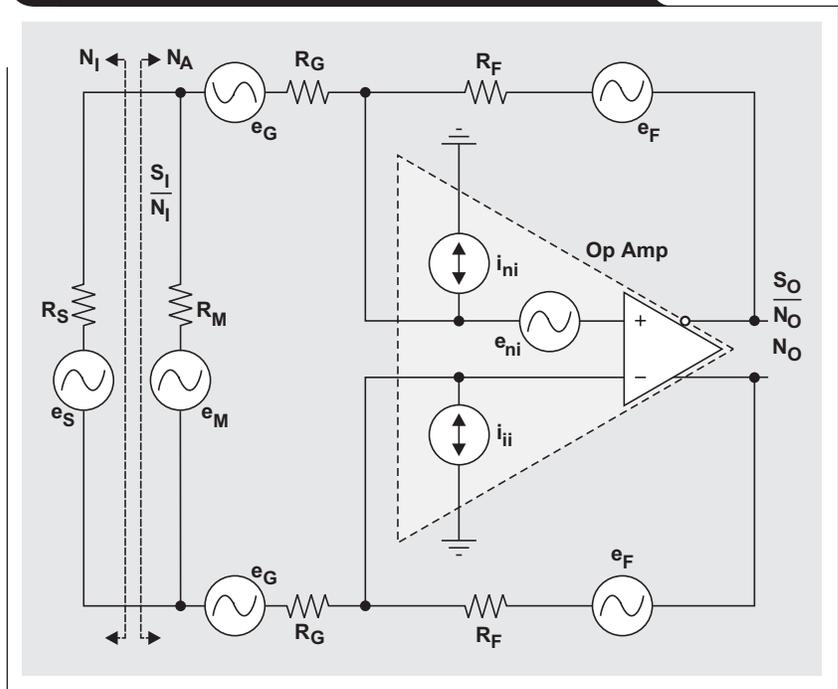

\*The virtual-short concept simplifies the analysis. Much more work is required to obtain the same results by other means such as nodal analysis.

to the input by their respective scaling factors and summed to find  $N_A$ ; i.e.,

$$N_A = c_1 e_{ni}^2 + c_2 i_{ni}^2 + c_3 i_{ii}^2 + c_4 e_T^2 + c_5 e_G^2 + c_6 e_F^2, \quad (3)$$

where  $c_1$  through  $c_6$  are the scaling factors.

The op amp's input voltage noise is  $e_{ni}$ . It appears directly at the amplifier's input and its scaling factor is 1 or unity, so that  $c_1 e_{ni}^2 = e_{ni}^2$ .

The op amp's non-inverting input current noise is  $i_{ni}$ . It develops a voltage through the parallel combination of  $R_S$  and  $R_T$ , which appears directly at the amplifier's input, so that

$$c_2 i_{ni}^2 = i_{ni}^2 \left( \frac{R_S R_T}{R_S + R_T} \right)^2$$

The op amp's inverting input current noise is  $i_{ii}$ . It develops a voltage through the parallel combination of  $R_F$  and  $R_G$  at the op amp's inverting input. By amplifier action, this voltage appears at the amplifier's input, so that

$$c_3 i_{ii}^2 = i_{ii}^2 \left( \frac{R_F R_G}{R_F + R_G} \right)^2$$

The noise voltage term  $e_T$  associated with  $R_T$  is equal to  $\sqrt{4kTR_T}$ . It is divided by the resistors  $R_S$  and  $R_T$ , so that

$$c_4 e_T^2 = 4kTR_T \left( \frac{R_S}{R_S + R_T} \right)^2$$

If  $R_T = R_S$ , then  $c_4 e_T^2 = kTR_T$ .

The noise voltage term  $e_G$  associated with  $R_G$  is equal to  $\sqrt{4kTR_G}$ . This noise is divided by the resistors  $R_F$  and  $R_G$  and applied to the op amp's inverting input. Again by amplifier action, noise from  $R_G$  appears at the amplifier's input, so that

$$c_5 e_G^2 = 4kTR_G \left( \frac{R_F}{R_F + R_G} \right)^2$$

The noise voltage term  $e_F$  associated with  $R_F$  is equal to  $\sqrt{4kTR_F}$  and appears at the amplifier's output. Dividing by the signal gain gives us

$$c_6 e_F^2 = 4kTR_F \left( \frac{R_G}{R_F + R_G} \right)^2$$

With all the terms in Equation 3 quantified, we can take the sum to find  $N_A$  and use  $N_A$  along with  $N_I$  in Equation 2 to find  $F$ .

### Inverting amplifier

Finding the input-referred noise of an inverting op amp amplifier is more cumbersome than finding that of a non-inverting op amp amplifier. The main problem is that the signal gain of the amplifier and the noise gain are different.

Figure 2 shows a noise analysis diagram for an inverting op amp amplifier with the noise sources identified.

To find the input-referred noise, it is easiest in some cases to find the output noise and then divide by the signal gain of the amplifier.

The noise voltage delivered to the input from the source is divided by the resistors  $R_S$  and  $R_M$  in parallel with  $R_G$ . Therefore,

$$N_I = 4kTR_S \left[ \frac{R_M R_G}{R_S (R_M + R_G) + (R_M R_G)} \right]^2$$

$R_M$  is typically selected so that  $R_M \parallel R_G = R_S$ , in which case  $N_I = kTR_S$ .

The amplifier's input-referred voltage noise is a combination of  $e_{ni}$ ,  $i_{ni}$ , and  $i_{ii}$  with associated impedances  $e_T$ ,  $e_G$ ,  $e_F$ , and  $e_M$ . These are all referred to the input by their respective scaling factors and summed to find  $N_A$ ; i.e.,

$$N_A = c_1 e_{ni}^2 + c_2 i_{ni}^2 + c_3 i_{ii}^2 + c_4 e_T^2 + c_5 e_G^2 + c_6 e_F^2 + c_7 e_M^2, \quad (4)$$

where  $c_1$  through  $c_7$  are the scaling factors.

The op amp's input voltage noise,  $e_{ni}$ , at the op amp's non-inverting input appears at the amplifier output as a function of the amplifier noise gain,

$$1 + \frac{R_F}{R_G + \frac{R_S R_M}{R_S + R_M}}$$

and is then referred back to the amplifier input as a function of the signal gain,  $R_F/R_G$ . Thus,

$$c_1 e_{ni}^2 = e_{ni}^2 \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2 **$$

The op amp's non-inverting input current noise is  $i_{ni}$ . It develops a voltage through  $R_T$  that appears directly at the amplifier's input, so that

$$c_2 i_{ni}^2 = i_{ni}^2 \left( \frac{R_T R_G}{R_F} + \frac{R_T R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$$

It is hard to see how to calculate the op amp's inverting input current noise,  $i_{ii}$ . Basically, due to amplifier action, the inverting node is at ground so that no current is drawn through the input resistor  $R_G$ . The noise current flows through  $R_F$ , producing a voltage at the output equal to  $i_{ii} R_F$ . Referring to the amplifier's input results in  $c_3 i_{ii}^2 = i_{ii}^2 (R_G)^2$ .

The noise voltage term  $e_T$  associated with  $R_T$  is equal to  $\sqrt{4kTR_T}$ . Just like  $e_{ni}$ , it appears at the output as a function

\*\*The gain is actually  $-R_F/R_G$ ; but since it is squared, the minus sign is ignored in this analysis.

of the amplifier noise gain and is then referred back to the amplifier input as a function of the signal gain, so that

$$c_4 e_T^2 = kTR_F \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$$

The noise voltage term  $e_G$  associated with  $R_G$  is equal to  $\sqrt{4kTR_G}$ . It is divided by the resistors  $R_G$  and  $R_S$  in parallel with  $R_M$  en route to the amplifier's input, so that

$$c_5 e_G^2 = 4kTR_G \left( \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$$

The noise voltage term  $e_F$  associated with  $R_F$  is equal to  $\sqrt{4kTR_F}$  and appears directly at the amplifier's output. Dividing by the signal gain gives us

$$c_6 e_F^2 = 4kTR_F \left( \frac{R_G}{R_F} \right)^2$$

The noise source  $e_M$  associated with the input termination matching resistor  $R_M$  is equal to  $\sqrt{4kTR_M}$ . It is divided by the resistors  $R_M$  and  $R_S$  in parallel with  $R_G$ , so that

$$c_7 e_M^2 = 4kTR_M \left[ \frac{R_S R_G}{R_M (R_S + R_G) + R_S R_G} \right]^2$$

With all the terms in Equation 4 quantified, we can take the sum to find  $N_A$  and use  $N_A$  along with  $N_I$  in Equation 2 to find F.

### Fully differential amplifier

Fully differential op amp amplifiers are very similar to inverting op amp amplifiers, and the analysis follows very closely. Figure 3 shows the noise analysis diagram.

The source resistance generates thermal noise equal to  $\sqrt{4kTR_S}$ . The noise voltage delivered to the input from the source is divided by the resistors  $R_S$  and  $R_M$  in parallel with  $2R_G$ . Therefore,

$$N_I = 4kTR_S \left( \frac{\frac{2R_M R_G}{R_M + 2R_G}}{R_S + \frac{2R_M R_G}{R_M + 2R_G}} \right)^2$$

$R_M$  is typically selected so that  $R_M \parallel 2R_G = R_S$ , in which case  $N_I = kTR_S$ .

The amplifier's input-referred voltage noise is a combination of  $e_{ni}$ ,  $i_{ni}$ , and  $i_{ii}$  with associated impedances  $e_G$ ,  $e_F$ , and  $e_M$ . These are all referred to the input by their respective scaling factors and summed to find  $N_A$ ; i.e.,

$$N_A = c_1 e_{ni}^2 + c_2 i_{ni}^2 + c_3 i_{ii}^2 + c_4 e_G^2 + c_5 e_F^2 + c_6 e_M^2 \quad (5)$$

where  $c_1$  through  $c_6$  are the scaling factors.

In this analysis it is assumed that the two input resistors  $R_G$  are equal and that the two feedback resistors  $R_F$  are equal.

The op amp's input voltage noise,  $e_{ni}$ , at the op amp's input appears at the amplifier output as a function of the amplifier noise gain,

$$1 + \frac{R_F}{R_G + \frac{R_S R_M}{2(R_S + R_M)}}$$

and is then referred back to the amplifier input as a function of the signal gain,  $R_F/R_G$ . Thus,

$$c_1 e_{ni}^2 = e_{ni}^2 \left[ \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{2(R_S + R_M)}} \right]^2$$

Since the input resistors are equal and the feedback resistors are equal, the op amp's non-inverting input current noise,  $i_{ni}$ , and inverting input current noise,  $i_{ii}$ , have the same scaling factors. Due to amplifier action, the input nodes of the op amp are ac grounds so that no current is drawn through the input resistors  $R_G$ . All the noise current flows through  $R_F$ , producing a voltage at the output equal to  $i_{ni} R_F$  or  $i_{ii} R_F$ . Referring to the amplifier's input results in  $c_2 i_{ni}^2 = i_{ni}^2 (R_G)^2$  and  $c_3 i_{ii}^2 = i_{ii}^2 (R_G)^2$ .

The noise voltage term  $e_G$  associated with each  $R_G$  is equal to  $\sqrt{4kTR_G}$ . It is divided by the resistors  $R_G$  and one-half  $R_S$  in parallel with  $R_M$ , so that

$$c_4 e_G^2 = 2 \times 4kTR_G \left[ \frac{R_G}{R_G + \frac{R_S R_M}{2(R_S + R_M)}} \right]^2$$

The noise voltage term  $e_F$  associated with each  $R_F$  is equal to  $\sqrt{4kTR_F}$  and appears directly at the amplifier's output. Dividing by the signal gain gives us

$$c_5 e_F^2 = 4kTR_F \left( \frac{R_G}{R_F} \right)^2$$

The noise source  $e_M$  associated with the input termination matching resistor  $R_M$  is equal to  $\sqrt{4kTR_M}$ . It is divided by the resistors  $R_M$  and  $R_S$  in parallel with  $2R_G$ , so that

$$c_6 e_M^2 = 4kTR_M \left( \frac{\frac{2R_S R_G}{R_S + 2R_G}}{R_M + \frac{2R_S R_G}{R_S + 2R_G}} \right)^2$$

As before, with all the terms in Equation 5 quantified,  $N_A$  can be calculated and used with  $N_I$  in Equation 2 to find the noise factor.

**Table 1. Comparison of calculated vs. measured noise figure**

OP AMP	CONFIGURATION	$e_{ni}$ (nV)	$i_{ni}$ (pA)	$i_{ii}$ (pA)	$R_F$ ( $\Omega$ )	$R_G$ ( $\Omega$ )	$R_T$ ( $\Omega$ )	$R_M$ ( $\Omega$ )	CALCULATED NF (dB)	MEASURED NF (dB)
THS3202	Non-inverting	1.65	13.5	20	255	49.9	49.9	—	13.6	13.0
THS3202	Inverting	1.65	13.5	20	255	49.9	—	—	11.6	11.5
THS4501	Fully differential	7	1.7	1.7	392	392	—	56.2	30.1	30.6

## Conclusion

The input-referred voltage noise and current noise, along with the circuit configuration and component values, can be used to calculate noise figure. This is a tedious task at best. Setting up a spreadsheet for each topology where component values and op amp specs can be entered is recommended. In this way, various scenarios can be quickly tested. Verification by testing the circuit with a noise figure analyzer is always suggested.

As an example of how well the theory outlined in this article matches test results, the noise figure of three op amp

amplifiers configured as previously detailed were measured with an Agilent N8973A noise figure analyzer. Table 1 shows that the results are good, with the input current and voltage noise specifications given as typical values.

## Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/THS3202](http://www.ti.com/sc/device/THS3202)

[www.ti.com/sc/device/THS4501](http://www.ti.com/sc/device/THS4501)

## Appendix—Summary of noise terms in op amp amplifiers

### Signal input noise ( $N_I$ ) terms

AMPLIFIER CONFIGURATION	NOISE SOURCE	NOISE CONTRIBUTION
Non-inverting	Source thermal noise	$4kTR_S \left( \frac{R_T}{R_S + R_T} \right)^2$
Inverting	Source thermal noise	$N_I = 4kTR_S \left[ \frac{R_M R_G}{R_S (R_M + R_G) + (R_M R_G)} \right]^2$
Fully differential	Source thermal noise	$4kTR_S \left( \frac{\frac{2R_M R_G}{R_M + 2R_G}}{R_S + \frac{2R_M R_G}{R_M + 2R_G}} \right)^2$

## Appendix—Summary of noise terms in op amp amplifiers (Continued)

### Device input noise ( $N_A$ ) terms

AMPLIFIER CONFIGURATION	NOISE SOURCE	NOISE CONTRIBUTION
Non-inverting	Op amp input-referred voltage noise	$e_{ni}^2$
	Op amp non-inverting input-referred current noise	$i_{ni}^2 \left( \frac{R_S R_T}{R_S + R_T} \right)^2$
	Op amp inverting input-referred current noise	$i_{ii}^2 \left( \frac{R_F R_G}{R_F + R_G} \right)^2$
	Termination resistor thermal noise voltage	$4kTR_T \left( \frac{R_S}{R_S + R_T} \right)^2$
	Gain resistor thermal noise voltage	$4kTR_G \left( \frac{R_F}{R_F + R_G} \right)^2$
	Feedback resistor thermal noise voltage	$4kTR_F \left( \frac{R_G}{R_F + R_G} \right)^2$
Inverting	Op amp input-referred voltage noise	$e_{ni}^2 \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Op amp non-inverting input-referred current noise	$i_{ni}^2 \left( \frac{R_T R_G}{R_F} + \frac{R_T R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Op amp inverting input-referred current noise	$i_{ii}^2 (R_G)^2$
	Non-inverting bias matching resistor thermal noise voltage	$4kTR_T \left( \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Gain resistor thermal noise voltage	$4kTR_G \left( \frac{R_G}{R_G + \frac{R_S R_M}{R_S + R_M}} \right)^2$
	Feedback resistor thermal noise voltage	$4kTR_F \left( \frac{R_G}{R_F} \right)^2$
	Inverting termination matching resistor thermal noise voltage	$4kTR_M \left[ \frac{R_S R_G}{R_M (R_S + R_G) + R_S R_G} \right]^2$

## Appendix—Summary of noise terms in op amp amplifiers (Continued)

### Device input noise ( $N_A$ ) terms (Continued)

AMPLIFIER CONFIGURATION	NOISE SOURCE	NOISE CONTRIBUTION
Fully differential	Op amp input-referred voltage noise	$e_{ni}^2 \left[ \frac{R_G}{R_F} + \frac{R_G}{R_G + \frac{R_S R_M}{2(R_S + R_M)}} \right]^2$
	Op amp non-inverting input-referred current noise	$i_{ni}^2 (R_G)^2$
	Op amp inverting input-referred current noise	$i_{ii}^2 (R_G)^2$
	Gain resistor thermal noise voltage	$2 \times 4kTR_G \left[ \frac{R_G}{R_G + \frac{R_S R_M}{2(R_S + R_M)}} \right]^2$
	Feedback resistor thermal noise voltage	$2 \times 4kTR_F \left( \frac{R_G}{R_F} \right)^2$
	Termination matching resistor thermal noise voltage	$4kTR_M \left( \frac{\frac{2R_S R_G}{R_S + 2R_G}}{R_M + \frac{2R_S R_G}{R_S + 2R_G}} \right)^2$

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		Toll-Free Number
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

**C011905**

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLYT094