

Why use a wall adapter for ac input power?

By Robert Kollman, Senior Applications Manager, Power Management, and John Betten, Applications Engineer, Member Group Technical Staff

Introduction


A DSL modem was chosen to examine the tradeoffs of using a wall adapter versus using an offline power supply. DSL modems are being widely deployed, with the number of new subscribers expected to grow at greater than a 50% compounded annual rate over the next four years. The number of new subscribers is expected to grow from 7 million this year to over 25 million in 2004. Because the DSL modem is a consumer product, cost is a very sensitive issue in its design; this cost ripples down into the power supply architecture selection. Designers are faced with two popular choices. In the first, a 50/60-Hz transformer, rectifier, and filter generate a low dc voltage that is then converted to well regulated outputs. In the second, ac input power is rectified and filtered, and a high-frequency switcher converts the resulting high-voltage dc to regulated voltages for the DSL electronics. While the second approach is generally cheaper in high-volume applications, it significantly complicates the modem design. The power supply is typically implemented on the same circuit card as the remainder of the electronics, and the high dc voltage introduces issues of agency approvals, noise, and size.

Table 1 presents typical VoIP DSL modem power supply requirements. Modems are generally required to run from ac wall power that has a wide voltage and frequency range. As with many modern systems, a number of low voltages power various analog and digital functions. In addition, two higher negative voltages power a telephony interface. The -24-V output provides power for the loop current while the telephone is in use. A -72-V output powers the phone ringing circuitry. As contrasted with the lower voltages, these outputs have widely varying load ranges, from essentially no load when the phone system is not in use, to full load on either output depending on whether the line is in use or simply ringing. Efficiency is generally not a critical issue as long as the heat can be removed; consequently, low-cost linear regulators are widely used.

Table 1. Typical VoIP DSL modem power supply requirements

PARAMETER	REQUIREMENTS			
Input voltage(s)	115/230 Vac, 50/60 Hz			
Output power	9.7 W max			
Output parameters	Voltage (V)	Max Current (A)	Max Ripple (mV_{pp})	Regulation (%)
	+5	0.65	50	±5
	+3.3	0.75	30	±3
	+1.8	0.40	30	±3
	+1.5	0.40	30	±3
	-28	0.05	500	±15
	-72	0.02	1000	±15
Efficiency	Very system-dependent from 50 to 85%			

Figure 1. A simple ac-to-dc unregulated wall adapter

 

What is an ac/dc wall adapter?

A wall adapter's function is to step down the raw 115/230-Vac line voltage into a safer, lower-voltage dc output that can be readily accepted by either the end use equipment or another power supply input. The output voltage tolerance over which the equipment being powered can operate determines whether additional voltage regulation is required. Some circuits, such as battery chargers, may not require a tightly regulated input voltage, and an unregulated dc input voltage may work just fine. In this case, the simplest way to generate that voltage is shown in Figure 1.

This circuit generates one output voltage; but multiple well regulated outputs are often needed. The most common ways to generate these voltages are with switching regulators, linear regulators, or a combination of both. If the unregulated input voltage is higher than the output voltages, multiple buck converters and/or linear regulators are often the best solution. Linear regulators would be used if the output current is not large so that excessive power is not dissipated in the device. In the case where only a single regulated output is needed, the switching converter can be placed either inside the ac/dc wall adapter, making this the entire power supply, or added as part of the end-use circuit. Depending on the goals of the overall product, either choice may be used. For example, if a smaller or lighter product is desired, then a regulated wall adapter would be used. If aesthetics, integration, or heavy loading are important goals, then putting the switcher with the end-use circuit would be the best solution.

Figure 2 shows the output voltage variation with an unregulated wall adapter. When loaded lightly, the output voltage is at its maximum because the output capacitor peak detects the transformer secondary. The capacitor stays fully charged during the entire line period due to low current draw. As the load is increased, the dc output voltage starts to droop. A large amount of primary winding resistance and leakage inductance is designed into the transformer to limit energy in a fault condition. A large portion of the leakage inductance is due to the separation between the primary and secondary windings required for UL approval. This can be in the form of either a split bobbin with the primary and secondary windings on opposite halves of the core or a large amount of insulating tape between the layer stacks. With increasing load current, a larger share of the transformer's voltage drops across the winding resistance and leakage inductance, reducing the

output voltage. Since the output diodes only conduct when the secondary voltage on the transformer exceeds the voltage on the output capacitor, the output capacitor provides the load current during a large portion of the line period. The larger the load becomes, the more voltage droop there will be across the output capacitor, since it must support the load entirely. Eventually, as the load is increased beyond its design limits, the output diodes and/or the transformer windings will overheat and fail as open circuits, reducing the output to zero volts. This failure does not usually happen instantly; and, as Figure 3 shows, peak output powers of approximately 150% of maximum power can be obtained for a duration of several seconds. However, this peak power occurs at voltages significantly lower than nominal.

Continued on next page

Figure 2. A 9-V/1.2-A ac/dc unregulated wall adapter output voltage


 


Figure 3. 50% additional peak power is available for short durations

 

Continued from previous page

What's the wall adapter approach?


Figure 4 shows a sample design of a DSL modem powered by a wall adapter. A wall adapter converts wall power to an unregulated 9 Vdc. With load ranges from 0 to 100% and input voltage tolerances of greater than $\pm 10\%$, the 9-V output can have a variation of over 6 to 15 V. Since the wall adapter is outside the modem and isolated, the 9-V input to the product does not represent a safety issue and can be simply routed within the modem. The 9-V input then drives multiple power stages to provide the user voltages. Buck converters and linear regulators generate the lower voltages for the digital and analog circuits, while a flyback power supply feeds the telephony interface circuits.

What's the offline approach?

Figure 5 represents the block diagram of an offline switcher for powering the DSL modem. The 115 Vac is rectified and filtered to provide an unregulated dc voltage of 240 Vdc to nearly 400 Vdc. This high voltage is switched by the fly-back converter primary FET and rectified into dc on the secondary side. The main regulated output voltage is

sensed and feedback to the primary side is used to maintain regulation over input line and output load variations. The telephony output voltages are unregulated and will vary some with line/load, while the lower voltage secondaries use linear regulators. The power transformer and the feedback optocoupler provide the required isolation between the primary input and secondary outputs. Care must be taken in the design of the power transformer to assure that proper spacing is maintained between primary and secondary windings to prevent arcing. Interwinding capacitances, improper grounding, and poor layouts can allow differential and common-mode currents to flow in the primary and/or secondaries and create noise voltages on the outputs as well as put EMI back into the source voltage. The input filter must be designed to suppress these currents to meet agency approvals. The designer must also be careful to use the proper voltage clearances between the optocoupler leads and between the transformer primary and secondary leads on the PWB itself, as well as between adjacent layers. The high voltage and isolation requirements present on the offline converter make the design somewhat more complicated than the wall adapter power supply.

Figure 4. Wall adapter power supply block diagram

 

So which approach should you use?

Figure 6 shows the two approaches in approximately the same scale, and many of the differences are very apparent. The wall adapter is large since it must operate at line frequency; however, it is generally located outside the product and will not impact the product size. The adapter is very aesthetically unpleasing, as it can take up more than one slot on a power strip or hang from a wall plug. However, as you look further downstream, it becomes clear why so

many products use the adapter. The wiring from it to the product is simpler due to lack of safety issues. The power supply in the product is simpler since it does not need to provide safety isolation or significant EMI filtering. As shown in the power supply in Figure 6b, EMI filter components and clearances can represent a third of the offline switcher board area. In addition, the offline power supply is another 20–30% larger since it has a transformer on board.

Continued on next page

Figure 5. Offline power supply block diagram


 


Figure 6. Wall adapter approach (a) requires significantly less PWB area

 

Continued from previous page

Table 2 presents a comparison of the two approaches. The first comparison is physical size. As shown in Figure 6, the wall adapter approach results in the smallest modem size, with an advantage of at least 4 in². The size of the design could be further reduced with the substitution of linear regulators for the buck power supplies. Component height favors the wall adapter approach also, as the input EMI filter components and power transformer of the offline approach drive its height 0.2 inches taller. Overall power supply weight favors the offline approach with its high-frequency transformer versus the very heavy line frequency transformer of the wall adapter approach.

Table 2 also includes relative costs of the two approaches. It includes product cost as well as engineering development time. In the very high-volume applications, where development cost does not represent a significant portion of the total cost, the offline approach has a slight cost advantage. Additionally, the offline inventory costs will be lower because a \$0.25 line cord will be needed rather than a \$2.00 wall adapter. However, in the lower-volume applications, the wall adapter has an advantage because it represents a simpler design with much lower qualification costs. Amortizing agency approvals over small production runs increases the costs of the offline approach. UL will take a much closer look at products with high voltage in them versus those where the high voltage is isolated within an approved wall adapter. The additional safety concerns will lengthen the time to market, necessitating additional time to make sure the design is correct before it is qualified. The DSL modems are also sensitive to power supply noise. The offline approach will switch 400 V on the primary that will have a higher likelihood of generating noise problems. All these factors raise the schedule risk of the offline approach, as the layout of the PWB will be more critical. Consequently, the offline approach will take a little more debug time.

So when is a wall adapter an appropriate choice? It is when production volumes are low, or when getting the product out quickly is key. It is typically not when production volumes are going to be high.

Table 2. Offline approach is cheaper but carries higher risk

	AC/DC POWER SUPPLY	WALL ADAPTER AND DC/DC POWER SUPPLY
PWB area (in ²)	10	6
Component height (in)	0.5	0.3
Weight (lbs)	0.4	1.6
Aesthetics	Integrated in product	Big ugly tacky transformer
Relative cost (10K units)	2.5	2.0
Relative cost (1M units)	1.0	1.1
UL	HV in product	Simpler approval
Relative time to market	Additional 2-4 weeks	Baseline
Relative risk	Highest	Lowest

For further information, contact:

GCI Technologies
1301 Precision Drive
Plano TX 75074-8636
Tel: (972) 423-8411

Power Supplies for Residential Telephony Systems
Robert Kollman and John Betten
Texas Instruments
12500 TI Boulevard
Dallas TX 75143

Related Web sites

www.ti.com/sc/docs/products/analog/device.html

Replace *device* with tl431a, tl1451a, tlc272, tps5103, tps76715, tps76718, tps76733 or ucc3809-2

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		ti-china@ti.com

C011905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated