

TPS65552A powers portable photoflash

By Scot Lester (Email: scotlester@ti.com)

Portable Power DC/DC Applications

Upper-end equipment for film-based or digital photography requires Xenon flash tubes to photograph in low-light conditions. Xenon flash tubes provide a burst of high-intensity light that is essential for photography of objects at a distance, moving at high speeds, or in low-light conditions. The light spectrum generated by a Xenon gas-discharge tube closely replicates that of the sun, providing very accurate color reproduction.

Xenon flash tubes require a high voltage across their electrodes to flash once a trigger signal is applied. This voltage is typically around 300 V. All of the energy needed to flash the lamp is stored in a bulk capacitor called a photoflash capacitor. Once the lamp is triggered, all of the energy stored in the photoflash capacitor is discharged through the flash tube to produce light. The stored energy in the photoflash capacitor is provided by a specialized boost converter that charges the photoflash capacitor up to 300 V from a much lower battery-input voltage. In the past, this converter was built of bulky discrete components that were difficult to incorporate into the space available in small devices such as cameras.


The Texas Instruments (TI) TPS65552A greatly simplifies and reduces the size of the photoflash charger circuit. Figure 1 shows a photoflash capacitor charger based on

this device. The TPS65552A provides all the necessary charging controls, output feedback, charge completion status, insulated gate bipolar transistor (IGBT) driver, and circuit protections necessary to implement a small, efficient photoflash charger.

The TPS65552A is based on a flyback topology. The output voltage is sensed during the off period of the internal switch, at which time the output voltage is reflected back to the input through the transformer. This eliminates the need for a bulky, high-voltage feedback network on the input and also provides electrical isolation from the input to the output. Once the output voltage reaches its target value, the TPS65552A automatically stops charging and an open-collector output goes low, thus signaling a “ready to flash” condition. This output can drive a status-indicating LED or an input to a microcontroller.

The I_PEAK pin of the TPS65552A controls the peak current that flows through the primary of the flyback transformer, T1, during each switch cycle. To adjust the capacitor charging time, the primary current can be dynamically adjusted from 0.9 to 1.8 A by changing the voltage applied to the I_PEAK pin. This feature allows a microcontroller to dynamically control the current draw of the charger for power management. For example, in a digital still camera,

Figure 1. TPS65552A photoflash capacitor charger

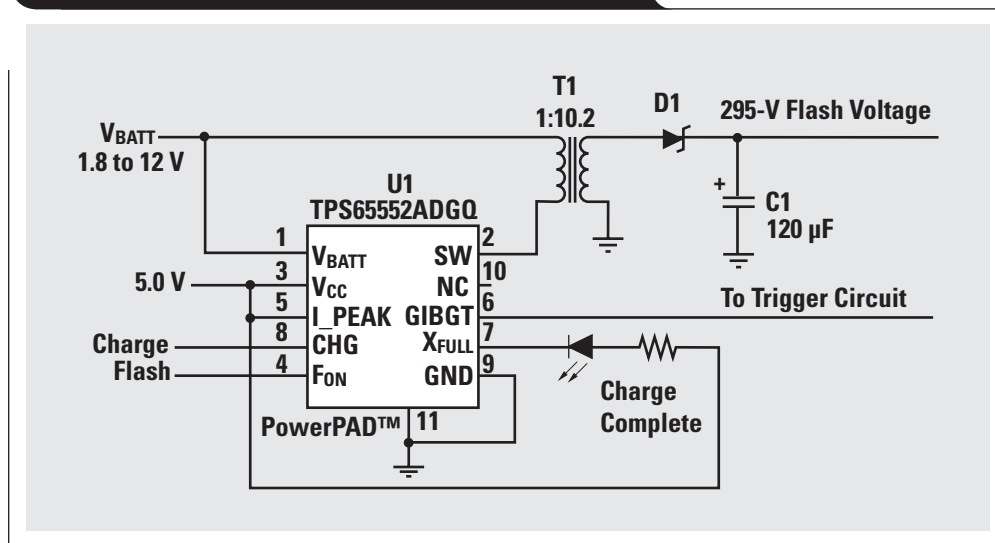

a microcontroller can reduce the charger current when a high-current zoom motor is operating, so that both the zoom motor and charger can function at the same time without exceeding the maximum current capability of the camera's battery (see Figure 2). This feature can also be used to extend battery run time. Reducing the peak currents during charging reduces the average current consumption so that a weak battery can still charge the photoflash capacitor.

Historically, the flash has been triggered with a push-button switch or a silicon-controlled rectifier (SCR). However, newer flash modes such as red-eye reduction use multiple bursts of the Xenon lamp. The lamp is triggered for a short flash that does not fully discharge the photoflash capacitor. Then, after a short delay, the lamp is retriggered for the main flash. The push button and SCR cannot reliably start and stop the lamp midflash. The IGBT is capable of handling the currents, which are typically 150 A during a flash. However, like a MOSFET, the IGBT gate requires a large current pulse to quickly turn on; so a high-current driver is required.

The TPS65552A has an integrated high-current buffer to drive the IGBT gate used in the trigger circuit. The IGBT can be driven on and off during flashes to support flash modes such as red-eye reduction or evaluated through the lens (E-TTL).

Reference

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title **TI Lit. #**

1. "Integrated Photo Flash Charger and IGBT Driver," TPS65552A Datasheetslvs567


Related Web sites

power.ti.com
www.ti.com/sc/device/TPS65552A

Table 1. Typical parts list for circuit in Figure 2

DEVICE	DESIGNATOR	DESCRIPTION	MANUFACTURER
330 FW 120A	C1	Capacitor, aluminum, 120 µF, 330 VDC, ±20%	Rubycon
C3216X7R2J223KT	C2	Capacitor, ceramic, 0.022 µF, 630 V, X7R, 10%	TDK
ES1G	D1	Diode, rectifier, 1 A, 400 V	Diodes Inc.
36FT050	FL1	Flash tube, 400 V max	Xicon
SSM25G45EM	Q1	Transistor, N-channel IGBT, 450 V, 150 A	Silicon Standard
CTX16-17360	T1	Transformer, flyback, 1:10.2	Coiltronics
422-2304	T2	Transformer, trigger	Xicon

Figure 2. Complete photoflash module with power and flash management

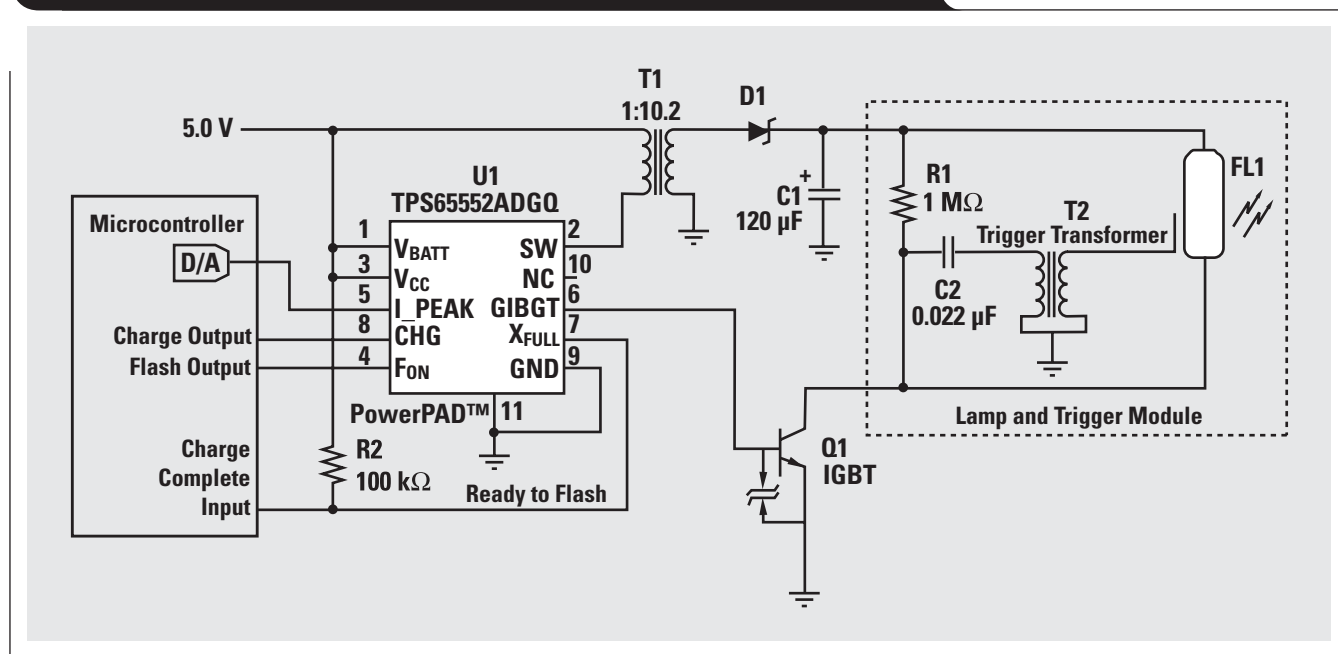

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (4) 95 98 10 701
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	180 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+49 (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	Malaysia	1-800-80-3973
China	800-820-8682	New Zealand	0800-446-934
Hong Kong	800-96-5941	Philippines	1-800-765-7404
India	+91-80-41381665 (Toll)	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Fax	+886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		
			ti-china@ti.com

C062706

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: PowerPAD is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2006 Texas Instruments Incorporated