

# A 3-A, 1.2-V<sub>OUT</sub> linear regulator with 80% efficiency and P<sub>LOST</sub> < 1 W

By Jeff Falin (Email: j-falin1@ti.com)

HPA Portable Power Applications

## Introduction

Using linear regulators for higher-current (>1-A), low-output voltage applications has been a challenge for many years due to the regulator's dropout requirements, related inefficiency, cumbersome output capacitor requirements for stability, and large inrush currents at startup. The Texas Instruments (TI) dual input rail TPS74x01 solves these problems.

## Linear regulator topology review

The primary drawback of linear regulators for higher-current applications is their low efficiency, computed as  $V_{OUT}/V_{IN}$ . The power lost ( $P_{LOST}$ ) in a linear regulator, computed as

$$1 - \frac{V_{OUT}}{V_{IN}} \times P_{IN} = (V_{IN} - V_{OUT}) \times I_{OUT},$$

must be dissipated by its package. The TO-263 or D2PAK package is the largest surface-mount package in which linear regulators are available. Without additional airflow, its maximum power dissipation capability is approximately 2.75 W (assuming it is soldered to a large copper plane for heat sinking). Many higher-current, "low-dropout" linear regulators with PMOS pass elements have minimum input voltages of 2.5 to 2.7 V, not only to power the internal

LDO drive circuitry but also to drive the PMOS FET hard enough to provide higher output currents.


Therefore, using many PMOS-pass-element-based linear regulators for output voltages below 1.8 V and output currents above 2.5 A is cumbersome and costly due to the additional airflow and/or external heat sinking required to dissipate the heat generated by the regulator.

Since NMOS FETs have inherently lower  $r_{DS(on)}$  than similarly current-rated PMOS FETs, an NMOS FET pass element needs less  $V_{IN} - V_{OUT}$  drop to provide the same current. However, the source-follower configuration of the NMOS-based regulator requires that the gate of the FET be at least a threshold voltage drop (typically 1 V) above the output voltage. The regulator needs either an internal charge pump to provide a higher gate-drive voltage or, more simply, a second low-power input rail from an existing 5-V or 3.3-V bias supply. This is the reasoning behind the development of the dual-rail, NMOS-pass-element-based TPS74x01 family of linear regulators.

## Dropout

As shown in Figure 1, the TPS74x01 regulators have two input voltages, one providing the low-current bias voltage to power the internal circuitry that controls the NMOS pass device and one as a second power input. Since all the

**Figure 1. Block diagram of the TPS74201 and TPS74401 linear regulators**

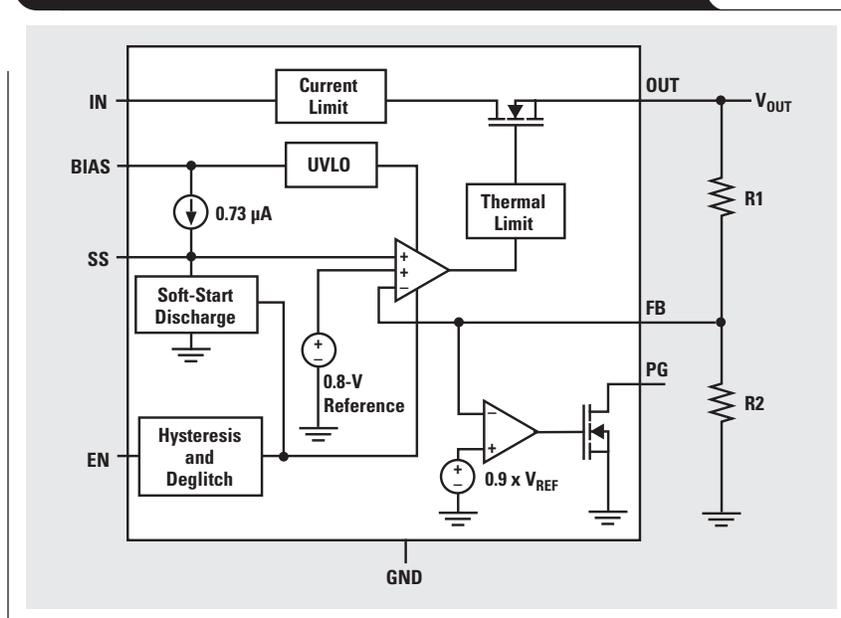

internal circuits run off the higher BIAS input, the device is capable of achieving regulation from a low-voltage input supply. In fact, the power input,  $I_{IN}$ , is limited only by the output voltage and dropout of the device.

There are two different specifications for dropout voltage with the TPS74x01. The first is referred to as  $V_{IN}$  dropout and is for users who wish to apply an external bias voltage to achieve low dropout. This specification assumes that  $V_{BIAS}$  is at least 1.62 V above  $V_{OUT}$ . Such an application might be a low-ripple, 1.2-V, 3-A power rail for an FPGA transceiver where  $V_{IN}$  and  $V_{BIAS}$  are provided by 1.5-V and 3.3-V switching supplies, respectively. In this configuration, the 3 × 3-mm QFN package, which is capable of dissipating 1.9 W at 55°C, needs to dissipate only

$$(1.5 \text{ V} - 1.2 \text{ V}) \times 3 \text{ A} = 0.9 \text{ W},$$

thereby achieving  $1.2 \text{ V}/1.5 \text{ V} = 80\%$  efficiency.


The second specification is referred to as  $V_{BIAS}$  dropout and is for users who wish to tie the IN and BIAS pins together. This allows the device to be used in applications where an auxiliary bias voltage is not available or low dropout is not required. Dropout is limited by BIAS in these applications because  $V_{BIAS}$  provides the gate drive to the pass FET and therefore must be 1.4 V above  $V_{OUT}$ . For example, the TPS74201 can provide a 3.3-V, 1.0-A soft-starting supply (discussed later) from a 5-V rail with  $3.3 \text{ V}/5 \text{ V} = 66\%$  efficiency and can dissipate

$$(5 \text{ V} - 3.3 \text{ V}) \times 1.0 \text{ A} = 1.7 \text{ W}.$$

## Stability and transient response

Until recently, linear regulator loop stability presented a challenge to analog IC designers because one of the control-loop poles, created by the output capacitor and the impedance at the load, varies in frequency location based on the output current. Regulators with the NMOS pass element in source-follower configuration have always been slightly easier to compensate because their output impedances are lower than similarly rated PMOS regulators in common-source configurations. This means that the NMOS regulator's moving pole is higher in frequency than the comparably rated PMOS counterpart and so is further away from the internal error amplifier's pole(s). Older methods of ensuring stability were either to roll off the control-loop response at low frequency, thereby killing transient response, or to counteract the moving pole with a zero created by an output capacitor with a certain amount of equivalent series

**Figure 2. Load transient response with various output capacitors**

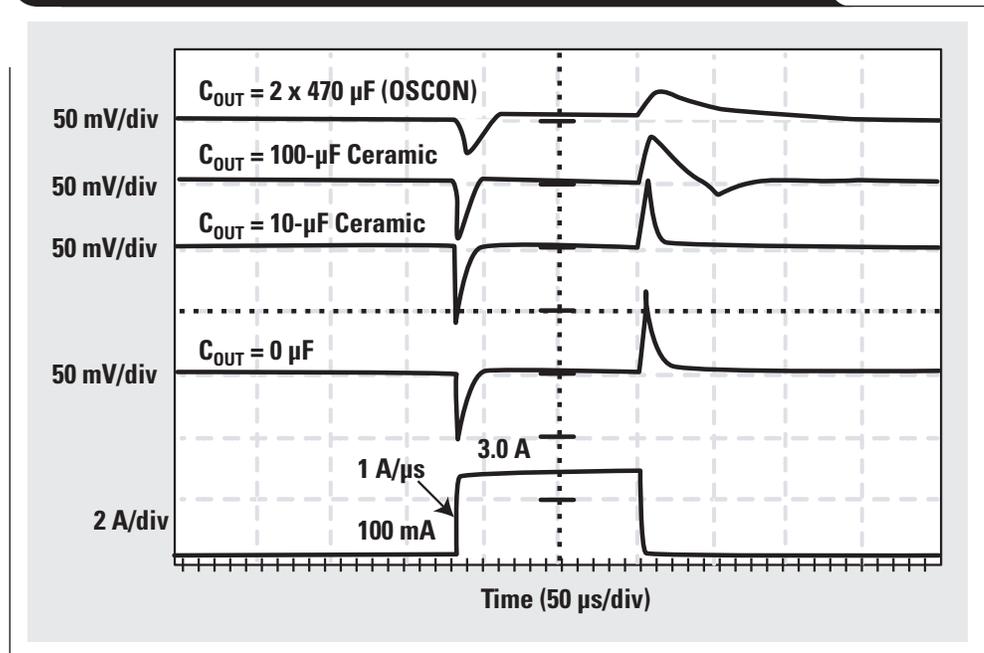

resistance (ESR). Using a patented feedback control topology, the TPS74x01 family, configured with  $V_{BIAS} = 3.3 \text{ V}$ ,  $V_{IN} = 1.8 \text{ V}$  and  $V_{OUT} = 1.5 \text{ V}$ , achieves fast transient response times (see Figure 2) with no output capacitors but is still stable with larger capacitors having ESR. The absence of output voltage ringing after the load transient shows that the regulator is very stable with no output capacitance.

Since the TPS74x01 family is stable with no output capacitor but has such fast transient response, local bypass capacitance for the device under power may be sufficient to meet the transient requirements of many FPGAs and DSPs. This reduces total solution cost by eliminating the need to have multiple bulk capacitors for the power rail.

## Soft start and sequencing

Many older linear regulators start up fast because the feedback loop senses the low output voltage and turns on the pass FET hard. For some applications, fast startup is required; however, such fast turn-on causes large inrush currents, up to the current-limit rating of the device, to charge output capacitors. These large currents may pull down the input power bus and cause system-level problems. To achieve a linear and monotonic soft start that reduces peak inrush current during startup and minimizes startup transients seen by the input power bus, the TPS74201 and TPS74401 error amplifiers track the voltage ramp of the external soft-start capacitor until its voltage exceeds the internal reference. The soft-start ramp time is dependent on the soft-start charging current ( $I_{SS}$ ), soft-start capacitance ( $C_{SS}$ ), and the internal reference voltage ( $V_{REF}$ ). It can be calculated with

$$t_{SS} = \frac{V_{REF} \times C_{SS}}{I_{SS}}.$$

Note that since the soft start is voltage-controlled, the startup is not dependent on the output load.

Instead of an SS pin, the TPS74301 version has a TRACK pin. As summarized in Figure 3, with the center tap of a resistor divider from an external supply connected to TRACK, the TPS74301's output voltage will track the external supply until the TRACK voltage reaches 0.8 V. This feature can be used to implement simultaneous or ratiometric sequencing. It is useful for minimizing the stress on ESD structures that are present between the Core and I/O power pins of many processors and/or for managing integrated power-on reset circuitry. All members of the TPS74x01 family facilitate implementation of sequential sequencing by tying the integrated PG signal to the EN pin of a following supply.

**Conclusion**

With a dual input rail and low dropout voltage, the TPS74x01 family has made linear regulators more appealing than switching regulators, reducing board size and cost and providing comparable efficiency for powering many lower-voltage, higher-output-current power rails. The family's additional features—including controllable soft starting, tracking, and integrated PG—manage start-up problems that have plagued linear regulators in the past. Add in

the fast transient response, which minimizes the total number of output capacitors, and you have a nearly ideal dc/dc converter.

**References**


For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. "1.5-A LDO with Programmable Soft-Start," TPS74201 Datasheet . . . . .	.sbvs064
2. "1.5A Ultra-Low Dropout Linear Regulator with Programmable Sequencing," TPS74301 Datasheet . . . . .	.sbvs065
3. "3.0A Ultra-Low Dropout Linear Regulator," TPS74401 Datasheet . . . . .	.sbvs066

**Related Web sites**

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with TPS74201, TPS74301, or TPS74401

**Figure 3. Various sequencing methods using the TRACK pin**

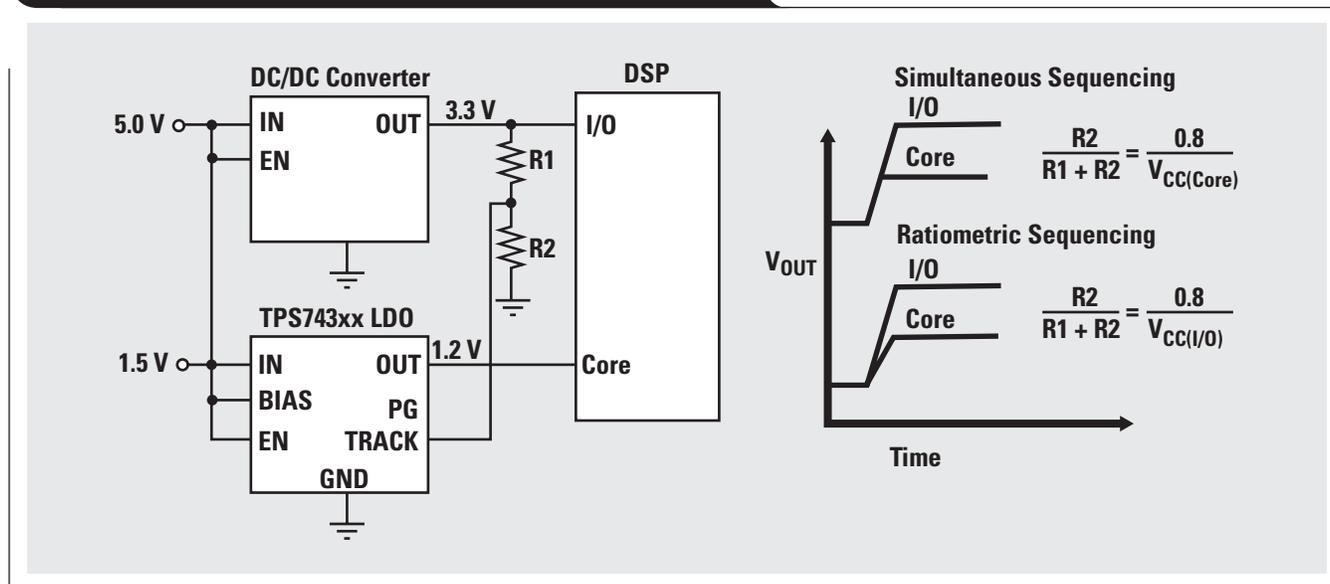

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Management	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (4) 95 98 10 701
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	180 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	Malaysia	1-800-80-3973
China	800-820-8682	New Zealand	0800-446-934
Hong Kong	800-96-5941	Philippines	1-800-765-7404
India	+91-80-41381665 (Toll)	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Fax	+886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		
			<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

### C062706

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2006 Texas Instruments Incorporated