

# Using power solutions to extend battery life in MSP430™ MCU applications

By Michael Day

Applications Manager, Portable Power Products  
(Updated by Ritu Khanna, 4Q 2019)


The MSP430™ MCU is the lowest-power microprocessor available in the market. Its inherently low-power operation is ideal for battery-powered applications where frequent battery replacement is undesirable. This article shows two simple but effective power solutions that further minimize MSP430 power consumption and extend battery life.

In an attempt to prolong battery life, software engineers go to great lengths to optimize code, minimize memory accesses, etc. Hardware engineers focus on ways to shut down unused circuitry, ensure that all quiescent currents and leakage paths are minimized, and maximize power-supply efficiency.

In most cases, engineers eliminate any DC/DC conversion altogether if the system's source voltage falls within the MSP430's input operating range. Many MSP430 designs do not need an input power supply because the MSP430 device family accepts extremely wide variations in input voltage. For example, the MSP430FG4618 operates with an input voltage of between 1.8 V and 3.6 V. Because of this wide input range, many MSP430 designs operate directly from a battery without additional power conversion. Examples of input sources that do not need power conversion are dual alkaline, nickel metal hydride, and nickel cadmium batteries, as well as primary lithium-ion coin cells.

An often overlooked technique for extending battery life is to add an input power supply, even if it is otherwise not needed. Adding a power supply between the input-voltage source and the MSP430 to increase battery life is contradictory to conventional thinking. This is because of two things that all power supplies have in common: They have quiescent current ( $I_q$ ) at no load that sinks current from the battery to ground; and they have less than 100% efficiency, which dissipates power in the power supply. Even power supplies optimized for low-power and battery-powered applications have less than 100% efficiency, with quiescent currents that continually drain battery capacity. Typical power-supply efficiencies for an MSP430 application operating at 3.0 V from two AA batteries is 85 to 92%. Typical  $I_q$  values range from 15 to 50  $\mu$ A. Conventional thinking says that removing this power supply and

Figure 1. MSP430FG4618's supply current versus its supply voltage

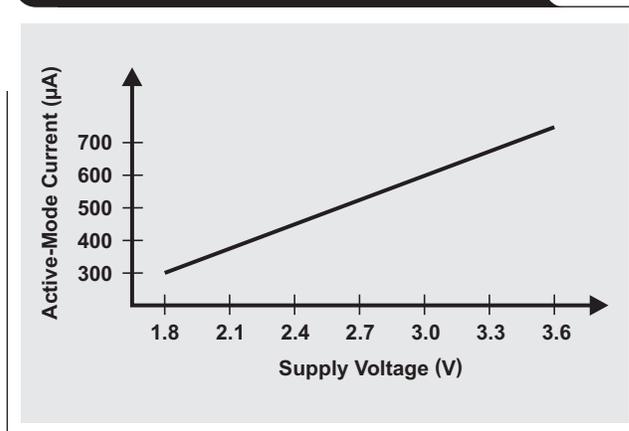

operating the application directly from the battery will extend battery life by an additional 8 to 15% because the effective efficiency will then be 100%.

MSP430 supply current varies linearly with input voltage, so operating the system with lower voltages reduces both MSP430 input current and overall power consumption. Figure 1 shows the variation in the MSP430FG4618's 1-MHz active-mode supply current ( $I_{AM}$ ) versus its supply voltage.

Operating at the lowest required input voltage minimizes battery current, but this requires the insertion of a power supply. Regardless of topology, this power supply will be less than 100% efficient. A common design scenario is an MSP430 operating from two series-connected AA alkaline batteries that supply 3.2 V when new and 1.8 V when discharged. The designer must choose between two power-system topologies. The first is to operate directly from the battery voltage, which results in a higher MSP430 input current. The second is to insert a power supply between the battery and the MSP430. After considering the power supply's efficiency and quiescent current, many designers quickly choose to operate directly from the input source. Few designers are aware that adding a power supply can actually provide significant improvements in battery life, even with efficiency and quiescent-current concerns.

Designers must deviate from conventional thinking that efficiency is the most important figure of merit in a power system. In a battery-powered system, battery current drain is the main concern. The examples in Figure 2 help make this point. System 1 in Figure 2a operates directly from two AA alkaline batteries. An equivalent power supply in this example has 100% efficiency and 0- $\mu$ A quiescent current. All power delivered from the battery is available to the MSP430. For System 2 in Figure 2b, a TPS7A02 LDO has been inserted. The LDO's efficiency is defined by  $V_{OUT}/V_{IN}$ , which averages to approximately 90% over the entire voltage range of the batteries. The LDO also draws 25 nA of quiescent current from the battery. When only efficiency and quiescent current are considered, System 1 clearly wins. However, System 2 draws less current from the batteries, which extends the system's operating time.

Figure 3 compares the two systems' battery currents. When the battery voltage is above 2.2 V, System 1 consumes more battery current because the MSP430 operating current is a linear function of input voltage. System 2 consumes a constant current because the LDO maintains a constant 2.2 V at the MSP430. As the battery voltage drops to 2.2 V and below, the two MSP430s consume the same current. System 2 consumes an additional 25 nA due to the TPS7A02's quiescent current ( $I_q$ ). When the input voltage is above 2.2 V, System 2's reduced battery current results in longer system run time.


Two lab experiments were conducted with an MSP430FG4618 operating at 5 MHz while powered by two AAA alkaline batteries. These experiments were set up to correspond with the two systems in the previous example. In this second example, System 1, with the MSP430 powered directly from the batteries, operated for 223 hours before shutting down. System 2, which used a TPS7A02 to drop the MSP430 operating voltage to 2.2 V, operated for 298 hours before shutting down. The addition of the TPS7A02 LDO, which operates at 90% efficiency with these operating conditions, extended battery life by 30%.

When designing an MSP430 power system, an engineer should pay close attention to selecting the proper operating voltage. Minimizing the nominal operating voltage will provide significant improvements in a system's run time.


**Related Web sites**

- [power.ti.com](http://power.ti.com)
- [www.ti.com/msp430](http://www.ti.com/msp430)
- [www.ti.com/product/MSP430FG4618](http://www.ti.com/product/MSP430FG4618)
- [www.ti.com/product/TPS7A02](http://www.ti.com/product/TPS7A02)
- [www.ti.com/product/TPS7A03](http://www.ti.com/product/TPS7A03)

**Figure 2. Two alkaline-system configurations**

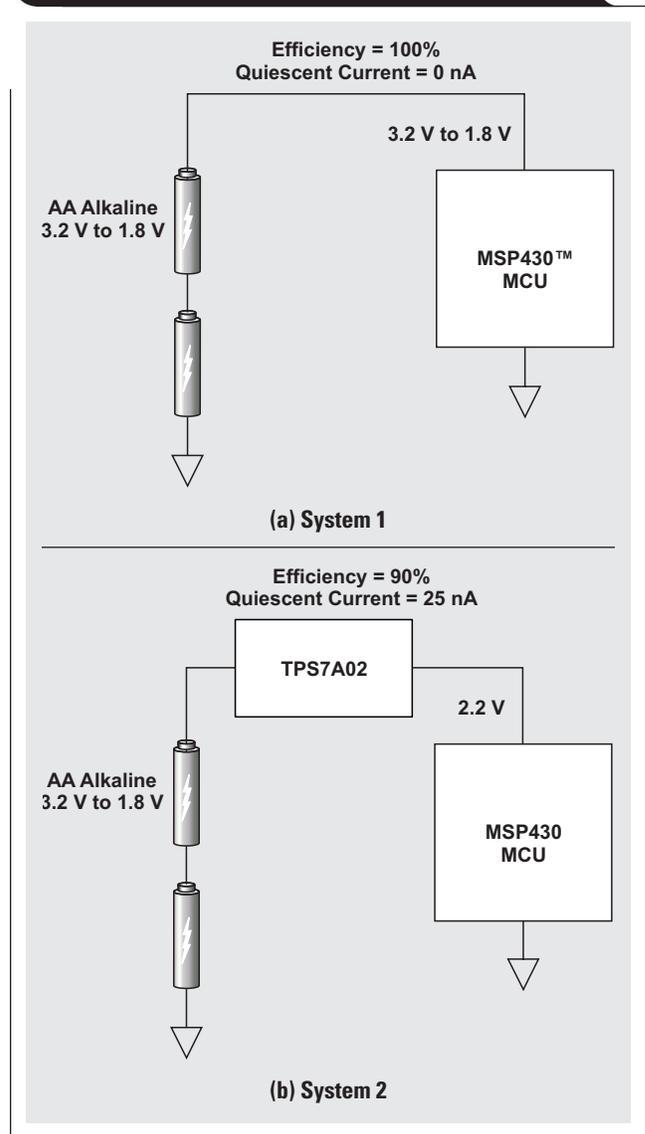

**Figure 3. MSP430's operating current versus battery voltage**

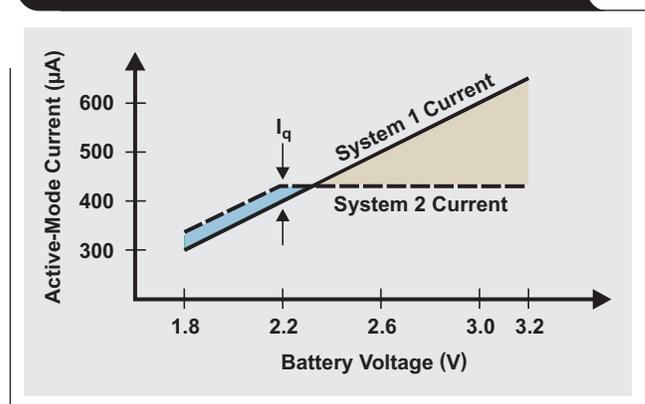

## TI Worldwide Technical Support

---

### **TI Support**

Thank you for your business. Find the answer to your support need or get in touch with our support center at

[www.ti.com/support](http://www.ti.com/support)

China: <http://www.ti.com.cn/guidedsupport/cn/docs/supporthome.tsp>

Japan: <http://www.tij.co.jp/guidedsupport/jp/docs/supporthome.tsp>

### **Technical support forums**

Search through millions of technical questions and answers at TI's E2E™ Community (engineer-to-engineer) at

[e2e.ti.com](http://e2e.ti.com)

China: <http://www.deyisupport.com/>

Japan: <http://e2e.ti.com/group/jp/>

### **TI Training**

From technology fundamentals to advanced implementation, we offer on-demand and live training to help bring your next-generation designs to life. Get started now at

[training.ti.com](http://training.ti.com)

China: <http://www.ti.com.cn/general/cn/docs/gencontent.tsp?contentId=71968>

Japan: <https://training.ti.com/jp>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011617

E2E and MSP430 are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

© 2009, 2019 Texas Instruments Incorporated.  
All rights reserved.



SLYT356A

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated