

# Designing DC/DC converters based on ZETA topology

By Jeff Falin

*Senior Applications Engineer*

## Introduction

Similar to the SEPIC DC/DC converter topology, the ZETA converter topology provides a positive output voltage from an input voltage that varies above and below the output voltage. The ZETA converter also needs two inductors and a series capacitor, sometimes called a flying capacitor. Unlike the SEPIC converter, which is configured with a standard boost converter, the ZETA converter is configured from a buck controller that drives a high-side PMOS FET. The ZETA converter is another option for regulating an unregulated input-power supply, like a low-cost wall wart. To minimize board space, a coupled inductor can be used. This article explains how to design a ZETA converter running in continuous-conduction mode (CCM) with a coupled inductor.


## Basic operation

Figure 1 shows a simple circuit diagram of a ZETA converter, consisting of an input capacitor,  $C_{IN}$ ; an output capacitor,  $C_{OUT}$ ; coupled inductors L1a and L1b; an AC coupling capacitor,  $C_C$ ; a power PMOS FET, Q1; and a diode, D1. Figure 2 shows the ZETA converter operating in CCM when Q1 is on and when Q1 is off.


To understand the voltages at the various circuit nodes, it is important to analyze the circuit at DC when both switches are off and not switching. Capacitor  $C_C$  will be in parallel with  $C_{OUT}$ , so  $C_C$  is charged to the output voltage,  $V_{OUT}$ , during steady-state CCM. Figure 2 shows the voltages across L1a and L1b during CCM operation.

When Q1 is off, the voltage across L1b must be  $V_{OUT}$  since it is in parallel with  $C_{OUT}$ . Since  $C_{OUT}$  is charged to  $V_{OUT}$ , the voltage across Q1 when Q1 is off is  $V_{IN} + V_{OUT}$ ; therefore the voltage across L1a is  $-V_{OUT}$  relative to the drain of Q1. When Q1 is on, capacitor  $C_C$ , charged to  $V_{OUT}$ , is connected in series with L1b; so the voltage across L1b is  $+V_{IN}$ , and diode D1 sees  $V_{IN} + V_{OUT}$ .

**Figure 1. Simple circuit diagram of ZETA converter**

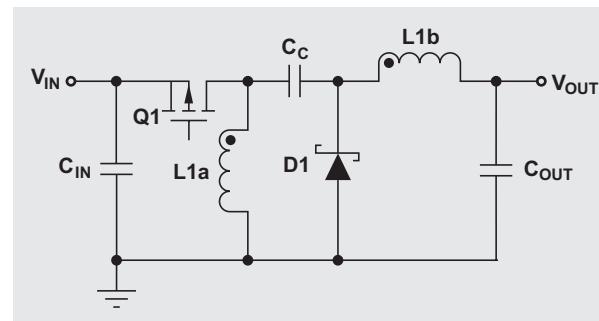

**Figure 2. ZETA converter during CCM operation**

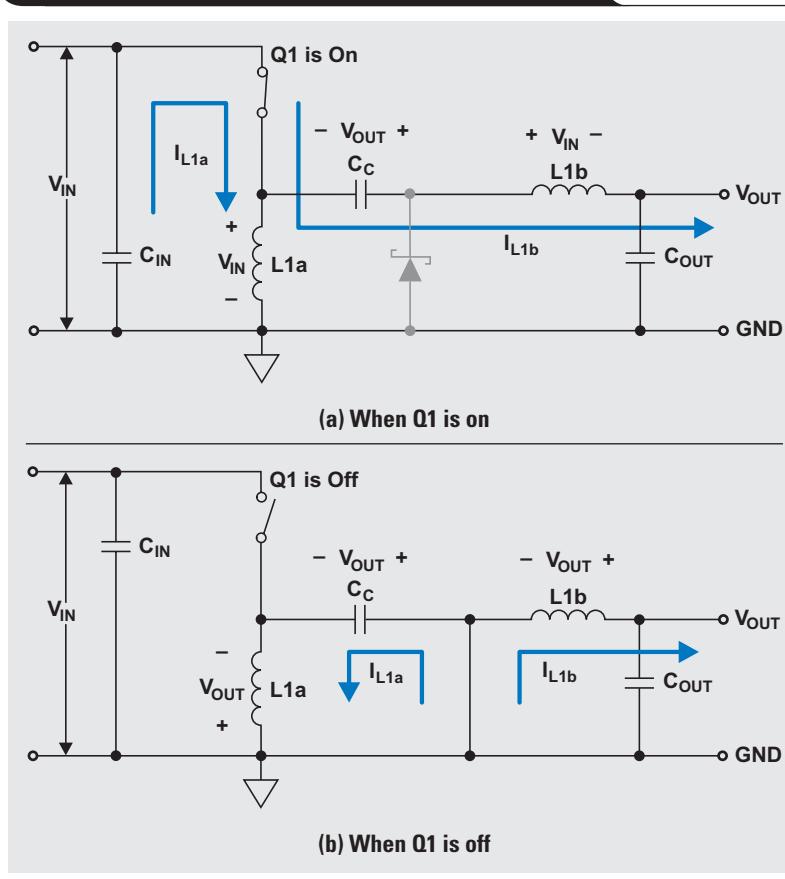

The currents flowing through various circuit components are shown in Figure 3. When Q1 is on, energy from the input supply is being stored in L1a, L1b, and C<sub>C</sub>. L1b also provides I<sub>OUT</sub>. When Q1 turns off, L1a's current continues to flow from current provided by C<sub>C</sub>, and L1b again provides I<sub>OUT</sub>.

### Duty cycle

Assuming 100% efficiency, the duty cycle, D, for a ZETA converter operating in CCM is given by

$$D = \frac{V_{OUT}}{V_{IN} + V_{OUT}}. \quad (1)$$

This can be rewritten as

$$\frac{D}{1-D} = \frac{I_{IN}}{I_{OUT}} = \frac{V_{OUT}}{V_{IN}}. \quad (2)$$

D<sub>max</sub> occurs at V<sub>IN(min)</sub>, and D<sub>min</sub> occurs at V<sub>IN(max)</sub>.

### Selecting passive components

One of the first steps in designing any PWM switching regulator is to decide how much inductor ripple current, ΔI<sub>L(PP)</sub>, to allow. Too much increases EMI, while too little may result in unstable PWM operation. A rule of thumb is to assign a value for K between 0.2 and 0.4 of the average input current. A desired ripple current can be calculated as follows:

$$\begin{aligned} \text{Desired } \Delta I_{L(PP)} &= K \times I_{IN} \\ &= K \times I_{OUT} \times \frac{D}{1-D}. \end{aligned} \quad (3)$$

In an ideal, tightly coupled inductor, with each inductor having the same number of windings on a single core, the coupling forces the ripple current to be split equally between the two coupled inductors. In a real coupled inductor, the inductors do not have equal inductance and the ripple currents will not be exactly equal. Regardless, for a desired ripple-current value, the inductance required in a coupled inductor is estimated to be half of what would be needed if there were two separate inductors, as shown in Equation 4:


$$L1a_{min} = L1b_{min} = \frac{1}{2} \times \frac{V_{IN} \times D}{\Delta I_{L(PP)} \times f_{SW(min)}} \quad (4)$$

To account for load transients, the coupled inductor's saturation current rating needs to be at least 1.2 times the steady-state peak current in the high-side inductor, as computed in Equation 5:

$$I_{L1a(PK)} = I_{OUT} \times \frac{D}{1-D} + \frac{\Delta I_L}{2} \quad (5)$$

Note that I<sub>L1b(PK)</sub> = I<sub>OUT</sub> + ΔI<sub>L</sub>/2, which is less than I<sub>L1a(PK)</sub>.

**Figure 3. ZETA converter's component currents during CCM**

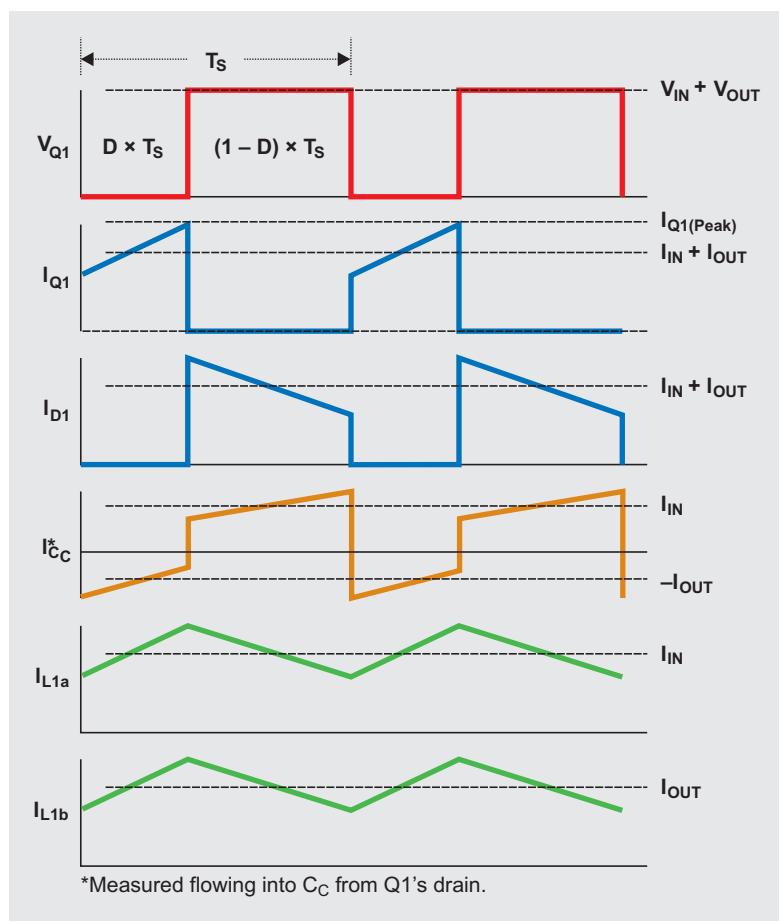

Like a buck converter, the output of a ZETA converter has very low ripple. Equation 6 computes the component of the output ripple voltage that is due solely to the capacitance value:

$$\Delta V_{C_{OUT}(PP)} = \frac{\Delta I_{L1b(PP)} [\text{at } V_{IN(max)}]}{8 \times C_{OUT} \times f_{SW(min)}}, \quad (6)$$

where f<sub>SW(min)</sub> is the minimum switching frequency. Equation 7 computes the component of the output ripple voltage that is due solely to the output capacitor's ESR:

$$\Delta V_{ESR-C_{OUT}(PP)} = \Delta I_{L1b(PP)} [\text{at } V_{IN(max)}] \times ESR_{C_{OUT}} \quad (7)$$

Note that these two ripple-voltage components are phase-shifted and do not directly add together. For low-ESR (e.g., ceramic) capacitors, the ESR component can be ignored. A minimum capacitance limit may be necessary to meet the application's load-transient requirement.

The output capacitor must have an RMS current rating greater than the capacitor's RMS current, as computed in Equation 8:

$$I_{C_{OUT}(RMS)} = \frac{\Delta I_{L1b(PP)} [\text{at } V_{IN(max)}]}{\sqrt{3}} \quad (8)$$

The input capacitor and the coupling capacitor source and sink the same current levels, but on opposite switching cycles. Similar to a buck converter, the input capacitor and the coupling capacitor need the RMS current rating,

$$I_{C_{IN}(RMS)} = I_{C_C(RMS)} = I_{OUT} \sqrt{\frac{V_{OUT}}{V_{IN(min)}}}. \quad (9)$$

Equations 10a and 10b compute the component of the output ripple voltage that is due solely to the capacitance value of the respective capacitors:

$$\Delta V_{C_{IN}(PP)} = \frac{D_{max} \times I_{OUT}}{C_{IN} \times f_{SW(min)}} \quad (10a)$$

$$\Delta V_{C_C(PP)} = \frac{D_{max} \times I_{OUT}}{C_C \times f_{SW(min)}} \quad (10b)$$

Equations 11a and 11b compute the component of the output ripple voltage that is due solely to the ESR value of the respective capacitors:

$$\begin{aligned} \Delta V_{ESR\_C_{IN}(PP)} &= (I_{IN(max)} + I_{OUT}) \times ESR_{C_{IN}} \\ &= \frac{I_{OUT}}{1 - D_{max}} \times ESR_{C_{IN}} \end{aligned} \quad (11a)$$

$$\begin{aligned} \Delta V_{ESR\_C_C(PP)} &= (I_{IN(max)} + I_{OUT}) \times ESR_{C_C} \\ &= \frac{I_{OUT}}{1 - D_{max}} \times ESR_{C_C} \end{aligned} \quad (11b)$$

Again, the two ripple-voltage components are phase-shifted and do not directly add together; and, for low-ESR capacitors, the ESR component can again be ignored. A typical ripple value is less than 0.05 times the input voltage for the input capacitor and less than 0.02 times the output voltage for the coupling capacitor.

### Selecting active components

The power MOSFET, Q1, must be carefully selected so that it can handle the peak voltage and currents while minimizing power-dissipation losses. The power FET's current rating will determine the ZETA converter's maximum output current.

As shown in Figure 3, Q1 sees a maximum voltage of  $V_{IN(max)} + V_{OUT}$ . Q1 must have a peak-current rating of  $I_{Q1(PK)} = I_{L1a(PK)} + I_{L1b(PK)} = I_{IN} + I_{OUT} + \Delta I_L$ . (12)

At the ambient temperature of interest, the FET's power-dissipation rating must be greater than the sum of the conductive losses (a function of the FET's  $r_{DS(on)}$ ) and the switching losses (a function of the FET's gate charge) as given in Equation 13:

$$\begin{aligned} P_{D\_Q1} &= P_{r_{DS(on)}} + P_{SWG} + P_{Gate} \\ &= I_{Q1(RMS)}^2 \times r_{DS(on)} \\ &\quad + (V_{IN(max)} + V_{OUT}) \times I_{Q1(PK)} \times Q_{GD} / I_{Gate} \times f_{SW(max)} \\ &\quad + V_{Gate} \times Q_G \times f_{SW(max)}, \end{aligned} \quad (13)$$

where  $Q_{GD}$  is the gate-to-drain charge,  $Q_G$  is the total gate charge of the FET,  $I_{Gate}$  is the maximum drive current, and  $V_{Gate}$  is the maximum gate drive from the controller. Q1's RMS current is

$$\begin{aligned} I_{Q1(RMS)} &= (I_{IN(max)} + I_{OUT}) \times \sqrt{D_{max}} \\ &= \frac{I_{OUT} \times V_{OUT}}{V_{IN(min)} \times \sqrt{D_{max}}}. \end{aligned} \quad (14)$$

The output diode must be able to handle the same peak current as Q1,  $I_{Q1(PK)}$ . The diode must also be able to withstand a reverse voltage greater than Q1's maximum voltage ( $V_{IN(max)} + V_{OUT}$ ) to account for transients and ringing. Since the average diode current is the output current, the diode's package must be capable of dissipating up to  $I_{OUT} \times V_{FWD}$ , where  $V_{FWD}$  is the Schottky diode's forward voltage at  $I_{OUT}$ .

### Loop design

The ZETA converter is a fourth-order converter with multiple real and complex poles and zeroes. Unlike the SEPIC converter, the ZETA converter does not have a right-half-plane zero and can be more easily compensated to achieve a wider loop bandwidth and better load-transient results with smaller output-capacitance values. Reference 1 provides a good mathematical model based on state-space averaging. The model excludes inductor DC resistance (DCR) but includes capacitor ESR. Even though the converter in Reference 1 uses ceramic capacitors, for the following design example, the inductor DCR was substituted for the capacitor ESR so that the model would more closely match measured values. The open-loop gain bandwidth (i.e., the frequency where the gain crosses zero with an acceptable phase margin of typically 45°), should be greater than the resonant frequency of L1b and  $C_C$  so that the feedback loop can dampen the nonsinusoidal ripple on the output with fundamental frequency at that resonant frequency.

### Design example

For this example, the requirements are for a 12-V, 1-W supply with  $\eta = 0.9$  peak efficiency. The load is steady-state, so few load transients are expected. The 2-A input supply is 9 to 15 V. A nonsynchronous voltage-mode controller, the Texas Instruments TPS40200, was selected, running with a switching frequency between 340 and 460 kHz. The maximum allowed ripple at the input and flying capacitor is respectively 1% of the maximum voltage across each. The maximum output ripple is 25 mV, and the maximum ambient temperature is 55°C. Because EMI is not a concern, an inductor with a lower inductance value was selected by using the minimum input voltage. Table 1 on the next page summarizes the design calculations given earlier. Equations 7 through 9 and Equation 11 were ignored because low-ESR ceramic capacitors with high RMS current ratings were used.

**Table 1. Computations for example ZETA-converter design**

BASED ON DESIGN EQUATION	COMPUTATION (ASSUMING $\eta = 1$ )	ADJUSTED FOR $\eta = 0.9$	SELECTED COMPONENT/RATING
<b>Passive Components</b>			
(1)	$D_{\max} = \frac{12 \text{ V}}{12 \text{ V} + 9 \text{ V}} = 0.57$	N/A	N/A
(1)	$D_{\min} = \frac{12 \text{ V}}{12 \text{ V} + 15 \text{ V}} = 0.44$	N/A	N/A
(2)	$I_{IN(\max)} = 1 \text{ A} \times \frac{0.57}{1 - 0.57} = 1.33 \text{ A}$	$\frac{1.33 \text{ A}}{0.9} = 1.48 \text{ A}$	N/A
(3)	Desired $\Delta I_{L(PP)}$ [at $V_{IN(\min)}$ ] = $0.3 \times 1.33 \text{ A} = 0.4 \text{ A}$	$\frac{0.4 \text{ A}}{0.9} = 0.44 \text{ A}$	N/A
(4) using $V_{IN(\min)}$	$L_{1a} = L_{1b} = \frac{1}{2} \times \frac{9 \text{ V} \times 0.57}{0.40 \text{ A} \times 340 \text{ kHz}} = 18.9 \mu\text{H}$	$18.9 \mu\text{H} \times 0.9 = 17.0 \mu\text{F}$	Coilcraft MSD1260: $22 \mu\text{H} - I_{RMS} = 1.76 \text{ A}$ in each winding simultaneously, $I_{SAT} = 5 \text{ A}$
(4) at $V_{IN(\min)}$	Actual $\Delta I_{L(PP)} = \frac{1}{2} \times \frac{9 \text{ V} \times 0.57}{22 \mu\text{H} \times 340 \text{ kHz}} = 0.34 \text{ A}$	N/A	
(5)	$I_{L1a(PK)} = 1.33 \text{ A} + \frac{0.34 \text{ A}}{2} = 1.50 \text{ A}$	$1.48 \text{ A} + \frac{0.34 \text{ A}}{2} = 1.65 \text{ A}$	
(4) at $V_{IN(\max)}$	Actual $\Delta I_{L(PP)} = \frac{1}{2} \times \frac{15 \text{ V} \times 0.44}{22 \mu\text{H} \times 340 \text{ kHz}} = 0.45 \text{ A}$	N/A	N/A
(6)	$C_{OUT(\min)} = \frac{0.44 \text{ A}}{8 \times 0.025 \text{ V} \times 340 \text{ kHz}} = 6.5 \mu\text{F}$	N/A	Two 10- $\mu\text{F}$ , 25-V X5R ceramics and one 4.7- $\mu\text{F}$ , 25-V X5R ceramic to provide good load-transient response and to accommodate ceramic capacitor derating
(10a) for $C_{IN}$	$C_{IN(\min)} = \frac{0.57 \times 1 \text{ A}}{0.01 \times 15 \text{ V} \times 340 \text{ kHz}} = 11.2 \mu\text{F}$	$\frac{11.2 \mu\text{F}}{0.9} = 12.4 \mu\text{F}$	Two 10- $\mu\text{F}$ , 25-V X5R ceramics and one 4.7- $\mu\text{F}$ , 25-V X5R ceramic to accommodate ceramic capacitor derating
(10b) for $C_C$	$C_{C(\min)} = \frac{0.57 \times 1 \text{ A}}{0.01 \times 12 \text{ V} \times 340 \text{ kHz}} = 14 \mu\text{F}$	$\frac{14 \mu\text{F}}{0.9} = 15.6 \mu\text{F}$	Three 10- $\mu\text{F}$ , 25-V X5R ceramics to accommodate ceramic capacitor derating
<b>Active Components</b>			
(12)	$I_{Q1(PK)} = 1.33 \text{ A} + 1 \text{ A} + 0.34 \text{ A} = 2.67 \text{ A}$	$1.48 \text{ A} + 1 \text{ A} + 0.34 \text{ A} = 2.82 \text{ A}$	N/A
(14)	$I_{Q1(RMS)} = \frac{1 \text{ A} \times 12 \text{ V}}{9 \text{ V} \times \sqrt{0.57}} = 1.77 \text{ A}$	$\frac{1.77 \text{ A}}{0.9} = 1.96 \text{ A}$	Fairchild FDC365P: -35-V, -4.3-A, 55-m $\Omega$ PFET
(13)	$P_{D-Q1} = (1.96 \text{ A})^2 \times 55 \text{ m}\Omega$ $+ (15 \text{ V} + 12 \text{ V}) \times 2.82 \text{ A} \times 2.2 \text{ nC} / 0.3 \text{ A} \times 460 \text{ kHz}$ $+ 8 \text{ V} \times 15 \text{ nC} \times 460 \text{ kHz} = 0.54 \text{ W}$	Included	
—	$P_{D-D1} = 1 \text{ A} \times 0.5 \text{ V} = 0.5 \text{ W}$	N/A	MBRS340: 40 V, 3 A, SMC

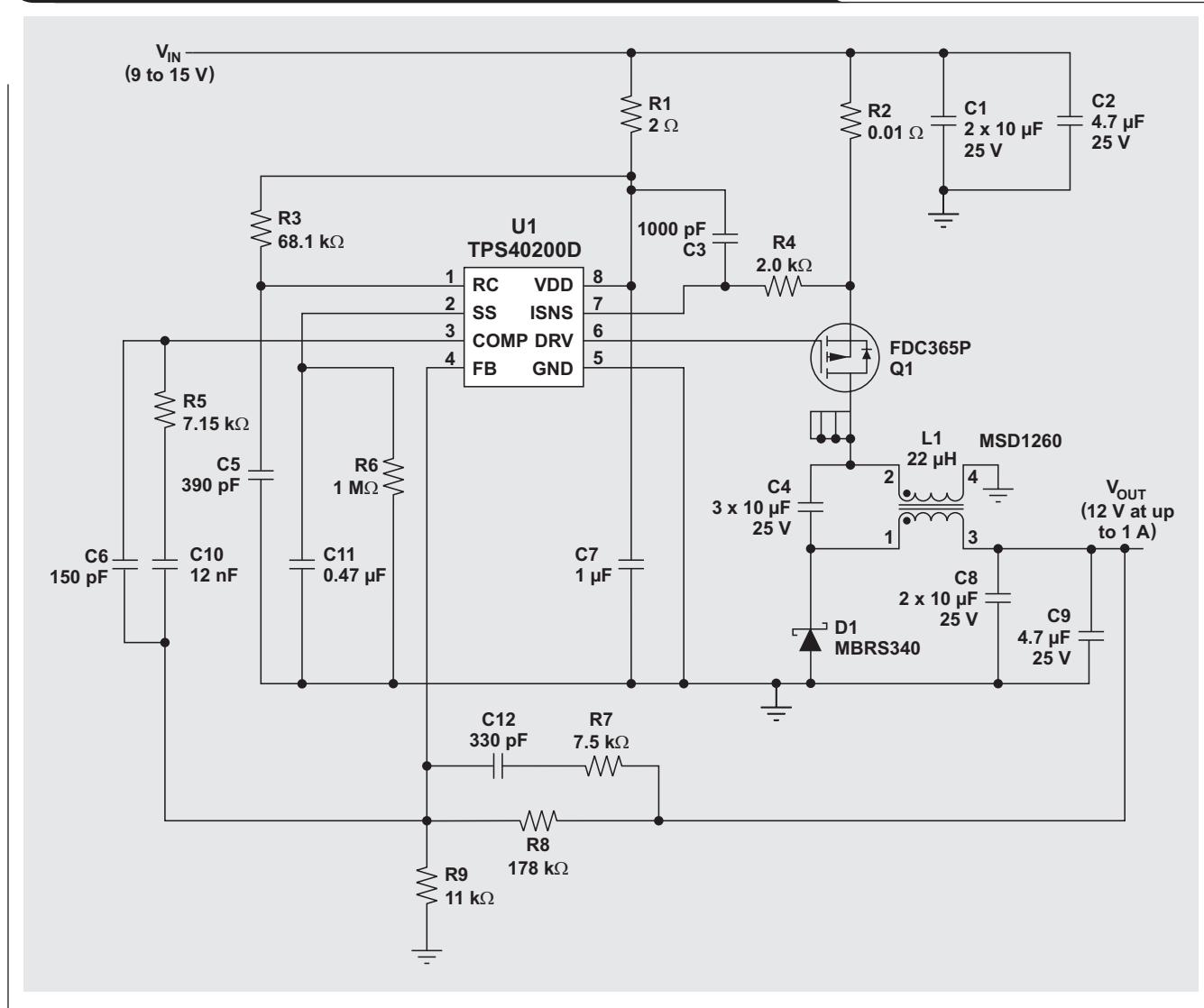
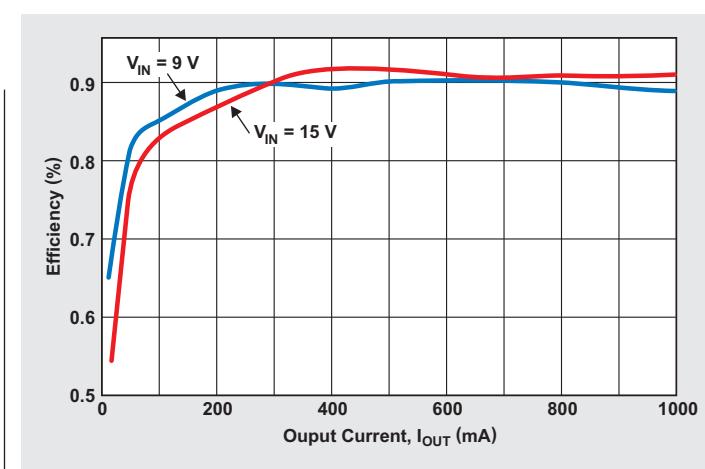
**Figure 4. ZETA-converter design with 9- to 15-V  $V_{IN}$  and 12-V  $V_{OUT}$  at 1 A**

Figure 4 shows the schematic and Figure 5 the efficiency of the ZETA converter. On the next page, Figure 6 shows the converter's operation in deep CCM, and Figure 7 shows the loop response.

### Conclusion

Like the SEPIC converter, the ZETA converter is another converter topology to provide a regulated output voltage from an input voltage that varies above and below the output voltage. The benefits of the ZETA converter over the SEPIC converter include lower output-voltage ripple and easier compensation. The drawbacks are the requirements for a higher input-voltage ripple, a much larger flying capacitor, and a buck controller (like the TPS40200) capable of driving a high-side PMOS.



**Figure 5. Efficiency of example ZETA-converter design**

**Reference**

- Eng Vuthchhay and Chanin Bunlaksananusorn, "Dynamic modeling of a zeta converter with state-space averaging technique," *Proc. 5th Int. Conf. Electrical Engineering/Electronics, Computer, Telecommunications and Information Technology (ECTI-CON) 2008*, Vol. 2, pp. 969–972.

**Related Web sites**

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/TPS40200](http://www.ti.com/sc/device/TPS40200)

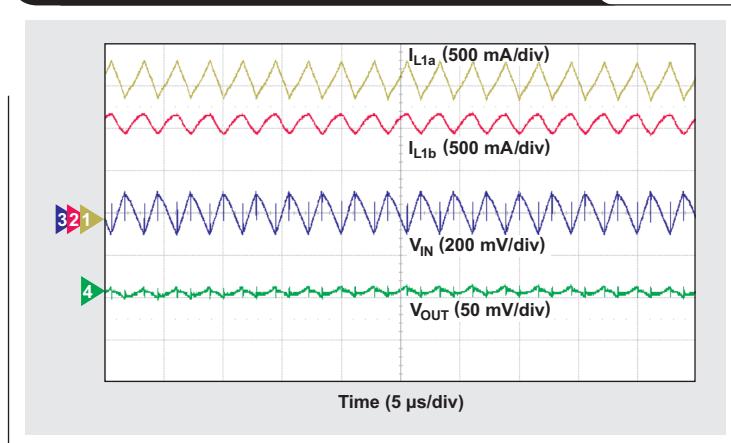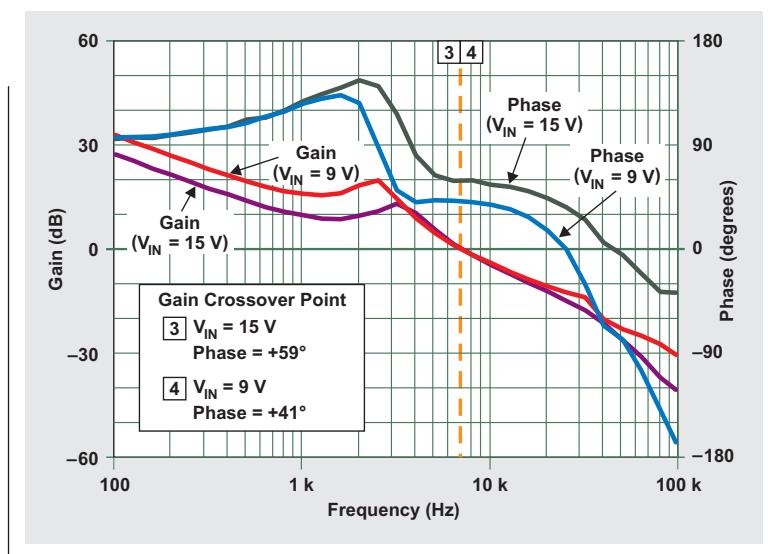**Figure 6. Operation at  $V_{IN} = 9\text{ V}$  and  $I_{OUT} = 1\text{ A}$** **Figure 7. Loop response at  $V_{IN} = 9\text{ V}$  and  $15\text{ V}$ , and  $I_{OUT} = 1\text{ A}$** 

# **TI Worldwide Technical Support**

---

## **Internet**

### **TI Semiconductor Product Information Center**

#### **Home Page**

[support.ti.com](http://support.ti.com)

### **TI E2E™ Community Home Page**

[e2e.ti.com](http://e2e.ti.com)

## **Product Information Centers**

**Americas** Phone +1(972) 644-5580

**Brazil** Phone 0800-891-2616

**Mexico** Phone 0800-670-7544

Fax +1(972) 927-6377

Internet/Email [support.ti.com/sc/pic/americas.htm](http://support.ti.com/sc/pic/americas.htm)

## **Europe, Middle East, and Africa**

### Phone

European Free Call 00800-ASK-TEXAS  
(00800 275 83927)

International +49 (0) 8161 80 2121

Russian Support +7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +49 (0) 8161 80 2045

Internet [support.ti.com/sc/pic/euro.htm](http://support.ti.com/sc/pic/euro.htm)

## **Japan**

Phone Domestic 0120-92-3326

Fax International +81-3-3344-5317

Domestic 0120-81-0036

Internet/Email International [support.ti.com/sc/pic/japan.htm](http://support.ti.com/sc/pic/japan.htm)

Domestic [www.tij.co.jp/pic](http://www.tij.co.jp/pic)

## **Asia**

### Phone

International +91-80-41381665

Domestic Toll-Free Number

Australia 1-800-999-084

China 800-820-8682

Hong Kong 800-96-5941

India 1-800-425-7888

Indonesia 001-803-8861-1006

Korea 080-551-2804

Malaysia 1-800-80-3973

New Zealand 0800-446-934

Philippines 1-800-765-7404

Singapore 800-886-1028

Taiwan 0800-006800

Thailand 001-800-886-0010

Fax +86-2-2378-6808

Email [tiasia@ti.com](mailto:tiasia@ti.com) or [ti-china@ti.com](mailto:ti-china@ti.com)

Internet [support.ti.com/sc/pic/asia.htm](http://support.ti.com/sc/pic/asia.htm)

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A042210**

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>	Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>	Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Energy	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Space, Avionics & Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>	Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>