

# Coupled inductors broaden DC/DC converter usage

By Jeff Falin

Senior Applications Engineer

## Introduction

Recently, inductor manufacturers have begun to release off-the-shelf coupled inductors. Consisting of two separate inductors wound on the same core, coupled inductors typically come in a package with the same length and width as that of a single inductor of the same inductance value, only slightly taller. The price of a coupled inductor is also typically much less than the price of two single inductors. The windings of the coupled inductor can be connected in series, in parallel, or as a transformer. This article highlights four DC/DC converter topologies that meet common application needs with coupled inductors.


Clearly understanding the specifications of coupled inductors is essential to using them to their full advantage. Most of these coupled inductors have the same number of turns—i.e., a 1:1 turns ratio—but some newer ones have a higher turns ratio. The coupling coefficient,  $K$ , of coupled inductors is typically around 0.95, much lower than a custom transformer's coefficient of greater than 0.99. The mutual inductance of coupled inductors makes them perform somewhat inefficiently in flyback applications and can cause non-ideal (e.g., rounded instead of triangular) inductor waveforms. Also, the current specifications for a coupled inductor are different depending on whether its windings are physically connected in series or in parallel. For example, when the windings are connected in series,

the equivalent inductance is more than twice the rated inductance due to the mutual inductance. The saturation and RMS current ratings must be applied to the current flowing simultaneously through both windings, unless otherwise stated in the data sheet. With this understanding of the specifications, some examples of coupled inductors in real applications can now be examined.

## More efficient SEPIC with smaller footprint

While not new, the DC/DC single-ended primary inductance converter (SEPIC) topology was not popular until recently, despite the ever-present need for a converter capable of regulating an output voltage that is in-between a higher and lower input voltage (for example, an unregulated wall wart providing 12 V). Any boost converter/controller can be configured as a SEPIC, but this was rarely used until recently. Two factors have contributed to the SEPIC's newfound popularity: (1) IC manufacturers have begun making more boost controllers with current-mode control to simplify compensation, and (2) inductor manufacturers have begun making single-packaged coupled inductors that minimize the converter's overall PCB footprint. Specifically, the power-supply footprint of many applications with two separate inductors can be reduced by a third when a coupled inductor is used instead. Figure 1 shows a SEPIC using the Texas Instruments (TI) TPS61170 and the Wuerth 744877220.

Figure 1. SEPIC using the TI TPS61170 and Wuerth 744877220

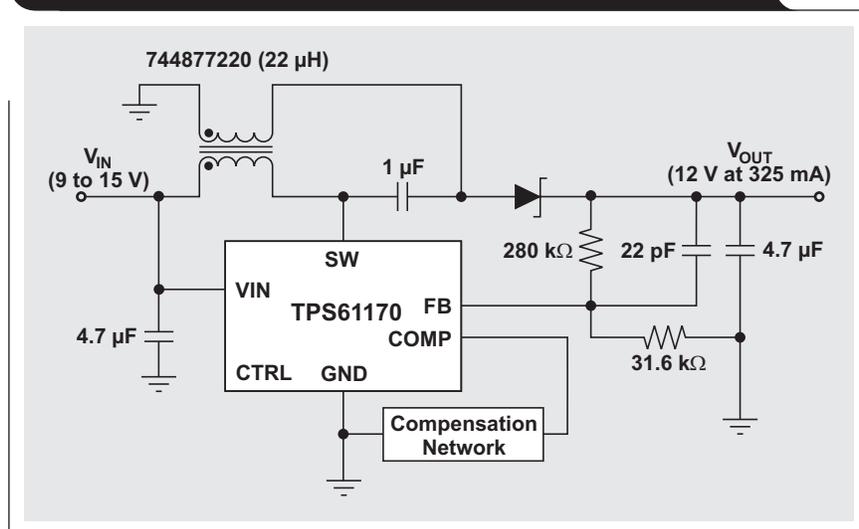

Even more appealing, using a SEPIC with a 1:1 coupled inductor forces the inductor ripple current to split between the two windings, allowing the use of half the inductance that two single inductors would require for the same ripple current. Compared to two single inductors at twice the inductance value in a package of the same size, the coupled inductor has lower DC resistance, which helps increase overall converter efficiency. Specifically, with a 15-V input and a 12-V, 325-mA output, the SEPIC in Figure 1 exceeds 91% efficiency. See Reference 1 for more information.

### ZETA converter with smaller footprint


A ZETA converter provides the same buck and boost functionality as a SEPIC by using two inductors and a coupling capacitor, but with a buck controller instead of a boost controller. Figure 2 shows the TI TPS40200 and the Coiltronics DRQ74 in a ZETA configuration. Benefiting

from the split-inductor ripple current like the SEPIC, this ZETA converter requires half the inductance for the same ripple current. Also like the SEPIC, its overall power-supply footprint is a third smaller than with two separate inductors. Since the output inductor current flows continuously to the output in a ZETA converter, the ZETA converter's output voltage has lower ripple than that of a SEPIC with the same inductance. Therefore, the ZETA may be a better fit for low-noise applications than a SEPIC. See Reference 2 for more information.

### Split-rail supply

Matching positive and negative power rails are common requirements in industrial applications, especially for amplifiers. A wide-input-range buck converter can be configured to provide a negative output voltage. Replacing the inductor of this inverting buck converter with a coupled inductor and adding a diode and capacitor turns this

Figure 2. ZETA converter with TI TPS40200 and Coiltronics DRQ74

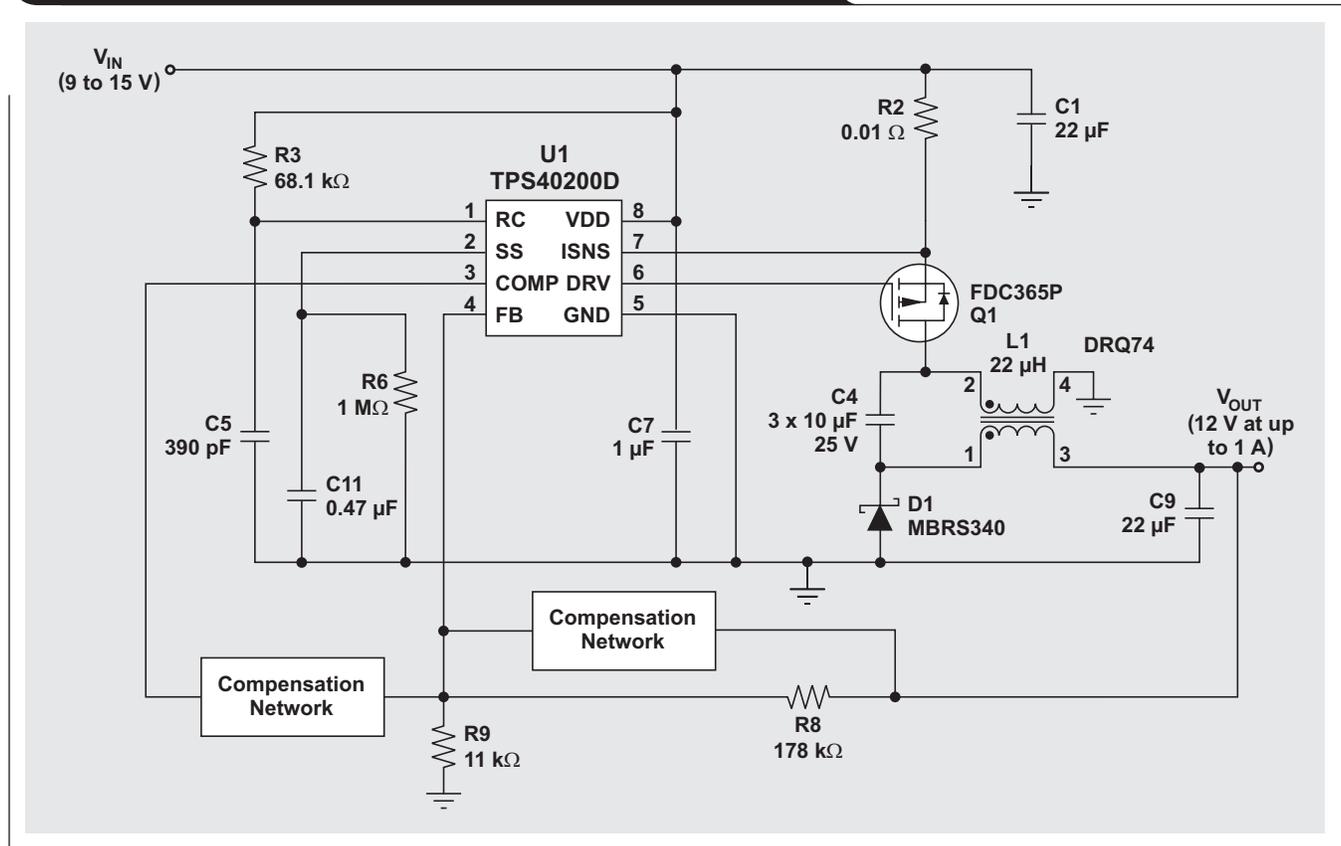

inverting buck converter into one with a dual output. Figure 3 shows the TI TPS54160 and the Coilcraft 150- $\mu$ H MSD1260 used in this fashion. Even though the difference between each rail is regulated instead of each rail being individually regulated, as long as the loads on each rail are somewhat close together, the coupled inductor assists in providing excellent regulation of each rail. See Reference 3 for more information.

**Higher output voltage**

The output voltage of a DC/DC converter with integrated FETs is limited by the converter's switch current rating. Tying a coupled inductor with a turns ratio greater than 1:1 to the converter's switch (SW) pin can extend the effective output-voltage range of any boost converter. For example, Figure 4 shows the TI TPS61040 boost converter with a 30-V absolute maximum current rating configured to provide 35 V or more, and the Coilcraft LPR4012-103B, which is a 1:2 coupled inductor. When the coupled inductor is configured with the multiple-winding side in series with the diode, the single wound inductor—and therefore the converter's switch FET—has only a third of the output voltage, minus the input voltage, across it.

**Conclusion**

Most inductor manufacturers have a family of coupled inductors with a turns ratio of 1:1 or higher. So, think out of the box! Coupled inductors may expand the application space for a favorite DC/DC converter IC.

**References**


For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

**Document Title**


**TI Lit. #**

1. Jeff Falin, "Designing DC/DC converters based on SEPIC topology," *Analog Applications Journal* (4Q 2008) . . . . . slyt309
2. Jeff Falin, "Designing DC/DC converters based on ZETA topology," *Analog Applications Journal* (2Q 2010) . . . . . slyt372
3. David G. Daniels, "Creating a split-rail power supply with a wide input voltage buck regulator," Application Report . . . . . slva369

**Figure 3. Split-rail buck converter using the TI TPS54160 and Coilcraft MSD1260**

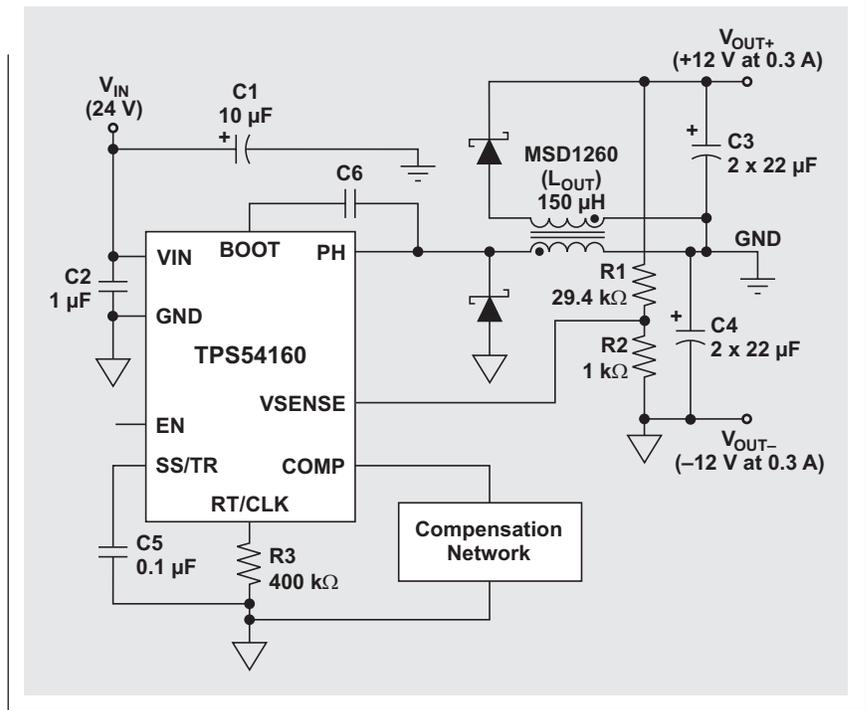

**Figure 4. TI TPS61040 and Coilcraft LPR4012-103B providing extended output voltage**

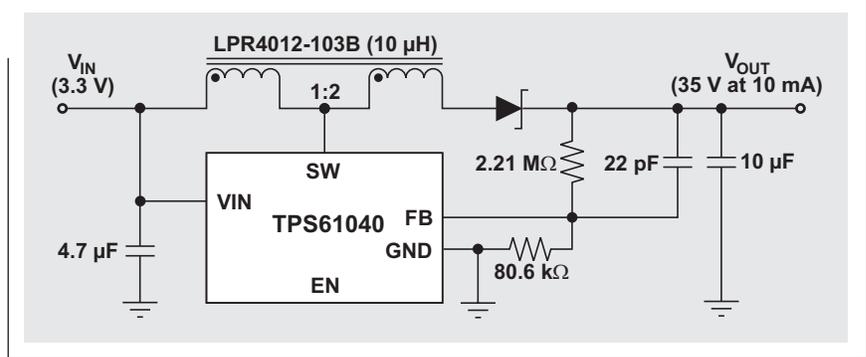

**Related Web sites**

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with TPS40200, TPS54160, TPS61040, or TPS61170

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A042210**

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>	Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>	Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Energy	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Space, Avionics & Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>	Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2010, Texas Instruments Incorporated