

# Designing an isolated I<sup>2</sup>C Bus<sup>®</sup> interface by using digital isolators

By Thomas Kugelstadt  
Senior Applications Engineer

The continuing changes in legislation concerning both the design and use of machinery and equipment require the isolation of almost any type of industrial system or interface. The inter-integrated circuit bus (I<sup>2</sup>C Bus<sup>®</sup>) is a single-ended, multi-master, two-wire bus; and, while designed only for short-distance I<sup>2</sup>C communication, it is no exception to isolation requirements.

The particular challenge in designing an isolated I<sup>2</sup>C interface by using standard digital isolators lies in the different operation modes between the two. The I<sup>2</sup>C Bus operates in bidirectional, half-duplex mode, while standard digital isolators are unidirectional devices. To make efficient use of one technology supporting the other, external circuitry is required that separates the bidirectional bus into two unidirectional signal paths without introducing significant propagation delay.


This article provides a short introduction to I<sup>2</sup>C Bus operation and then describes how to design an isolated I<sup>2</sup>C interface by adding only a few external components to a digital capacitive isolator.

## I<sup>2</sup>C Bus operation


The I<sup>2</sup>C uses open-drain technology, thus requiring the serial data line (SDA) and serial clock line (SCL) to be connected to V<sub>DD</sub> by resistors (see Figure 1). Pulling the line to ground is considered a logic “0,” and letting the line float is a logic “1.” This logic configuration is used as a channel-access method. Transitions of logic states must occur while SCL is low, because transitions while SCL is high indicate START and STOP conditions. Typical supply voltages are 3.3 V and 5 V, although systems with higher or lower voltages are permitted.

I<sup>2</sup>C communication uses a 7-bit address space with 16 reserved addresses, so a theoretical maximum of 112 nodes can communicate on the same bus. In praxis, however, the number of nodes is limited by the specified total bus capacitance of 400 pF, which restricts communication distances to a few meters. The specified signaling rates are 100 kbps (standard mode), 400 kbps (fast mode), 1 Mbps (fast mode plus), and 3.4 Mbps (high-speed mode).

Figure 1. The I<sup>2</sup>C Bus<sup>®</sup>

 

**Figure 2. Timing diagram of a complete data transfer**

 

The bus has two roles for nodes: master and slave. A master issues the clock and slave addresses and also initiates and ends data transactions. A slave receives the clock and addresses and responds to requests from the master. Figure 2 shows a typical data transfer between master and slave.

The master initiates a transaction by creating a START condition, then transmits the 7-bit address of the slave it wishes to communicate with. This is followed by a single READ/WRITE (R/W) bit, representing whether the master wishes to write to “0” or to read from “1,” the slave. The master then releases the SDA line to allow the slave to acknowledge the receipt of data.

The slave responds with an acknowledge (ACK) bit by pulling SDA low during the entire high time of the ninth clock pulse on SCL. Then the master continues in either transmit or receive mode (according to the R/W bit sent), while the slave continues in the complementary mode (receive or transmit, respectively).

The address and 8-bit data bytes are sent with the most significant bit (MSB) first. The START bit is indicated by a high-to-low transition of SDA while SCL is high. The STOP condition is created by a low-to-high transition of SDA while SCL is high.

If the master writes to a slave, it repeatedly sends a byte to the slave, which sends an ACK bit for each byte received. In this case, the master is in master-transmit mode and the slave is in slave-receive mode.

If the master reads from a slave, it repeatedly receives a byte from the slave while sending an ACK bit to acknowledge the receipt of every byte but the last one (see Figure 3). In this situation the master is in master-receive mode and the slave is in slave-transmit mode.

The master ends the transmission with a STOP bit or may send another START bit to maintain bus control for further transfers.

When writing to a slave, a master mainly operates in transmit mode and changes to receive mode only when receiving acknowledgment from the slave.

When reading from a slave, the master starts in transmit mode and then changes to receive mode after sending a READ request (R/W bit = 1) to the slave. The slave continues in the complementary mode until the end of a transaction.

Note that the master ends a reading sequence by not acknowledging the last byte received—i.e., by sending a NACK. This procedure resets the slave state machine and allows the master to send the STOP command.

**Figure 3. Changes in transmit/receive modes during a data transfer**

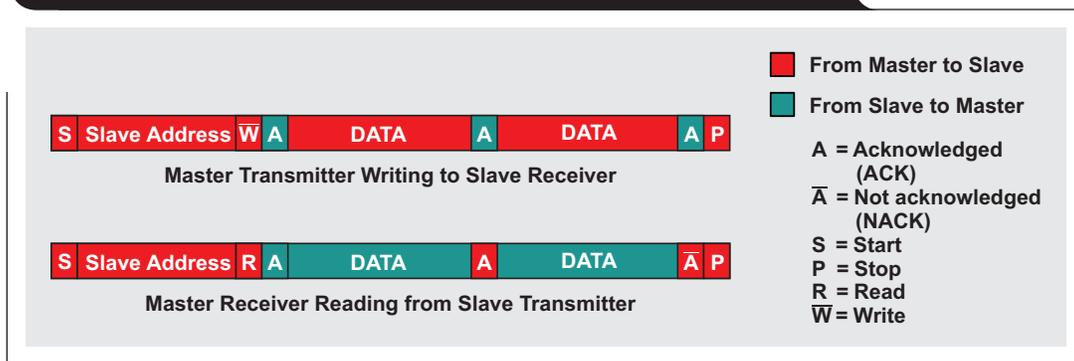
 


Figure 4. Isolating an I<sup>2</sup>C line by using a digital isolator

### Isolator design

Isolating an I<sup>2</sup>C signal path by using standard digital isolators requires splitting the half-duplex line into separate transmit and receive paths and converting the isolator's push-pull outputs into open-collector outputs via Schottky diodes (Figure 4). To prevent a transmitted signal from feeding back to its source, a comparator function is implemented that detects the direction of the signal flow and switches the signal paths accordingly.

Transistor Q1 and its surrounding resistor network provide the comparator function. Since the dominant switching level in I<sup>2</sup>C is logic low, the base of Q1 is so biased that a low level applied to SDA1 turns the transistor on, and a low level sent from SDA2 keeps Q1 at high impedance. While the R3/R2 voltage divider primarily determines the biasing, diode D3 provides temperature compensation. To prevent SDA2 from turning Q1 on, the low-level output at D1 is raised by a voltage drop across R1, which raises Q1's emitter potential,  $V_E$ , and decreases the base-emitter voltage below the minimum turn-on level. However, care must be taken to maintain  $V_E$  below the minimum input high-level threshold of SDA1, which the I<sup>2</sup>C specification lists as  $V_{IHmin} = 0.3 \times V_{CC}$ .

So, when the I<sup>2</sup>C Bus at SDA2 is pulled low, the low state passing in receive direction causes a voltage increase at

SDA1 that is just enough to block Q1 but well below  $V_{IHmin}$ , thus presenting a valid low for an I<sup>2</sup>C input. At the same time, R4 provides a logic high to the isolator input in transmit direction, preventing diode D2 from conducting. Once SDA2 is released and returns to the level of  $V_{CC2}$ , SDA1 follows after one propagation delay through the isolator. When the isolator is driven from the bus side (SDA2), the added signal delays for both the falling and the rising edges mainly consist of only one propagation delay through the isolator.

In the opposite direction, when SDA1 is pulled low, its maximum low-level output,  $V_{OLmax}$ , is significantly lower than  $V_E$  and causes Q1 to conduct. The low-state signal passing through the isolator in transmit direction forward biases D2, and SDA2 goes low. However, when SDA1 is released, its voltage cannot return to the level of  $V_{CC1}$  immediately due to the remaining low-level signal at SDA2. Instead, SDA1 rises to the necessary  $V_E$  potential that blocks Q1, and it will stay at this level until a high-impedance Q1 allows R4 to provide a logic high to the isolator input, thus releasing SDA2 and D1. Only then will SDA1 be able to return to the level of  $V_{CC1}$ .

When the isolator is driven from the device side (SDA1), the added signal delays for both edges increase due to the involvement of the comparator function.

Figure 5. Final isolator circuit

 


Figure 5 shows the final isolator circuit for the majority of I<sup>2</sup>C applications where the master is isolated from a slave bus. In this case, only the SDA line is bidirectional, while the SCL is unidirectional. For a multi-master system in which both lines must be bidirectional, the SDA circuit design can also be applied to the SCL when an ISO7242M isolator is used.

The typical propagation delays listed in Table 1 were measured under light capacitive loading at SDA1 and SDA2. Note that at low supply voltages, switching transients at Q1's collector might require a 10-pF filter capacitor to avoid false triggering of the internal isolator logic. Also, propagation delays can be reduced by switching a capacitor parallel to the upper base resistor to increase the charge injection into Q1's base.

**Related Web sites**

- [interface.ti.com](http://interface.ti.com)
- [www.ti.com/sc/device/ISO7231M](http://www.ti.com/sc/device/ISO7231M)
- [www.ti.com/sc/device/ISO7242M](http://www.ti.com/sc/device/ISO7242M)

Table 1. Propagation delays

SDA1 TO SDA2		SDA2 TO SDA1		CONDITION
RISING EDGE (ns)	FALLING EDGE (ns)	RISING EDGE (ns)	FALLING EDGE (ns)	
121	124	113	82	No caps
136	140	113	82	10 pF
103	136	113	82	10 pF + 1 nF
86	140	113	82	1 nF

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

support.ti.com

### TI E2E™ Community Home Page

e2e.ti.com

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

## Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

## Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

## Asia

Phone	
International	+91-80-41381665
Domestic	Toll-Free Number
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A122010**

E2E is a trademark of Texas Instruments. I<sup>2</sup>C Bus is a registered trademark of NXP B.V. Corporation. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated