

Measuring op amp settling time by using sample-and-hold technique

By Roger Liang, *Systems Engineer,*
and Xavier Ramus, *System Engineer, High-Speed Amplifiers*

Introduction

Modern high-speed operational amplifiers (op amps) are designed with settling time in the range of nanoseconds. This time is so brief that measuring it within a reasonable error band presents a challenging task not only on automatic test equipment (ATE) but also on the bench. In today's op amp datasheets, settling time is usually given as a simulated value due to the cost and challenges associated with implementing additional hardware to test it on the bench. Traditional high-speed oscilloscopes have only a 10-bit analog-to-digital converter, which limits any measurement resolution to a maximum of 0.1%.

This article describes a new methodology that has proven to be effective in making these measurements. Detailed is a relatively inexpensive and simple way to measure settling time that bases accuracy and precision on the relative speed of the waveform generator and the sample-and-hold circuit.

Step input for the device under test


In this article, settling time refers to the time that elapses from the application of an ideal step input to the time at which the device under test (DUT) enters and remains within a specified error band that is symmetrical about the final value. An ideal step input is easily generated in simulation, but there are no instruments that can produce an ideal step waveform in any lab setting. Even under ideal conditions, the output of overdamped and critically damped instruments would take a few RC time constants to monotonically settle to within tenths of a percent of the final value.

For underdamped systems, a step waveform can overshoot the final value, and ringing may occur. In practice, even critically damped systems have underdamped behaviors. Generally, the faster the fall time of the step waveform, the more overshoot and ringing one observes. This non-ideality is then propagated into the measured output waveform of the DUT. Fortunately, with the aid of computer-logged records of input and output data, the output can be normalized by lining up the two and subtracting the input from the output (with the DUT in a non-inverting unity-gain configuration).

Flat-bottom pulse generator

When the falling edge of a waveform generator is used as the input to the DUT, a flat-bottom pulse generator (FBPG)

Figure 1. Flat-bottom pulse generator (FBPG)

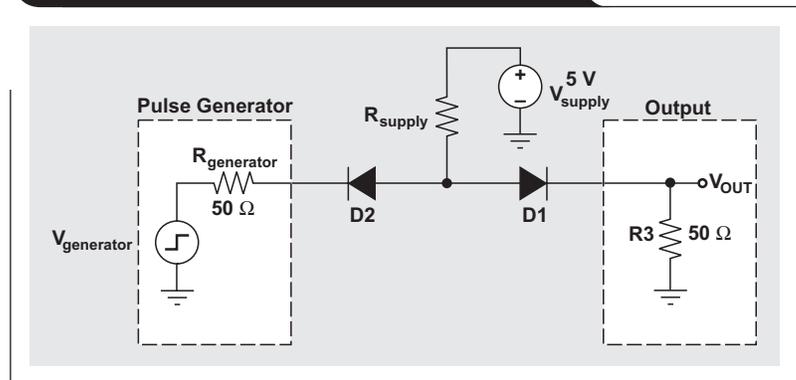

can be used to clean up the low-voltage level of the generated signal. The FBPG clamps the falling voltage to ground at the cost of a bigger overshoot. This gives test engineers some control over trade-offs in the test setup. Similarly, a flat-top pulse generator can be used to clean up the high-voltage level.

Figure 1 illustrates two back-to-back high-speed Zener diodes, each with a separate, adjustable power supply. As a rule of thumb, the setup should be started as follows: The R_{supply} should be adjusted to obtain 5 V at the D1/D2 connection, and the $V_{\text{generator}}$ output voltage should be adjusted to swing between a 2-V high and a -5-V low. This should bias the output at $2 V_{\text{PP}}$ and the low-voltage level at 0 V. When $V_{\text{generator}}$ is high, D2 is turned off and D1 is turned on. During this time, the output voltage becomes a function of D1's forward voltage (V_{supply}) and of the amount of current that flows through R_{supply} and D1. When the input is low, D1 is turned off and D2 is turned on. During this time, the output voltage swings to ground, and its slew rate is proportional to the amount of current that flows into the matching resistor, R3. The transient response is a function of the diode's capacitance, reverse recovery time, and forward recovery voltage.

Because of the diodes' nonlinearity, it does not make sense to derive rigorous equations to determine the DC levels and transient response of the FBPG. Instead, the equations can be simulated in software such as TINA-TI™ from Texas Instruments. Assuming that the pulse generator is very fast, the fall time and overshoot of the output waveform become functions of the diodes' speed and recovery time, as well as of the parasitic capacitance and inductance of the printed circuit board (PCB) on which the FBPG is built. In other words, the designer should pick the fastest, most robust diode and follow guidelines for


good PCB layout when using FBPG for generating high-speed waveforms.

Sample-and-hold methodology for measuring settling time

For the example presented here, the TI OPA615 (see Figure 2) was chosen to implement the sample-and-hold (S/H) functions of its wide-band operational transconductance amplifier (OTA), which is optimized for low input-bias current, and its fast and precise sampling OTA (SOTA), which also serves as a comparator and buffer. The analog input (V_{IN}) is sampled by the SOTA onto the capacitor (C_{HOLD}) when the Hold-Control pin is high. The voltage on C_{HOLD} is held and reflected at the output (V_{OUT}) when the Hold-Control pin swings low. During sampling, the voltage on C_{HOLD} is adjusted to the real-time voltage level on the input. If there is a large voltage difference between the input and C_{HOLD} and there are only a few nanoseconds of sampling time, then fast slewing is required. During holding, the voltage on C_{HOLD} invariably charges/discharges due to its leakage current and any biasing current needed for the OTA. The current-feedback loop ensures that the SOTA slews fast enough to capture the correct voltage level at V_{IN} .

Figure 3 shows an example of a S/H output of a 100-kHz sine-wave input. A waveform generator can be used to produce the input step function for the DUT and to synchronize a S/H signal to that step function. A S/H circuit can be used to capture points on the DUT's output waveform. Any

Figure 2. Sample-and-hold (S/H) circuit

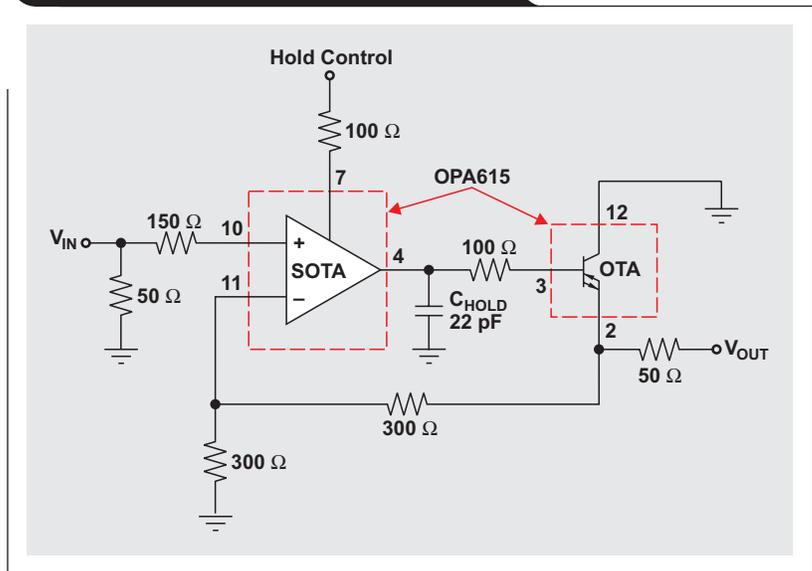

arbitrary waveform generator should work if it has a marker output that synchronizes with the output, thus creating a very convenient Hold-Control signal. The example test used a Tektronix AWG610, which has a sampling time of 2.6 Gbps and a minimum marker step of 100 ps, making it fast enough for most measurements of high-speed op amp settling time.

Figure 4 shows how to capture points on a curve by using a S/H circuit with the marker as the Hold-Control signal. The designer can capture sequential points on the curve by moving the marker position. After all the points

Figure 3. Example 1-MHz S/H output of a 100-kHz sine wave


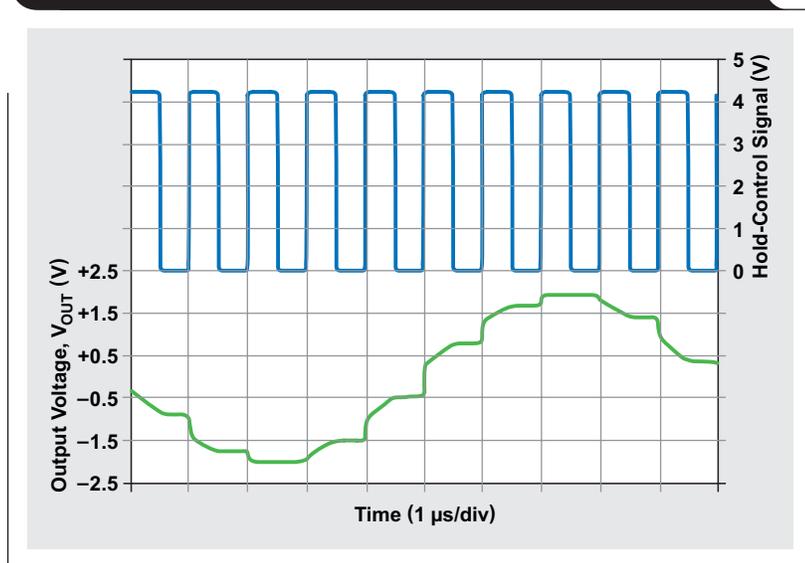


Figure 4. Example of AWG610 output and marker synchronization

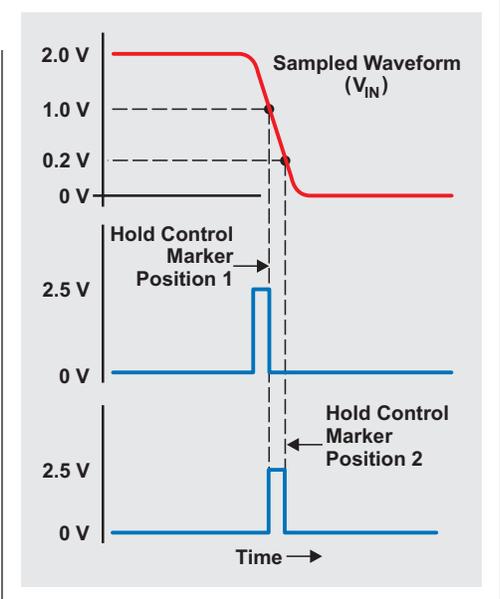

have been recorded, the S/H curve can be plotted and analyzed. Programming the waveform generator with software like MATLAB® or LabVIEW™ makes changing the marker and recording the results very simple. With the marker set in position 1, the S/H circuit tracks the V_{IN} voltage level when the marker is high and holds that value when the marker is low. At position 1, the output is held at 1 V. At position 2, the output is held at 0.2 V.

Figure 5 shows the test setup for measuring settling time where the AWG610 and OPA615 were used for the S/H functions. All signal lines were matched at 50 Ω . The output of the waveform generator was used as the test signal with two S/H circuits: One measured the input of the DUT (OPA656), and the other measured the DUT output. Digital multimeters (DMMs) were used to record the held values.

As an example of this method, take measuring a settling time of up to 100 ns. Assume that the waveform generator is programmed to continually output a square wave with a duty cycle of 50% and a period of 200 ns. The marker is initially set at the beginning of the falling edge of the waveform generator's output. The generator runs continually (executes many cycles of sampling and holding), and the S/H circuit integrates its output voltage to a steady DC value. This value is then recorded by the DMM, and the test engineer moves the marker to the next position, repeating this cycle until data for 100 ns has been recorded.

Figure 6 shows the plotted waveforms that resulted when the test setup in Figure 5 was used. To obtain a settling-time error waveform, the DC error was offset, and the output was normalized to the input. The result is shown in Figure 7.

Limitations and challenges

There are some limitations to the setup described here that should be kept in mind. When in doubt, the designer should always use the following equation:

$$I = C_{\text{HOLD}} \times dv/dt$$

For this equation, the size of the initial C_{HOLD} should be chosen based on three factors:

1. During the holding time, the OTA biasing current will flow in or out of the capacitor, thus affecting the accuracy of the voltage held.
2. Since a voltage droop will occur on the capacitor due to the biasing current, a delta voltage should be chosen based on the percentage of error within which the measurement should stay.
3. Delta time is the duration for which the sampled voltage is held and should be no longer than the planned settling time to be measured.

For example, C_{HOLD} should be no less than 50 pF under the following conditions: The biasing current of the OTA is 0.5 μA ; an error of less than 0.1% of a 1- V_{PP} signal is to be achieved; and the duration to be measured is 100 ns.

Figure 5. Test setup for measuring settling time

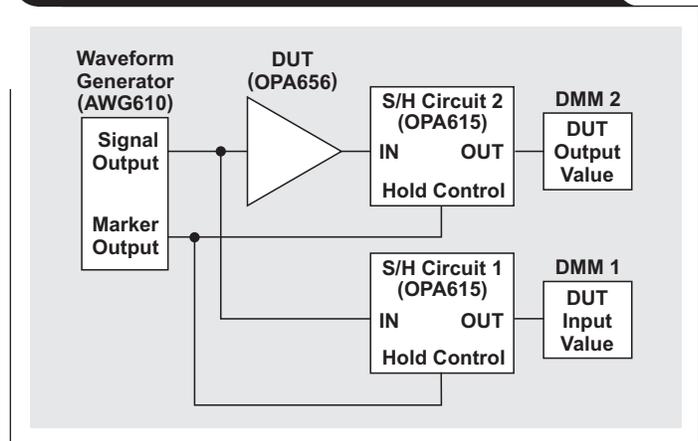


Figure 6. Step waveforms of op amp's input and output

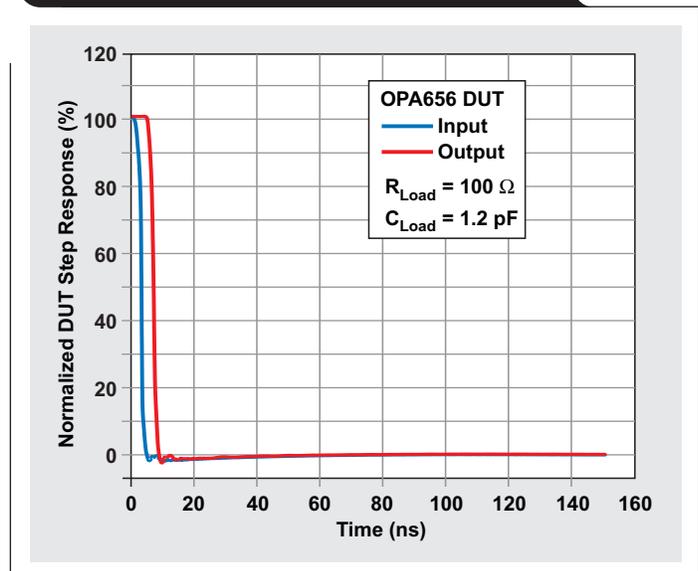


Figure 7. Op amp's normalized settling error


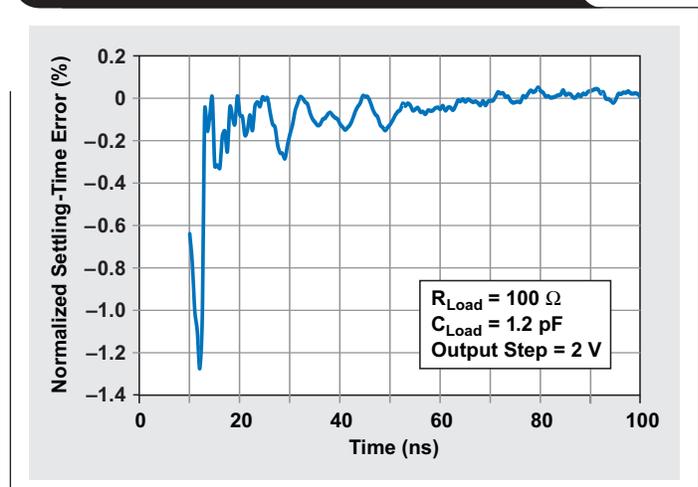


Figure 8. Charge leakage on sampling capacitor

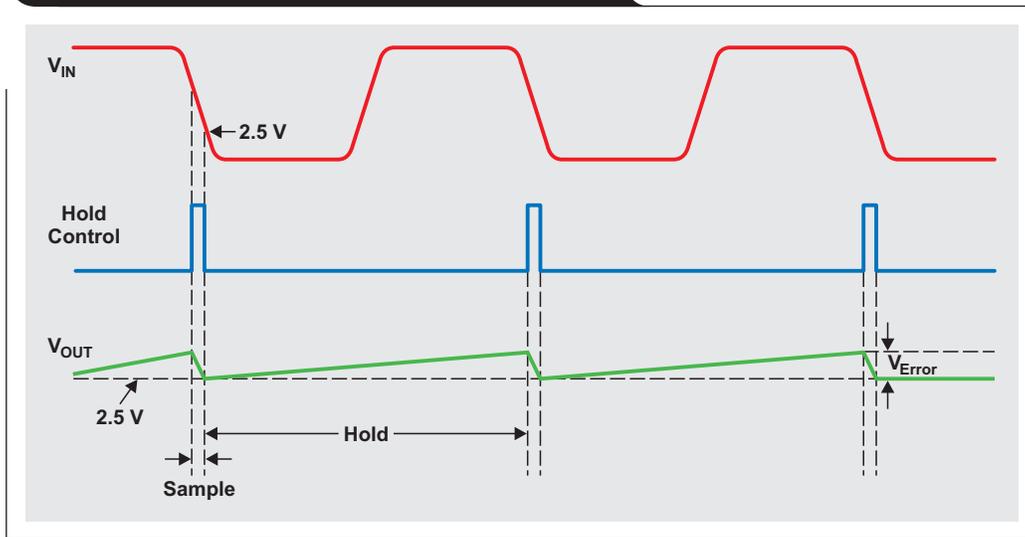

Other considerations

The duration of the sampling time could greatly affect the result of the measurement. During holding, the voltage on the sampling capacitor invariably strays from the supposed DC value because the OTA demands a biasing current. This voltage is then readjusted back to the expected DC value during sampling. The DMM that is reading the output of the S/H circuit is thus essentially taking an average value of this triangle waveform. This phenomenon is shown in Figure 8. To reduce this error, the holding time should be minimized and the capacitor size maximized. It should be kept in mind that the bigger the sampling capacitor is, the more S/H cycles (integration time) will be needed for the charges to integrate to a steady DC value.

Of course, increasing the sampling time does not mitigate the leakage problem. A minimum sampling time should be used that still guarantees the SOTA's holding-time delay and ensures enough time for the sampling capacitor's charge/discharge while it is tracking the S/H circuit's input. Figure 9 shows the recorded values of the op amp's settling time when different sampling times were used with the same holding and integration times. The results were measured against the same waveform taken from a 6-GHz, 10-bit oscilloscope, which showed a maximum overshoot of -60 mV. The measurement using a 20-ns sampling time matched that from the oscilloscope, but at the cost of applying a significant filter over the result. Conversely, the measurement using 6 ns applied a smaller filter but produced a bigger overshoot, which is an artifact of the measurement.


Conclusion

Numerous techniques exist for measuring settling time. This article has introduced a simple yet accurate technique that uses a relatively fast waveform generator and a S/H circuit. Knowing the limitations of this method, the user should be able to adjust any measurement parameters necessary to obtain the best results for a given settling-time range and expected accuracy.

Related Web sites

- amplifier.ti.com
- www.ti.com/product/OPA615
- www.ti.com/product/OPA656
- www.ti.com/tinati-ca

Figure 9. Settling time measured with different sampling times

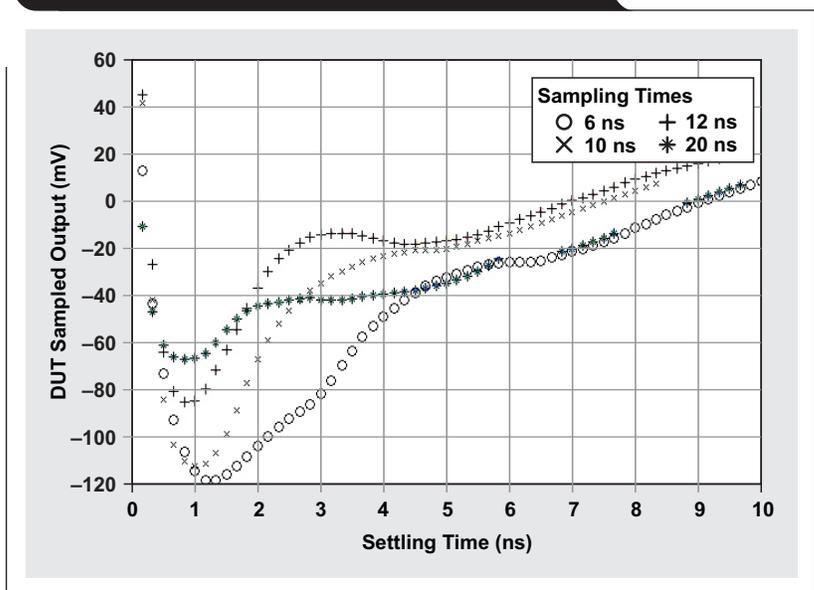

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E and TINA-TI are trademarks of Texas Instruments. LabVIEW is a trademark of National Instruments. MATLAB is a registered trademark of The MathWorks, Inc. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated