

Controlling switch-node ringing in synchronous buck converters

By Robert Taylor, *Applications Engineer*,
and Ryan Manack, *Field Applications Engineer*

Introduction

As power-supply efficiency becomes more important, faster switching speeds are necessary to reduce the losses. However, as switching speeds are increased, there are negative trade-offs that must be taken into account, such as a consequential increase in electromagnetic interference (EMI).

In a synchronous buck converter, fast-switching field-effect transistors (FETs) can experience significant voltage overshoots and ringing on the switch node. The magnitude of the ringing is a function of the high-side MOSFET's switching speed and the stray inductances in the layout and FET package. Proper techniques for circuit and layout design must be observed to keep the ringing below the absolute maximum rating of the synchronous FET.

This article focuses on three circuit designs that control switch-node ringing with either a boot resistor, a high-side gate resistor, or a snubber. Data is presented for each


approach, and the benefits of each are also discussed. These techniques can be nullified by poor power-supply layout, so it is important to take this into consideration as well. Please see Reference 1 for more information about layout.

Ringing caused by synchronous buck converter's parasitics

The circuit in Figure 1 shows the power-stage components for a synchronous buck converter. Included in this model are the parasitic inductances and capacitances responsible for switch-node ringing.

Assume that the converter is in steady state. During the portion of the switching cycle when the low-side FET is on, the power to the load is being provided only from the output inductance and capacitance. At this point, energy is being stored in the parasitic inductances of the low-side FET relative to $E = \frac{1}{2}L \times I^2$. At the end of the switching

Figure 1. Schematic showing parasitics of a buck converter

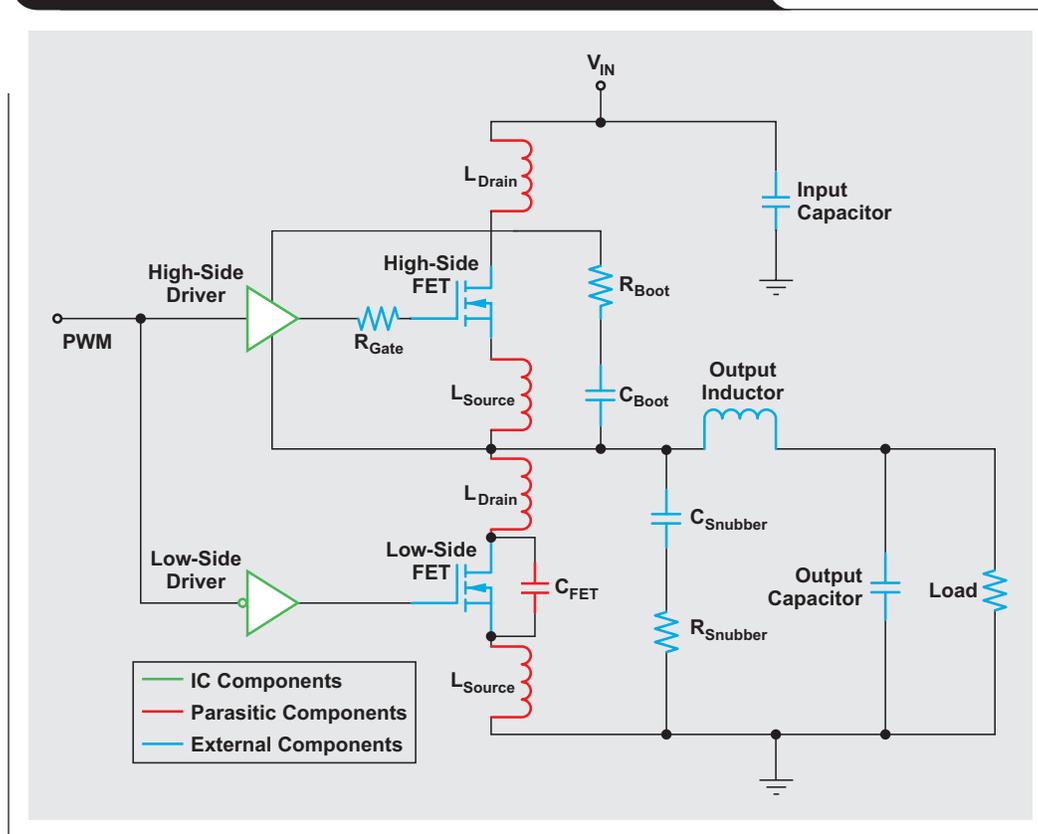

cycle, the converter prepares to switch the low-side FET off and the high-side FET back on to replenish power to the output L.

Strong gate drivers and a fast-switching FET allow the low-side FET to be turned off quickly. Assuming load conditions are sufficient to keep the inductor current flowing to the output, current is bypassed to the body diode of the low-side FET, and energy remains in the parasitic drain and source inductances of the low-side FET. After a fixed dead time, the high-side FET turns on, and the energy from the low-side and high-side FETs' parasitic inductances appears as an LC ringing waveform on the switch node.


The voltage magnitude of this ringing can exceed the absolute maximum drain-to-source voltage of the low-side MOSFET. Fast-switching MOSFETs such as the Texas Instruments (TI) CSD87350Q5D incorporate a stacked MOSFET pair that limits the parasitic inductances through innovative packaging techniques.

Reducing ringing

A test circuit with a 1.1-V/20-A buck converter was used to show the effects of switch-node ringing. This circuit used the TI TPS40304 600-kHz buck controller and the CSD87350Q5D fast-switching NexFET™ power block. The input-voltage range was 8 to 16 V. As a baseline reference, a switch-node waveform (Figure 2) and an efficiency plot (Figure 3) were generated without a boot resistor, high-side gate resistor, or snubber connected. The peak ringing with a 12-V input was 23.4 V. The efficiency at maximum load was 87.2%.

The boot resistor, high-side gate resistor, and snubber were optimized to reduce the overshoot to less than 20 V. This overshoot limit provided some margin to protect the FET, which had a 30-V maximum voltage rating. Figure 2 shows the overshoot for the baseline circuit and the reduced-ringing overshoot for the boot resistor, gate resistor, and snubber. The waveform for the gate resistor is very similar to that of the boot resistor. It is important to notice that only the magnitude of the ringing was affected by the boot-resistor and gate-resistor methods. The snubber method also changed the ringing frequency and damped out the ringing waveform. Figure 3 shows the measured efficiency for each of these conditions.

Figure 2. Waveforms of switch-node ringing with 12-V input

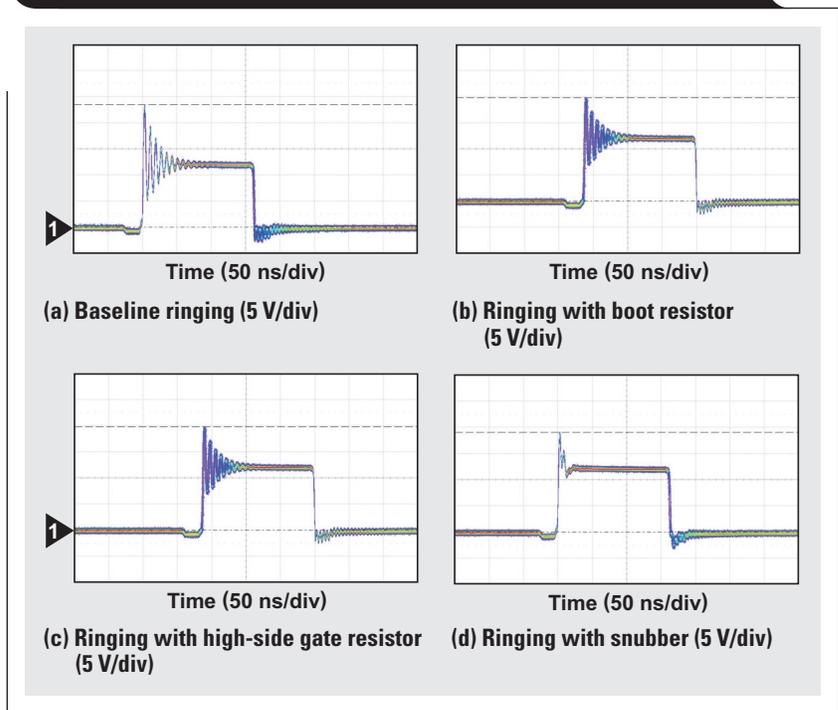

Using a boot resistor

The charge-pump circuit in Figure 1 uses C_{Boot} to boost the high-side gate supply above the supply voltage of the power stage. One way to reduce ringing is to include a boot resistor in series with the boot capacitor, which slows down the turn-on of the high-side FET. This allows more time for the parasitic network to discharge, ultimately limiting the ringing. The value of the boot resistor is determined by starting at 0 Ω and increasing the resistance until the desired ringing is achieved. To reduce the ringing for this design to below 20 V, a 6.8- Ω boot resistor was

Figure 3. Efficiency versus load current

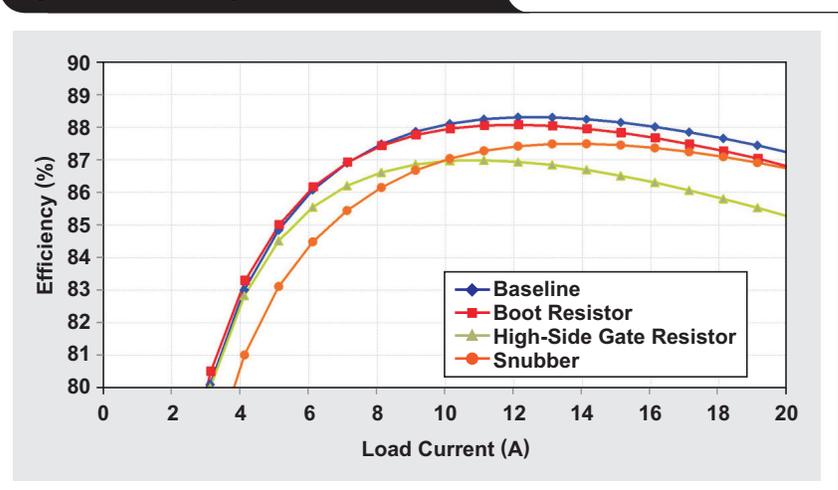


Table 1. Test data for three methods of reducing ringing

METHOD	RINGING (V)			FULL-LOAD EFFICIENCY (%)		
	V _{IN} = 8 V	V _{IN} = 12 V	V _{IN} = 16 V	V _{IN} = 8 V	V _{IN} = 12 V	V _{IN} = 16 V
Baseline	18.0	23.4	28.3	88.3	87.2	85.4
Boot Resistor	15.9	19.8	22.6	88.1	86.8	85.1
Gate Resistor	15.4	19.8	23.2	87.1	85.2	83.1
Snubber	14.2	19.1	23.7	88.1	86.7	84.7

required. It is interesting to note that the boot resistor affects only the turn-on of the high-side FET, making this method an efficient way to reduce ringing. However, if the boot resistor is made too large, the boot capacitor may not get fully charged in each cycle. In this case, the gate driver would not have sufficient voltage to keep the high-side FET on and could turn off in the middle of the cycle. This limits the amount of ringing that can be reduced with the boot-resistor method.

Using a high-side gate resistor

Using a resistor in series with the gate of the high-side FET is another effective way to reduce ringing. Similar to the boot-resistor method, this resistor slows down the turn-on of the high-side FET. However, because this resistor is in series with the gate, it is also in the discharge path, so it slows down the turn-off as well. To reduce the ringing for this design to below 20 V, a 6.8-Ω gate resistor was used. This method is the least efficient of the three choices.

Using a snubber

The third option to consider for reducing ringing is a snubber. The snubber circuit consists of a resistor and capacitor that are connected in series from the switch node to ground. The snubber circuit is used to damp the parasitic inductances and capacitances during the switching transitions. This circuit reduces the ringing voltage and frequency and also reduces the number of ringing cycles. This helps to reduce the EMI emitted by the system.

The procedure for choosing the capacitor and resistor components starts with measuring the ringing frequency of the original circuit. Once the frequency is determined, a capacitor is put in parallel with the low-side FET to change the ringing frequency to half the original value. When the frequency is half the original value, the parallel capacitor is equal to three times the parasitic capacitance of the original circuit. With the capacitance and frequency known, the parasitic inductance can be calculated by using the formula $f = \frac{1}{2\pi\sqrt{LC}}$, where f is the original ringing frequency and C is the parasitic capacitance. The resistor to critically damp the circuit is calculated from the equation $R = \sqrt{L/C}$. This resistor may or may not provide the necessary ringing reduction. Increasing the resistance results in an underdamped system, which allows more ringing but decreases power dissipation. Increasing the capacitance reduces the ringing but increases power dissipation. For the example, using a 2200-pF capacitor and a 1-Ω resistor reduced ringing to 19.1 V.

Conclusion

As MOSFET switching speeds continue to increase, controlling the switch-node ringing of a synchronous buck converter is critical. Doing so requires a good layout and proper analog-circuit design with a boot resistor, a high-side gate resistor, or a snubber. Table 1 shows the amount of ringing reduction achieved with the test circuit and the corresponding efficiency for each technique.

The boot resistor slows down the turn-on of the high-side FET without affecting the turn-off. In the design example, the boot resistor was the most efficient approach. However, if this method is used, proper care must be taken to prevent starving the gate. A resistor in series with the gate increases both the turn-on and turn-off times of the high-side MOSFET, which controls ringing on the rise and fall of the switch node. This approach burns the most power in the upper FET, reducing efficiency. An RC snubber reduces the frequency and overshoot of ringing, but it requires two extra components and has low efficiency at light loads.

Every power-supply design is unique, so each method should be inspected for its cost/benefit to the supply. Often, the best approach may even be a combination of all three circuits. The ultimate goal is to maintain a sufficient margin below the MOSFET's absolute maximum voltage rating while maintaining as much efficiency in the power stage as possible.

Reference

For more information related to this article, you can download an Acrobat® Reader® file at www.ti.com/lit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title

TI Lit. #

1. Robert Kollmann, "Constructing your power supply — layout considerations," 2004–05 TI Unitrode Design Seminar Series – SEM1600, Topic 4 SLUP230

Related Web sites

power.ti.com

www.ti.com/nexfet

www.ti.com/product/CSD87350Q5D

www.ti.com/product/TPS40304

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E and NexFET are trademarks of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated