

# Harnessing wasted energy in 4- to 20-mA current-loop systems

By Chris Glaser

Applications Engineer

A 4- to 20-mA current-loop signal is frequently used in industrial environments to transmit measurements across long distances, such as the temperature of a process or the pressure in a tank. This type of signaling is preferred because of its simplicity, noise immunity, safety, and ability to traverse great lengths without data corruption. These current loops are also low-power systems, since relatively low currents transmit the data. Previously, whatever power was not used or lost in the signal transmission was merely dissipated in the transmitter; but now, with modern integrated circuits, even this small amount of power can be harnessed to support necessary functions in these systems.

## The basics of 4- to 20-mA current-loop systems


Figure 1 shows a typical 4- to 20-mA current-loop system. A semiregulated 24-VDC source provides power to the current loop and to the transmitter element. The transmitter measures the signal of interest (such as temperature, pressure, and many others) and outputs a 4- to 20-mA current that is proportional to that signal. This current passes through the wiring to a receiver system. There, the current develops a voltage across a resistor that is read by an analog-to-digital converter (ADC) and then further processed. The loop is completed with a connection back to the voltage source that powers the loop.

These current loops provide several benefits in industrial applications:

- The current loops are simple circuits requiring only a crude power supply; a transmitter to make the measurement and source the current; a wire; and a receiver circuit. The power supply needs to provide only enough voltage to overcome the various voltage drops in the system; any excess loop voltage is just dropped across the transmitter. Due to the low current, this is only a small amount of power, which creates little heat.

- The current loop contains only one loop for current flow. Therefore, from Kirchhoff's current law, the current through all the elements in the loop is equal. This provides high noise immunity, which is critical in industrial environments.
- Safety is provided since the lowest signal level is 4 mA. If something in the loop is broken or becomes disconnected, the receiver reads no current, which demonstrates a fault instead of the lowest signal level.
- As long as the power-supply voltage is high enough to overcome system voltage drops, the desired current representing the measured signal is maintained by the transmitter. Thus, smaller wire gauges with their higher voltage drops and lower cost are used for the interconnections, requiring only an increase to the supply voltage. Most importantly, the relatively large voltage drops permitted across the wiring allow a large amount of wire to be used. This allows physical separation of the instrument being measured and the control room that processes the measurement, providing safety to those in the control room.

Figure 1. Basic 4- to 20-mA current-loop system

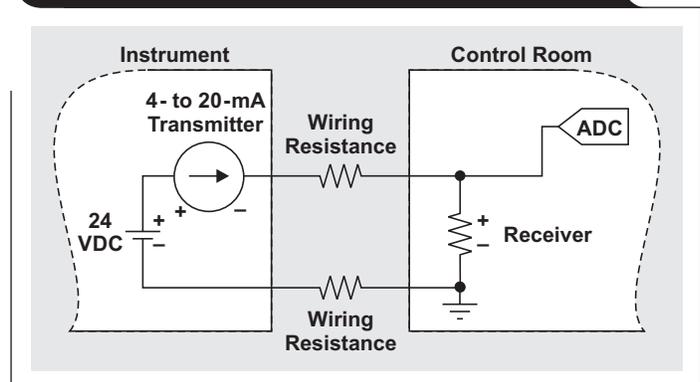

## Basic system improvement

The excess loop voltage that would otherwise be dropped across the transmitter can be harnessed and used to provide power to the receiver circuitry. Figure 2 shows a power supply inserted into the current loop. This power supply is located in the control room with the receiver circuitry it powers—efficiently converting the excess loop voltage to useful output power.

Since the receiver resistor is no longer ground-referenced, a level-shift circuit is likely necessary to interface with the data converter's input. This very simple circuit is provided by any high-side current-shunt monitor, such as the Texas Instruments (TI) INA138. These devices measure very small sense-resistor voltage drops at a common-mode voltage, thus lowering the necessary voltage drop across the receiver resistor. This allows more voltage for the power supply to harness, reducing the amount of wasted energy.

The power supply typically provides a regulated 3.3 V to power this level shifter, the data converter, and any other low-power devices in the control room. Examples of these devices are a microprocessor from TI's MSP430™ platform to review the incoming data and make decisions, and possibly a low-power RF device from TI's CC430 family to wirelessly transmit the data to other locations. A wireless transmitter is particularly useful if its cost is offset by savings from not having to buy and install the wire required for a particularly lengthy current loop. These devices must use very low power due to the limited amount of excess energy harnessed from the current loop.

Finally, the power supply must be able to operate with such a low-power source—4 mA being the minimum current, and 20 mA being the most it ever gets. Since the voltage generated by this current is the excess voltage in the loop, the power supply must accept a wide input-voltage range and still provide a regulated output. What is more difficult for the power supply is starting up the system from such a current-limited source. Typically, a higher output power is required during start-up to charge up the


output capacitors and provide the load with its start-up current. This can be much higher than what the system consumes in normal operation. If the power supply attempts to provide this higher power during start-up, its input power can exceed what the current loop provides. If this happens, the voltage into the power supply drops until the power supply turns off. Then, its input voltage rises again until it turns back on and repeats the process. Such start-up oscillations are a difficult challenge to be overcome when the power supply runs from such small amounts of input power.

## Energy-harnessing solution

As just described, the energy-harnessing power supply must have a wide input-voltage range, be able to operate on a very small amount of input power, and avoid start-up oscillations when powered from current-limited sources. TI's TPS62125 is such a power supply, because it operates from a 3- to 17-V input, requires only 11  $\mu$ A to operate, and has a programmable enable threshold voltage with adjustable hysteresis. The circuit recommended in the TPS62125 datasheet is used with three small modifications:

1. A 15-V Zener diode is added on the input to the device to protect it in cases where the excess loop voltage applied to it exceeds its 17-V rating. If a lower-voltage current-loop system is used, this diode may not be necessary. A Zener diode that clamps at a maximum of 15.6 V gives good results.
2. Bulk capacitance is added on the input to the device to store enough energy for start-up and load changes. Depending on the load's power demands during start-up, this capacitor may not be needed at all. A total of about 200  $\mu$ F provides a smooth start-up for the example load, which draws 50 mA at 3.3 V for 30 ms at start-up, and 10 mA once started. The bulk capacitance also provides stored energy for periodic higher power demands that might occur, such as for measuring a temperature, taking a reading with the data converter, or transmitting the data via an antenna.

**Figure 2. Harnessing excess loop voltage in 4- to 20-mA current loops**

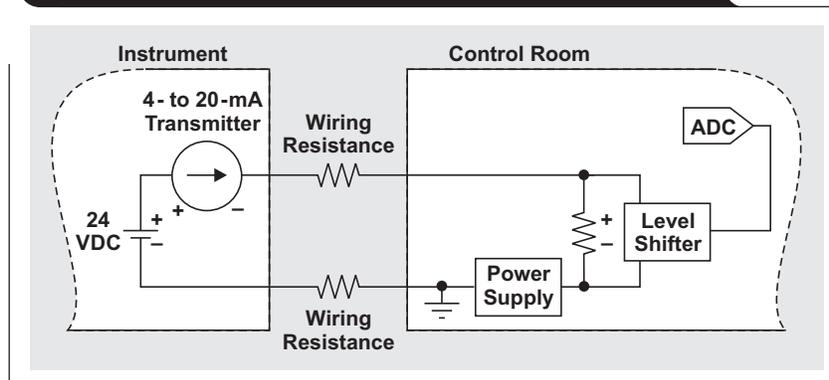


3. The device's enable threshold voltage is adjusted such that the device turns on when its voltage reaches 12 V. The device is programmed to turn off if its input drops down to 4 V. Once enabled, the device efficiently converts the harnessed energy to its 3.3-V output.

For an example power-supply solution, 4 V was chosen as the turn-off voltage in order to provide the required headroom of input voltage to output voltage, allowing the device to keep the 3.3-V output regulated. A turn-on voltage of 12 V was chosen for system considerations. It was assumed that the 24-V source varied between 18 and 30 V and that the voltage dropped in the current-loop sum to a maximum of 6 V, leaving a minimum of 12 V applied to the device under worst-case conditions. Thus, 12 V was chosen as the point at which to start the power supply, since it is the minimum voltage that would ever be applied to the device. Also, 12 V achieved sufficient separation between the turn-on and turn-off voltages such that the power supply started into its higher-powered load without start-up oscillations.


The described power-supply solution starts up from and runs off of TI's XTR111, a 4- to 20-mA current-loop transmitter delivering less than 4 mA at all times. Figure 3 shows this solution's start-up. Once the transmitter is enabled, it begins sourcing current, which raises the input voltage to the 12-V turn-on point of the power supply. The power supply's output voltage ramps up into regulation and immediately supplies the load's start-up current of 50 mA. This slightly reduces the input voltage of the power supply, but the supply keeps regulating the output voltage because of its wide voltage range and bulk input capacitor. After the 30-ms duration of the load's start-up power draw, the load current reduces to a steady-state, 10-mA level. The input voltage rises further and is clamped by the Zener diode at a safe 15-V level. As already noted, the current provided by the current loop remains below 4 mA at all times.

Figure 4 shows a close-up version of Figure 3. The power supply draws stored energy from the bulk capacitor to supply the start-up load current's demands, while the current loop provides less than 4 mA at all times. Drawing this energy reduces the input voltage by about 2 V, which is acceptable for this power supply.

**Figure 3. Start-up of energy-harnessing power supply**

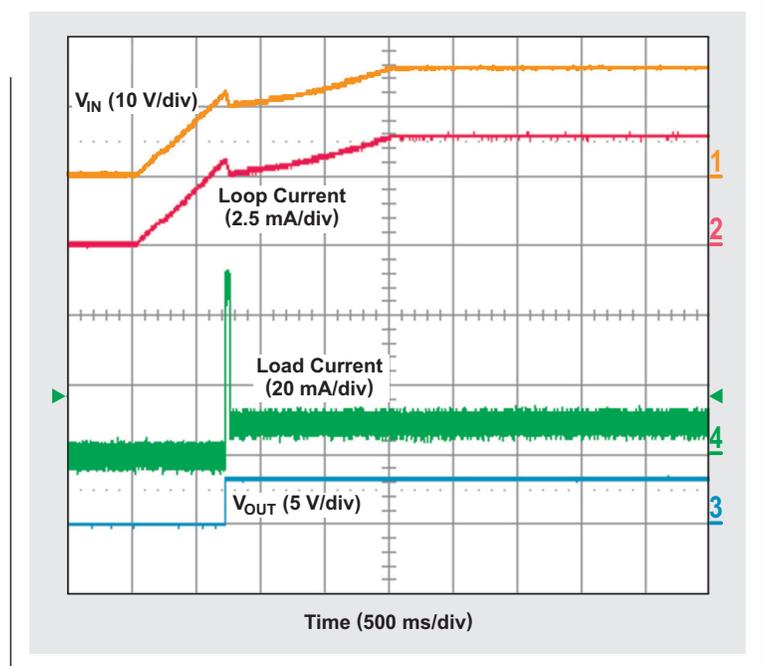

**Figure 4. Energy-harnessing power supply providing load's start-up current**

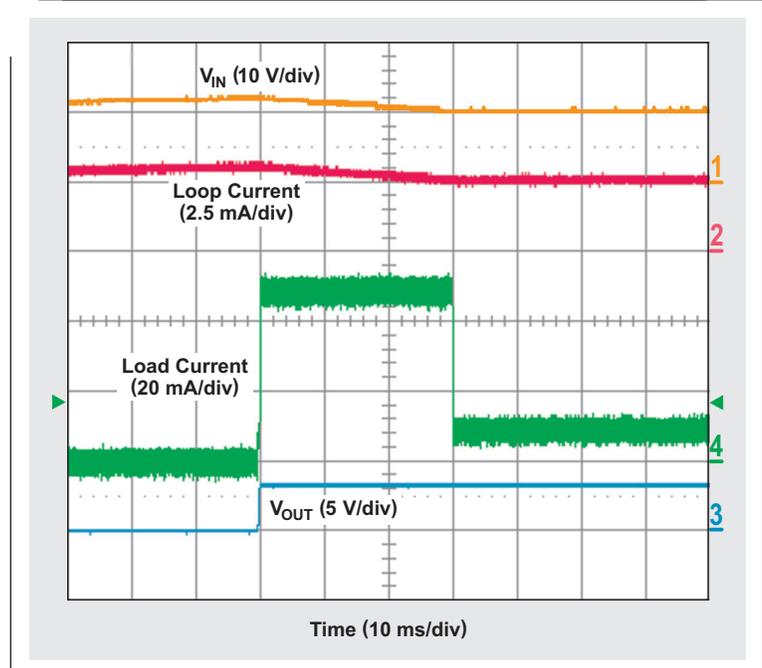

Finally, the energy-harnessing power supply stores enough energy in the bulk capacitor and operates over a wide enough input-voltage range to supply continuous pulses of power to the load. Figure 5 shows the supply providing 20 mA to the load for a duration of 100 ms every second, with the supply's output voltage remaining regulated.

### Conclusion

In 4- to 20-mA current-loop systems, energy that otherwise would be wasted can be harnessed for useful purposes. This energy powers data converters and microprocessors that the control room needs to process the incoming data from the current loop, but it can also power low-power RF transmitters that extend the application possibilities of

4- to 20-mA current loops, as well as potentially save costs in such systems by reducing the amount of wire required. A power supply that has a wide input-voltage range, operates on very small amounts of power, and starts from current-limited sources without oscillations enables the energy to be harnessed and the continued usefulness of these systems.

### Related Web sites

[power.ti.com](http://power.ti.com)


[www.ti.com/cc430](http://www.ti.com/cc430)

[www.ti.com/msp430](http://www.ti.com/msp430)

[www.ti.com/product/partnumber](http://www.ti.com/product/partnumber)

Replace *partnumber* with INA138, TPS62125, or XTR111

**Figure 5. Energy-harnessing power supply providing power pulses to the load**

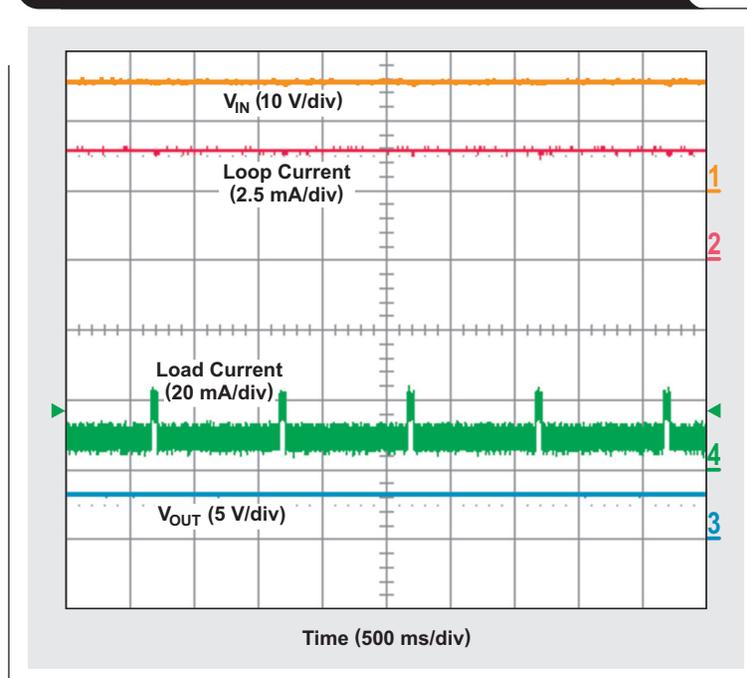

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	<a href="http://www.ti.com/asktexas">www.ti.com/asktexas</a>
Direct Email	<a href="mailto:asktexas@ti.com">asktexas@ti.com</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E and MSP430 are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)