

# Split-rail approaches extend boost-converter input-voltage ranges

By Haifeng Fan  
Systems Engineer


## Introduction

Wide-input-range DC/DC controllers usually have built-in undervoltage lockout (UVLO) circuits to prevent the converters from misoperating when the input voltage is below the UVLO threshold. However, the UVLO circuit might also cause undesirable shutdown in the event of a load transient or a supercapacitor discharge in applications where input voltage is above the UVLO threshold at start-up but later may drop below this threshold. In addition, these controllers normally cannot be used in applications where the input voltage is always under the UVLO threshold. This article presents several split-rail approaches to extend boost-converter input-voltage ranges, enabling the use of these controllers with input voltage lower than their UVLO thresholds. Design examples along with test results are provided to validate these approaches.

## Minimum input voltage of a boost converter

Figure 1 shows typical boost converters with a single input supply ( $V_{IN}$ ) that provides the input voltage to the power stage and the bias voltage to the controller. The minimum bias voltage to the controller at the  $V_{IN}$  pin is set by the controller's input UVLO threshold. To guarantee functionality of boost converters with high-side current sensing (Figure 1a), the minimum input voltage to the power stage is defined by the minimum common-mode voltage of the current-sense comparator. This is because the input voltage is also connected with the non-inverting input of the current-sense comparator. The minimum common-mode voltage of the current-sense comparator often is less than the controller's input UVLO threshold. For the boost converter with low-side current sensing (Figure 1b), the input voltage to the power stage is not directly connected to the current-sense

Figure 1. Boost converters in single-rail configuration

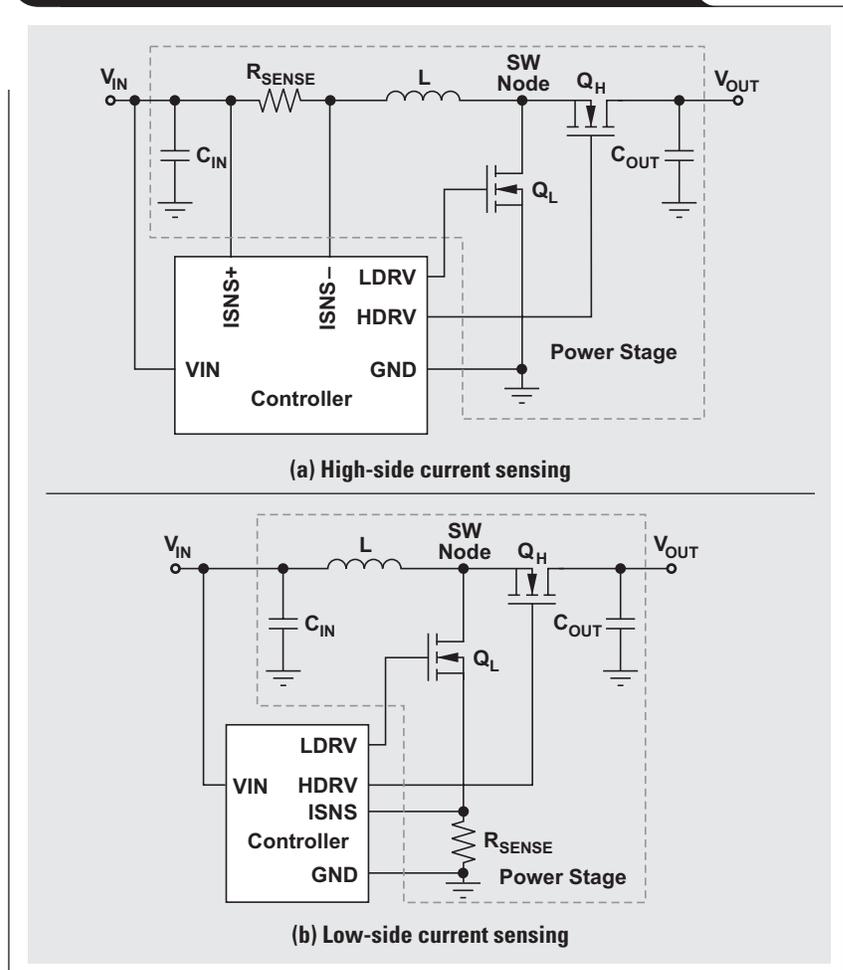

comparator. Therefore, it is not required to match the minimum common-mode voltage. Consequently, in the single-rail configuration where the input voltage to the power stage and the bias voltage to the controller are tied together, the controller's input UVLO threshold imposes a constraint on how low the input voltage to the boost power stage can go.

As shown in Figure 2, the input supply to the boost converter can be split into two rails: the power-stage input rail ( $V_{IN}$ ) and the controller's bias input rail ( $V_{BIAS}$ ). In the split-rail configuration, although  $V_{BIAS}$  is still required to be above the controller's UVLO threshold to turn on the controller,  $V_{IN}$  can go below the UVLO threshold. Since  $V_{BIAS}$  needs to supply only a very small amount of power, it can be generated by a charge pump or even share another voltage rail already existing in the system. As a result, the voltage range of the power rail ( $V_{IN}$ ) can be extended.


This article will discuss several approaches to implementing the split-rail configuration. The TPS43061 synchronous boost controller from Texas Instruments (TI) will be used to elaborate on the split-rail concept and to validate the presented approaches. This boost controller has a high-side current-sense comparator and an internal input UVLO circuit at the bias-supply input ( $V_{IN}$ ) pin.

Figure 3 shows the turn-off waveforms of the boost converter in the single-rail configuration shown in Figure 1a. The converter stops switching once  $V_{IN}$  falls below 3.9 V, which is the controller's UVLO turn-off threshold. The boost converter can be turned on only when  $V_{IN}$  rises above the UVLO turn-on threshold of 4.1 V.


### Extending input-voltage range after start-up

In some applications with only one input supply, the input-supply voltage is greater than the controller's UVLO turn-on threshold at start-up. However, it might fall below the input UVLO threshold afterwards, leading to undesired shutdown. For example, in power systems using a photovoltaic panel combined with a supercapacitor as an input supply, the input voltage may drop below the controller's UVLO turn-off threshold due to discharge. Another example is a power system powered by a USB power cable where the voltage drops significantly during a load transient, resulting in an unexpected system shutdown.


**Figure 2. Boost converters in split-rail configuration**

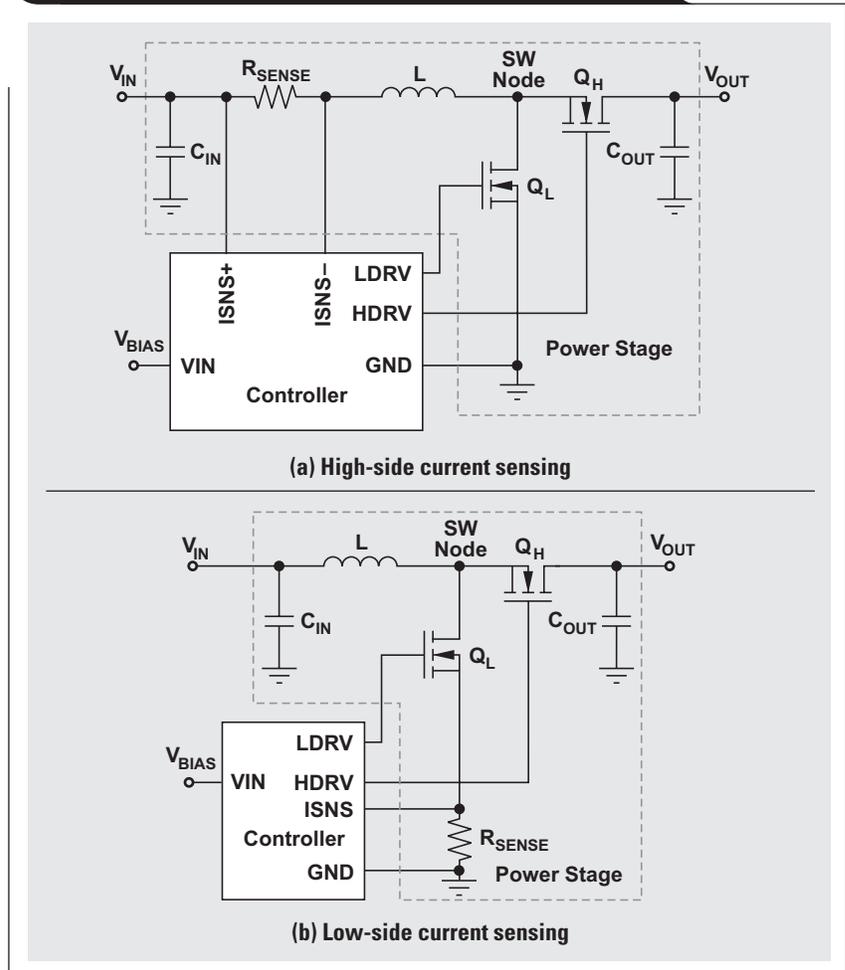

**Figure 3. Turn-off waveforms of boost converter in single-rail configuration**

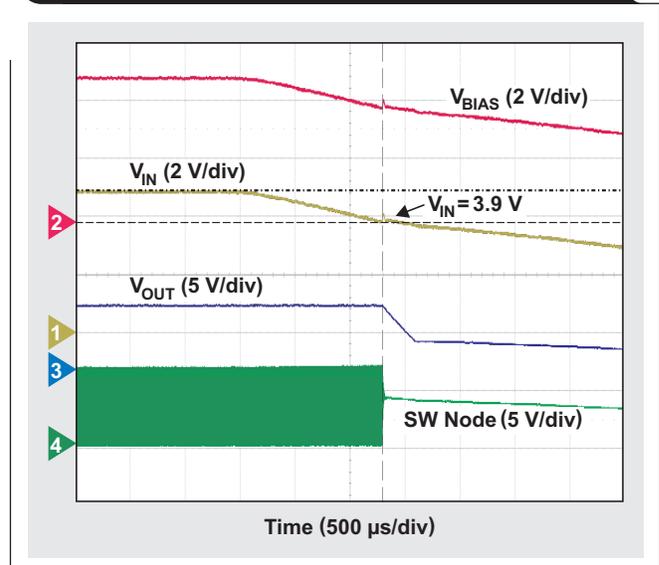

**Figure 4. Split-rail approach feeding  $V_{OUT}$  back as bias supply**

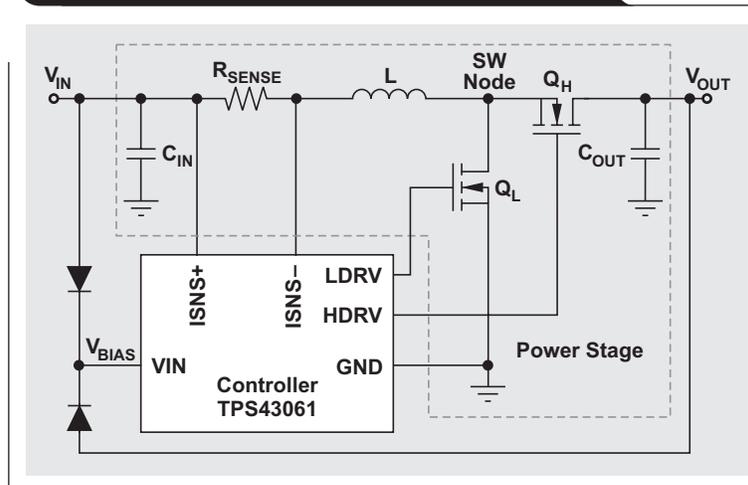


For these applications, if  $V_{OUT}$  is within the  $V_{BIAS}$  specification range, which is always higher than the UVLO turn-on threshold,  $V_{OUT}$  can be fed back as the bias supply ( $V_{BIAS}$ ) via a diode (Figure 4). After start-up,  $V_{BIAS}$  is clamped to  $V_{OUT}$  rather than  $V_{IN}$  and stays above the UVLO threshold even if  $V_{IN}$  drops below this threshold. The boost converter can maintain normal operation as long as  $V_{IN}$  can meet the current-sense comparator's requirement for the minimum common-mode voltage.

Figure 5 shows the turn-off waveforms of the boost converter shown in Figure 4, where  $V_{OUT}$  is set as 6 V and fed back as the bias supply. With diode's forward voltage drop neglected, the bias-supply voltage ( $V_{BIAS}$ ) is clamped to  $V_{OUT}$  rather than  $V_{IN}$  when  $V_{OUT}$  is higher than  $V_{IN}$  after start-up. Hence,  $V_{BIAS}$  stays above the 3.9-V UVLO turn-off threshold to avoid the undesired turn-off when  $V_{IN}$  falls below 3.9 V.  $V_{OUT}$  stays within regulation until  $V_{IN}$  falls below the minimum common-mode voltage of the current-sense comparator, in this example 1.9 V. This means that the minimum input voltage ( $V_{IN}$ ) has been extended from 3.9 V to 1.9 V after start-up.

### Extending the start-up input-voltage range

Lithium-Ion (Li-Ion) batteries are widely used in smartphones, tablet PCs, and other handheld devices. The voltage of a single-cell Li-Ion battery rated at 3.6 V usually ranges from 2.7 V to 4.2 V due to discharge and charge. This is lower than the UVLO threshold of some wide-input-range boost controllers, even before start-up. For these applications, neither a single-rail scheme nor a


**Figure 5. Turn-off waveforms of configuration shown in Figure 4**

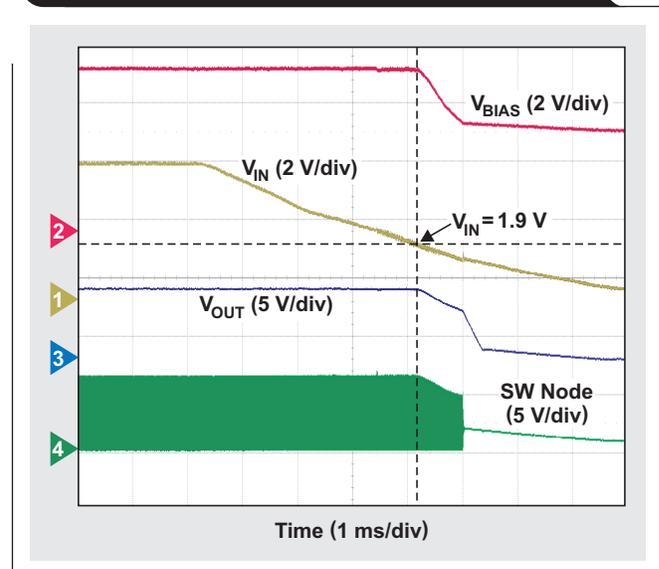

split-rail approach feeding  $V_{OUT}$  back as the bias supply works. A separate bias supply different from the battery input is needed.

Fortunately, a bias supply needs to supply only very low power. If there is another supply rail above the UVLO turn-on threshold already available in the system, it can be connected to  $V_{BIAS}$  while connecting the power rail ( $V_{IN}$ )

**Figure 6. Split-rail approach using charge pump to produce bias voltage**

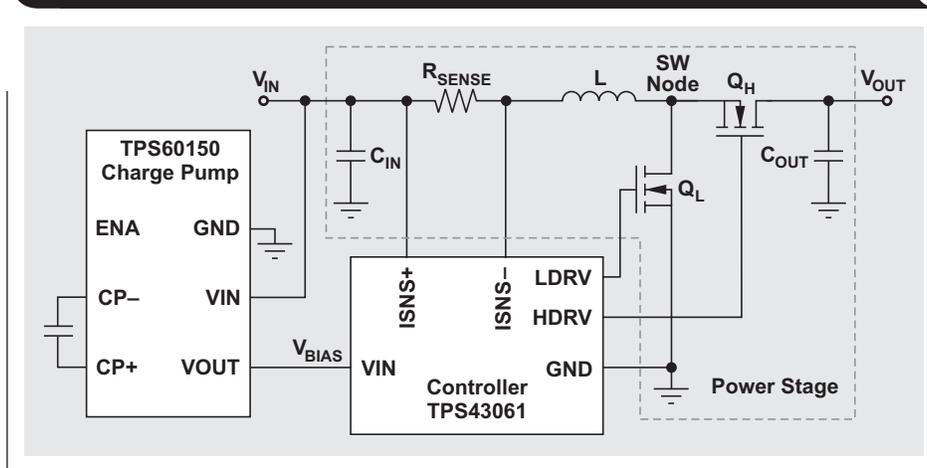

to the battery (Figure 2). If not, a charge pump can be added for a bias supply (Figure 6).

In this example, from the 2.7 V to 4.2 V of battery input, TI's TPS60150 charge pump produces a regulated 5-V supply, which is higher than the UVLO turn-on threshold of the TPS43061 controller, so it can be used as the bias supply. Using a charge pump with the split-rail approach, the boost converter can start up and operate with a single input supply that is lower than the boost controller's UVLO turn-on threshold.

Figure 7 shows the start-up waveforms of the boost converter shown in Figure 6. The converter can start up and operate with a single 2.7 V of supply since  $V_{BIAS}$  is regulated at 5 V, although  $V_{IN}$  is only 2.7 V. By using this split-rail approach, the boost converter's minimum operating input voltage is extended from 4.1 V to 2.7 V.


**Conclusion**

Two inputs are usually required for a boost converter to operate: the input supply to the power stage and the bias supply to the controller. The controller's UVLO threshold sets the low limit of the bias supply. It also places a constraint on the input supply to the power stage, if these two rails are connected to share one input supply. Split-rail approaches separate the power rail from the bias supply rail to eliminate the constraint on the minimum operating voltage of the power rail. This extends the input-voltage range of boost converters.

**References**

1. "Low quiescent current synchronous boost DC-DC controller with wide  $V_{IN}$  range," TPS43060/61 Datasheet. Available: [www.ti.com/slvsbp4-aaj](http://www.ti.com/slvsbp4-aaj)
2. "TPS60150 5V/140mA charge pump device," TPS60150 Datasheet. Available: [www.ti.com/slvs888-aaj](http://www.ti.com/slvs888-aaj)

**Figure 7. Start-up waveforms of configuration shown in Figure 6**

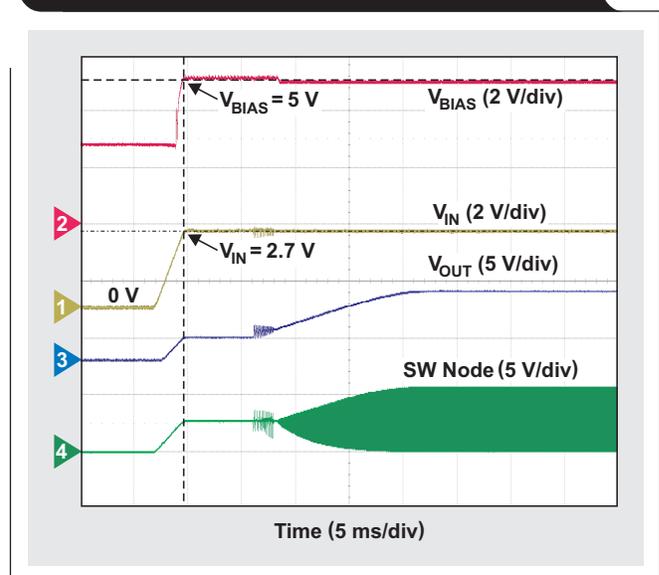

**Related Web sites**

- Power Management:  
[www.ti.com/power-aaj](http://www.ti.com/power-aaj)  
[www.ti.com/tps43060-aaj](http://www.ti.com/tps43060-aaj)  
[www.ti.com/tps43061-aaj](http://www.ti.com/tps43061-aaj)  
[www.ti.com/tps60150-aaj](http://www.ti.com/tps60150-aaj)  
 Subscribe to the AAJ:  
[www.ti.com/subscribe-aaj](http://www.ti.com/subscribe-aaj)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

**Americas** Phone +1(512) 434-1560

**Brazil** Phone 0800-891-2616

**Mexico** Phone 0800-670-7544

Fax +1(972) 927-6377  
Internet/Email [support.ti.com/sc/pic/americas.htm](http://support.ti.com/sc/pic/americas.htm)

### Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS  
(00800 275 83927)  
International +49 (0) 8161 80 2121  
Russian Support +7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +49 (0) 8161 80 2045  
Internet [www.ti.com/asktexas](http://www.ti.com/asktexas)  
Direct Email [asktexas@ti.com](mailto:asktexas@ti.com)

### Japan

Phone Domestic (toll-free number) 0120-92-3326  
Fax International +81-3-3344-5317  
Domestic 0120-81-0036  
Internet/Email International [support.ti.com/sc/pic/japan.htm](http://support.ti.com/sc/pic/japan.htm)  
Domestic [www.tij.co.jp/pic](http://www.tij.co.jp/pic)

### Asia

Phone Toll-Free Number

**Note:** Toll-free numbers may not support mobile and IP phones.

Australia 1-800-999-084  
China 800-820-8682  
Hong Kong 800-96-5941  
India 000-800-100-8888  
Indonesia 001-803-8861-1006  
Korea 080-551-2804  
Malaysia 1-800-80-3973  
New Zealand 0800-446-934  
Philippines 1-800-765-7404  
Singapore 800-886-1028  
Taiwan 0800-006800  
Thailand 001-800-886-0010

International +86-21-23073444  
Fax +86-21-23073686  
Email [tiasia@ti.com](mailto:tiasia@ti.com) or [ti-china@ti.com](mailto:ti-china@ti.com)  
Internet [support.ti.com/sc/pic/asia.htm](http://support.ti.com/sc/pic/asia.htm)

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A012014**

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)