

Five steps to a great PCB layout for a step-down converter

By Chris Glaser
Applications Engineer

Introduction

Especially for switch-mode power supplies (SMPSs), the printed circuit board (PCB) layout is a critical but often under appreciated step in achieving proper performance and reliability. Errors in the PCB layout cause a variety of misbehaviors including poor output voltage regulation, switching jitter, and even device failure. Issues like these should be avoided at all costs, since fixing them usually requires a PCB design modification. However, these pitfalls are easily circumvented if time and thought are spent during the PCB layout process before the first PCBs are ever ordered. This article presents five simple steps to ensure that your next step-down converter's PCB layout is robust and ready for prototyping.

When designing a server, tablet, or electronic point-of-sale machine, a best-practice option with the least risk is to simply copy the PCB layout example found on the evaluation module (EVM) and shown in the datasheet. However, this may not always be possible for various reasons. This article was created for these cases and details a five-step procedure to design a good PCB layout for any TPS62xxx integrated-switch, step-down converter. The internal MOSFETs and integrated loop-compensation circuitry greatly simplify the PCB layout of these devices by reducing the difficulty and time required to do the PCB layout. The versatile TPS62130A is used as the example step-down converter, which can be used in each of the above applications. Figure 1 shows the completed schematic of a typical circuit.

Step #1. Place and route the input capacitor

The input capacitor is the single-most important component for reliable operation of any step-down converter. As such, it should be the first component placed in the layout after the IC. Route the capacitor to the IC immediately after it is placed, so that nothing else can be routed in its path. Extra parasitic inductance between the input capacitor's terminals, both power and ground, and the IC's PVIN

Figure 1. TPS62130A circuit used to step-down 12-V to 3.3-V


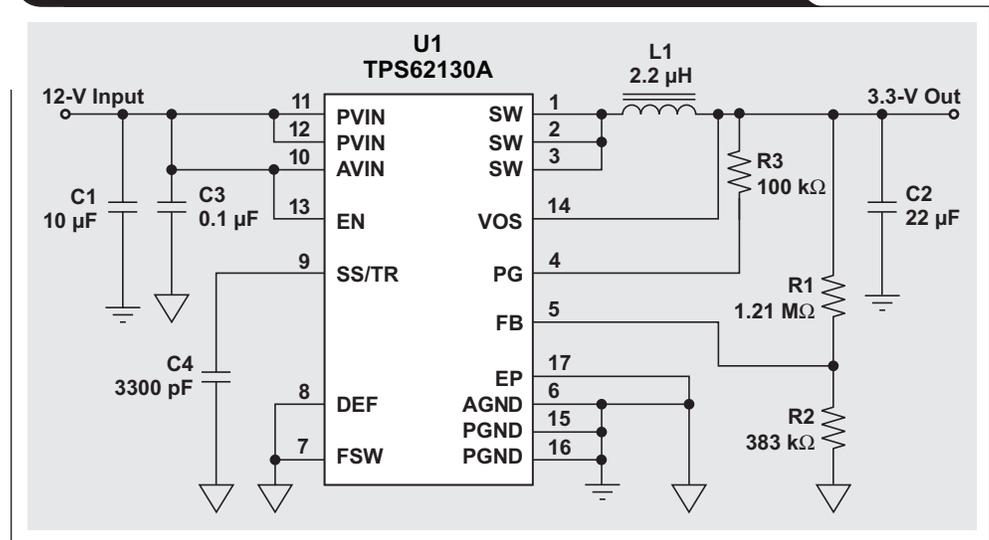


Figure 2. Layout and routing of the IC and the input capacitor to reduce voltage spikes

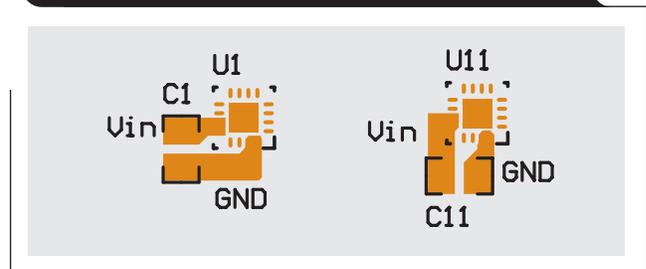

and PGND terminals creates excessive voltage spikes due to the switching action from $V = L \times di/dt$. This can lead to IC failure.


Place the input capacitor as close to the IC as allowed by manufacturing rules. Planes connect the input capacitor's terminals to the IC's. Making such a wide and short plane connection minimizes trace inductance. Add vias to connect to the system's input voltage and ground. These are added in Step #5 as they are less important. Figure 2 shows the correct placement and routing of the input capacitor and IC. Two circuits are shown due to two acceptable input-capacitor placements (C1 and C11) based on the TPS62130A's pinout (U1 and U11). Pin 1 of the IC is in the bottom right corner.

Step #2. Place and route the inductor and SW-node snubber

The second most important component to place and route is the inductor and SW-node snubber, if required. Snubber circuits are occasionally required to reduce the electromagnetic interference (EMI) of SMPSs by slowing down the rise and fall times of the SW node. Unfortunately, slowing down these timings reduces efficiency by increasing switching losses. Since the SW-node voltage swings from the input voltage to ground with very fast rise and fall times, it is the main generator of EMI in a SMPS. Modern SMPSs typically incorporate some EMI reduction techniques, which generally eliminate the need for a snubber. To be effective, add a resistor/capacitor (RC) snubber to the PCB layout at this step. This is where it has the shortest possible routing between the SW and PGND (GND) pins, minimizing its parasitic inductance.^[1]

To reduce radiated EMI, place the inductor as close as possible to the IC with the area of the SW-node copper kept to a minimum. All copper connected to the SW node is one plate of a parasitic capacitor, whose other plate is each node in the circuit. This capacitor is a noise coupling path. By keeping the SW node small, the area of the capacitor plate is minimized and the coupling reduced. Rotate the inductor as needed in order to keep the SW node small and to make an easy connection to the output capacitor (Step #3). Figure 3 shows proper inductor placement (L1 and L11) with and without the RC snubber (R14 and C15) from SW to PGND (GND).

Figure 3. Layout and routing of the inductor and RC snubber to minimize EMI

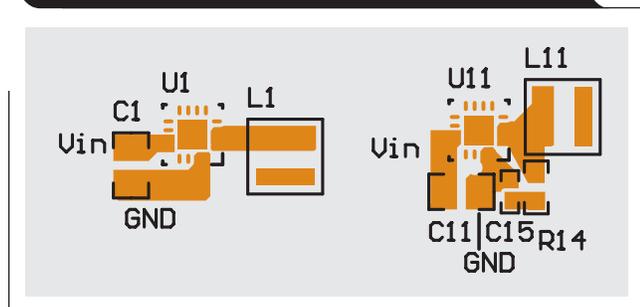

Step #3. Place and route the output capacitor and VOS pin


The output capacitor completes the routing of the power components (internal MOSFETs, input capacitor, output capacitor, inductor, and optional snubber). It is the final component connected to the power ground terminal in the system and is placed to minimize the distance from the inductor back to power ground. An improper output capacitor placement typically causes poor output voltage regulation.

Each power component is placed and routed to minimize the paths between them. Keeping these loop areas small enables the best operation of the SMPS. Finally, no vias should be used to route these components, because

vias add significant inductance to the trace. In some specific cases, vias may be used on the SW-node connection. See the special considerations section at the end of this article.

The most critical small-signal connection is the VOS input pin. An improper or noisy VOS pin connection causes poor output voltage regulation, switching jitter, and in some cases, IC failure. Route the VOS pin now to ensure that it has priority over other signal routings. Make the VOS pin trace short and direct to the output capacitor. Due to the TPS62130A's pinout, route the VOS pin with two vias and a dedicated trace to the output capacitor. This gives priority to the power components in the circuit. To reduce noise pickup, isolate the two vias from all other connections except for the VOS pin and output voltage plane on the top layer. Do not route the TPS62130A's VOS pin directly on the top layer, as this breaks the PGND connection which is more important. Figure 4 shows proper placement and routing for C2 and C12 output capacitors and a good VOS-pin routing on the bottom layer.

Figure 4. PCB layout and routing of the output capacitor and the VOS pin for good regulation

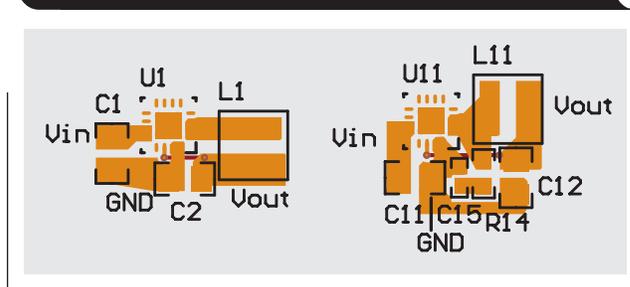


Step #4. Place and route the small-signal components

The small-signal components comprise all analog and digital components not directly related to the power conversion. These are components like the FB pin voltage divider, soft-start capacitor, and any small-value decoupling capacitors (0.1 μF for example). While the noisier power components and their nodes generate noise, the analog small-signal components are sensitive to noise. Place each of these components close to the IC with a short and direct routing to keep their noise sensitivity low. It is especially important to keep the FB node as small as possible to minimize noise pickup and provide good output voltage regulation. Use a common analog or quiet ground. Keep all components on a single side of the PCB for ease of routing. Common issues with poor placement and routing of small-signal components include poor output voltage regulation, erratic soft-start operation, and device operational problems.

Any digital signals, such as the EN and PG pin circuitry, are the least important to place and route, so do these last. Digital pins typically have a low impedance driving source. Any pull-up or pull-down resistors required

generally can be placed anywhere along the signal's path and do not need to be located close to the SMPS. Figure 5 shows proper placement and routing of the small-signal components: FB resistors (R1, R2 and R11, R12), SS/TR capacitor (C4 and C14), AVIN decoupling capacitor (C3 and C13), and PG pin pull-up resistor (R3 and R13).

Figure 5. Layout and routing of digital and small-signal components

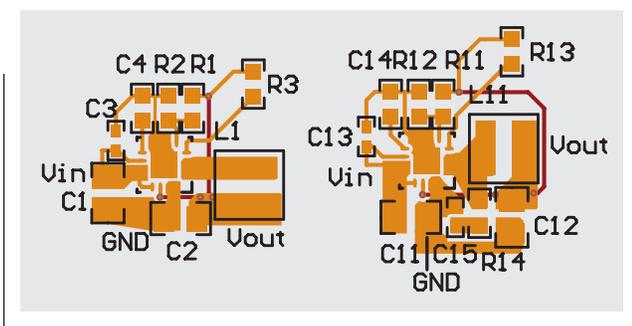


Step #5. Make a single-point ground and connect to the rest of the system

Always follow the datasheet's specific recommendations for grounding. Generally, this means keeping one ground for power components, which are noisy, and a separate ground for the small-signal components, which are quiet. By following the recommendations and steps given above, this is already done. Next, join these two grounds at a single point, typically the exposed thermal pad under the IC, which should also be connected to ground. Referring to Figure 5, the only edit needed to the grounds is to completely pour a copper plane between the PGND pins and the exposed thermal pad. The TPS62130A datasheet goes further to make this connection mandatory. Not making this connection might cause noise-related issues, such as poor output voltage regulation, or possibly improper logic levels for the digital input pins. This is due to voltage shifts between the grounds during operation. Properly connecting the grounds also provides the best thermal relief of the device.

With the grounding finished, it's time to connect this circuit to the rest of the system. This can be done with vias as the input voltage, output voltage, and ground are typically routed on planes on inner PCB layers to reach the various circuits. Starting with ground, vias are best placed directly under the IC so that the exposed thermal pad conducts its heat down into the PCB layers. This is required to achieve the IC's best thermal performance. Vias are also typically placed at the input- and output-capacitor's ground terminal. Placing vias into the system ground plane on the quiet grounded components is not generally recommended because this can couple noise from the ground plane into these nets. These grounds are best routed directly back to the AGND pin, where they make a single point connection to the exposed thermal pad.

Vias are also needed to connect the input and output voltages back into the system. It is best to place the vias outside the circuit, versus between the input capacitor and IC, for example, to not obstruct critical routings between components. A good rule of thumb for the number of vias necessary is to use one via per amp of current flowing. However, more is better if room allows. A finished layout is shown in Figure 6.


Figure 6. Finished PCB layout and routing with vias and single-point ground

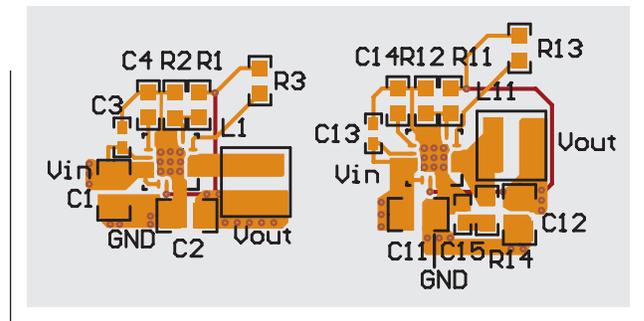

Special considerations

Always consult the device's datasheet for specific layout recommendations and a recommended layout example. Directions and examples provided are sufficient for most devices' layouts. One type of layout that generates some confusion is commonly found on wafer chip-scale packages (WCSPs), such as the TPS62360. In many WCSP step-down converters, the IC's pinout places the SW pin between the VIN and PGND (GND) pins. If following Step #1, the input capacitor blocks access to the SW pin unless the SW pin is routed underneath the input capacitor. Some think this is undesirable because that trace must be rather thin to be routed between the terminals of a small component, such as the input capacitor. This then looks like Figure 7.

Figure 7. Recommended layout of the TPS62360 in a WCSP package^[2]

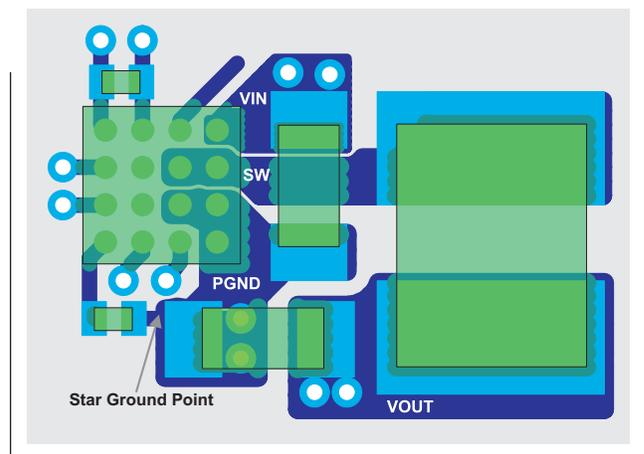

The preferred PCB layout method is to route the SW pin underneath the input capacitor (Figure 7). While the SW trace is thin, it is also very short, which keeps the SW node small. This follows Step #2 to reduce EMI. If it is not possible to route such a trace, then use vias to connect the SW pin to the inductor. Vias in this connection merely create additional EMI by the longer routing. However, the added inductance of these vias is not critical as this parasitic inductance is in series with the inductor's inductance. Using vias in this path is a better choice than moving the input capacitor out of its ideal location.

Conclusion

When designing the PCB layout for a SMPS, always consult the device's datasheet and EVM for examples and specific recommendations. But for cases when it is not possible to exactly follow these, or in the rare case where these are not present, five simple steps allow for a good step-down converter layout:

1. Place and route the input capacitor.
2. Place and route the inductor and SW-node snubber.
3. Place and route the output capacitor and VOS pin.
4. Place and route the small-signal components.
5. Make a single-point ground and connect to the rest of the system.

Doing these steps will generate a robust design that gives good performance for servers, tablets, electronic point-of-sale machines, and any other system that uses step-down converters.

References

1. Jeff Falin, "Minimizing Ringing at the Switch Node of a Boost Converter," Application Note, Texas Instruments, September 2006. Available: www.ti.com/1q15-slva255
2. Layout example taken from the TPS62360 datasheet, figure 52, page 35. Available: www.ti.com/lit/slvsau9

Related Web sites

www.ti.com/1q15-TPS62130A

www.ti.com/1q15-TPS62360

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com