

# Transient-testing platforms and automation techniques for LDOs and buck regulators

By Kern Wong

Principal Design Application Engineer, Mobile Lighting and Power

## Introduction


With mobile processors in wireless devices operating in the gigahertz range, there is increasing consumer demand for higher performance, longer battery life, smaller size, and lower cost. Therefore, the design of power management circuits is becoming an increasingly complex issue. Low dropout regulators (LDOs) and switching regulators are indispensable components in portable systems with standalone regulators and power management units (PMUs). As high-speed and portable communications devices employ regulators that require faster response time, it is necessary to rigorously validate regulator performance and merits in order to ensure reliable power management products. Key performance parameters include line transient, load transient, startup, load and line regulation, and several others. To have a complete analysis of these parameters, it is necessary to have state-of-the-art tools for the hardware test platform and mature methodology. These tools allow accurate and high sample rates for parameter characterization in addition to supporting automation techniques that speeds up testing and ensures repeatable results.

## Implementing high-edge-rate and reusable test apparatus

For an accurate assessment of the key parameters of a regulator, it is necessary to generate steps in line voltage and load current that are fast with respect to the regulator's control-loop response time. Lab equipment and many commercial instruments that use operational amplifiers (op amps), passive components, and large driver chains can limit the rise and fall times of the stimulus signals with large excursions. To obtain high-speed edge rates for load transients ( $\gg 1 \text{ A}/\mu\text{s}$ ) and line transients ( $\gg 0.1 \text{ V}/\mu\text{s}$ , with input caps), practically no off-the-shelf products are available.

It is possible for a slow-transient stimulus to make a poor regulator look good. In response, incremental research and development (R&D) led to simpler designs that are low in parasitic L and C, which can be readily built and duplicated for use in design and application labs. Setting up a respectable test jig is half the solution. To achieve optimal response, the device under test (DUT) must be properly wired or socketed onto the printed

Figure 1. Antiquated setup for transient testing

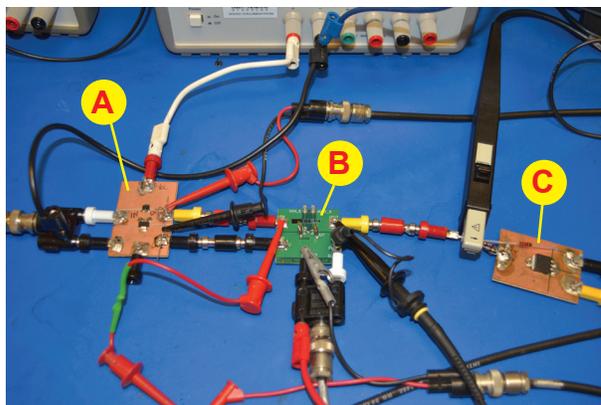

A. Emitter followers and pulse generator create  $V_{IN}$  step voltage during line transient tests.

B. Device under test (DUT) is an LDO evaluation board (EVB).

C. PCB for NMOS transient load switch. A constant load is applied during line transient tests.

circuit board (PCB). Also important is proper selection of optimal ground and supply conduits, bypassing, charge reservoirs, and external support components. After all, it is the merits of the DUT that should be ascertained, not the parasitic or the unwanted effects from improper components and physical layout.


## Preamble on test hardware challenges and limitations

In a load-transient test, the regulator's input is powered by a constant voltage source and the output is rapidly switched to a greater resistive load or current sink. A line-transient test is similar in that a line-voltage step is rapidly injected at the regulator input while its output is supported with a constant load. Figure 1 shows a typical test setup for transient testing. The setup is relatively modularized for ease of assembly and the long cable lengths were adequate for legacy technology. However, this setup is not satisfactory for today's requirement because of parasitics, ground loops, and higher voltages and currents.


### Test-jig parasitics and automation

A transient-testing program for semi-automated testing was initiated in January of 2013 for PMUs and regulators. A universal regulator test bed was conceived and constructed to verify its merits. Figures 2 and 3 show an LDO regulator test jig that can accommodate an evaluation board (EVB) via machined socket pins for semi-automated testing. The schematic is shown in Figure 4.

**Figure 2. Transient test jig with LDO EVB (blue PCB)**

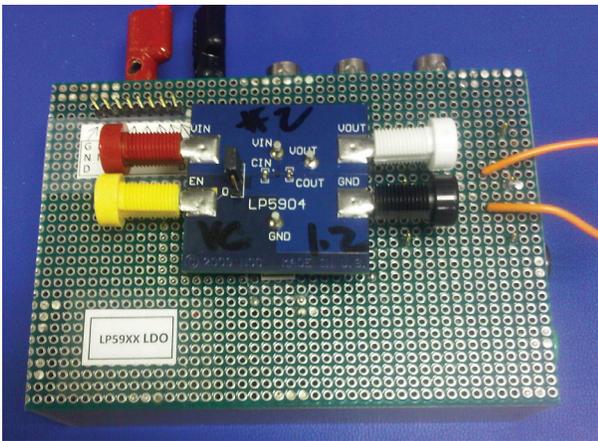


**Figure 3. Back side of LDO test jig**

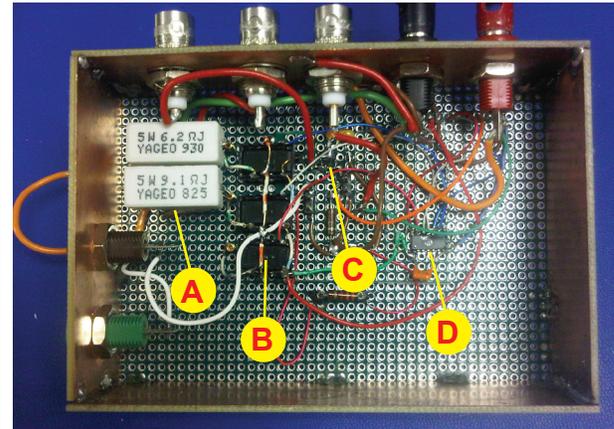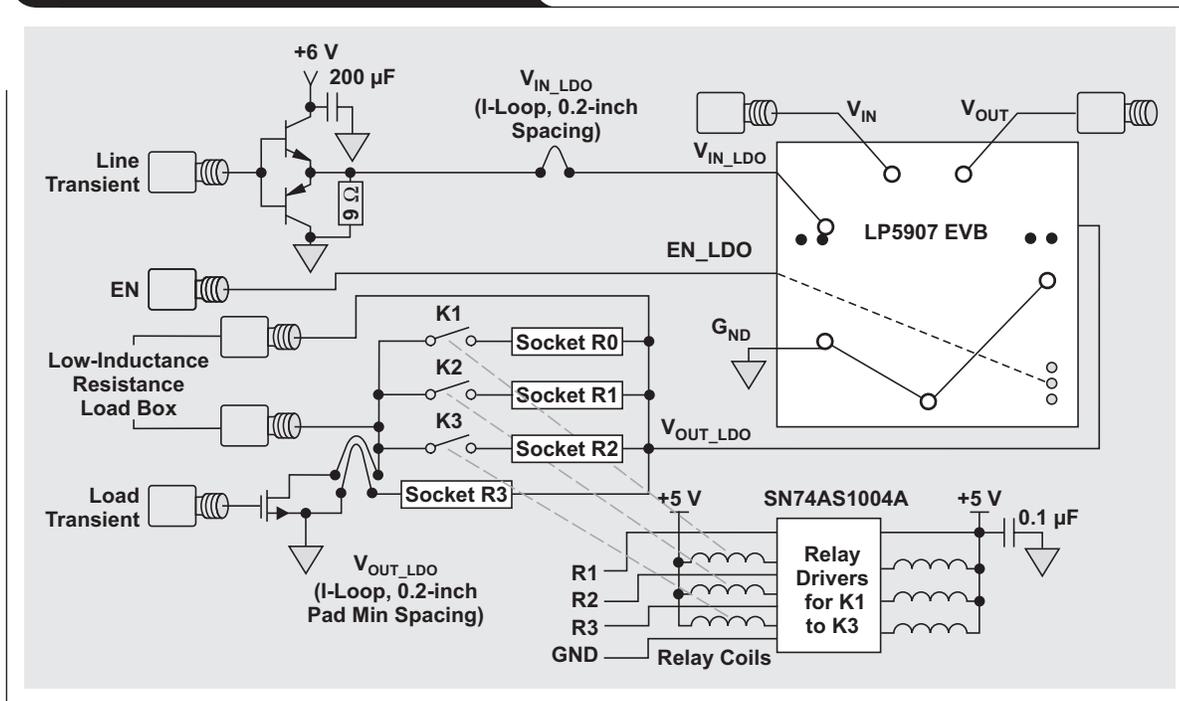


- A. NFET load step switch (under resistors).
- B. Relays to select load.
- C. NPN follower.
- D. 48-mA relay drivers.

**Figure 4. Schematic for the LDO test jig**




Figures 5 through 7 show a similar transient test jig and schematic for a buck regulator.

**Figure 5. Transient test jig and buck-regulator EVB (green PCB)**

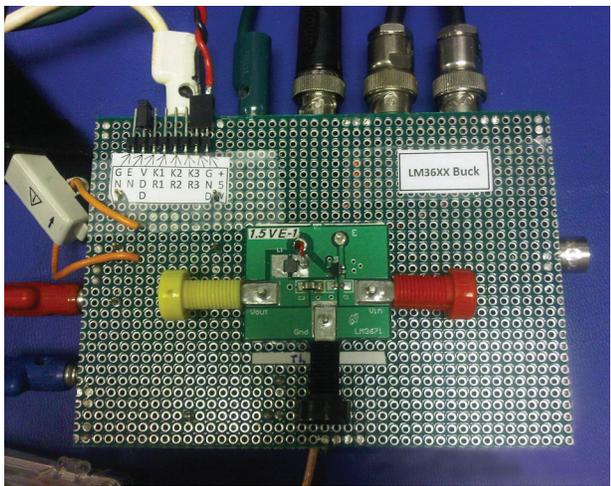


**Figure 6. Back side of buck-regulator test jig**

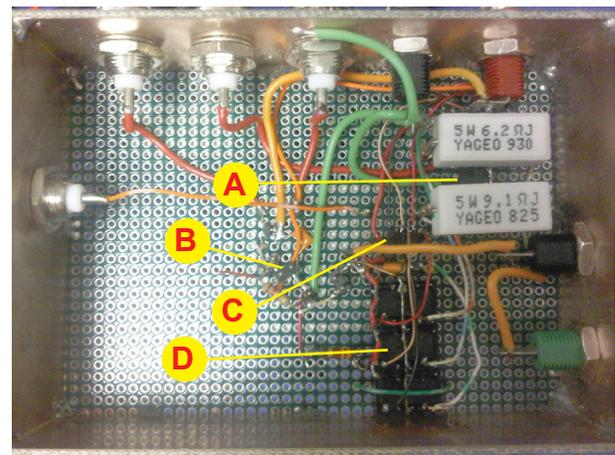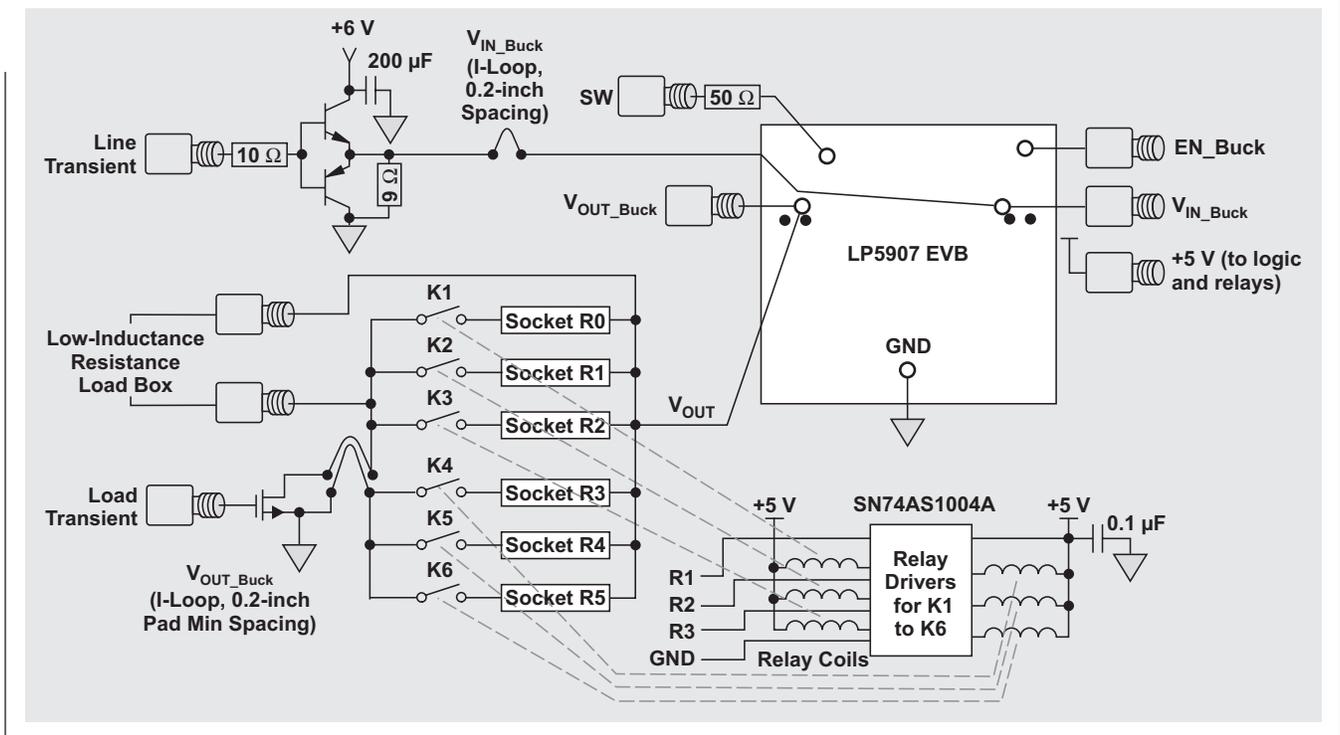

- A. NFET load step switch (under resistors).
- B. NPN follower for line step.
- C. 48-mA relay drivers.
- D. Relays to select load.

**Figure 7. Schematic for the buck regulator test jig**




### Further enhancements

The test jigs were successful in achieving the design goals in that they significantly reduced parasitics and current loops, thus enabling faster edge-rate stimulus for validating targeted products. In June of 2013, a follow-up enhanced design for a higher-performance, integrated transient test jig. This jig is capable of accommodating today's high-bandwidth and fast-edge-rate products and future generations.

As shown in Figure 8, the enhanced jig was designed with a circular PCB configuration and can either adapt an EVB of a DUT for maximum flexibility. An alternate DUT layout is to solder it on the PCB for optimal performance. Radio frequency (RF) plumbing was used on the board and PCB traces were matched and impedance controlled. The jig also provides a rechargeable battery pack that provides clean and quiet power to the DUT for low-noise applications.

**Figure 8. Enhanced test jig with resistive loads on board**

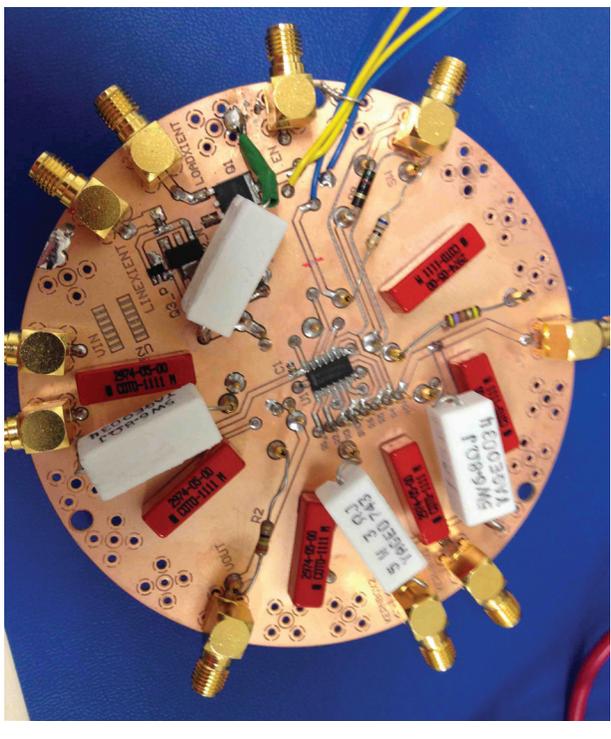

For more extreme test requirements, the jig was redesigned to interface with temperature-cycling, air-stream systems that can be sealed air tight with no leakage, which will avoid icing at extreme temperatures. The result is the castle-shaped metal housing structure shown in Figure 9 that supports a personality card PCB for the EVB. An alternative could be a circular PCB with a direct on-board DUT mount. Also, a high-temperature transparent plastic adapter was included to interface to a temp-cycling housing.

**Figure 9. Temperature-cycling test jig with personality PCB for PMUs**




### Architecture and automated test flow

A block diagram of the test environment for the automated test platform is shown in Figure 10.

The supply block provides all the voltage inputs and the line-transient input to the DUT. The load block provides multiple resistive loads that are controlled with relays. The control block is responsible for interfacing with the DUT and also for changing the supply and load settings. The measurement block is responsible for measuring the input and output voltages and currents.

**Figure 10. Generic test environment**

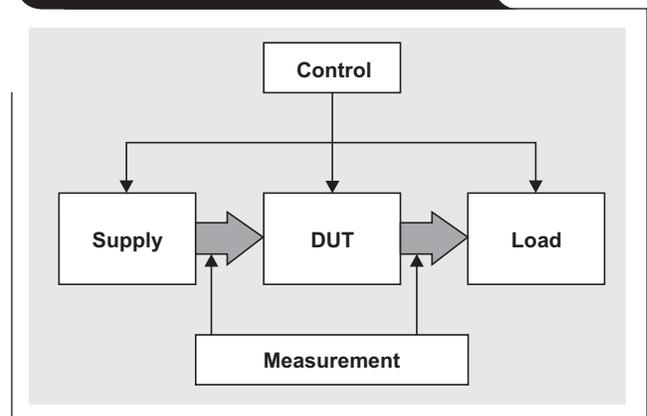

### LDO test jig

Based on the jig schematic in Figure 4, the line-transient input is connected to a function generator to provide the line transient input to the LDO. Since the function generator cannot source a lot of current, an emitter follower is used to increase the current being sourced to the input. A 9- $\Omega$  resistor is connected at the output of the emitter follower circuit to provide fast discharge of the input capacitor during the fall time of the input line transient.

For tests that do not require a line transient, a constant DC voltage is provided through the line transient input, which is connected to the input of the LDO. The enable (EN) input is available to provide a pulse for the startup test using a function generator. In other test cases, the enable pin is supplied with a constant DC voltage for regular enable operation. The load-transient input is also controlled by a function generator that switches the NMOSFET continuously for a load-transient test. There is a base load (1-mA load for the LDO), which is always connected to the output of the LDO. However, it can be disconnected, if required. Three other resistive loads are controlled by using three relays. In turn, these relays are controlled via a computer through a USB relay controller.

### Buck test jig

The system architecture of the buck-regulator test jig shown in Figure 7 is virtually the same as for the LDO jig. The only major change is the addition of three new relays. These were added because of the complicated nature of the load-transient tests for a buck IC. Unlike a LDO, load transients consist of different base current for load-transient testing. For example, for a LDO, the load transients required are 1 mA to 20 mA, 1 mA to 100 mA and 1 mA to 250 mA. However, for a buck, the various load-transient tests require 1 mA to 50 mA, 50 mA to 400 mA, 200 mA to 400 mA, and 0.6 A to 1 A. Hence, there are additional relays. The PCB design has some other changes. The buck is a switching regulator, thus, there is an additional switching pin to probe. This pin is isolated from other parts of the board by creating 20-mm segregation on both sides of this trace and pin. The tests for the buck test platform are exactly the same as for the LDO platform.

### PCB design and issues

There are two major concerns on the layout of the redesigned automation test platform for high-performance validation. The first concern is maintaining high edge rates and signal integrity of the stimuli. The test setup is designed to produce fast line and load transients for the DUT. However, impedance mismatches and cross-talk between traces can significantly affect these high-speed lines. The second concern is voltage drops in power lines caused by attenuation from long traces. Hence, proper PCB design following good RF techniques is required. Also, it is necessary to measure a signal as close to its origin as possible to mitigate voltage drop or parasitic effects.

### Lab equipment deployed

For line/load-transient and startup testing, the test platform includes a programmable power supply, three function generators, one oscilloscope, and a test jig. The power supply is used to provide power to the test circuitry required to carry out line- and load-transient testing. The power supply is also used to power the enable pin of the DUT and the relay driver chip, which allows the user to select different loads for a particular test. The function generators are used for generating pulse waveforms (using the arbitrary function waveform) for the line-transient step, load-transient step, and to pulse the enable pin.

The oscilloscope measures the input and output voltages and currents. The test platform is also used to observe the enable pin for the startup test. Designed as a plug-and-play test platform where the DUT needs to be installed on the test jig, this architecture methodology allows the reuse of the platform for different DUTs. The test setup relies on instruments that are controlled by a laptop running LabVIEW<sup>®</sup> software and connected via a general purpose interface bus (GPIB). All instruments, except for the oscilloscope, are daisy chained using GPIB cables that are connected to the laptop using a USB to GPIB cable. The oscilloscope is directly connected to the laptop with a USB cable. BNC to SMA cables are used to measure or probe all the signals.

### LabVIEW tool (LVT) for test automation

Visual basic routines for virtual instruments (VIs) are written to automate the transient tests. These tests consist of three blocks. The first block of the LVT test selects the loads for the test. The second block includes the feedback correction loop that continuously measures the rise and fall times of the input-transient stimulus and corrects for the output of the function generator until the correct rise and fall times are measured by the oscilloscope. The third block of the LVT test captures a screenshot of the output and input voltage once the feedback is completed. It also obtains the measured rise and fall times and the maximum and minimum output voltages. The LVT obtains the minimum, maximum and mean of all the parameters directly from the scope. It also calculates the average of the maximum and minimum value measured. The LVT then populates a matrix of measurements and graphs that are displayed on the front panel. These measurements are also written to a text file in the Text Files folder. The screen shots are saved to a pen drive inserted into the oscilloscope. The name of these files are decided based on the kind of load and edge-rate setting. However, the names can be changed in the block diagram of the LVT.

## Conclusion

The platform for automating high-speed transient testing is very multi-disciplinary because it requires capabilities beyond typical validation and test R&D. Included are a wide range of disciplines such as basic knowledge of startup-and-transient behavior characteristics for linear and switching regulators, best practices plus novel techniques for test and measurement, board-level system design, and software development.

With the prototyping test jigs for both LDO and buck ICs, the proposed test procedures can be validated and automated for line-transient, load-transient and startup tests. Stimulus edge rates can be achieved in the nanosecond range with proper drive, interfacing, and termination. High-speed waveform-capture sampling can be done with high-performance test equipment and probes. Serial-interface control of device modes, operation, and test equipment can be programmed on the fly to automate testing. Furthermore, closed-loop control and monitoring facilitates programming the timed events and electrical parametric stimuli in addition to accurately logging response time delays.

## Acknowledgments

The author thanks Sheng Jin, Applications Manager MLP at Texas Instruments and Aditya Jain, our dedicated intern. Thanks also to Hoang Duong, Robin Gupta, and Hak-Leong Ng.

## References

1. Kern Wong, "High-Speed Load/Line Transient Jigs and App Report for Testing Fast Response POL Regulators," Texas Instruments Application Report (SNOA895), April 2013.
2. Kern Wong, "Myths surrounding PSRR specifications," TI E2E Power House blog, October 22, 2013.
3. Load Transient Testing Simplified, Texas Instruments Application Report (SNOA507), November 2007.

## Related Web sites

Product information:

**LP5907**

**LM3671**

LabVIEW tool information:

**[www.ni.com/labview](http://www.ni.com/labview)**

Subscribe to the AAJ:

**[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)**

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)